 





FUNDAMENTOS DE COMPUTADORES II

MICROARQUITECTURA SEGMENTADA



 
PROCESADOR SEGMENTADO SIN GESTION DE CONFLICTOS




ALUop	op ₅	funct7 ₅	funct3	ALUctr
00 ^(sumar)	X	X	XXX	000 ^(A + B)
01 ^(restar)	X	X	XXX	001 ^(A - B)
10 ^(operar)	0	X	000 ^(addi)	000 ^(A + B)
10 ^(operar)	1	0	000 ^(add)	000 ^(A + B)
10 ^(operar)	1	1	000 ^(sub)	001 ^(A - B)
10 ^(operar)	X	X	010 ^(slt/slti)	101 ^(A < B)
10 ^(operar)	X	X	110 ^(or/ori)	011 ^(A B)
10 ^(operar)	X	X	111 ^(and/andi)	010 ^(A & B)



Op	ImmSrc
0000011 ^(lw)	00 ^(tipo-I)
0100011 ^(sw)	01 ^(tipo-S)
0010011 ^(tipo-I)	00 ^(tipo-I)
0110011 ^(tipo-R)	-
1100011 ^(beq)	10 ^(tipo-B)
1101111 ^(jal)	11 ^(tipo-I)

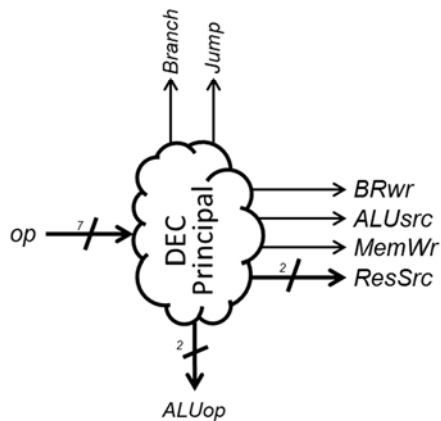

op	Branch	Jump	BRwr	ALUsrc	ALUop	MemWr	ResSrc
0000011 ^(lw)	0	0	1	1	00 ^(sumar)	0	00
0100011 ^(sw)	0	0	0	1	00 ^(sumar)	1	-
0010011 ^(tipo-I)	0	0	1	1	10 ^(operar)	0	01
0110011 ^(tipo-R)	0	0	1	0	10 ^(operar)	0	01
1100011 ^(beq)	1	0	0	0	01 ^(restar)	0	-
1101111 ^(jal)	0	1	1	-	-	0	10

 


```

if ( (Rs1E ≠ 0) & BRwrM & (Rs1E = RdM) ) then      ( ForwardA ← 10(anticipar MEM) )
  elsif( (Rs1E ≠ 0) & BRwrW & (Rs1E = RdW) ) then  ( ForwardA ← 01(anticipar WB) )
  else                                               ( ForwardA ← 00(no anticipar) )

if ( (Rs2E ≠ 0) & BRwrM & (Rs2E = RdM) ) then      ( ForwardB ← 10(anticipar MEM) )
  elsif( (Rs2E ≠ 0) & BRwrW & (Rs2E = RdW) ) then  ( ForwardB ← 01(anticipar WB) )
  else                                               ( ForwardB ← 00(no anticipar) )

```

 

```

if ( (ResSrcE = 0) & BRwrE & ((Rs1D = RdE) | (Rs2D = RdE)) ) then ( lwStall ← 1 ) (parar pipeline)
else                                                                ( lwStall ← 0 ) (no parar pipeline)
StallF = StallD = lwStall
FlushD = PCsrcE
FlushE = lwStall | PCsrcE

```