



Module 1: From digital systems to computers

Introduction to computers II

José Manuel Mendías Cuadros

*Dpto. Arquitectura de Computadores y Automática
Universidad Complutense de Madrid*





Outline

- ✓ Application-specific circuit
- ✓ General purpose data paths + controller.
- ✓ General purpose circuit: computer.
- ✓ Von-Neumann model.
- ✓ Processor architecture.
- ✓ Processor organization.
- ✓ Other basic concepts.

These slides are based on:

- Katzalin Olcoz et al. *Fundamentos de Computadores II. UCM*
- Chris Terman. *Computation Structures. MIT Open Courseware*



Application-specific circuit




- An algorithm is implemented in hardware connecting:
 - Data path: performs operations and stores partial results.
 - Controller: sequences the operations according to the algorithm.

```

A = Ain;
B = Bin;
R = 0;
for( C=0; C<32; C++ )
{
    if( B0==1 )
        R = R+A;
    A = A<<1;
    B = B>>1;
};
Rout = R;

```

Algorithm to multiply two
32-bit numbers

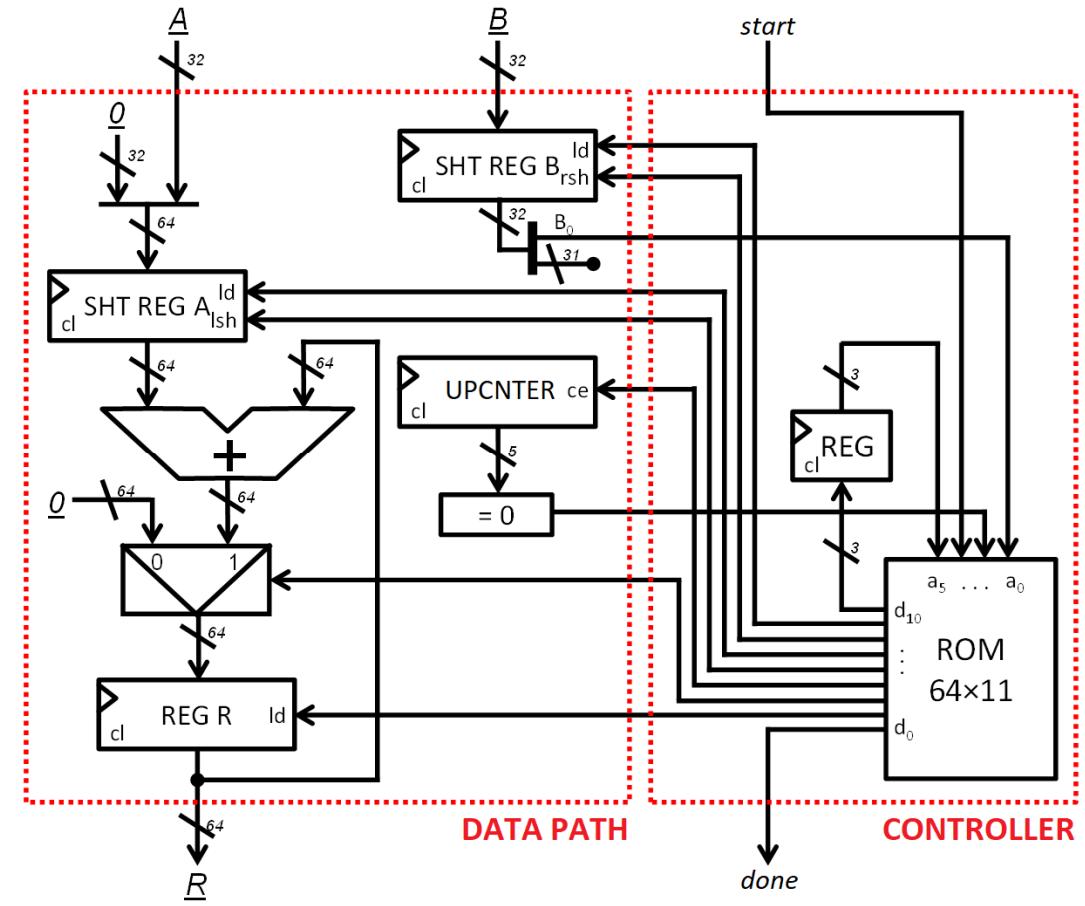



Application-specific circuit




- The circuits obtained through algorithmic design **are very efficient**, but they have **one single behavior**.
 - Different algorithms require **different circuits**.
 - To **change its behavior, a hardware redesign must be performed**.

```

A = Ain;
B = Bin;
R = 0;
if( A!=0 && B!=0 )
{
  while( A!=B )
    if( A>B )
      A = A-B;
    else
      B = B-A;
  R = A;
};
Rout = R;

```

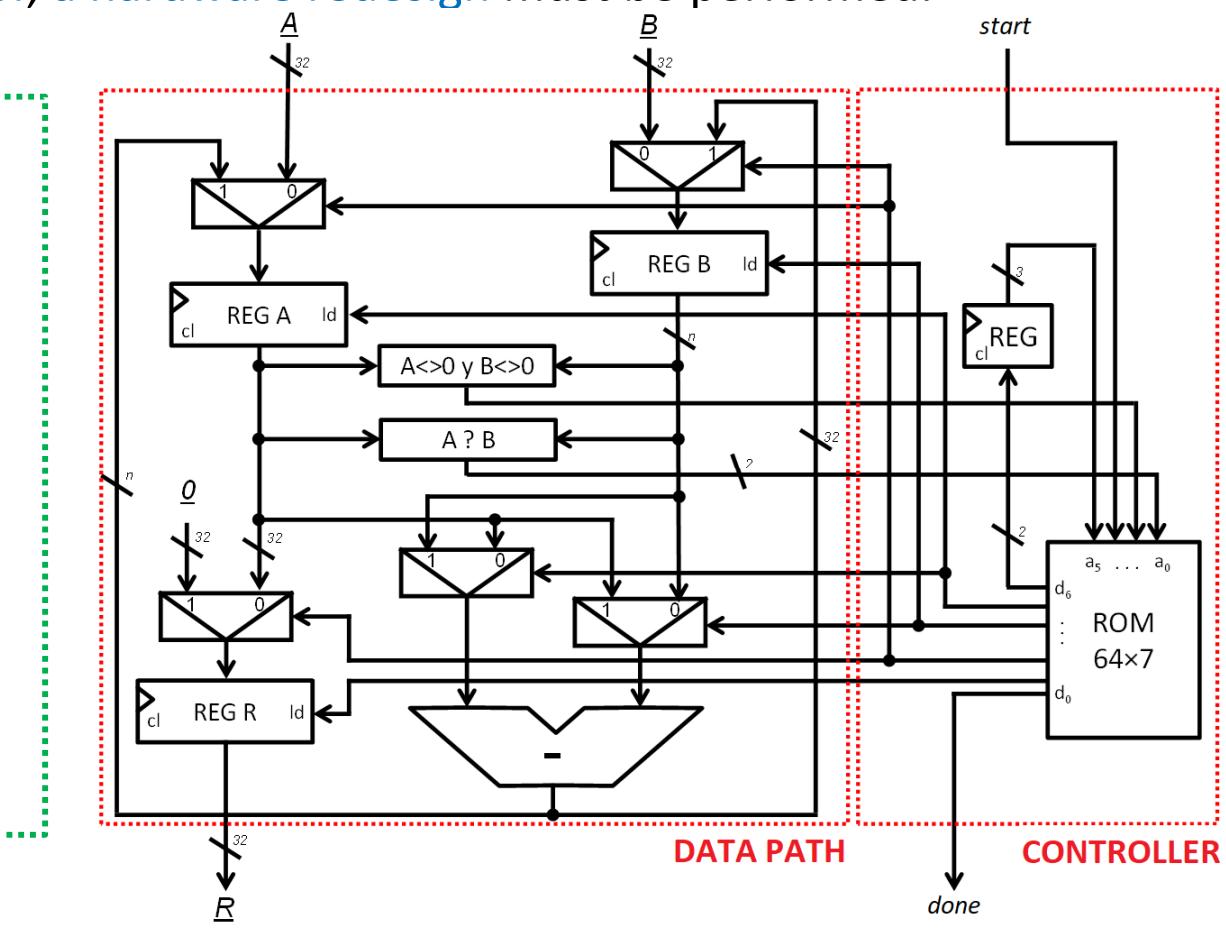Algorithm to calculate the GCD
of two **32-bit** numbers





Application-specific circuit




- In general, these **data paths** are **very specific** because for each algorithm:
 - The **number of registers** depends on the number of variables
 - The **number and type of functional units** depends on the number and type of calculations to be performed.
 - The **number of connections** is maximized to perform simultaneously as many register transfers in parallel as possible.
 - The **width of each interconnection** depends on the widths required by each calculation.
- Besides, these **controllers** are **very specific** because:
 - The **number of control/status signals** of each data path is different.
 - They follow a fixed **state sequence** stored in the ROM

General purpose data path



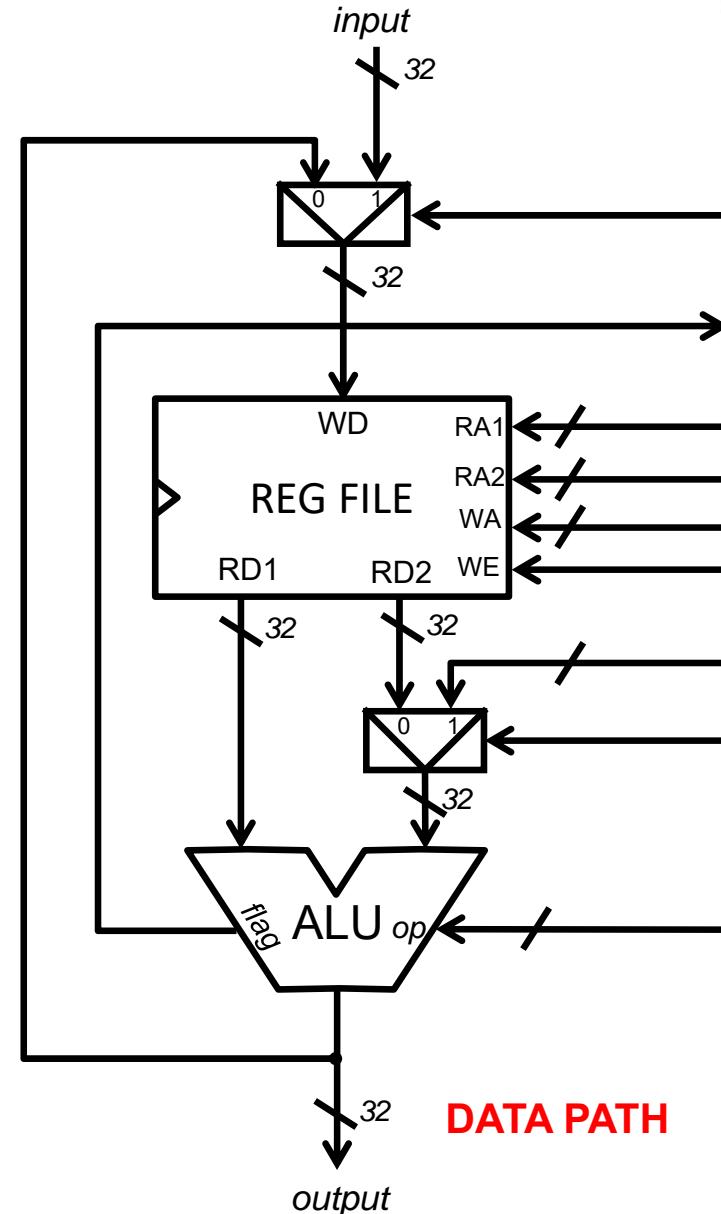- However, it is possible to design a more generic data path:




General purpose data path



- However, it is possible to design a more generic data path:

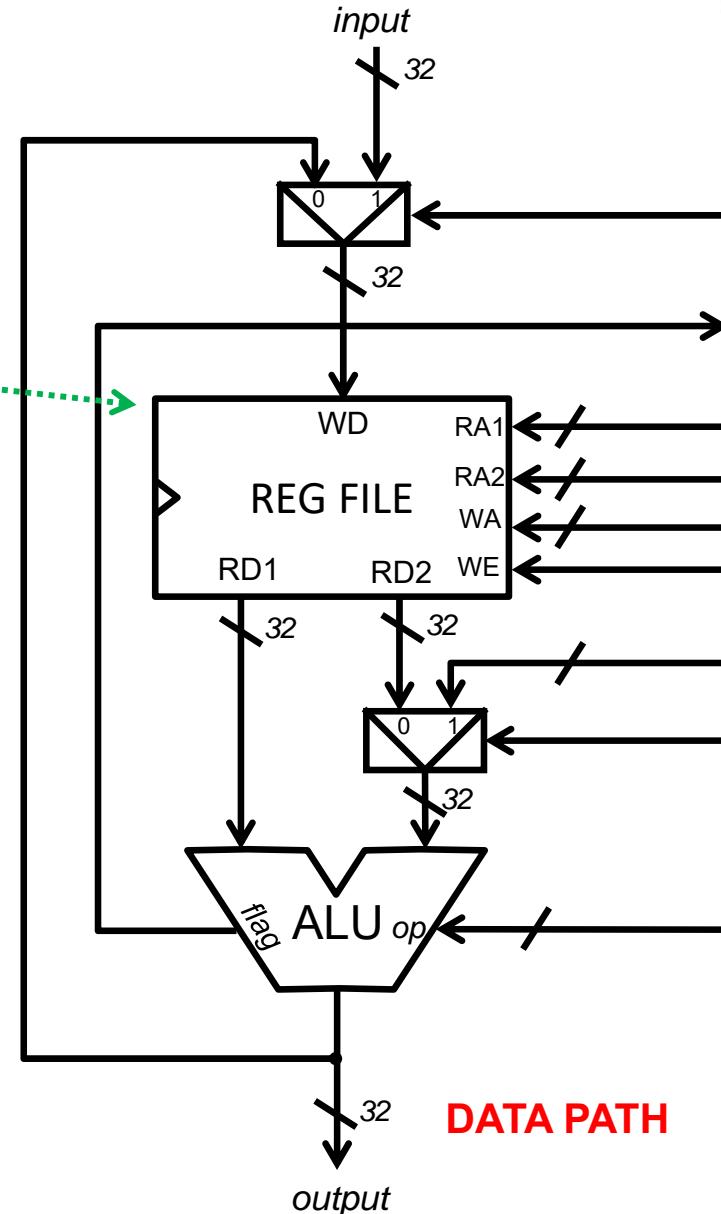
A *register file* with a large enough number of registers is used



General purpose data path



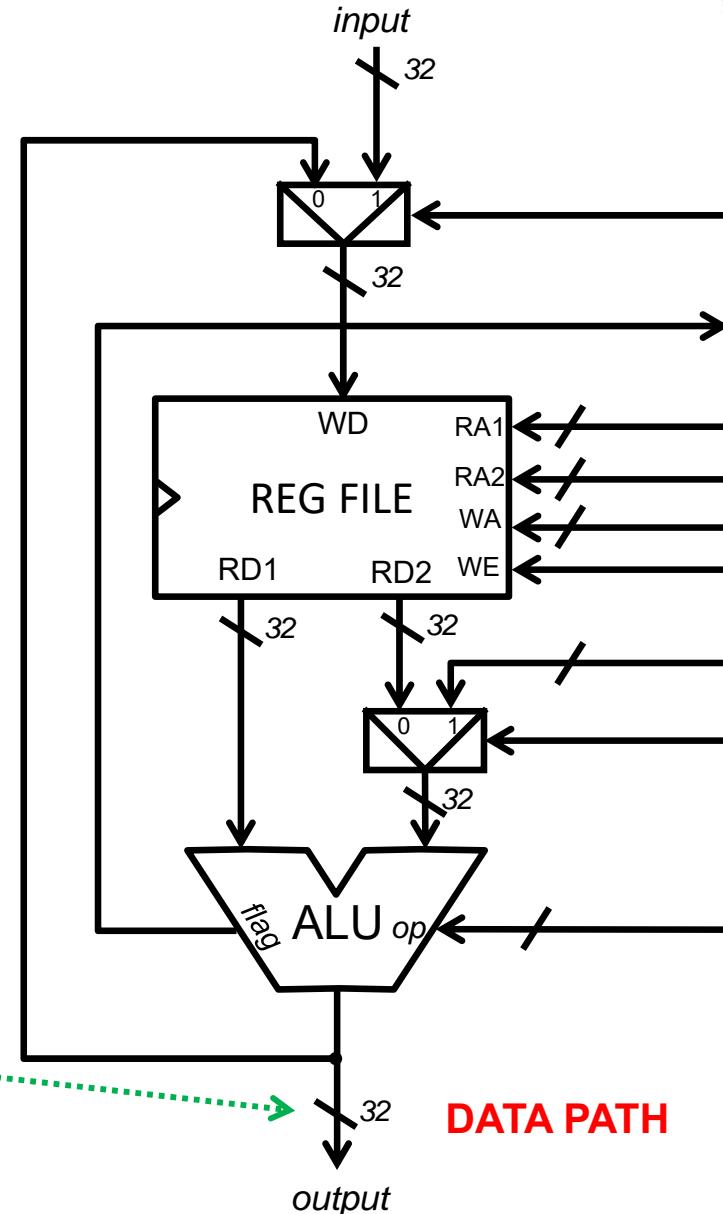- However, it is possible to design a more generic data path:




A *homogeneous data width* is chosen, wide enough for all the interconnections

General purpose data path



- However, it is possible to design a more generic data path:

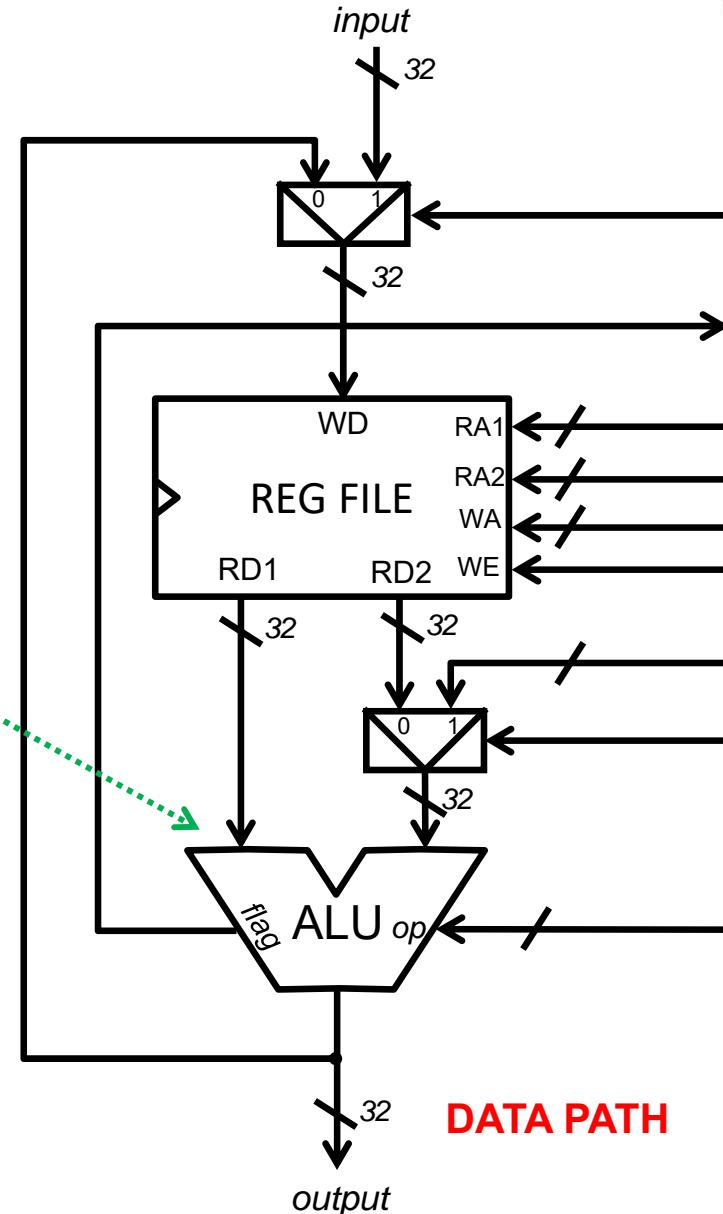A *generic ALU* is chosen, able to perform a wide enough range of arithmetic, logic and relational operations




General purpose data path



- However, it is possible to design a more generic data path:

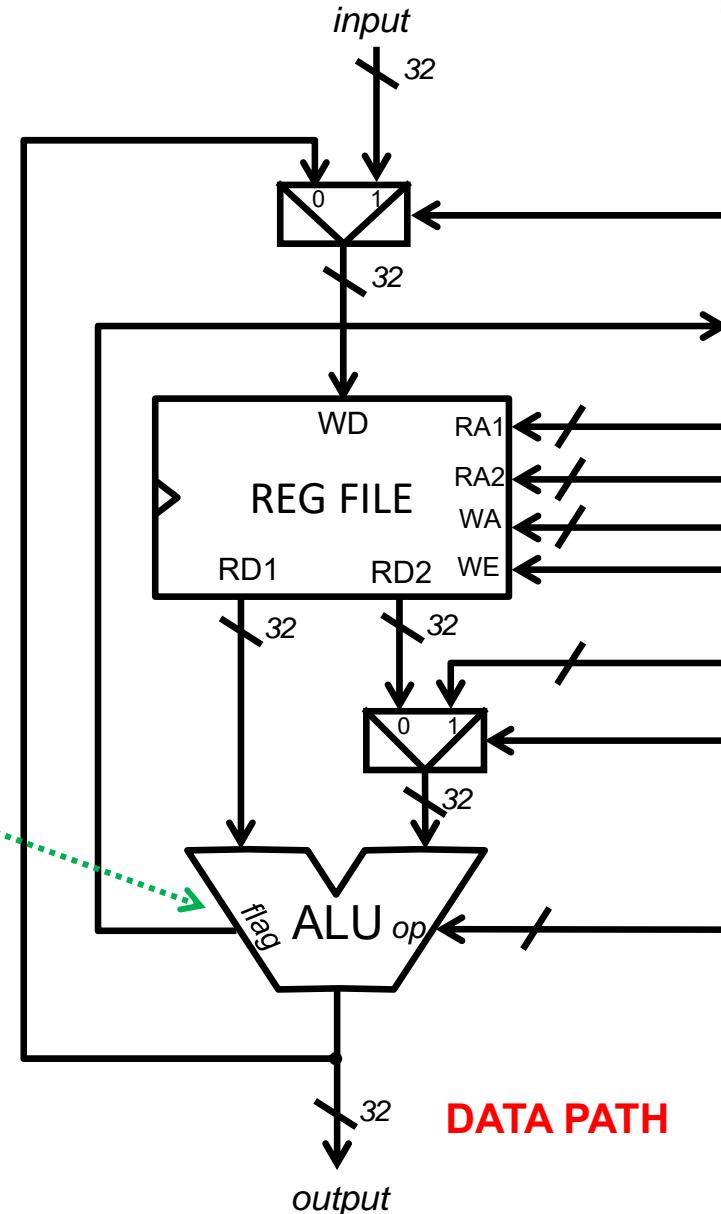The ALU has enough flags to indicate if the operands meet any kind of relation




General purpose data path



- However, it is possible to design a more generic data path:

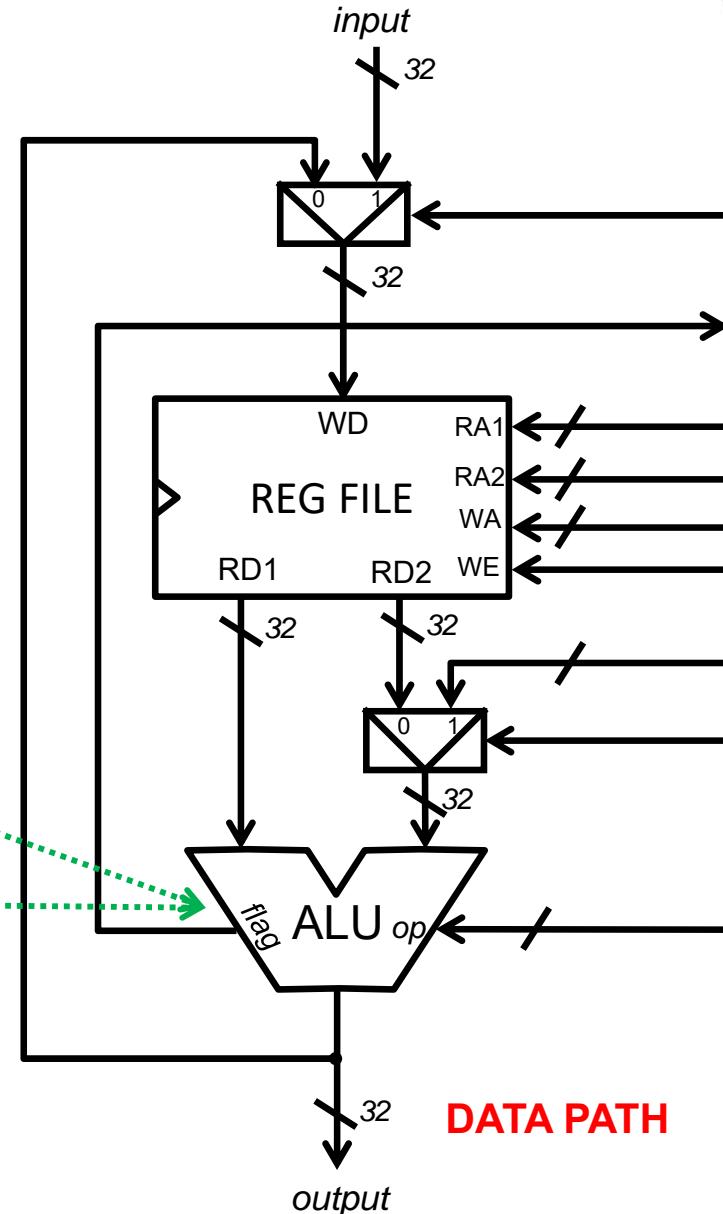The ALU has enough flags to indicate if the operands meet any kind of relation
Just for this case, let us assume that there is only one flag that takes the value of 1 when the ALU performs a comparison operation that it true





General purpose data path


Multiplication

Algorithm to multiply two 32-bit numbers

```
A = Ain;  
B = Bin;  
R = 0;  
for( C=0; C<=31; C++ )  
{  
    if( B0==1 )  
        R = R+A;  
    A = A<<1;  
    B = B>>1;  
};  
  
Rout = R;
```

Inputs and register transfers

S0 R0 ← input

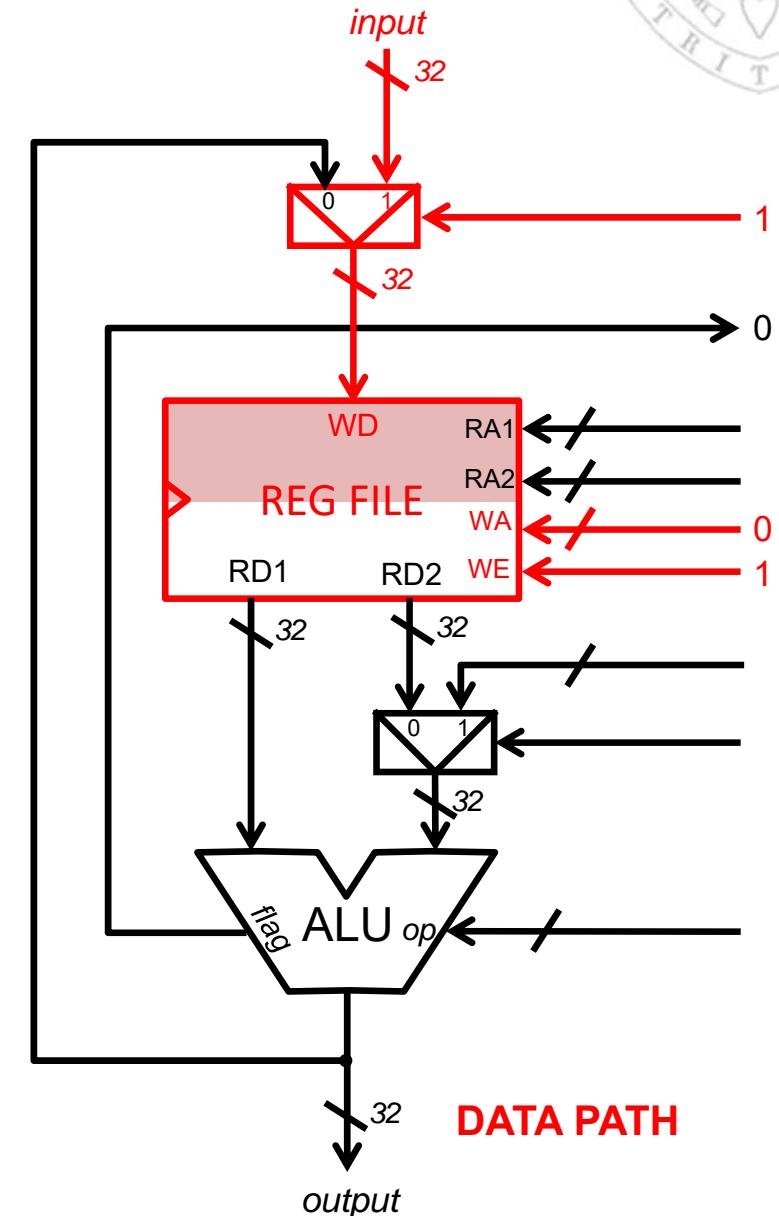

R0 is A



General purpose data path


Multiplication

Algorithm to multiply two 32-bit numbers

```
A = Ain;  
B = Bin;  
R = 0;  
for( C=0; C<=31; C++ )  
{  
    if( B0==1 )  
        R = R+A;  
    A = A<<1;  
    B = B>>1;  
};  
  
Rout = R;
```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input

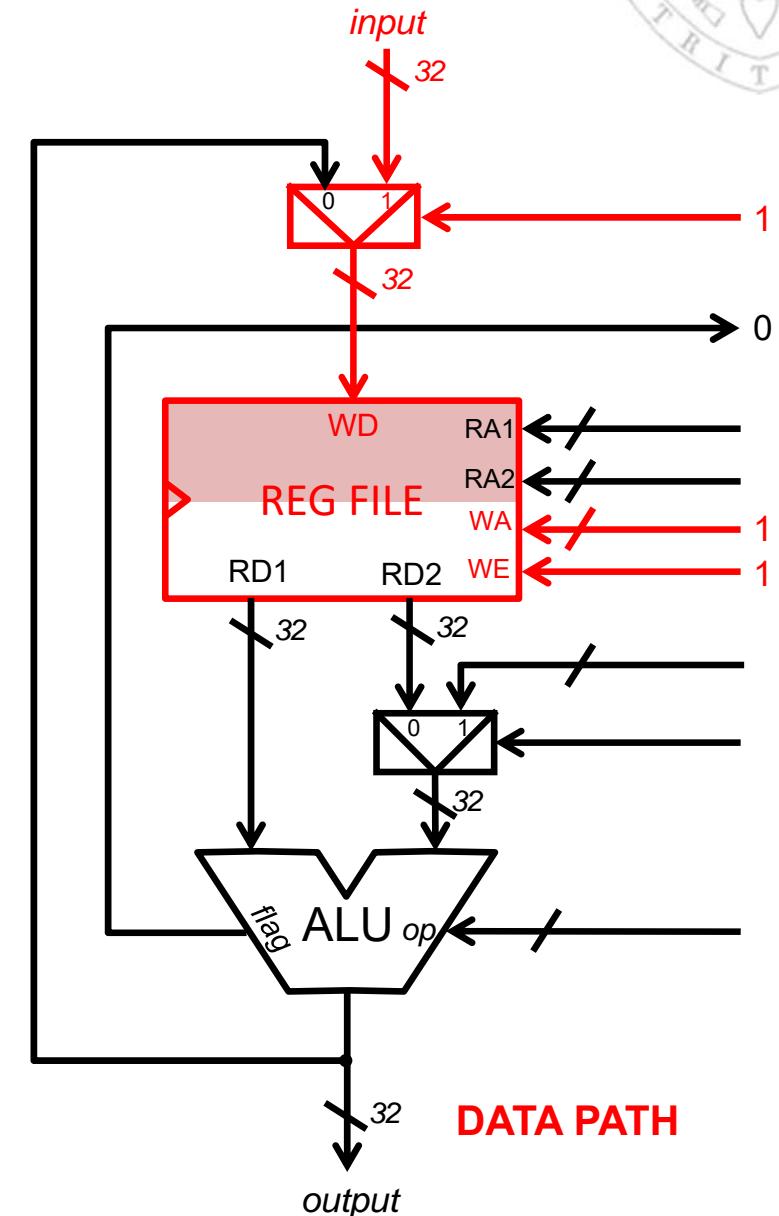

R0 is A R1 is B



General purpose data path


Multiplication

Algorithm to multiply two 32-bit numbers

```
A = Ain;  
B = Bin;  
R = 0;  
for( C=0; C<=31; C++ )  
{  
    if( B0==1 )  
        R = R+A;  
    A = A<<1;  
    B = B>>1;  
};  
  
Rout = R;
```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 - R2

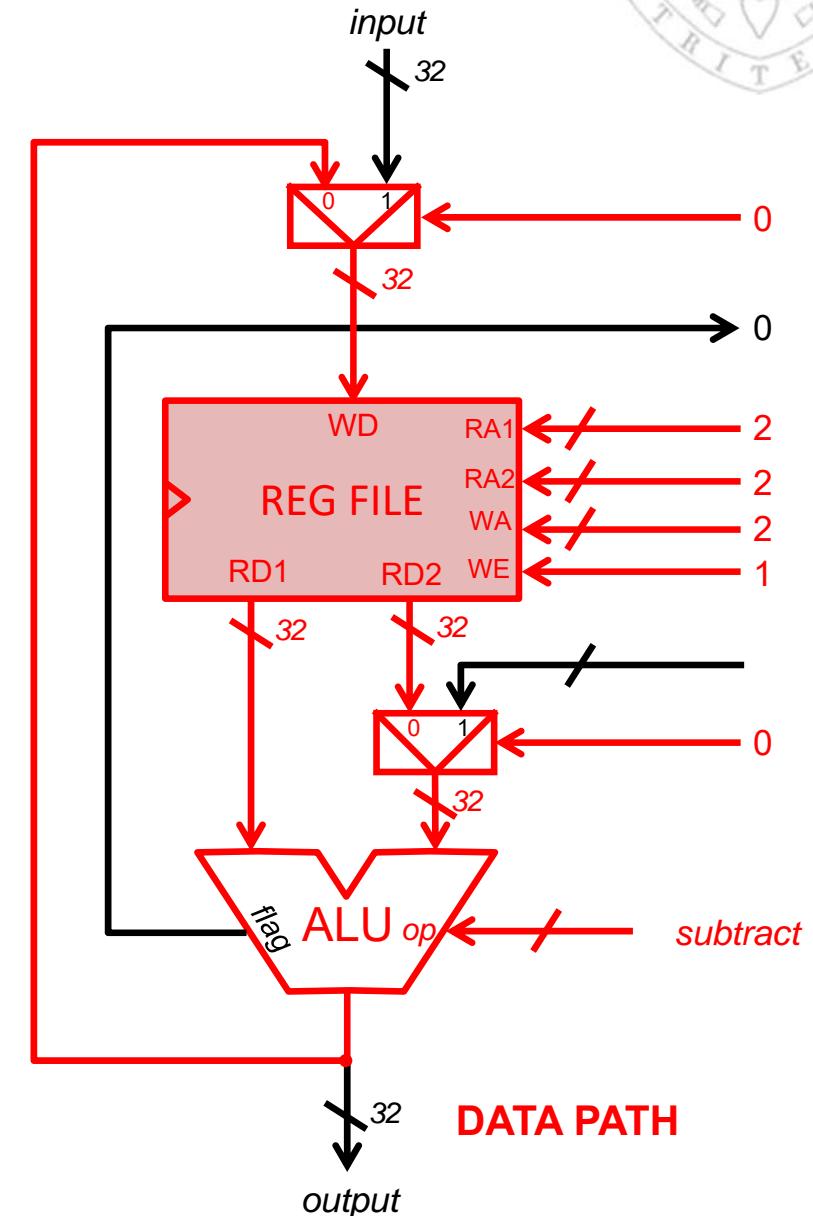

R0 is A R1 is B R2 is R



General purpose data path


Multiplication

Algorithm to multiply two 32-bit numbers

```
A = Ain;  
B = Bin;  
R = 0;  
for( C=0; C<=31; C++ )  
{  
    if( B0==1 )  
        R = R+A;  
    A = A<<1;  
    B = B>>1;  
};  
  
Rout = R;
```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 - R2
S3	R3 ← R3 - R3

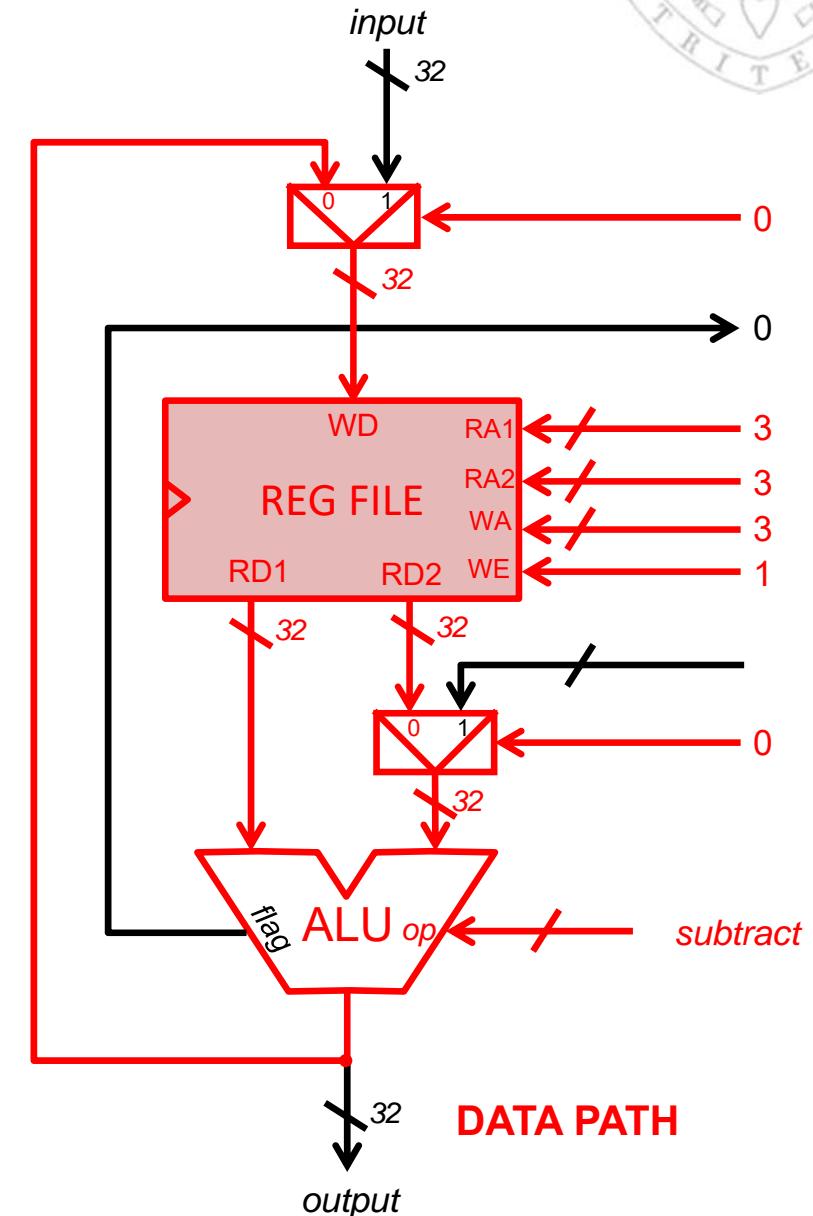

R0 is A R1 is B R2 is R R3 is C



General purpose data path

Multiplication

Algorithm to multiply two 32-bit numbers

```


A = Ain;
B = Bin;
R = 0;
for( C=0; C<=31; C++ )
{
    if( B0==1 )
        R = R+A;
    A = A<<1;
    B = B>>1;
};
Rout = R;

```

Inputs and register transfers

S0	R0 \leftarrow input
S1	R1 \leftarrow input
S2	R2 \leftarrow R2 - R2
S3	R3 \leftarrow R3 - R3
S4	if R3 > 31, go to S12

R0 is A R1 is B R2 is R R3 is C

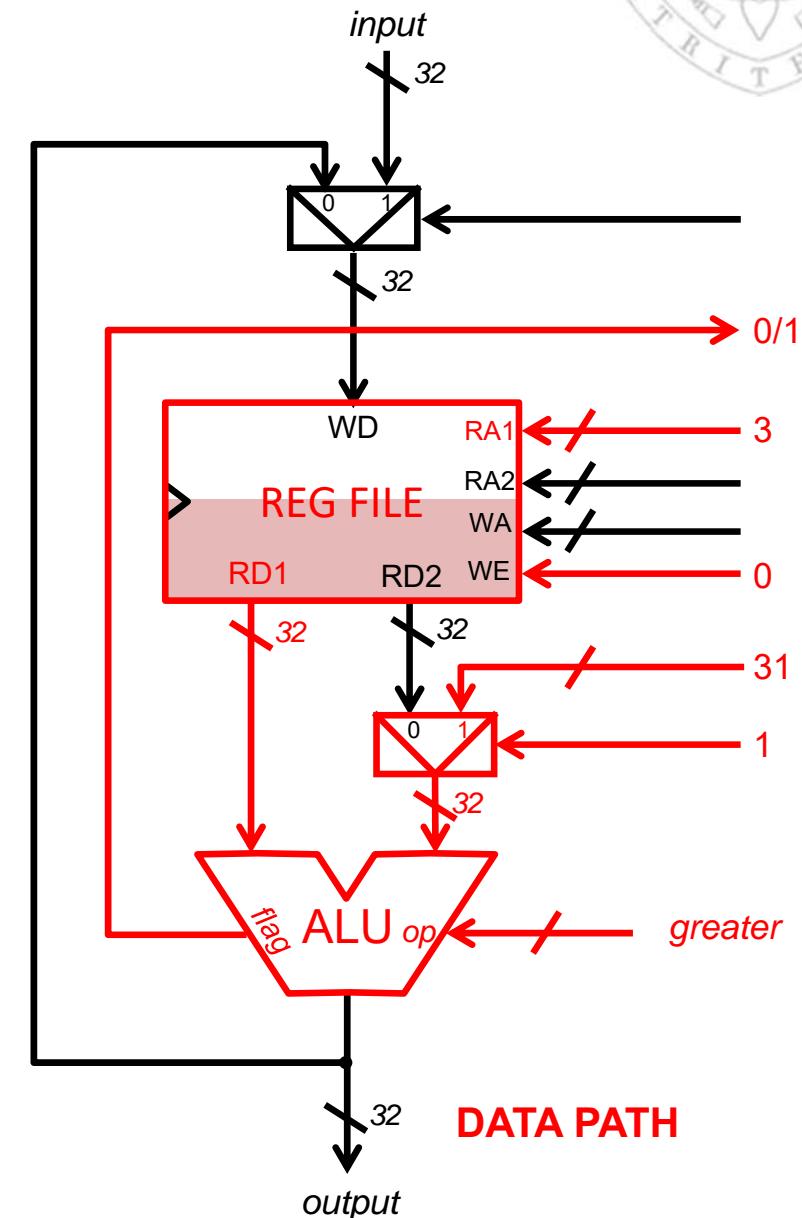



General purpose data path


Multiplication

Algorithm to multiply two 32-bit numbers

```
A = Ain;  
B = Bin;  
R = 0;  
for( C=0; C<=31; C++ )  
{  
    if( B0==1 )  
        R = R+A;  
    A = A<<1;  
    B = B>>1;  
};  
  
Rout = R;
```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 - R2
S3	R3 ← R3 - R3
S4	if R3 > 31, go to S12
S5	R4 ← R1 & 1

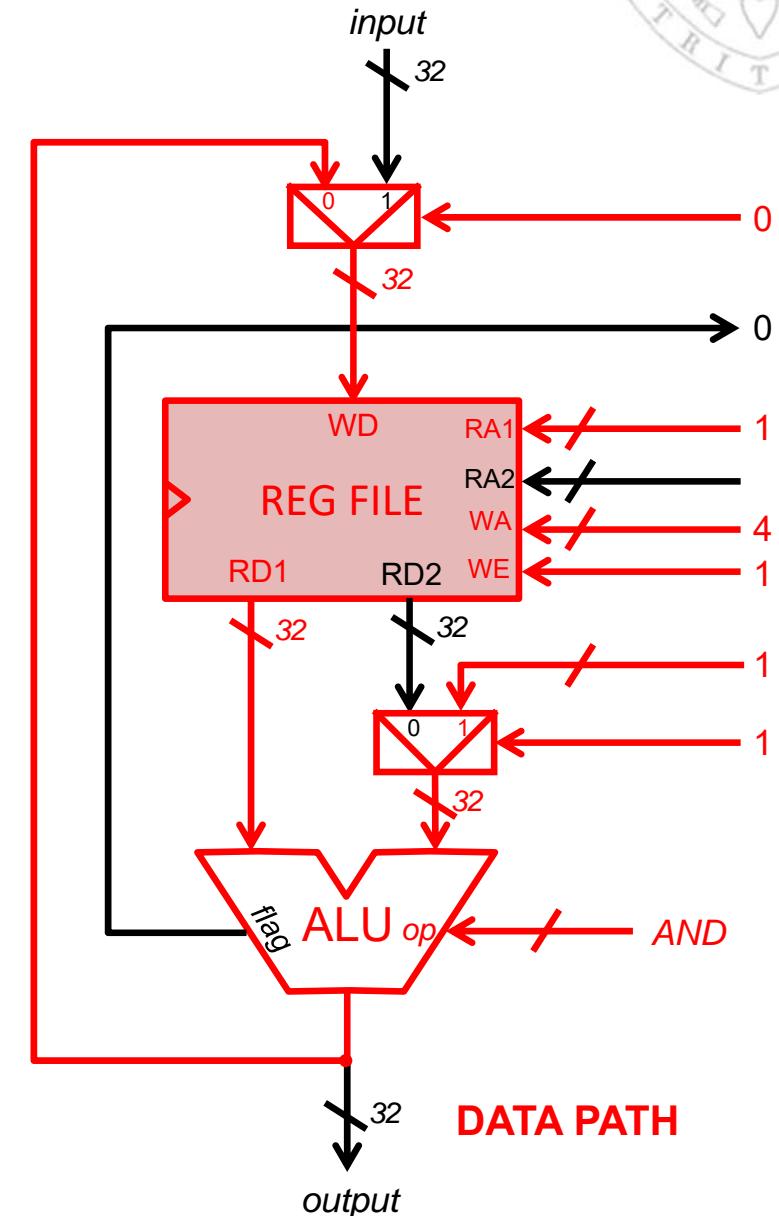

R0 is A R1 is B R2 is R R3 is C



General purpose data path

Multiplication

Algorithm to multiply two 32-bit numbers

```


A = Ain;
B = Bin;
R = 0;
for( C=0; C<=31; C++ )
{
    if( B0==1 )
        R = R+A;
    A = A<<1;
    B = B>>1;
};

Rout = R;

```

Inputs and register transfers

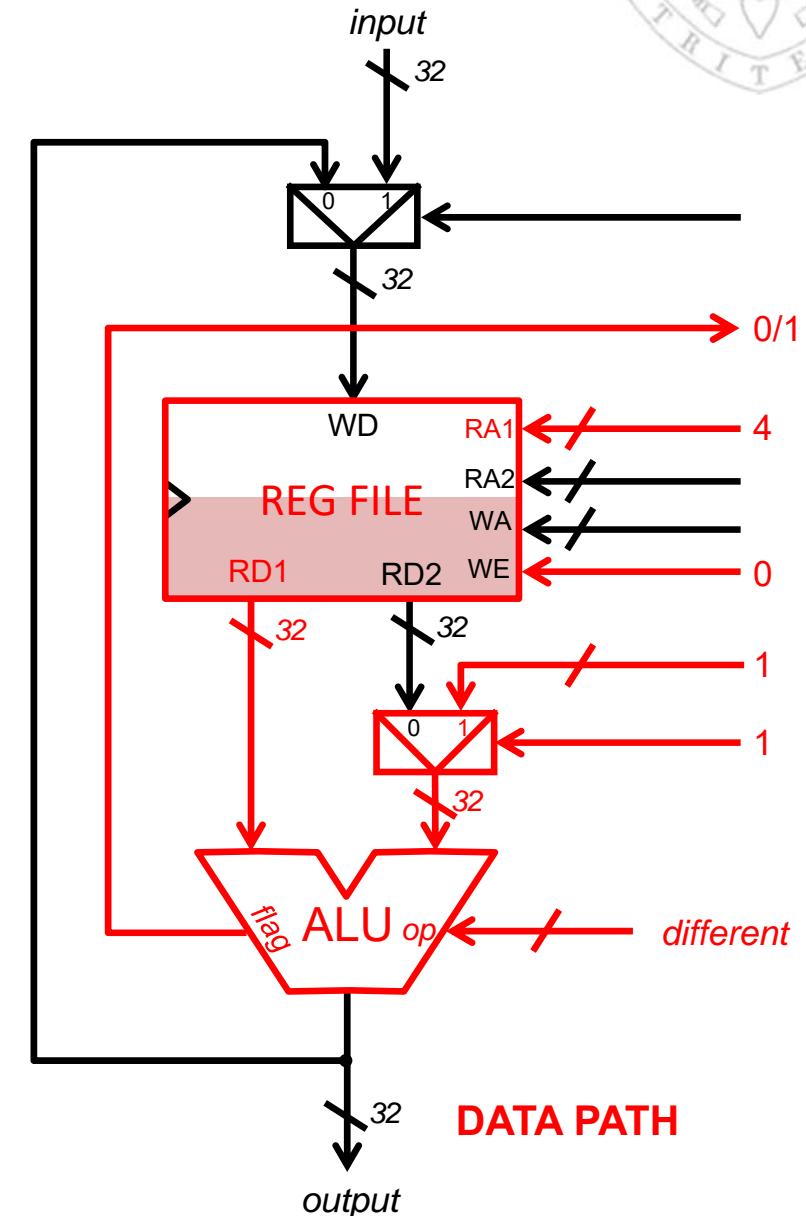- S0 R0 ← input
- S1 R1 ← input
- S2 R2 ← R2 – R2
- S3 R3 ← R3 – R3
- S4 if R3 > 31, go to S12
- S5 R4 ← R1 & 1
- S6 if R4 != 1, go to S8



R0 is A R1 is B R2 is R R3 is C



General purpose data path

Multiplication

Algorithm to multiply two 32-bit numbers

```


A = Ain;
B = Bin;
R = 0;
for( C=0; C<=31; C++ )
{
    if( B0==1 )
        R = R+A;
    A = A<<1;
    B = B>>1;
};

Rout = R;

```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 - R2
S3	R3 ← R3 - R3
S4	if R3 > 31, go to S12
S5	R4 ← R1 & 1
S6	if R4 != 1, go to S8
S7	R2 ← R2 + R0

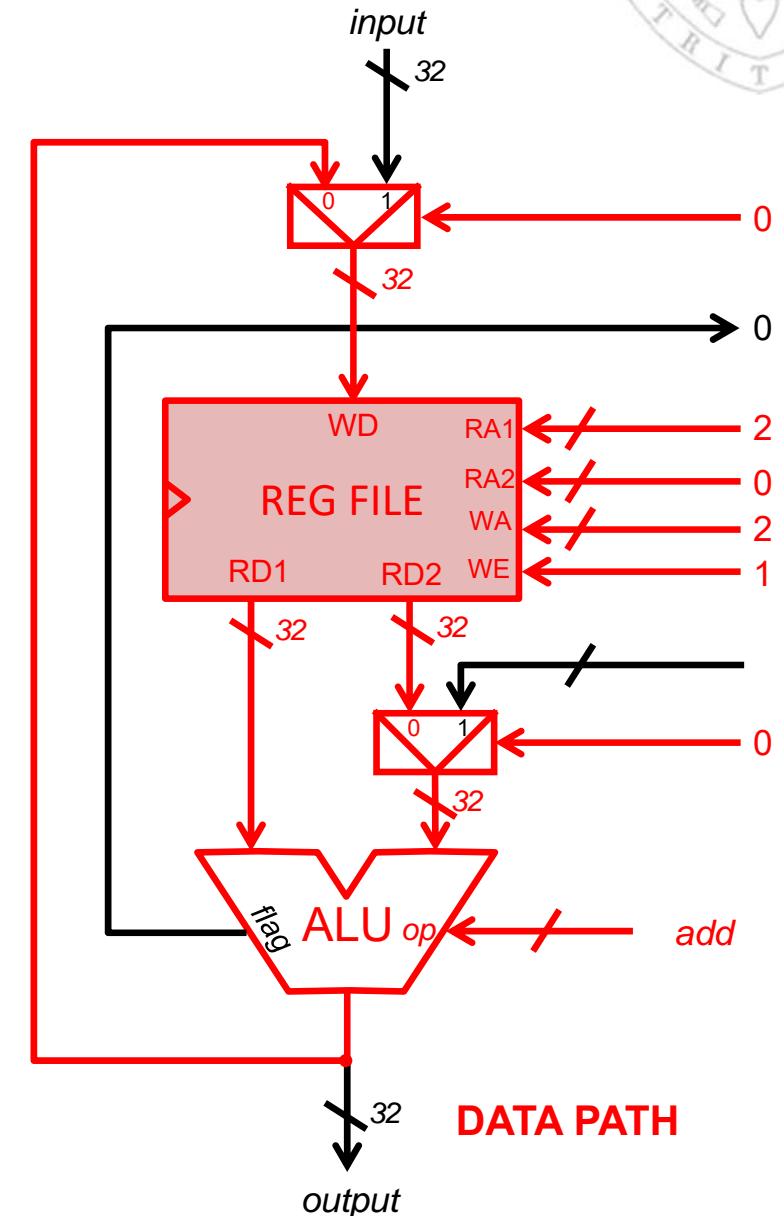

R0 is A R1 is B R2 is R R3 is C



General purpose data path


Multiplication

Algorithm to multiply two 32-bit numbers

```
A = Ain;  
B = Bin;  
R = 0;  
for( C=0; C<=31; C++ )  
{  
    if( B0==1 )  
        R = R+A;  
    A = A<<1;  
    B = B>>1;  
};  
  
Rout = R;
```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 - R2
S3	R3 ← R3 - R3
S4	if R3 > 31, go to S12
S5	R4 ← R1 & 1
S6	if R4 != 1, go to S8
S7	R2 ← R2 + R0
S8	R0 ← R0 << 1

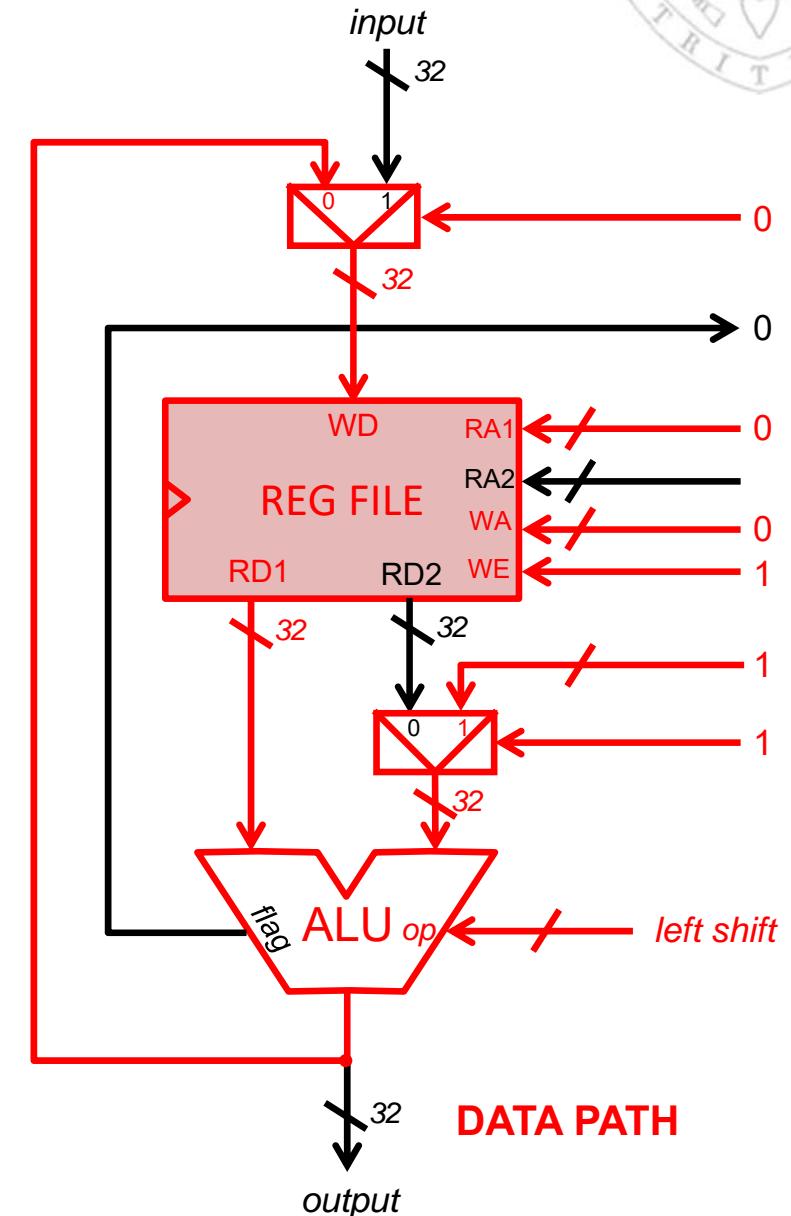

R0 is A R1 is B R2 is R R3 is C



General purpose data path

Multiplication

Algorithm to multiply two 32-bit numbers

```


A = Ain;
B = Bin;
R = 0;
for( C=0; C<=31; C++ )
{
    if( B0==1 )
        R = R+A;
    A = A<<1;
    B = B>>1;
};

Rout = R;

```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 - R2
S3	R3 ← R3 - R3
S4	if R3 > 31, go to S12
S5	R4 ← R1 & 1
S6	if R4 != 1, go to S8
S7	R2 ← R2 + R0
S8	R0 ← R0 << 1
S9	R1 ← R1 >> 1

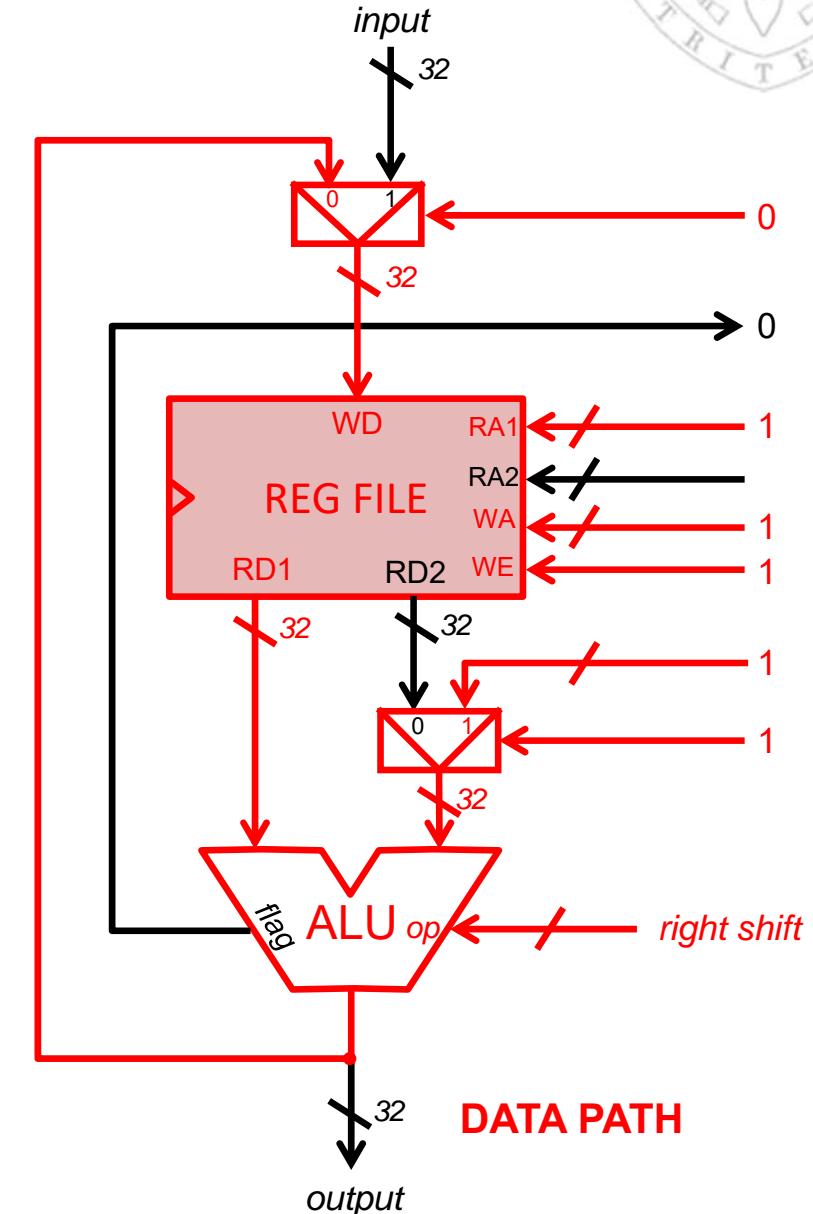

R0 is A R1 is B R2 is R R3 is C



General purpose data path

Multiplication

Algorithm to multiply two 32-bit numbers

```

A = Ain;
B = Bin;
R = 0;
for( C=0; C<=31; C++ )
{
    if( B0==1 )
        R = R+A;
    A = A<<1;
    B = B>>1;
};


Rout = R;

```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 - R2
S3	R3 ← R3 - R3
S4	if R3 > 31, go to S12
S5	R4 ← R1 & 1
S6	if R4 != 1, go to S8
S7	R2 ← R2 + R0
S8	R0 ← R0 << 1
S9	R1 ← R1 >> 1
S10	R3 ← R3 + 1

R0 is A R1 is B R2 is R R3 is C

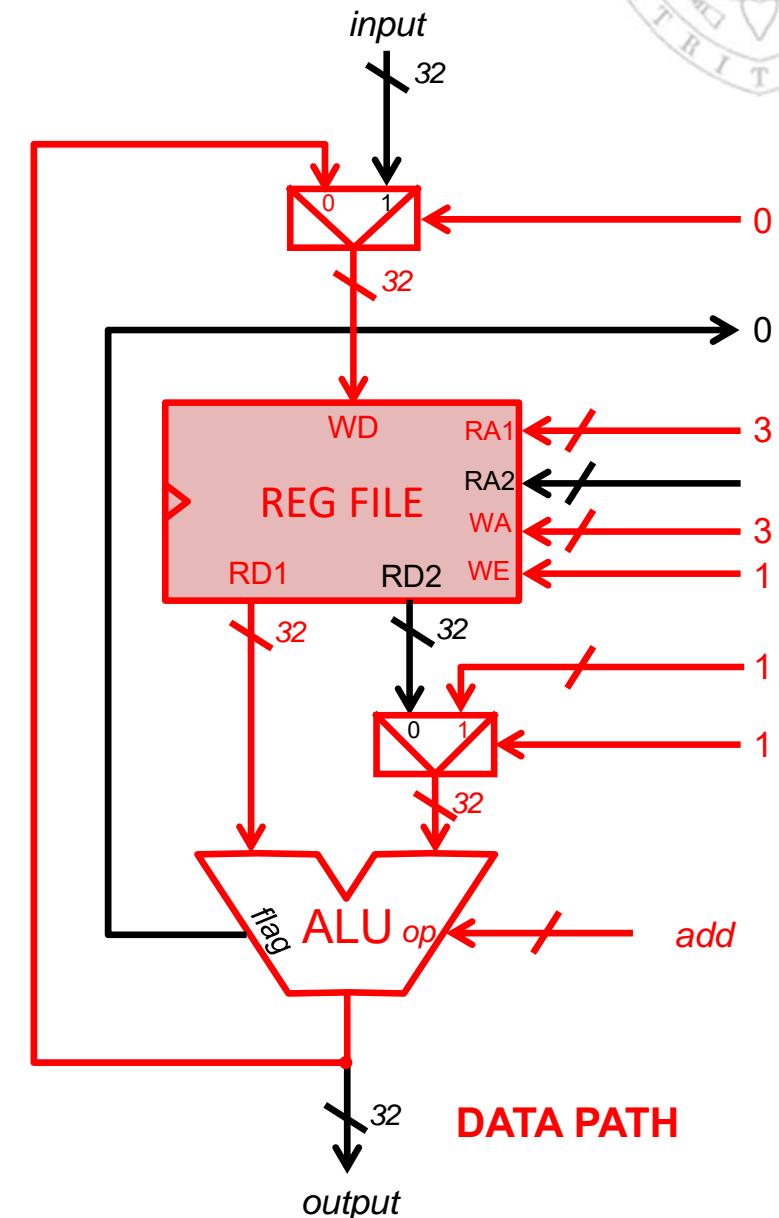



General purpose data path


Multiplication

Algorithm to multiply two 32-bit numbers

```
A = Ain;  
B = Bin;  
R = 0;  
for( C=0; C<=31; C++ )  
{  
    if( B0==1 )  
        R = R+A;  
    A = A<<1;  
    B = B>>1;  
};  
  
Rout = R;
```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 - R2
S3	R3 ← R3 - R3
S4	if R3 > 31, go to S12
S5	R4 ← R1 & 1
S6	if R4 != 1, go to S8
S7	R2 ← R2 + R0
S8	R0 ← R0 << 1
S9	R1 ← R1 >> 1
S10	R3 ← R3 + 1
S11	if R0 == R0, go to S4

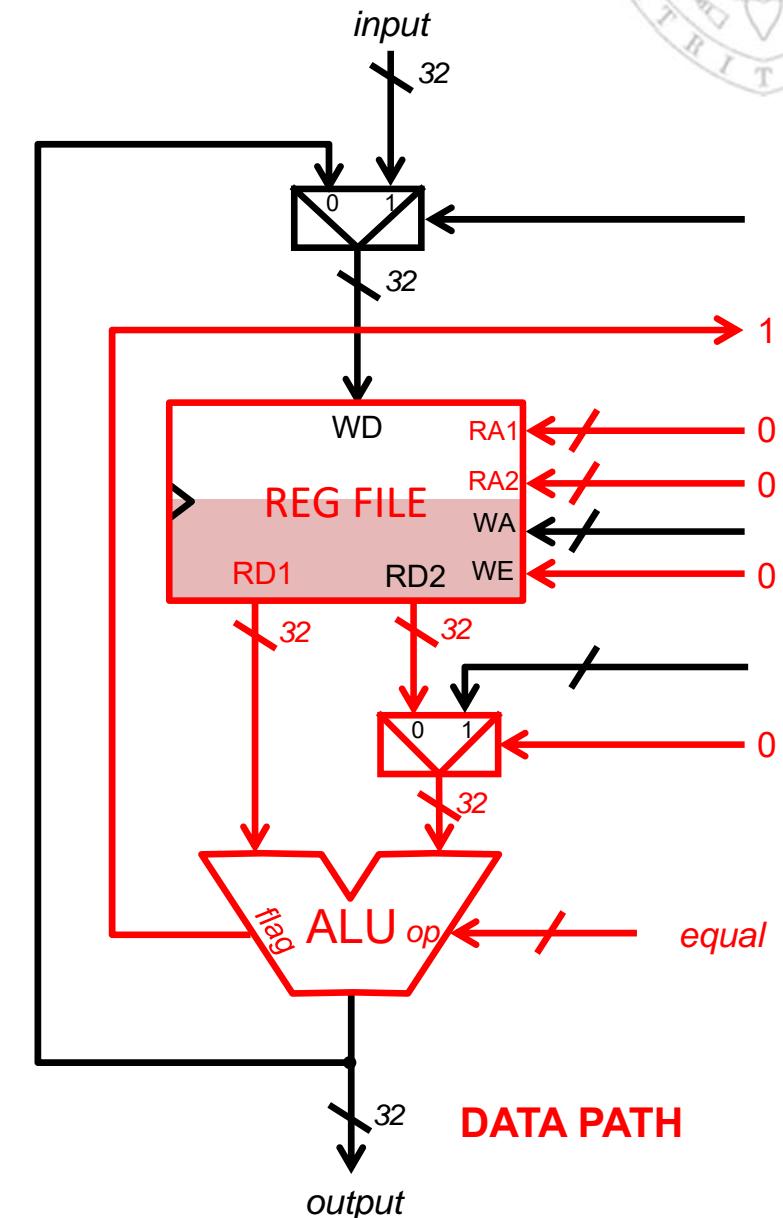

R0 is A R1 is B R2 is R R3 is C



General purpose data path

Multiplication

Algorithm to multiply two 32-bit numbers

```

A = Ain;
B = Bin;
R = 0;
for( C=0; C<=31; C++ )
{
    if( B0==1 )
        R = R+A;
    A = A<<1;
    B = B>>1;
};


Rout = R;

```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 - R2
S3	R3 ← R3 - R3
S4	if R3 > 31, go to S12
S5	R4 ← R1 & 1
S6	if R4 != 1, go to S8
S7	R2 ← R2 + R0
S8	R0 ← R0 << 1
S9	R1 ← R1 >> 1
S10	R3 ← R3 + 1
S11	if R0 == R0, go to S4
S12	output ← R2

R0 is A R1 is B R2 is R R3 is C

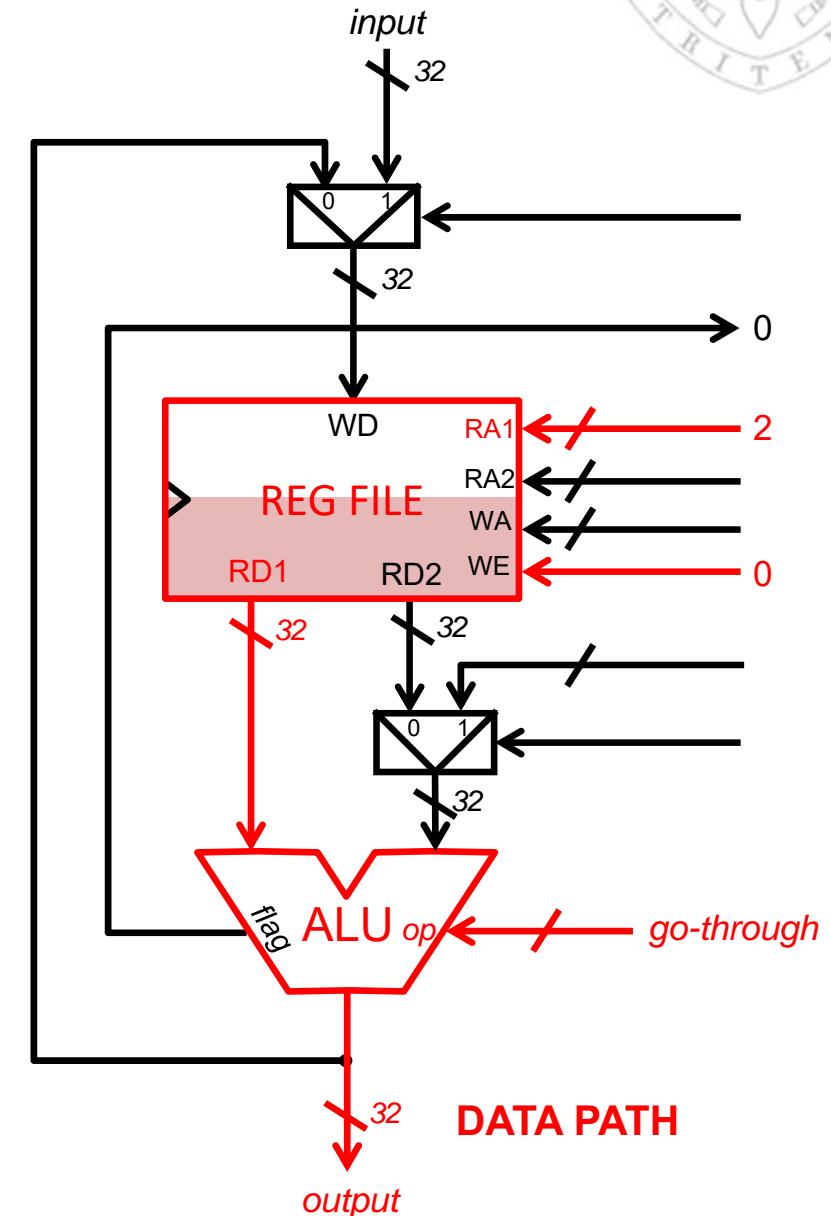



General purpose data path

Multiplication

15/01/23 version

module 1:
From digital systems to computers

Algorithm to multiply two 32-bit numbers

```

A = Ain;
B = Bin;
R = 0;

for( C=0; C<=31; C++ )
{
    if( B0==1 )

        R = R+A;


    A = A<<1;
    B = B>>1;
}

Rout = R;

```

Inputs and register transfers

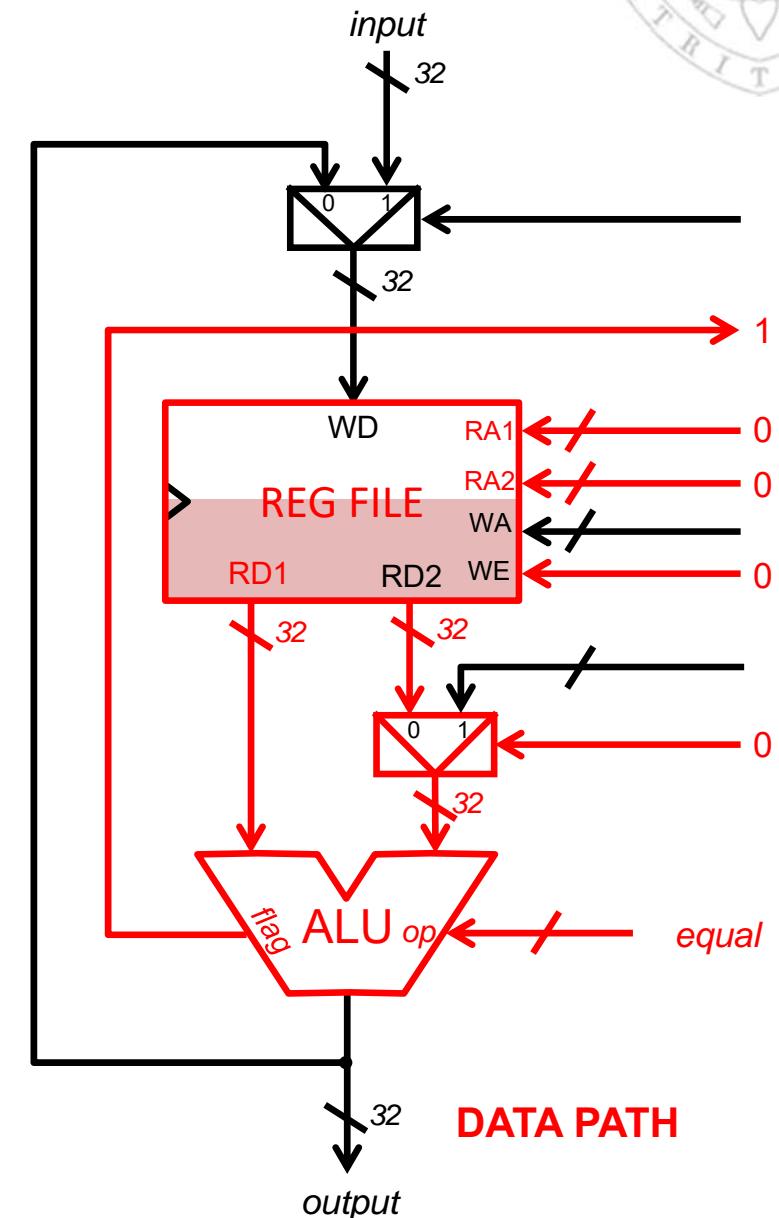S0 R0 ← input
S1 R1 ← input
S2 R2 ← R2 – R2
S3 R3 ← R3 – R3
S4 if R3 > 31, go to S12
S5 R4 ← R1 & 1
S6 if R4 != 1, go to S8
S7 R2 ← R2 + R0
S8 R0 ← R0 << 1
S9 R1 ← R1 >> 1
S10 R3 ← R3 + 1
S11 if R0 == R0, go to S4
S12 output ← R2
S13 if R0 == R0, go to S0





General purpose data path

Greatest common divisor


Algorithm to calculate the GCD
of two 32-bit numbers

```
A = Ain;  
B = Bin;  
R = 0;  
  
if( A!=0 && B!=0 )  
{  
    while( A!=B )  
        if( A>B )  
            A = A-B;  
        else  
            B = B-A;  
  
    R = A;  
};  
Rout = R;
```

Inputs and register transfers

S0 R0 \leftarrow input

R0 is A

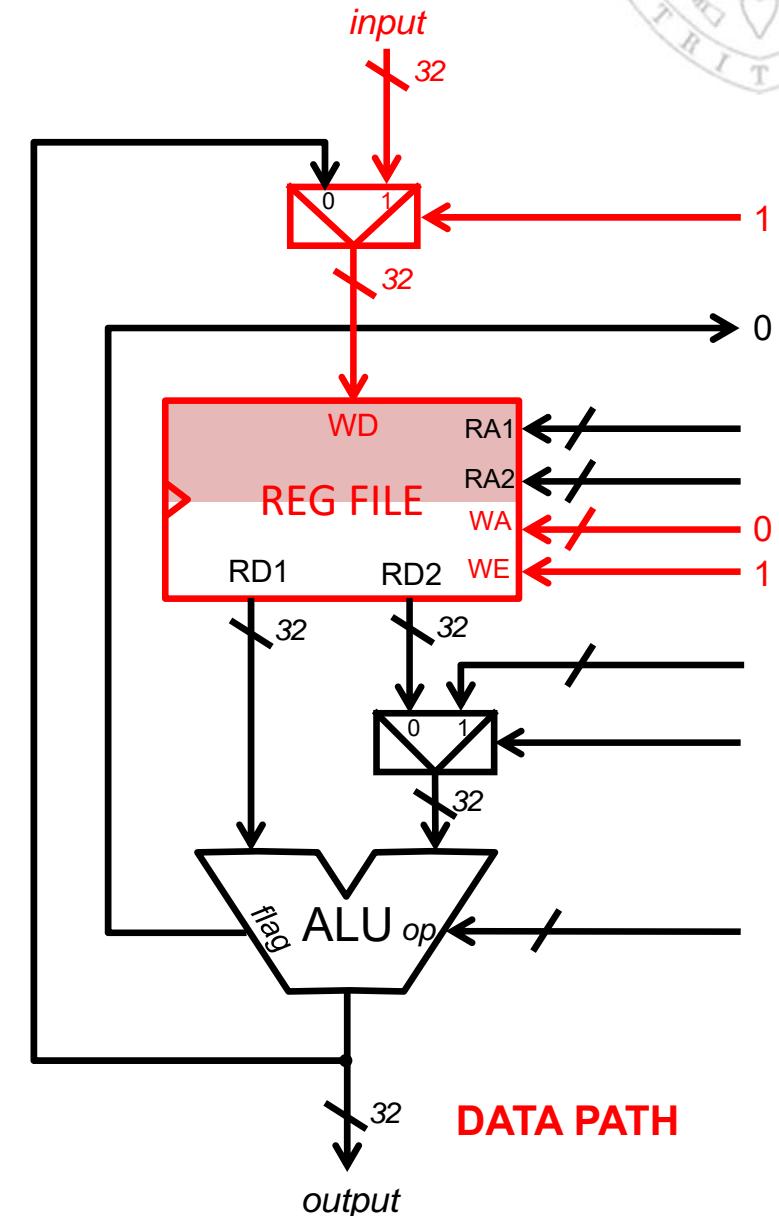



General purpose data path

Greatest common divisor

Algorithm to calculate the GCD
of two 32-bit numbers


```
A = Ain;  
B = Bin;  
R = 0;  
if( A!=0 && B!=0 )  
{  
    while( A!=B )  
        if( A>B )  
            A = A-B;  
        else  
            B = B-A;  
  
    R = A;  
};  
Rout = R;
```

Inputs and register transfers

S0 R0 ← input

S1 R1 ← input

R0 is A R1 is B

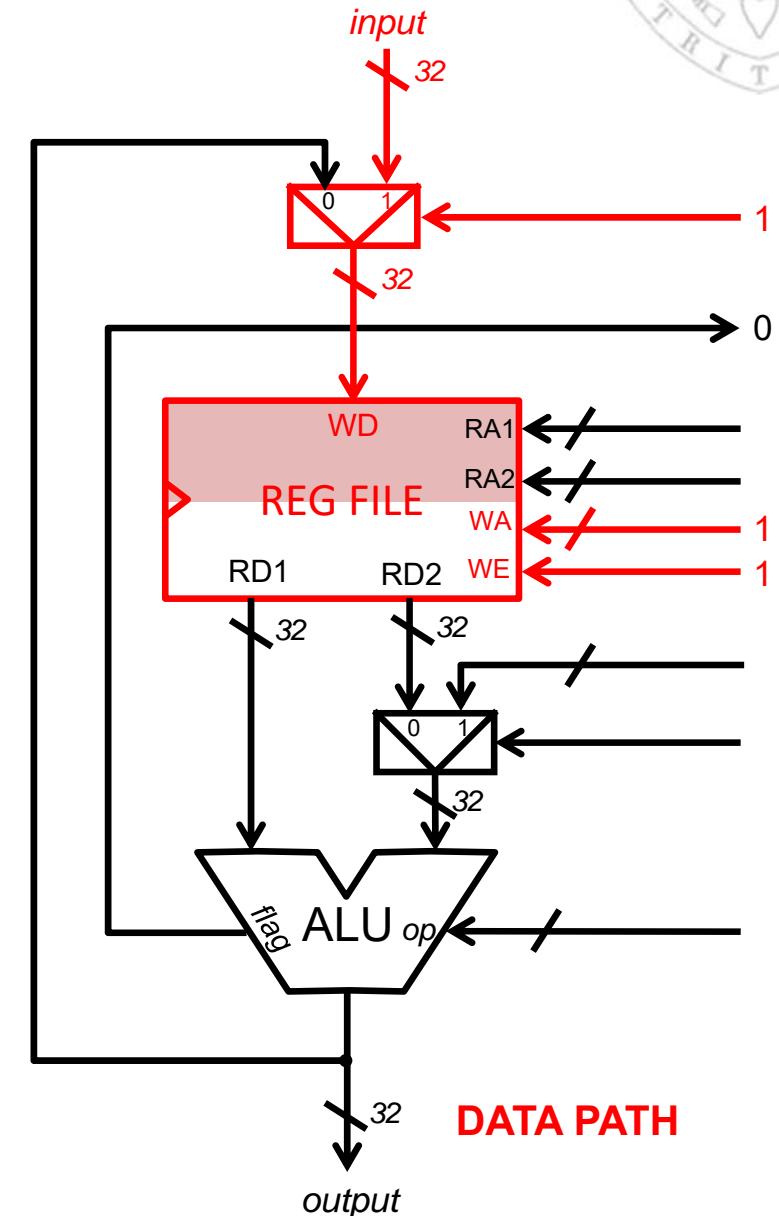

General purpose data path

Greatest common divisor



*Algorithm to calculate the GCD
of two 32-bit numbers*

```
A = Ain;
B = Bin;
R = 0;

if( A!=0 && B!=0 )
{
    while( A!=B )
        if( A>B )
            A = A-B;
        else
            B = B-A;


    R = A;
};

Rout = R;
```

Inputs and register transfers

S0	R0 \leftarrow input
S1	R1 \leftarrow input
S2	R2 \leftarrow R2 - R2

R0 is A R1 is B R2 is R

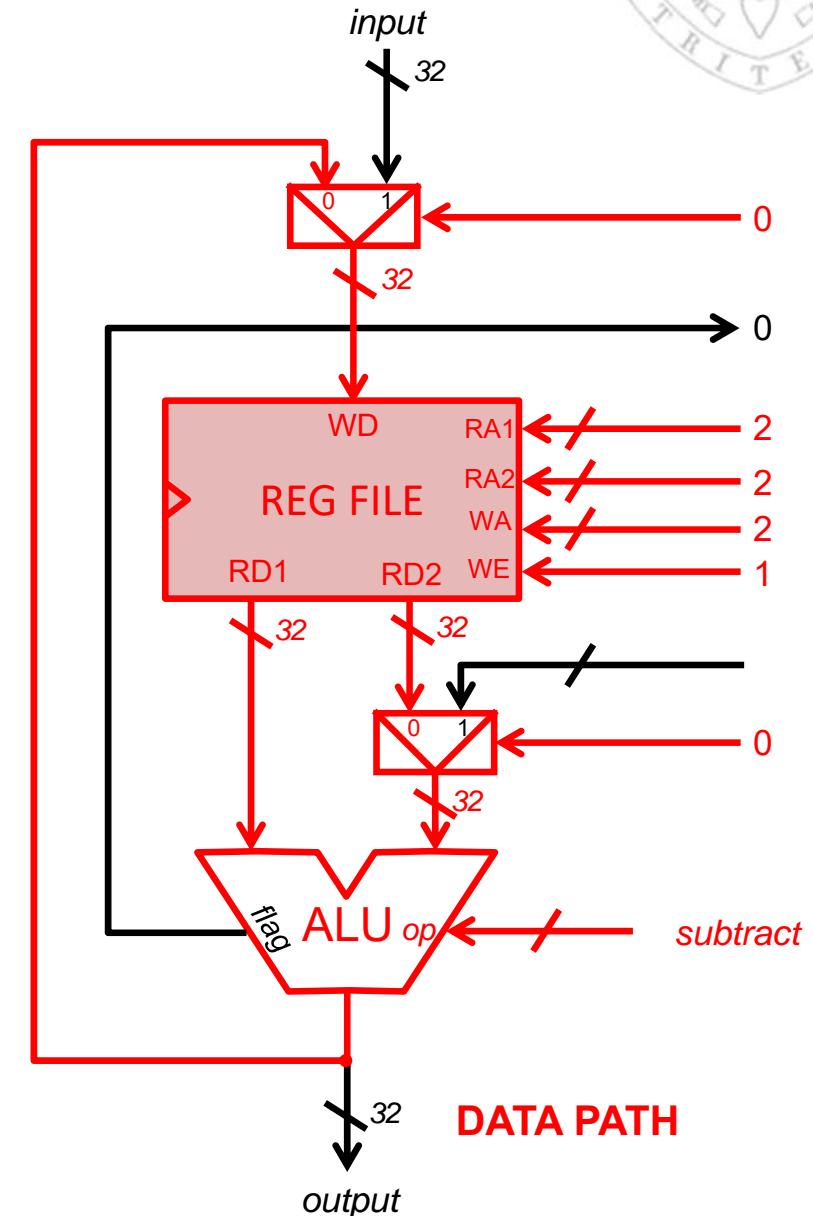



General purpose data path

Greatest common divisor

*Algorithm to calculate the GCD
of two 32-bit numbers*

```
A = Ain;
B = Bin;
R = 0;


if( A!=0 && B!=0 )
{
    while( A!=B )
        if( A>B )
            A = A-B;
        else
            B = B-A;

    R = A;
}
Rout = R;
```

Inputs and register transfers

S0	R0 \leftarrow input
S1	R1 \leftarrow input
S2	R2 \leftarrow R2 - R2
S3	if R0 == 0, go to S12

R0 is A R1 is B R2 is R

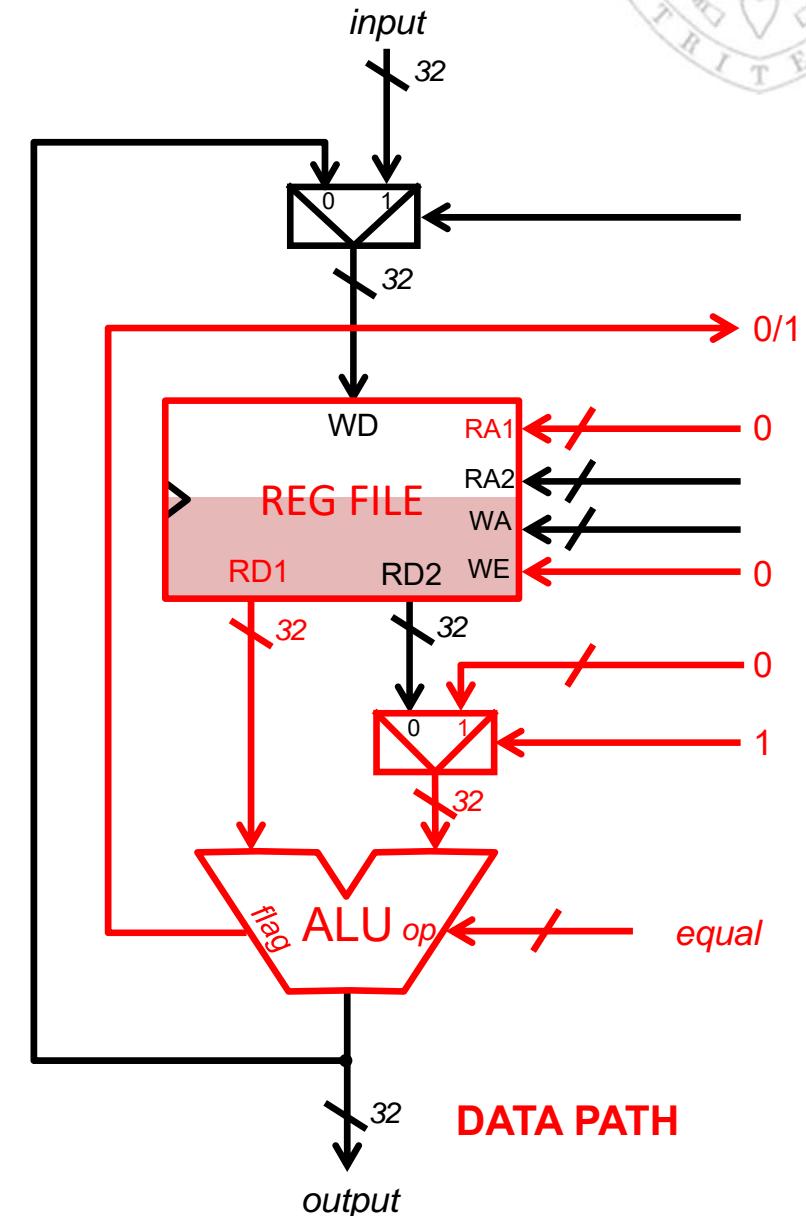



General purpose data path

Greatest common divisor

*Algorithm to calculate the GCD
of two 32-bit numbers*

```
A = Ain;
B = Bin;
R = 0;


if( A!=0 && B!=0 )
{
    while( A!=B )
        if( A>B )
            A = A-B;
        else
            B = B-A;

    R = A;
}
Rout = R;
```

Inputs and register transfers

S0	R0 \leftarrow input
S1	R1 \leftarrow input
S2	R2 \leftarrow R2 - R2
S3	if R0 == 0, go to S12
S4	if R1 == 0, go to S12

R0 is A R1 is B R2 is R

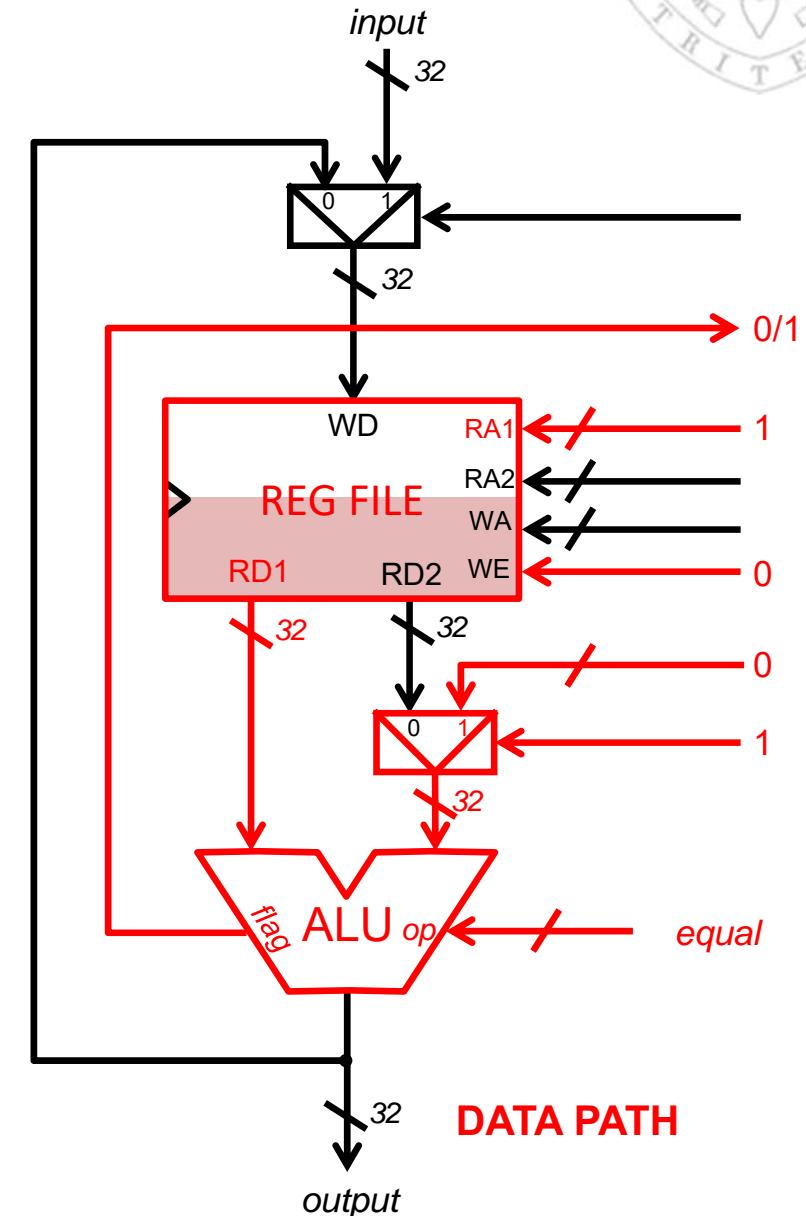



General purpose data path


Greatest common divisor

*Algorithm to calculate the GCD
of two 32-bit numbers*

```
A = Ain;  
B = Bin;  
R = 0;  
if( A!=0 && B!=0 )  
{  
    while( A!=B )  
        if( A>B )  
            A = A-B;  
        else  
            B = B-A;  
  
    R = A;  
}  
Rout = R;
```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 – R2
S3	if R0 == 0, go to S12
S4	if R1 == 0, go to S12
S5	if R0 == R1, go to S11

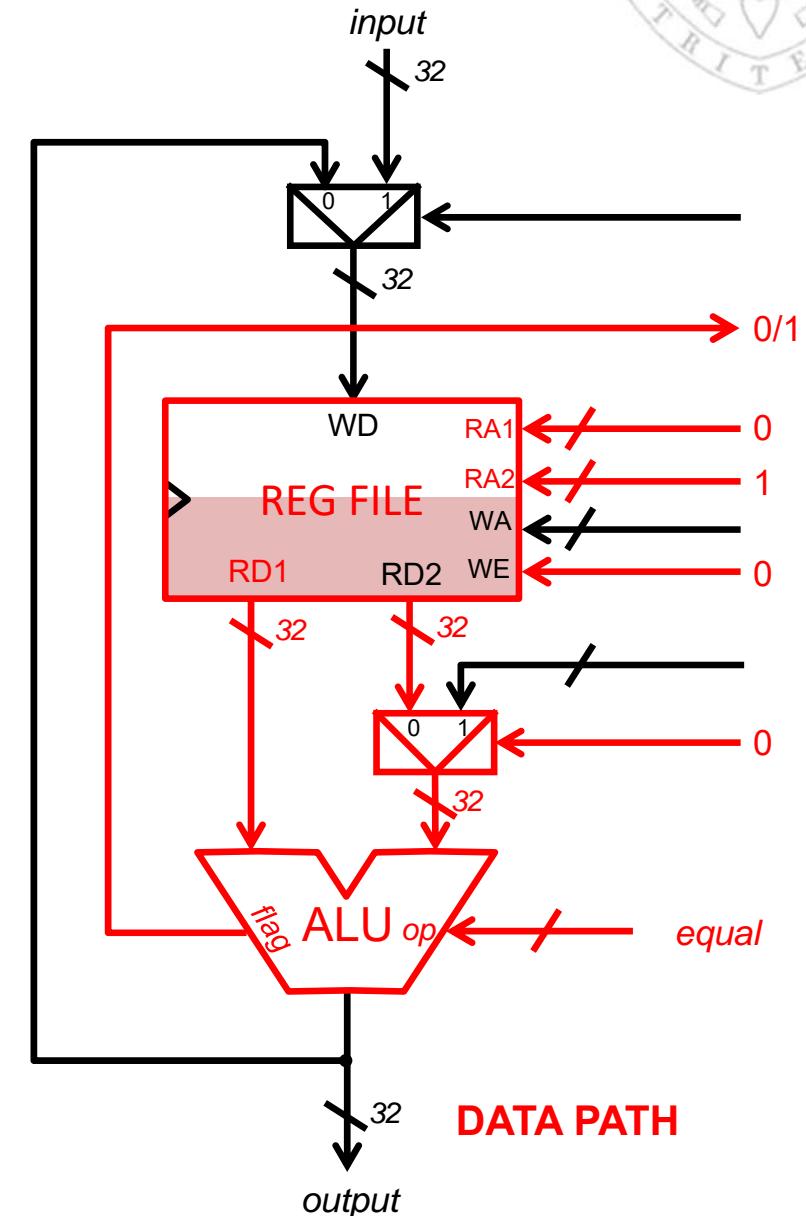

R0 is A R1 is B R2 is R



General purpose data path

Greatest common divisor

*Algorithm to calculate the GCD
of two 32-bit numbers*


```
A = Ain;
B = Bin;
R = 0;

if( A!=0 && B!=0 )
{
    while( A!=B )
        if( A>B )
            A = A-B;
        else
            B = B-A;

    R = A;
}
Rout = R;
```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 – R2
S3	if R0 == 0, go to S12
S4	if R1 == 0, go to S12
S5	if R0 == R1, go to S11
S6	if R0 <= R1, go to S9

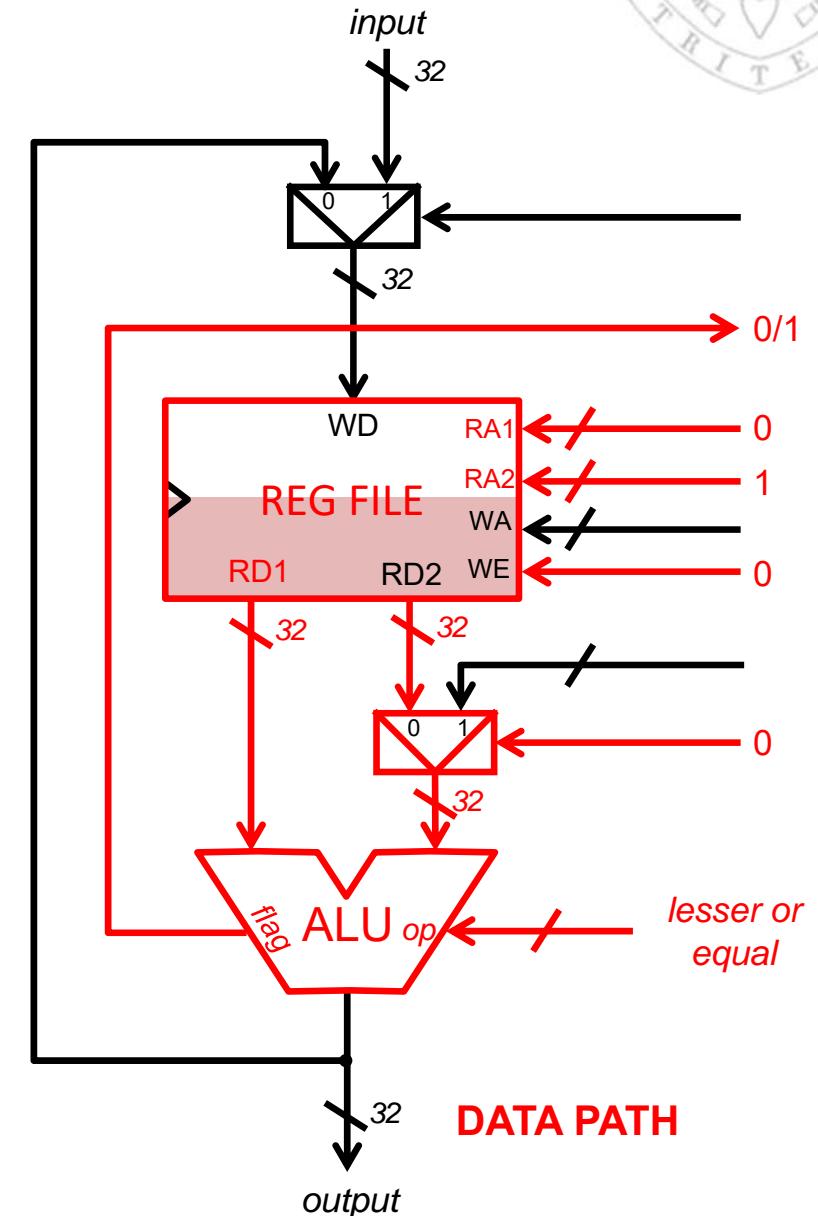

R0 is A R1 is B R2 is R



General purpose data path

Greatest common divisor

*Algorithm to calculate the GCD
of two 32-bit numbers*

```
A = Ain;
B = Bin;
R = 0;


if( A!=0 && B!=0 )
{
    while( A!=B )
        if( A>B )
            A = A-B;
        else
            B = B-A;

    R = A;
};

Rout = R;
```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 – R2
S3	if R0 == 0, go to S12
S4	if R1 == 0, go to S12
S5	if R0 == R1, go to S11
S6	if R0 <= R1, go to S9
S7	R0 ← R0 – R1

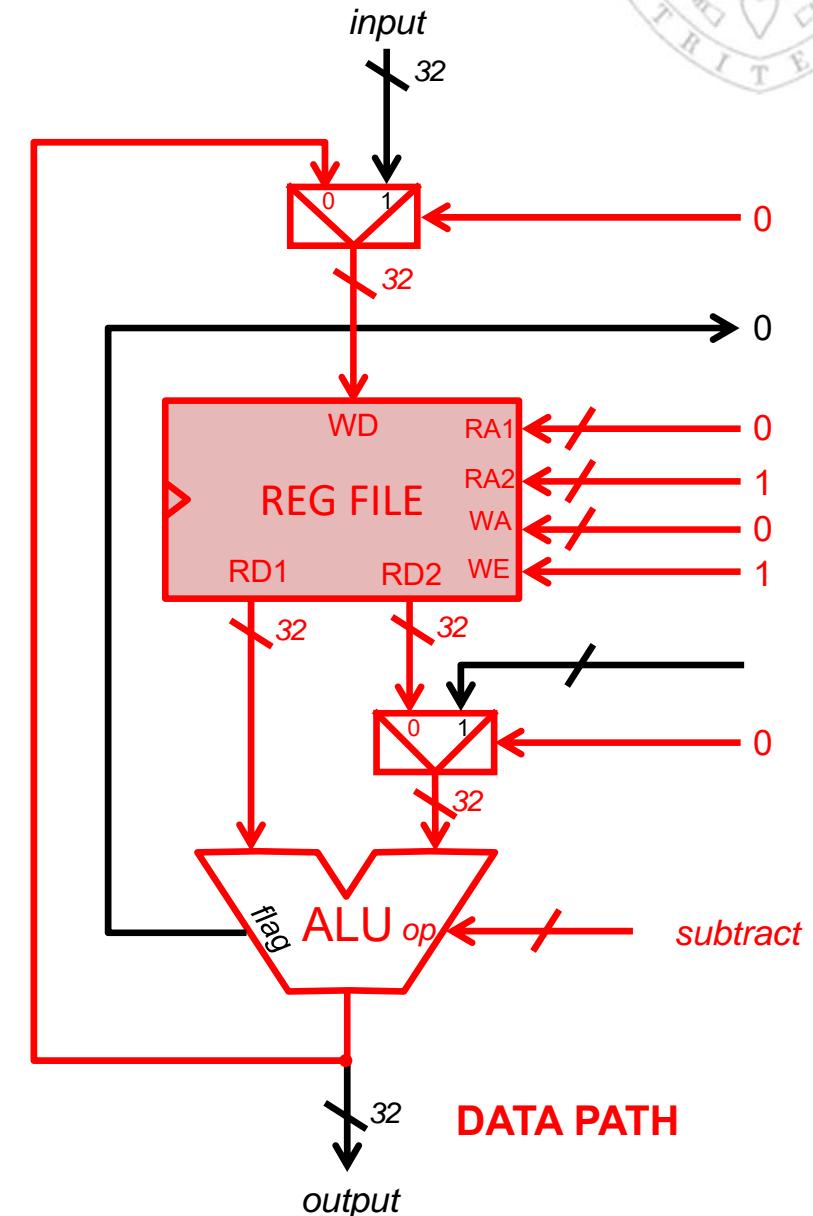

R0 is A R1 is B R2 is R



General purpose data path

Greatest common divisor

*Algorithm to calculate the GCD
of two 32-bit numbers*

```

A = Ain;
B = Bin;
R = 0;

if( A!=0 && B!=0 )
{
    while( A!=B )
        if( A>B )
            A = A-B;
        else
            B = B-A;


    R = A;
};

Rout = R;

```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 – R2
S3	if R0 == 0, go to S12
S4	if R1 == 0, go to S12
S5	if R0 == R1, go to S11
S6	if R0 <= R1, go to S9
S7	R0 ← R0 – R1
S8	if R0 == R0, go to S5

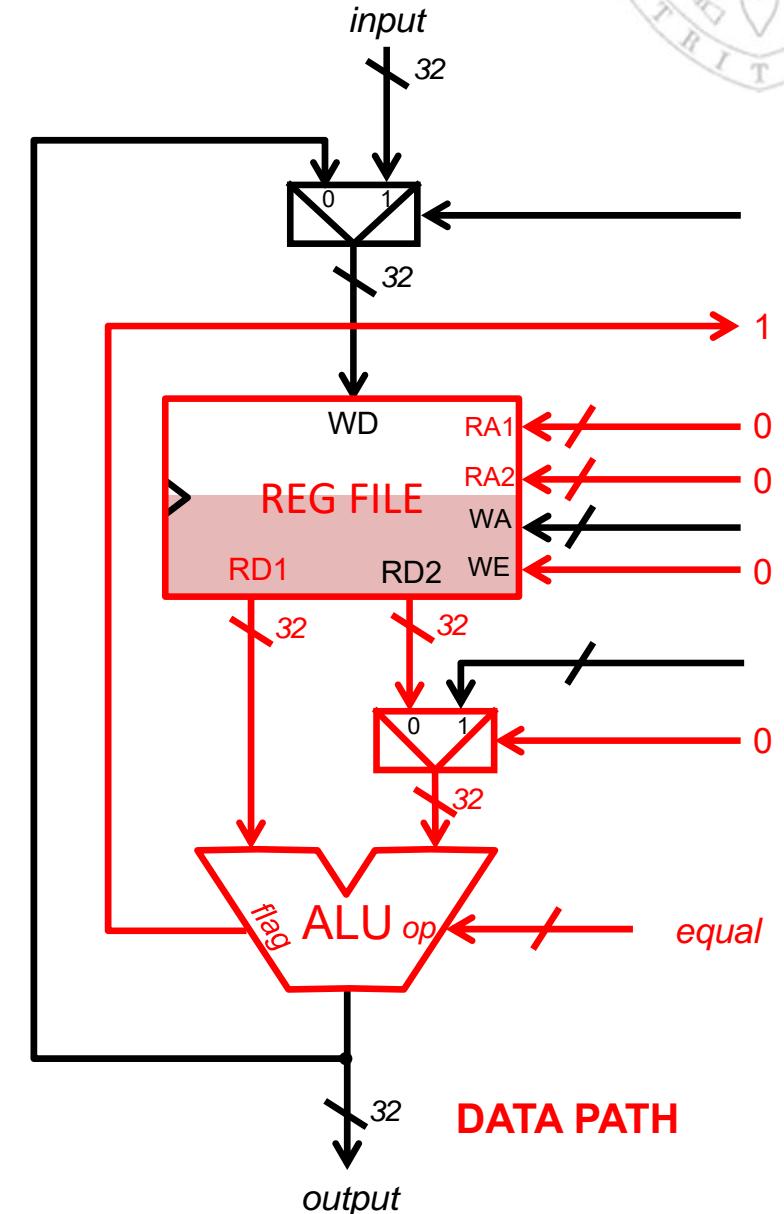

R0 is A R1 is B R2 is R



General purpose data path

Greatest common divisor

15/01/23 version


module 1:
From digital systems to computers

Algorithm to calculate the GCD of two 32-bit numbers

```
A = Ain;  
B = Bin;  
R = 0;  
if( A!=0 && B!=0 )  
{  
    while( A!=B )  
        if( A>B )  
            A = A-B;  
        else  
            B = B-A;  
  
    R = A;  
}  
Rout = R;
```

Inputs and register transfers

S0	R0 \leftarrow input
S1	R1 \leftarrow input
S2	R2 \leftarrow R2 – R2
S3	if R0 == 0, go to S12
S4	if R1 == 0, go to S12
S5	if R0 == R1, go to S11
S6	if R0 <= R1, go to S9
S7	R0 \leftarrow R0 – R1
S8	if R0 == R0, go to S5
S9	R1 \leftarrow R1 – R0

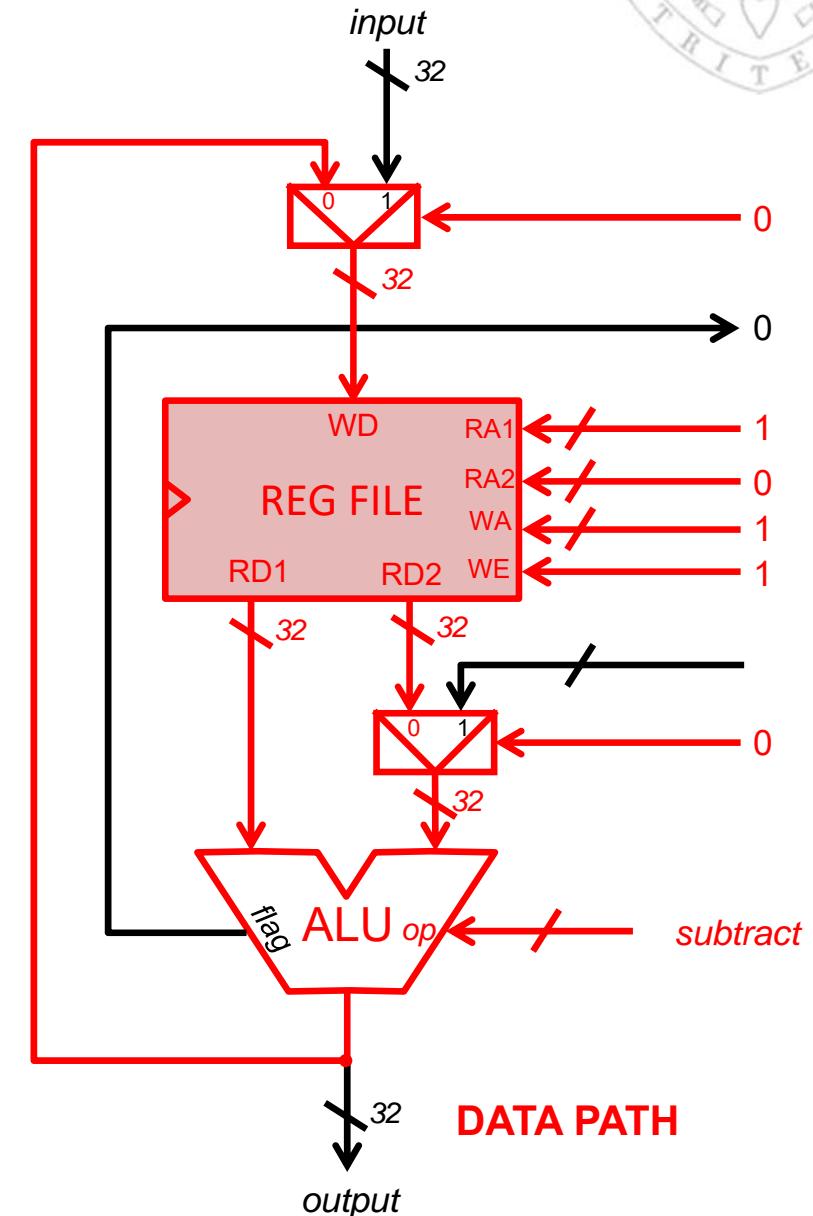



General purpose data path

Greatest common divisor

*Algorithm to calculate the GCD
of two 32-bit numbers*

```
A = Ain;
B = Bin;
R = 0;

if( A!=0 && B!=0 )
{
    while( A!=B )
        if( A>B )
            A = A-B;
        else
            B = B-A;


    R = A;
};

Rout = R;
```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 – R2
S3	if R0 == 0, go to S12
S4	if R1 == 0, go to S12
S5	if R0 == R1, go to S11
S6	if R0 <= R1, go to S9
S7	R0 ← R0 – R1
S8	if R0 == R0, go to S5
S9	R1 ← R1 – R0
S10	if R0 == R0, go to S5

R0 is A R1 is B R2 is R

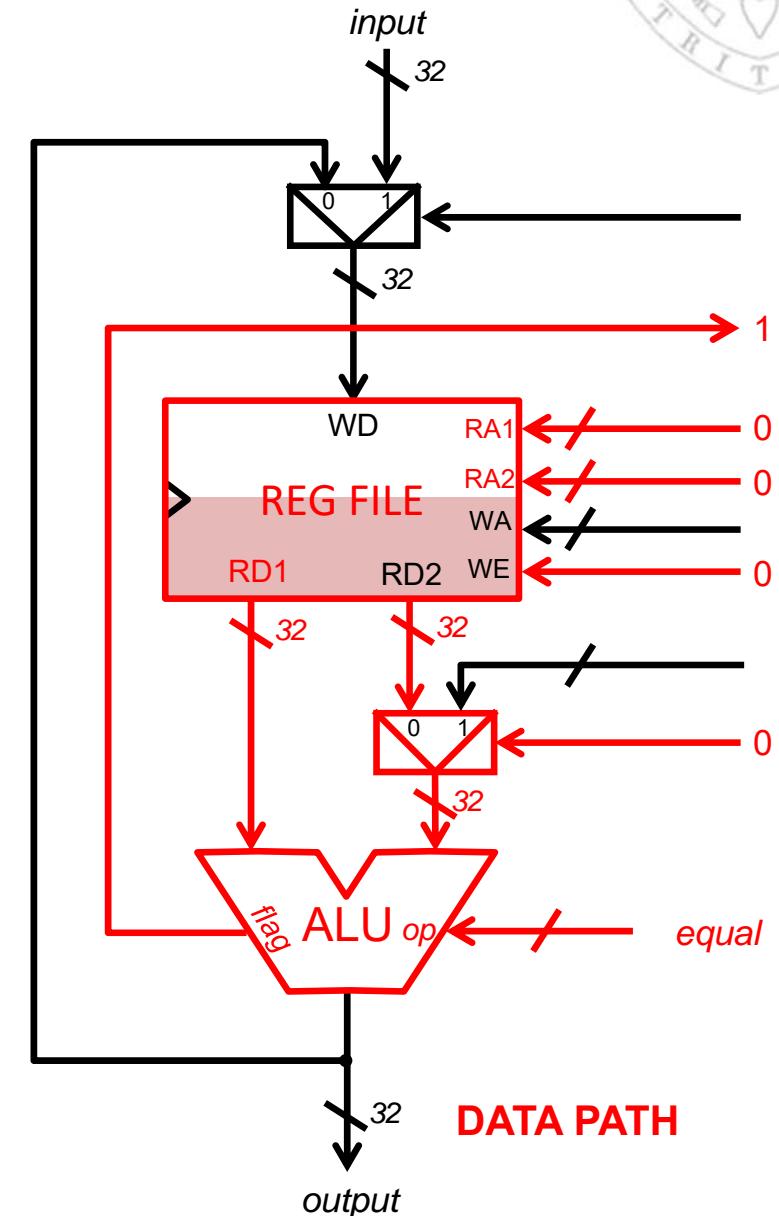



General purpose data path

Greatest common divisor

*Algorithm to calculate the GCD
of two 32-bit numbers*

```

A = Ain;
B = Bin;
R = 0;
if( A!=0 && B!=0 )
{
    while( A!=B )
        if( A>B )
            A = A-B;
        else
            B = B-A;


    R = A;
}
Rout = R;

```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 – R2
S3	if R0 == 0, go to S12
S4	if R1 == 0, go to S12
S5	if R0 == R1, go to S11
S6	if R0 <= R1, go to S9
S7	R0 ← R0 – R1
S8	if R0 == R0, go to S5
S9	R1 ← R1 – R0
S10	if R0 == R0, go to S5
S11	R2 ← R0 + 0

R0 is A R1 is B R2 is R

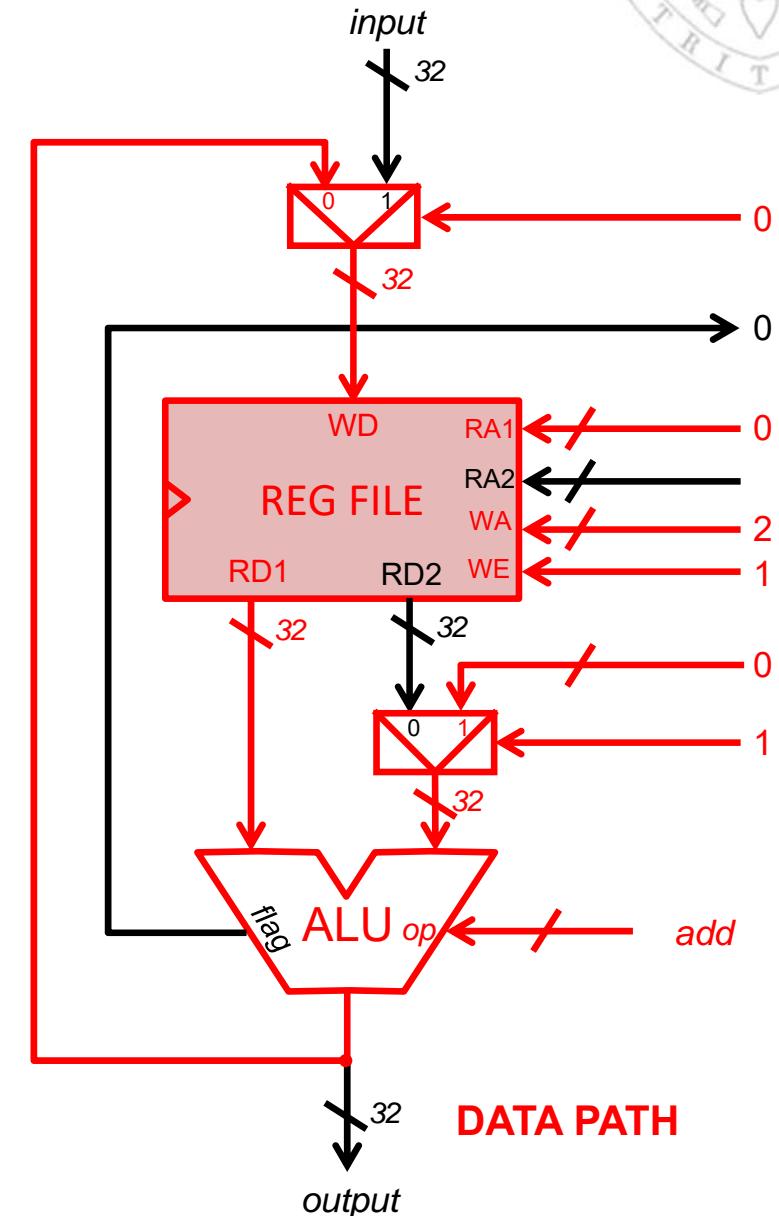



General purpose data path

Greatest common divisor

*Algorithm to calculate the GCD
of two 32-bit numbers*

```
A = Ain;
B = Bin;
R = 0;

if( A!=0 && B!=0 )
{
    while( A!=B )
        if( A>B )
            A = A-B;
        else
            B = B-A;


    R = A;
};

Rout = R;
```

Inputs and register transfers

S0	R0 ← input
S1	R1 ← input
S2	R2 ← R2 – R2
S3	if R0 == 0, go to S12
S4	if R1 == 0, go to S12
S5	if R0 == R1, go to S11
S6	if R0 <= R1, go to S9
S7	R0 ← R0 – R1
S8	if R0 == R0, go to S5
S9	R1 ← R1 – R0
S10	if R0 == R0, go to S5
S11	R2 ← R0 + 0
S12 output ← R2	

R0 is A R1 is B R2 is R

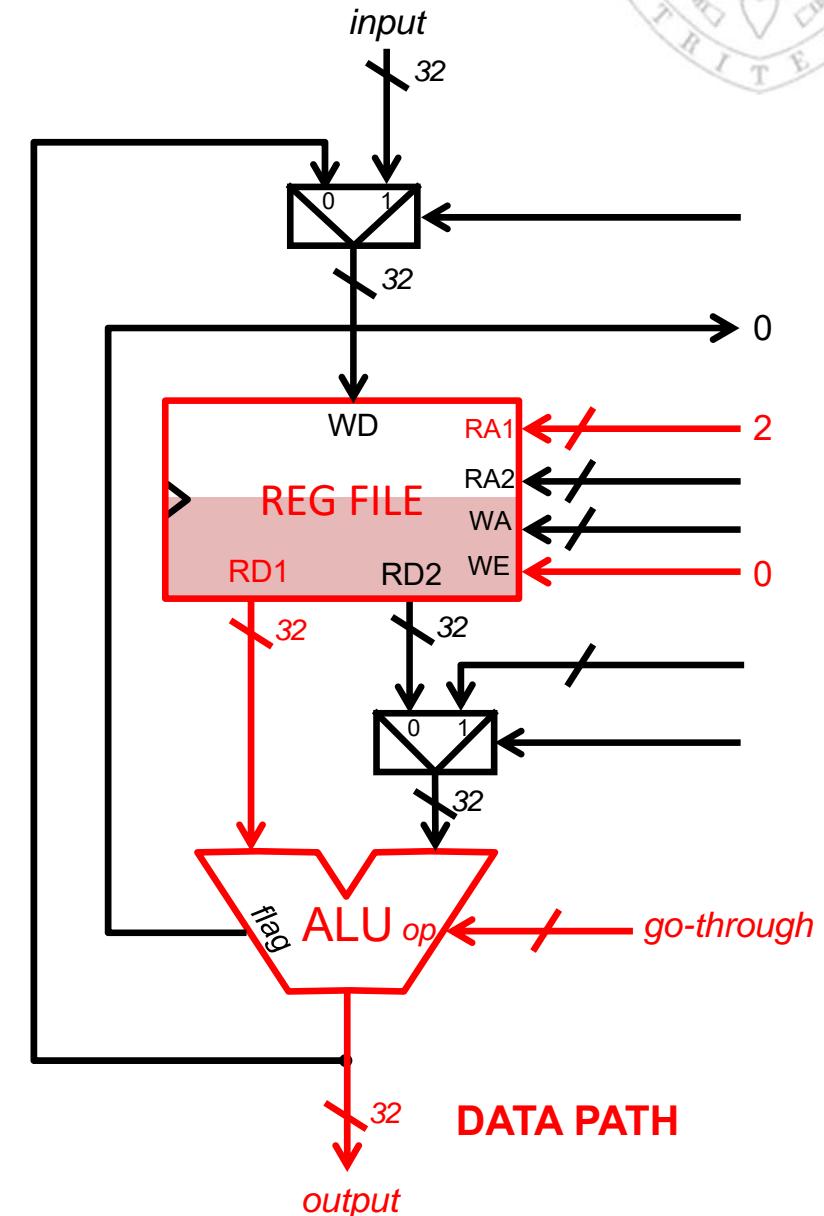



General purpose data path

Greatest common divisor

*Algorithm to calculate the GCD
of two 32-bit numbers*

```

A = Ain;
B = Bin;
R = 0;
if( A!=0 && B!=0 )
{
    while( A!=B )
        if( A>B )
            A = A-B;
        else
            B = B-A;


    R = A;
}
Rout = R;

```

Inputs and register transfers

S0	R0 \leftarrow input
S1	R1 \leftarrow input
S2	R2 \leftarrow R2 - R2
S3	if R0 == 0, go to S12
S4	if R1 == 0, go to S12
S5	if R0 == R1, go to S11
S6	if R0 <= R1, go to S9
S7	R0 \leftarrow R0 - R1
S8	if R0 == R0, go to S5
S9	R1 \leftarrow R1 - R0
S10	if R0 == R0, go to S5
S11	R2 \leftarrow R0 + 0
S12	output \leftarrow R2
S13	if R0 == R0, go to S0

R0 is A R1 is B R2 is R

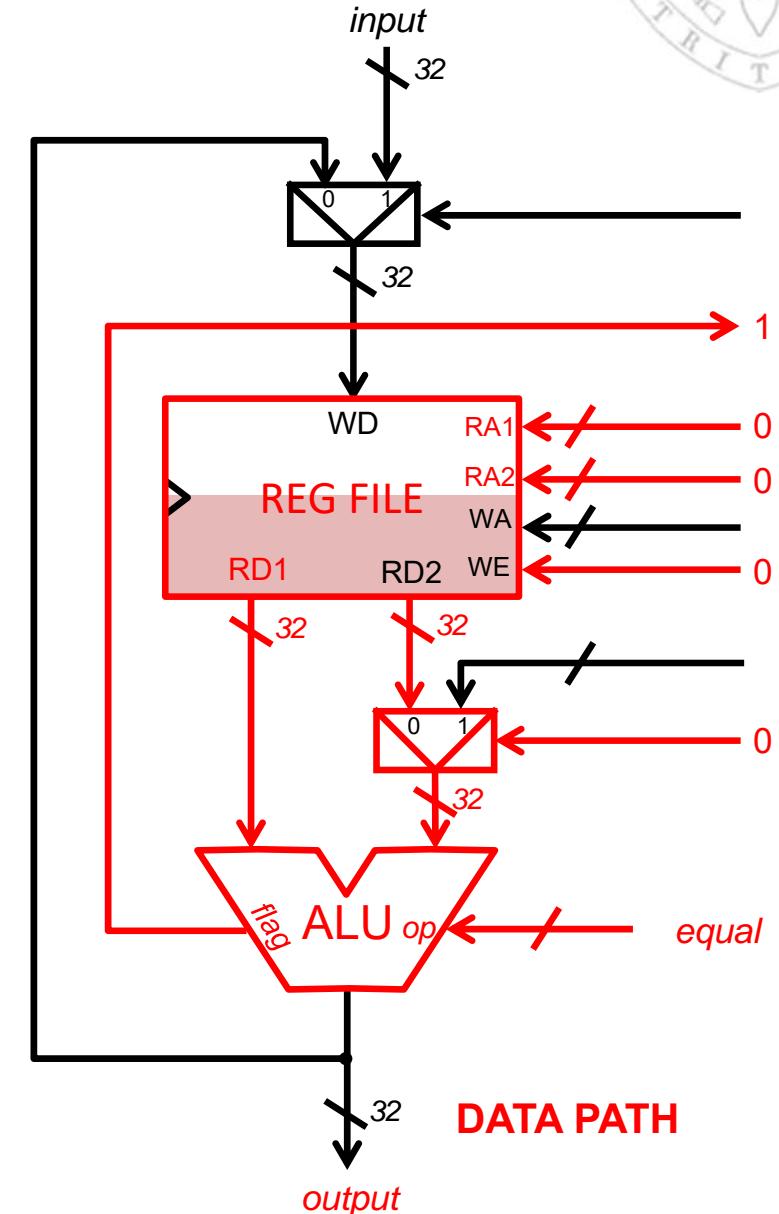

ROM-implemented controller

Multiplication



Inputs and register transfers

S0	$R0 \leftarrow \text{input}$
S1	$R1 \leftarrow \text{input}$
S2	$R2 \leftarrow R2 - R2$
S3	$R3 \leftarrow R3 - R3$
S4	if $R3 > 31$, go to S12
S5	$R4 \leftarrow R1 \& 1$
S6	if $R4 \neq 1$, go to S8
S7	$R2 \leftarrow R2 + R0$
S8	$R0 \leftarrow R0 \lll 1$
S9	$R1 \leftarrow R1 \ggg 1$
S10	$R3 \leftarrow R3 + 1$
S11	if $R0 == R0$, go to S4
S12	$\text{output} \leftarrow R2$
S13	if $R0 == R0$, go to S0

ROM content (not encoded)

addr	op	rd	rs1	rs2	const	offset	next addr.
0	<i>load</i>	0	-	-	-	-	<i>addr+1</i>
1	<i>load</i>	1	-	-	-	-	<i>addr+1</i>
2	<i>subtract</i>	2	2	2	-	-	<i>addr+1</i>
3	<i>subtract</i>	3	3	3	-	-	<i>addr+1</i>
4	<i>branch if > const</i>	-	3	-	31	12	<i>addr+1 or 12</i>
5	<i>AND const</i>	4	1	-	1	-	<i>addr+1</i>
6	<i>branch if diff const</i>	-	4	-	1	8	<i>addr+1 or 8</i>
7	<i>add</i>	2	2	0	-	-	<i>addr+1</i>
8	<i>left shift const</i>	0	0	-	1	-	<i>addr+1</i>
9	<i>right shift const</i>	1	1	-	1	-	<i>addr+1</i>
10	<i>add const</i>	3	3	-	1	-	<i>addr+1</i>
11	<i>branch if equal</i>	-	0	0	-	4	4
12	<i>store</i>	-	2	-	-	-	<i>addr+1</i>
13	<i>branch if equal</i>	-	0	0	-	0	0

ROM-implemented controller

Greatest common divisor




Inputs and register transfers

S0	$R0 \leftarrow \text{input}$
S1	$R1 \leftarrow \text{input}$
S2	$R2 \leftarrow R2 - R2$
S3	if $R0 == 0$, go to S12
S4	if $R1 == 0$, go to S12
S5	if $R0 == R1$, go to S11
S6	if $R0 \leq R1$, go to S9
S7	$R0 \leftarrow R0 - R1$
S8	if $R0 == R0$, go to S5
S9	$R1 \leftarrow R1 - R0$
S10	if $R0 == R0$, go to S5
S11	$R2 \leftarrow R0 + 0$
S12	$\text{output} \leftarrow R2$
S13	if $R0 == R0$, go to S0


ROM content (not encoded)

addr	op	rd	rs1	rs2	const	offset	next addr.
0	<i>load</i>	0	-	-	-	-	<i>addr+1</i>
1	<i>load</i>	1	-	-	-	-	<i>addr+1</i>
2	<i>subtract</i>	2	2	2	-	-	<i>addr+1</i>
3	<i>branch if > const</i>	-	0	-	0	12	<i>addr+1 or 12</i>
4	<i>branch if > const</i>	-	1	-	0	12	<i>addr+1 or 12</i>
5	<i>branch if equal</i>	-	0	1	-	11	<i>addr+1 or 11</i>
6	<i>branch if <=</i>	-	0	1	-	9	<i>addr+1 or 9</i>
7	<i>subtract</i>	0	0	1	-	-	<i>addr+1</i>
8	<i>branch if equal</i>	-	0	0	-	5	5
9	<i>subtract</i>	1	1	0	-	-	<i>daddr+1</i>
10	<i>branch if equal</i>	-	0	0	-	5	5
11	<i>add const</i>	2	0	-	0	-	<i>addr+1</i>
12	<i>store</i>	-	2	-	-	-	<i>addr+1</i>
13	<i>branch if equal</i>	-	0	0	-	0	0


Generic data path + controller

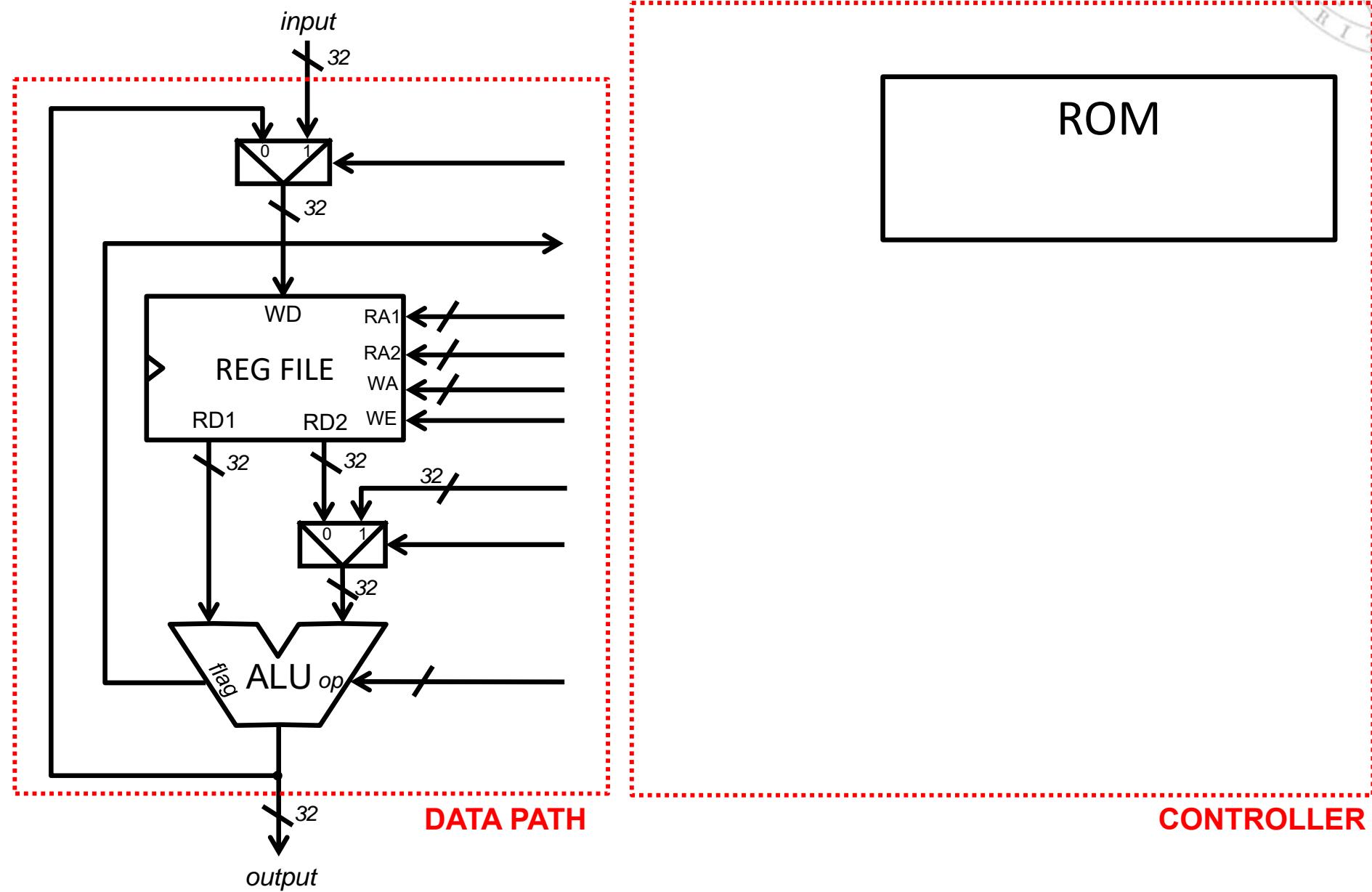


Generic data path + controller

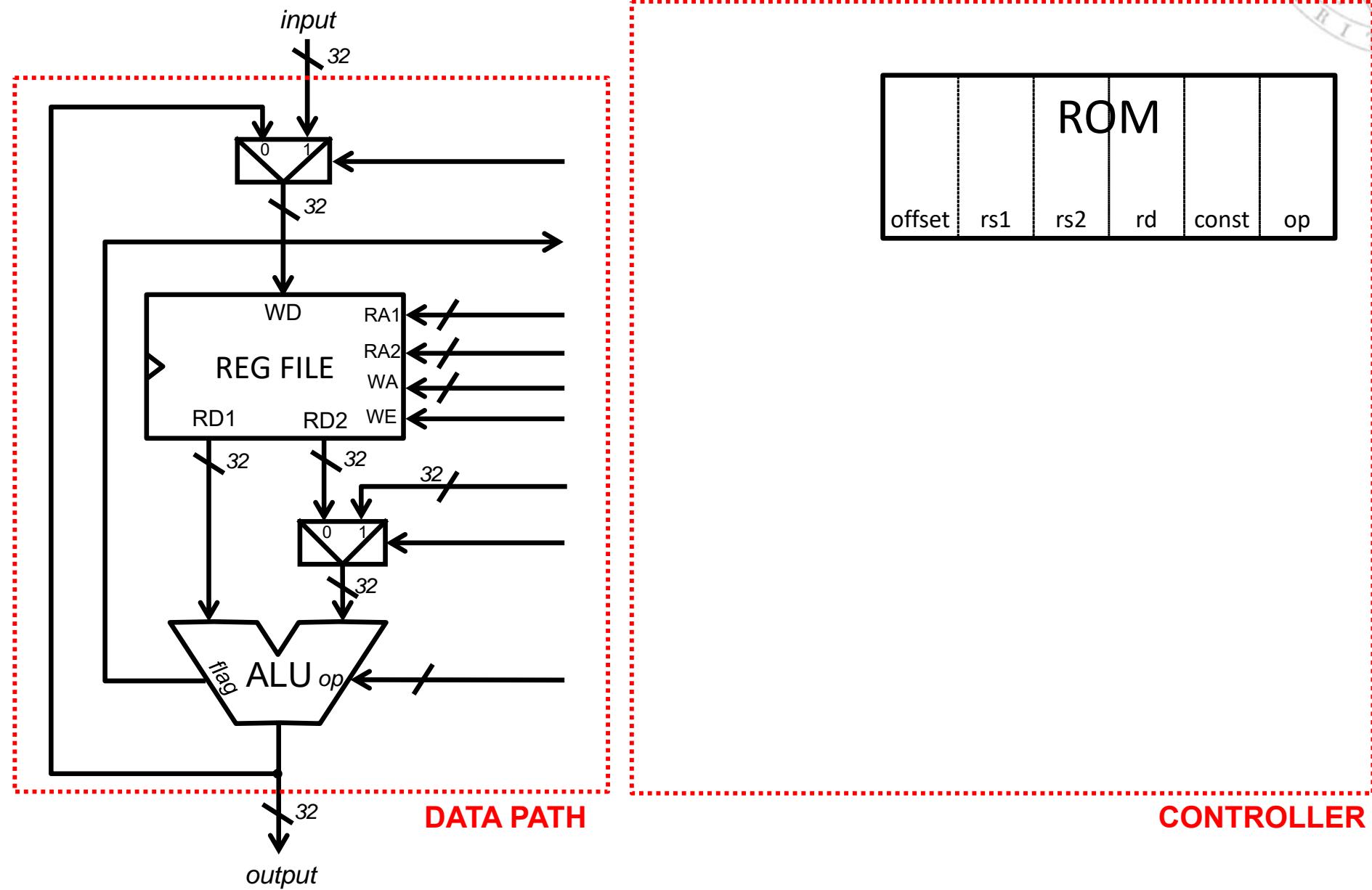


Generic data path + controller

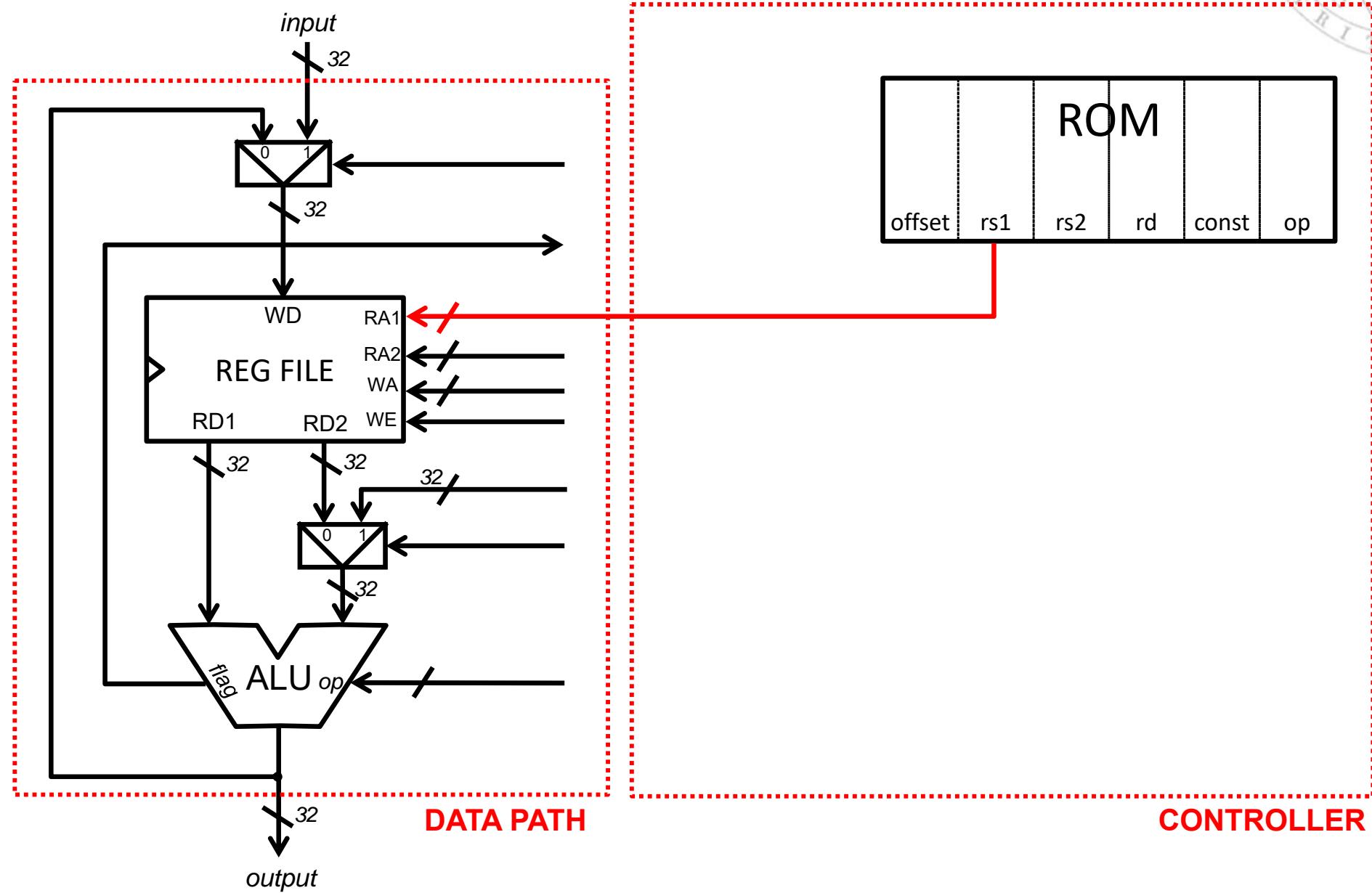


Generic data path + controller

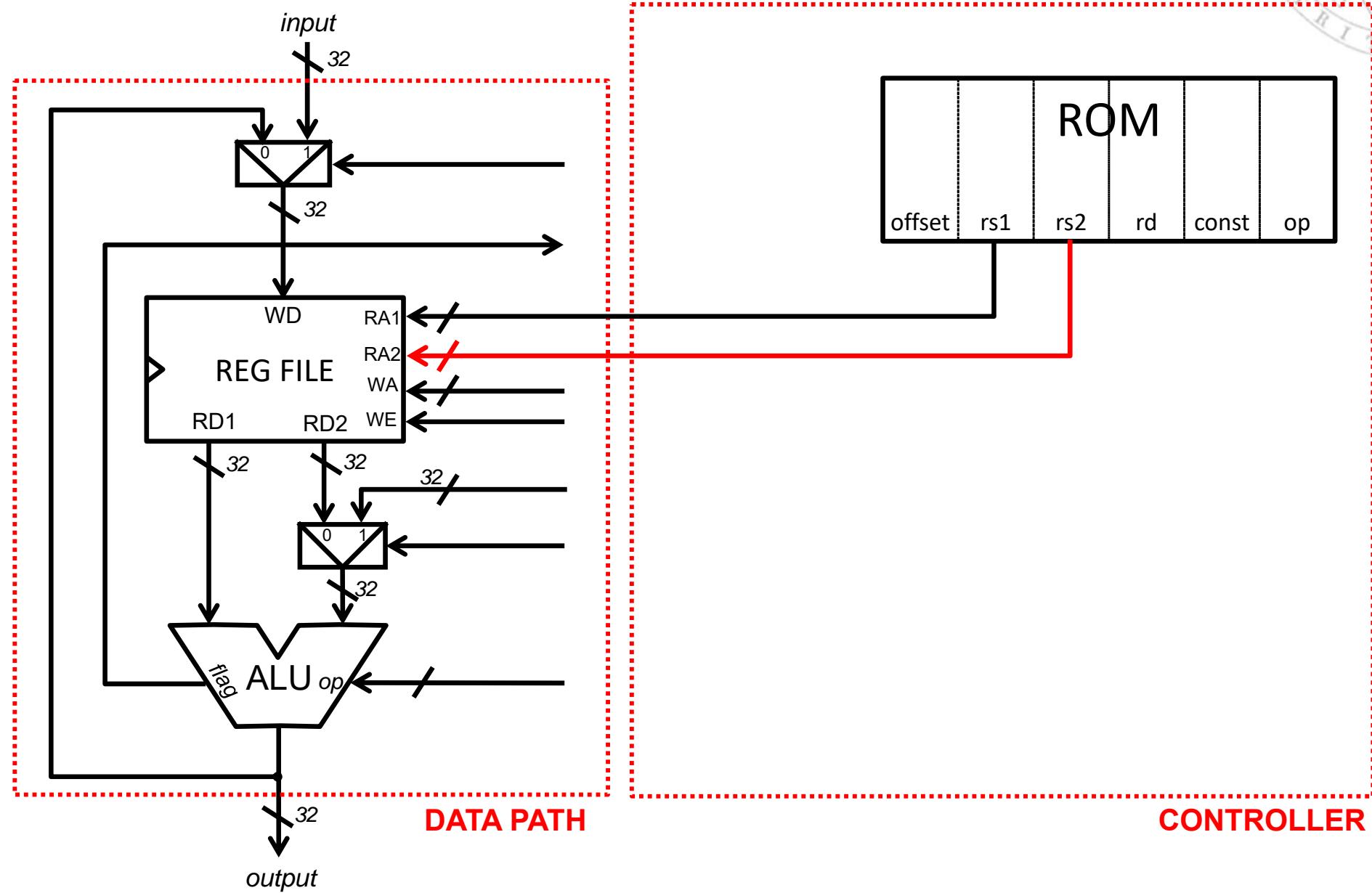


Generic data path + controller

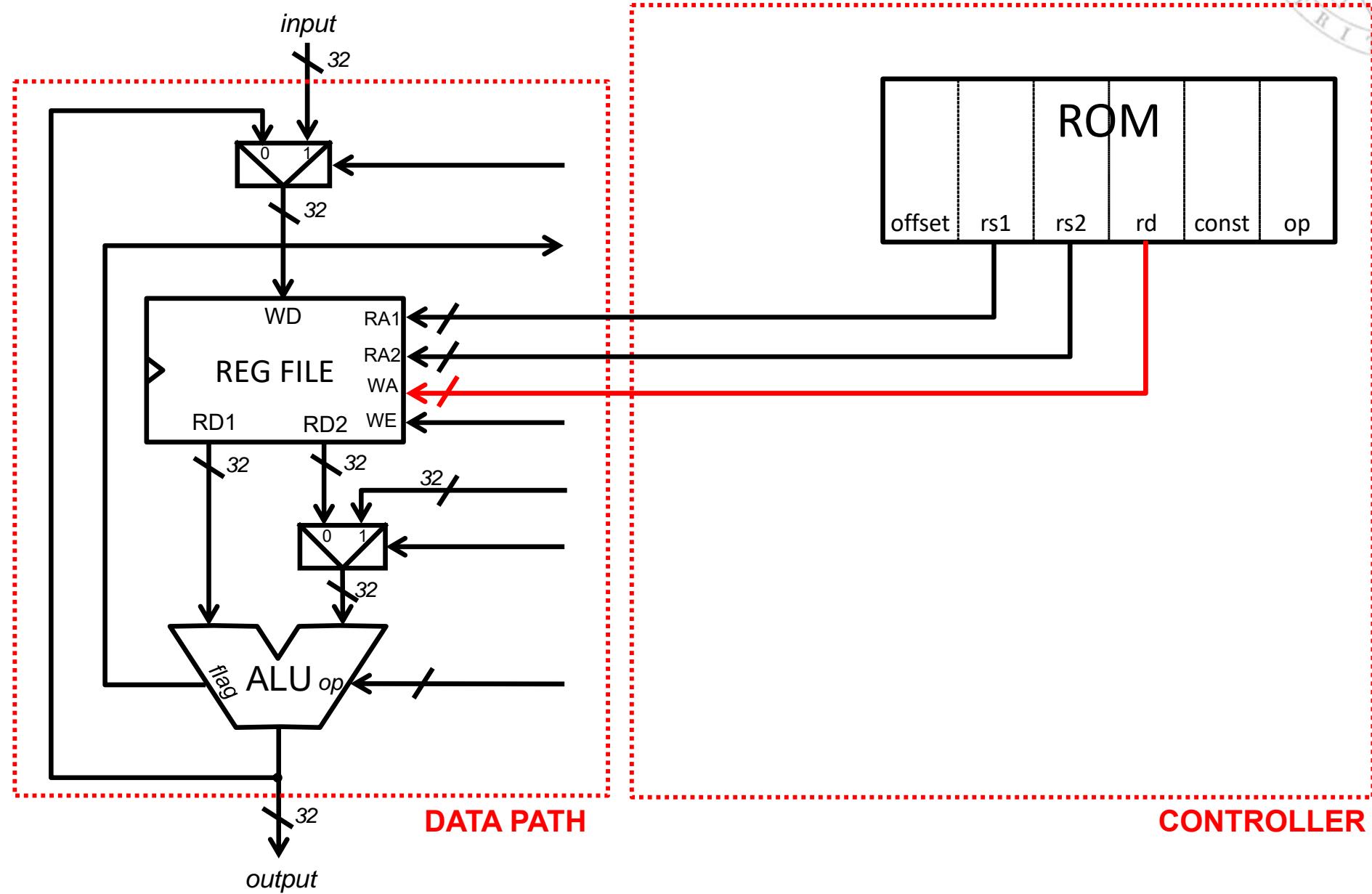


Generic data path + controller

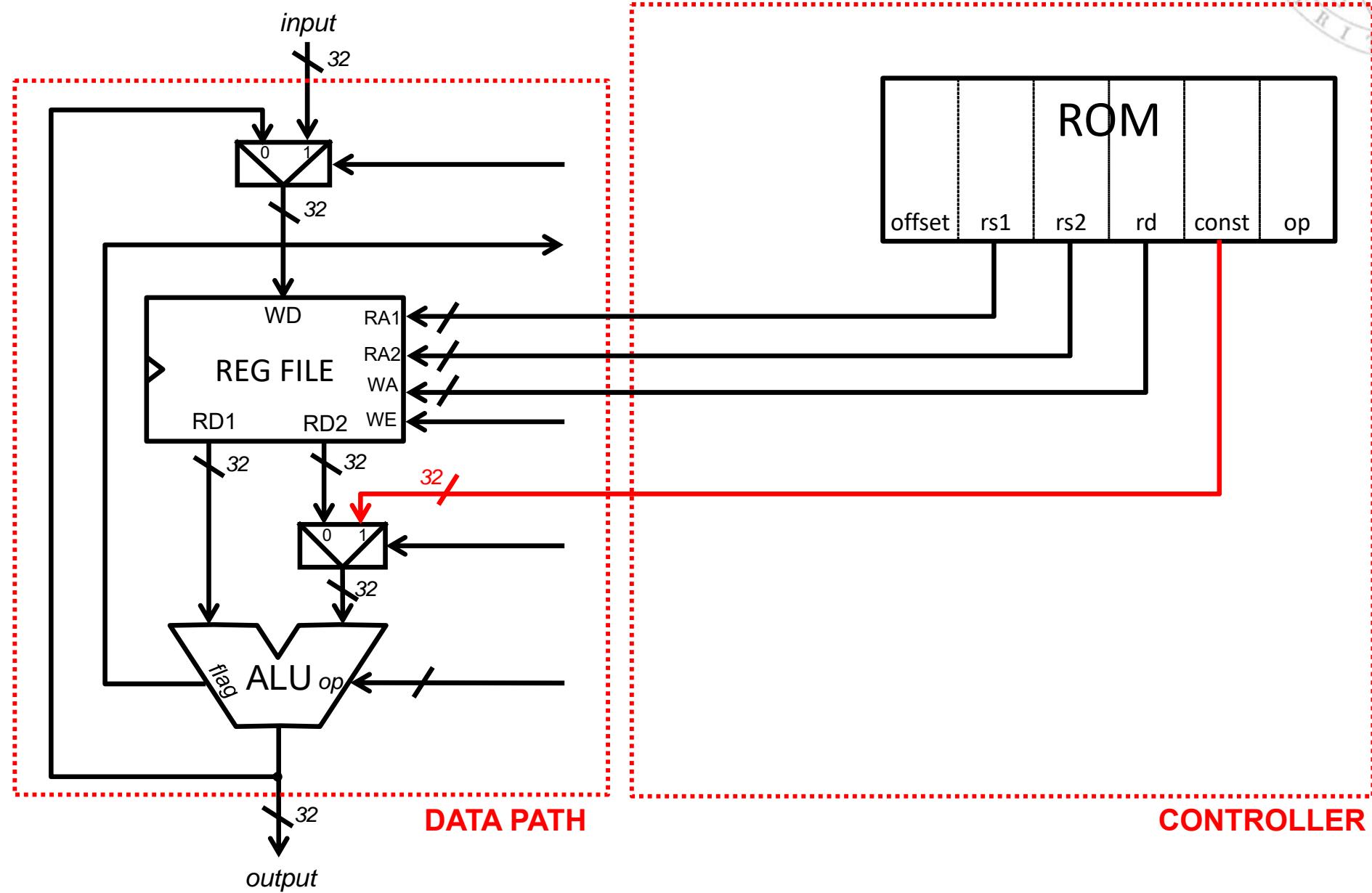


Generic data path + controller

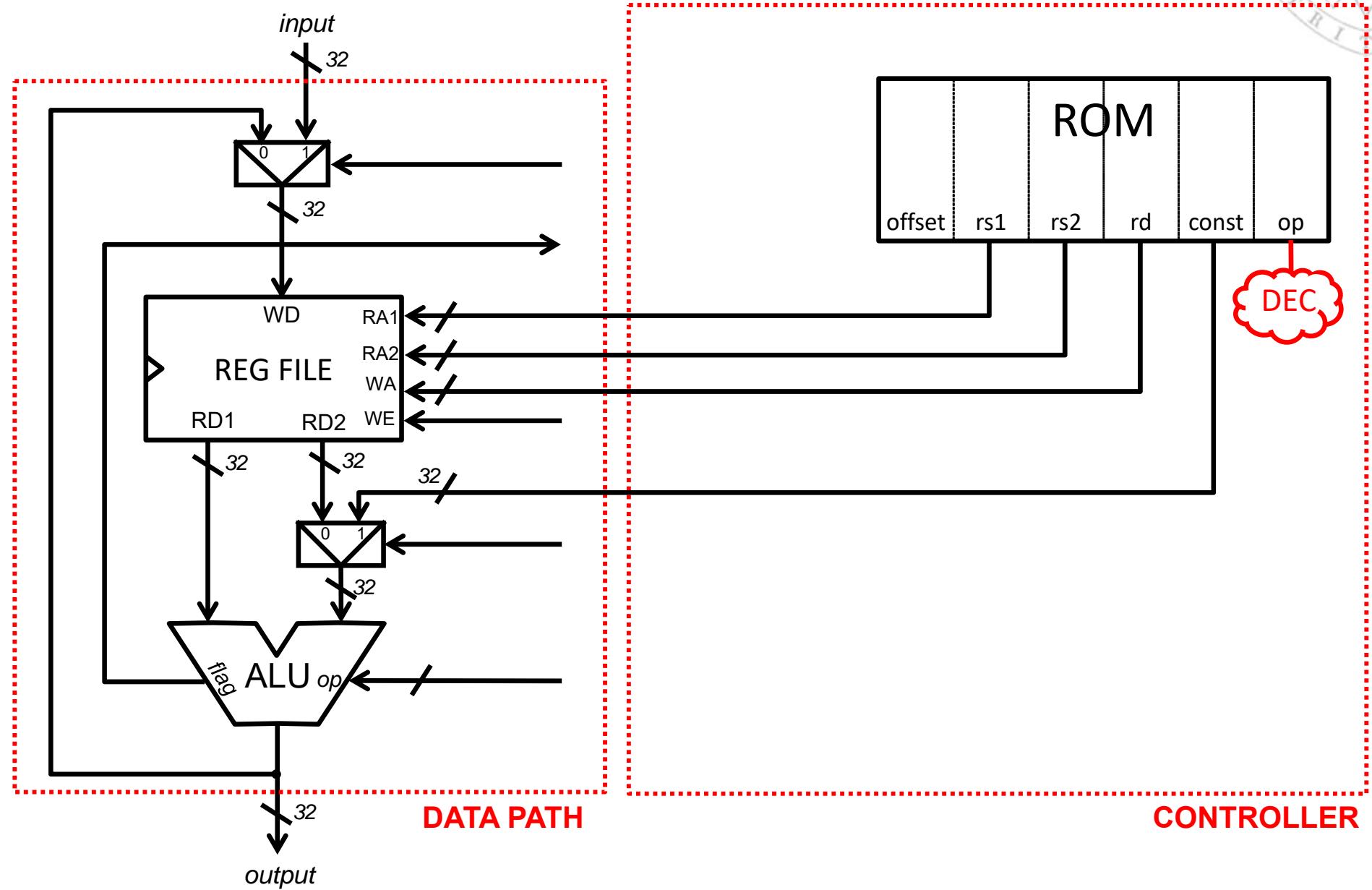


Generic data path + controller

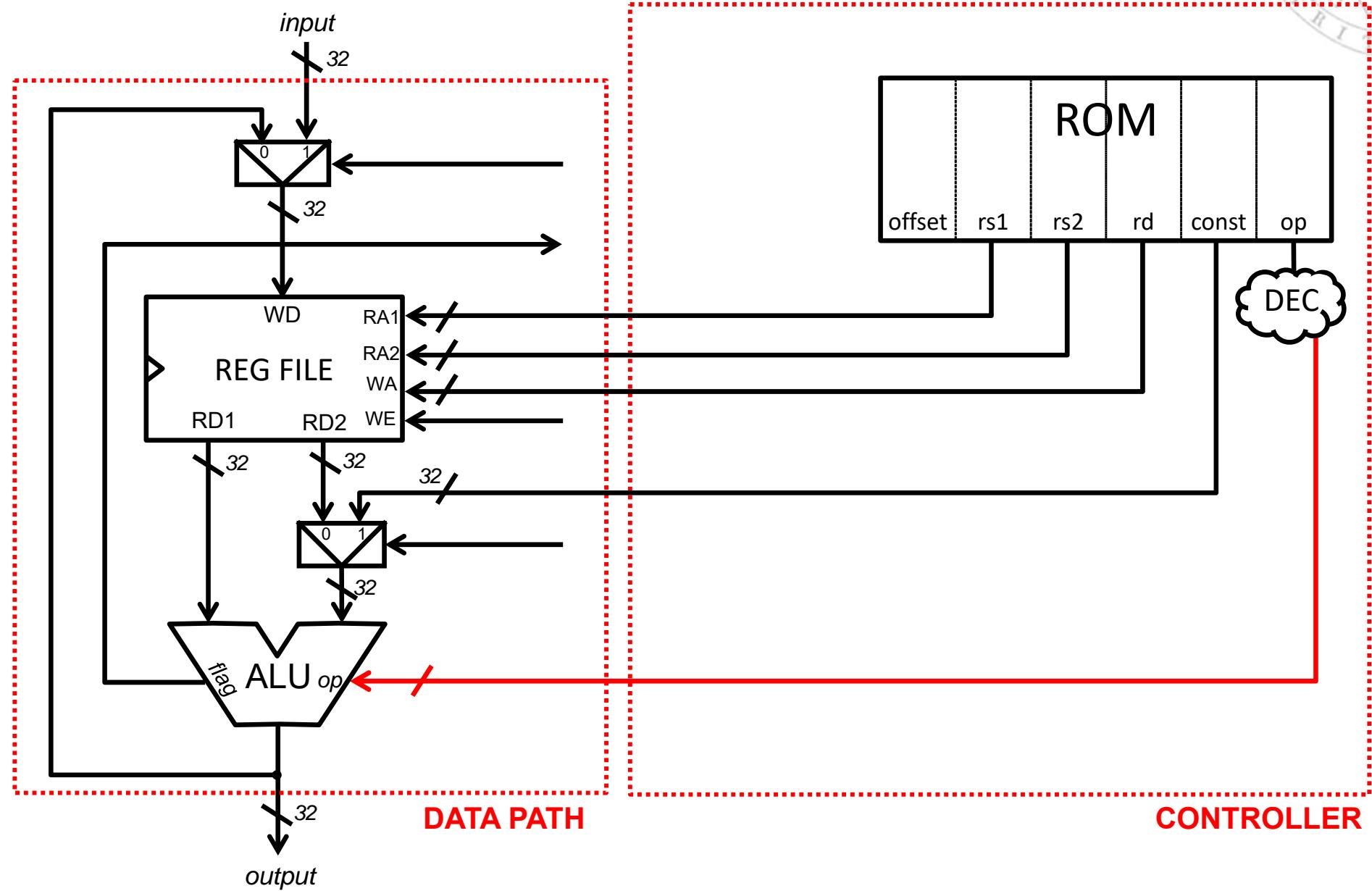


Generic data path + controller

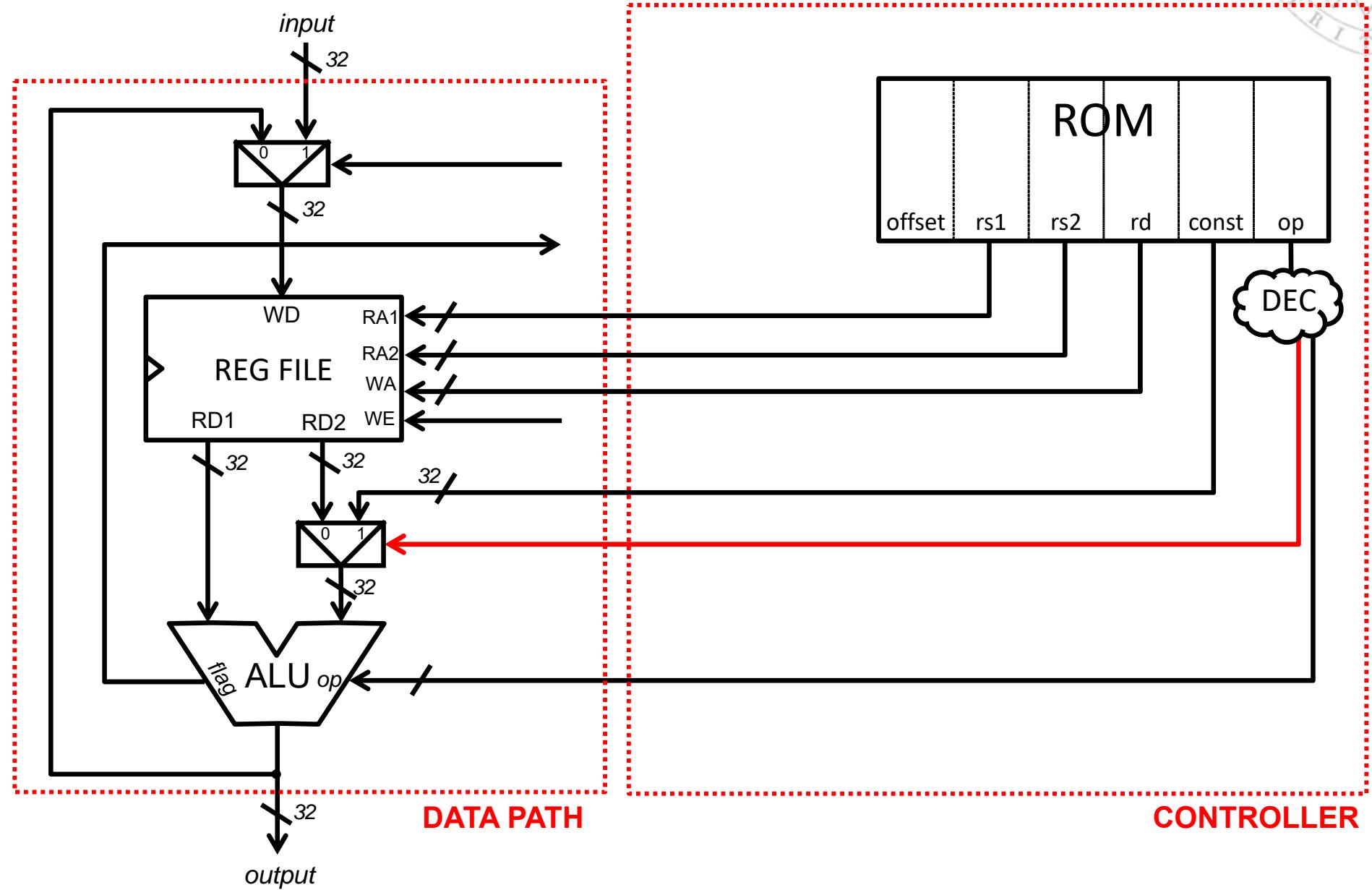


Generic data path + controller

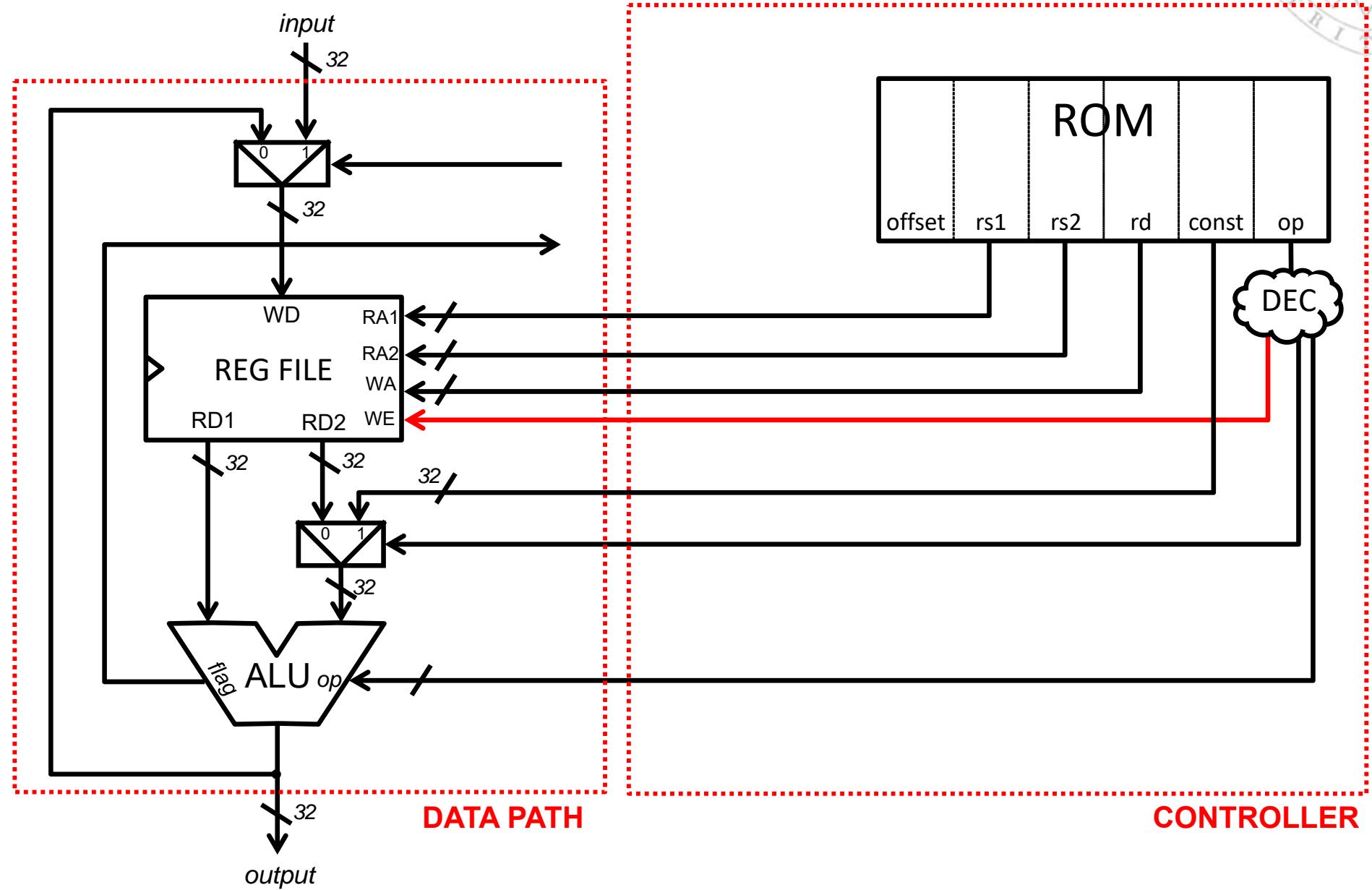

Generic data path + controller

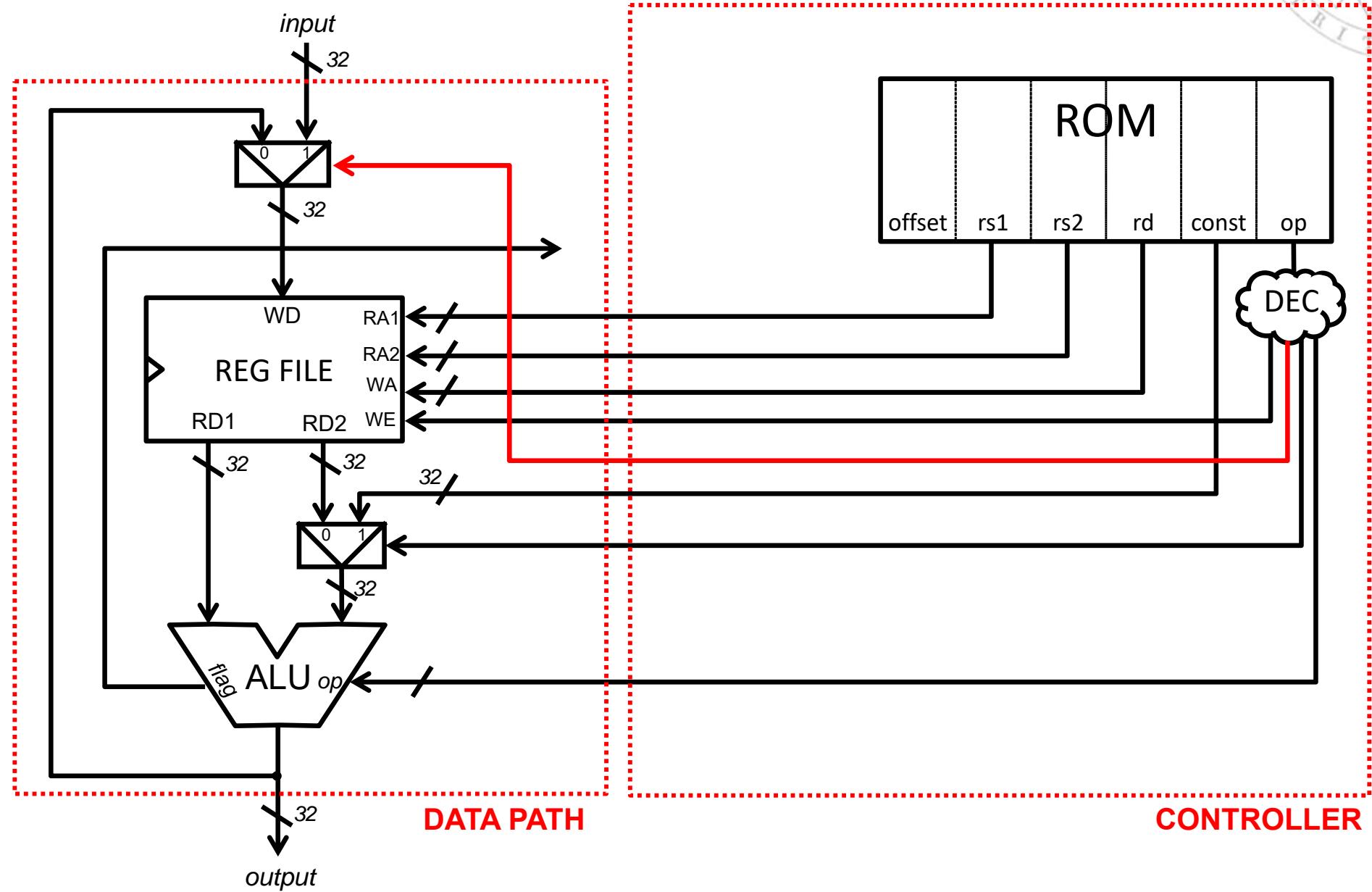


Generic data path + controller

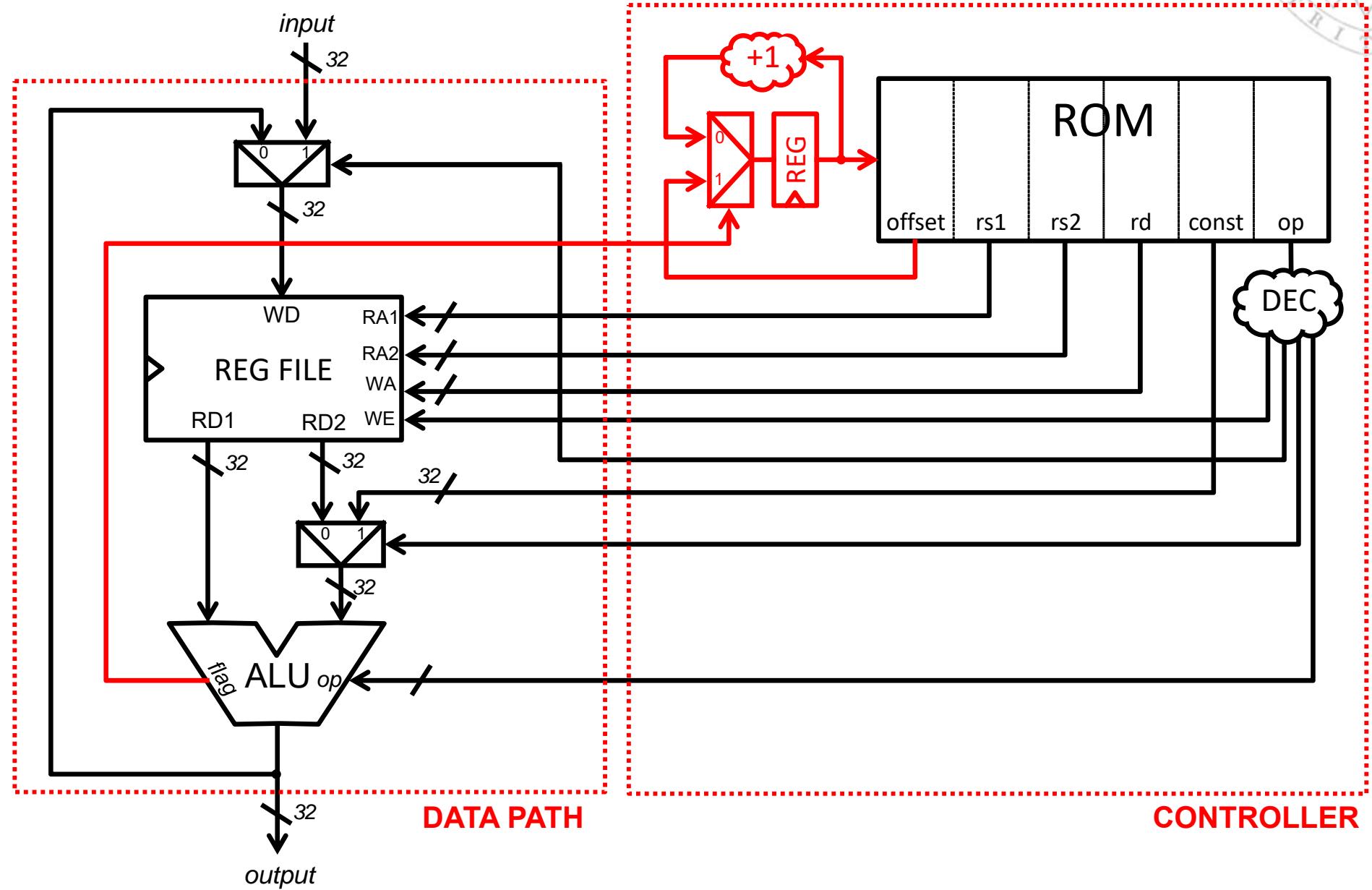



Generic data path + controller

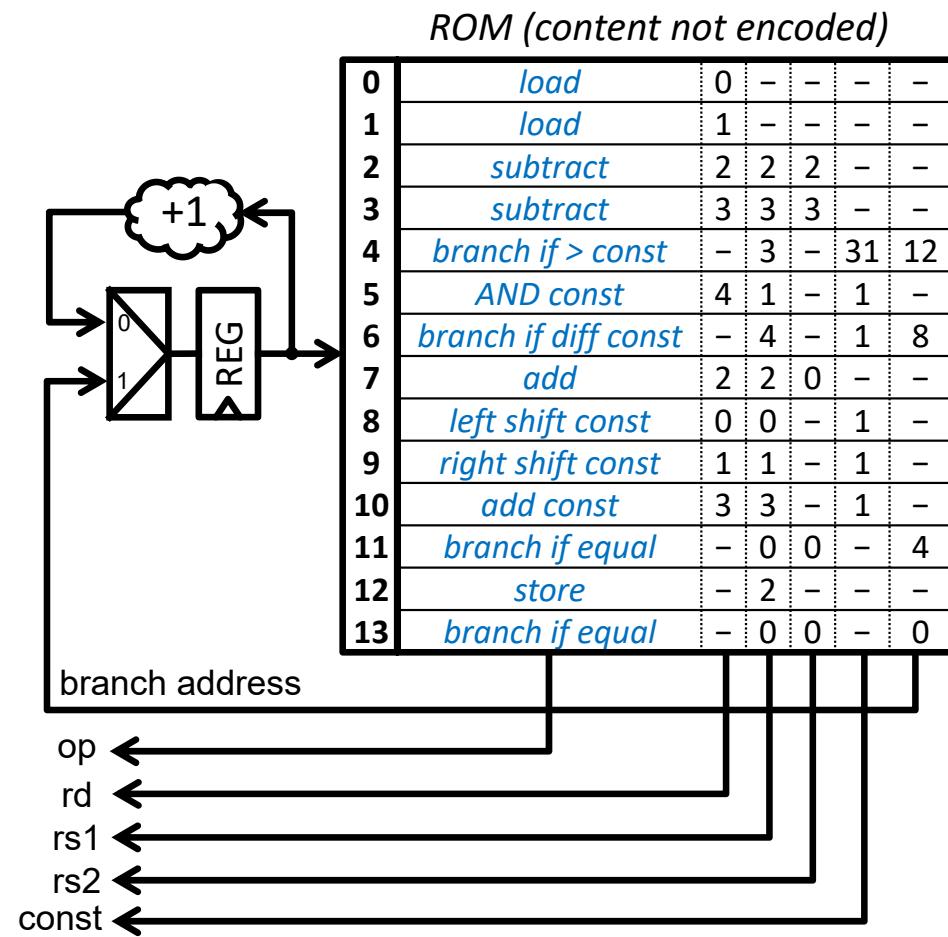
- In this controller, many elements that are common to a generic processor can be found:





Generic data path + controller

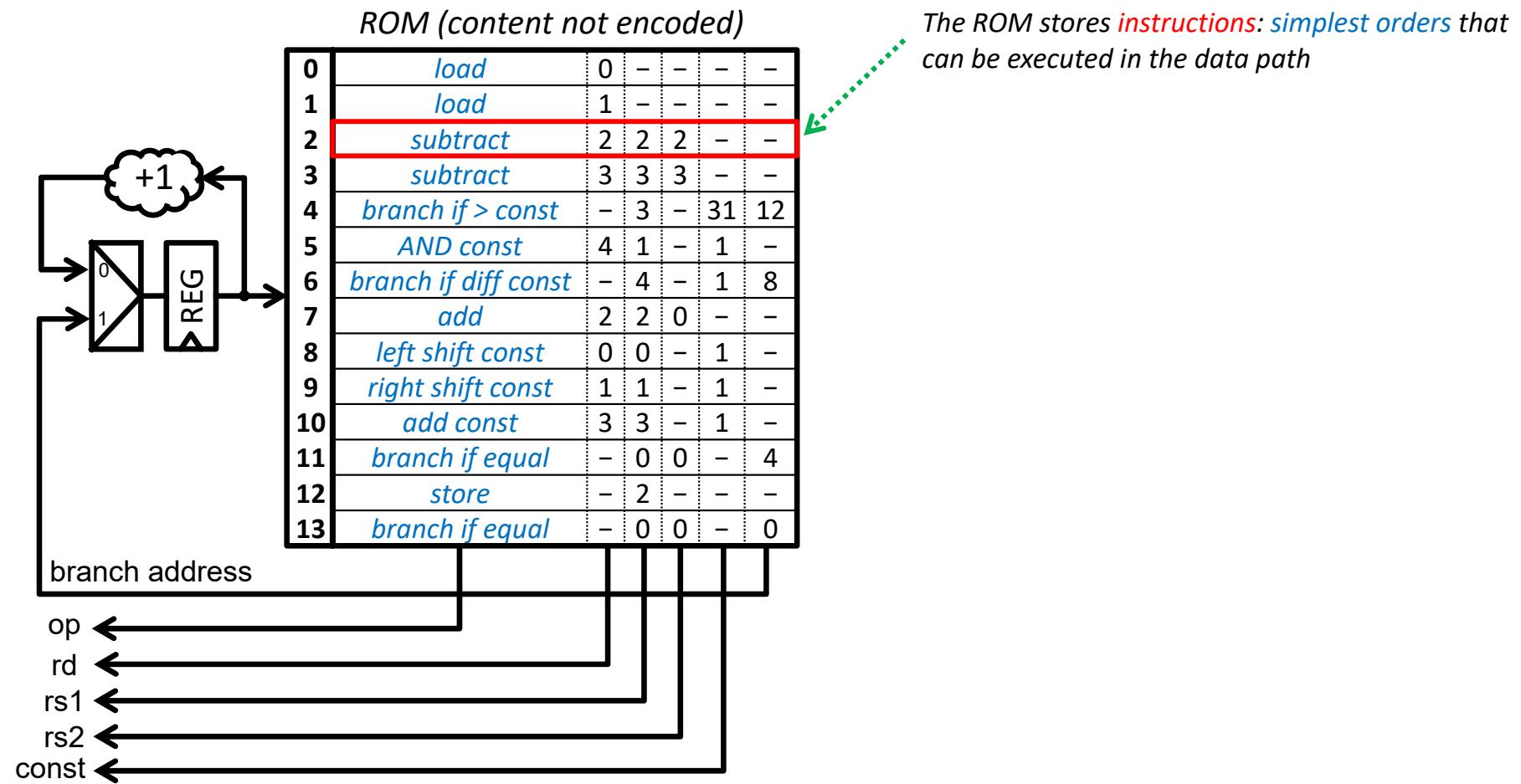
- In this controller, many elements that are common to a generic processor can be found:





Generic data path + controller

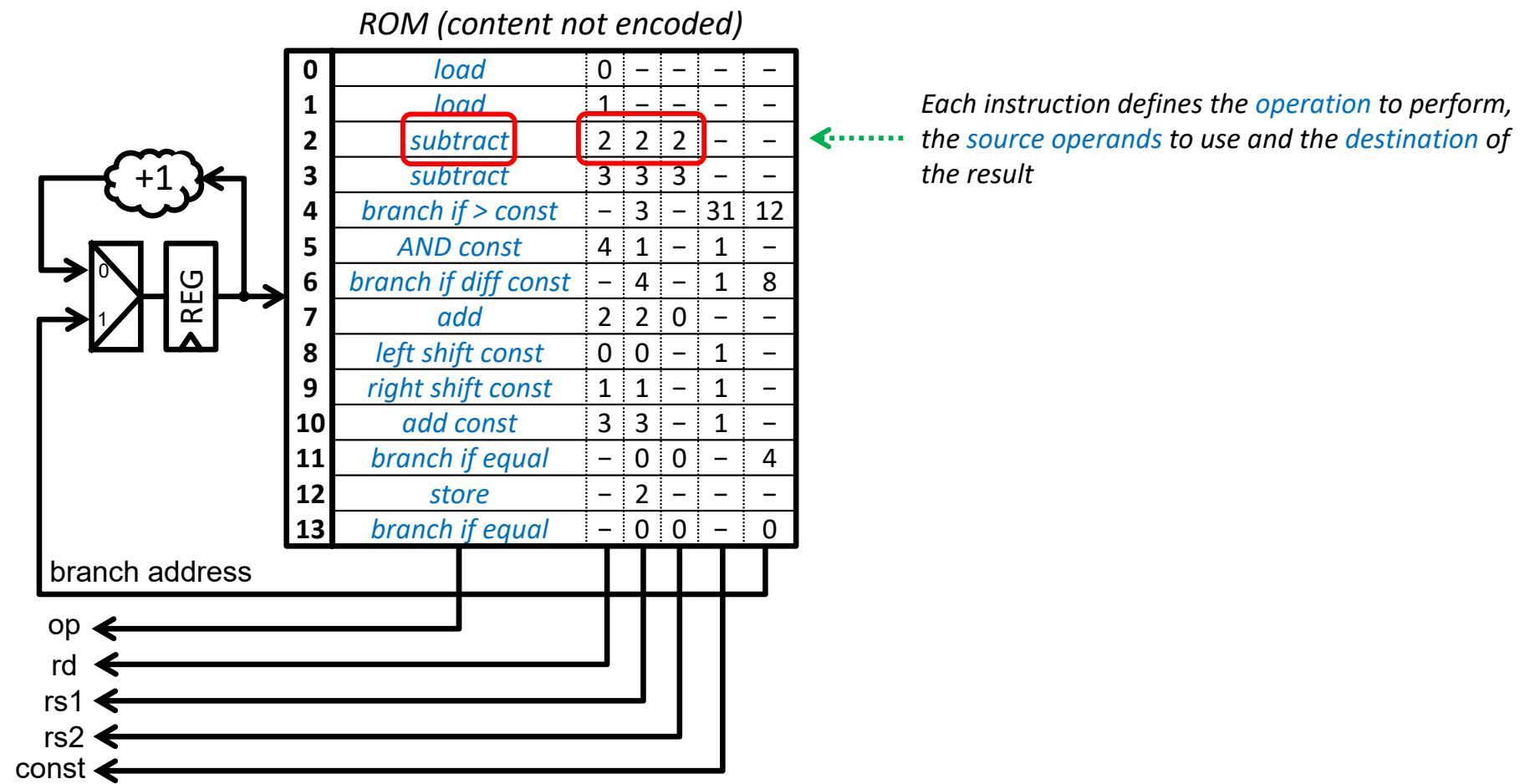
- In this controller, many elements that are common to a generic processor can be found:





Generic data path + controller

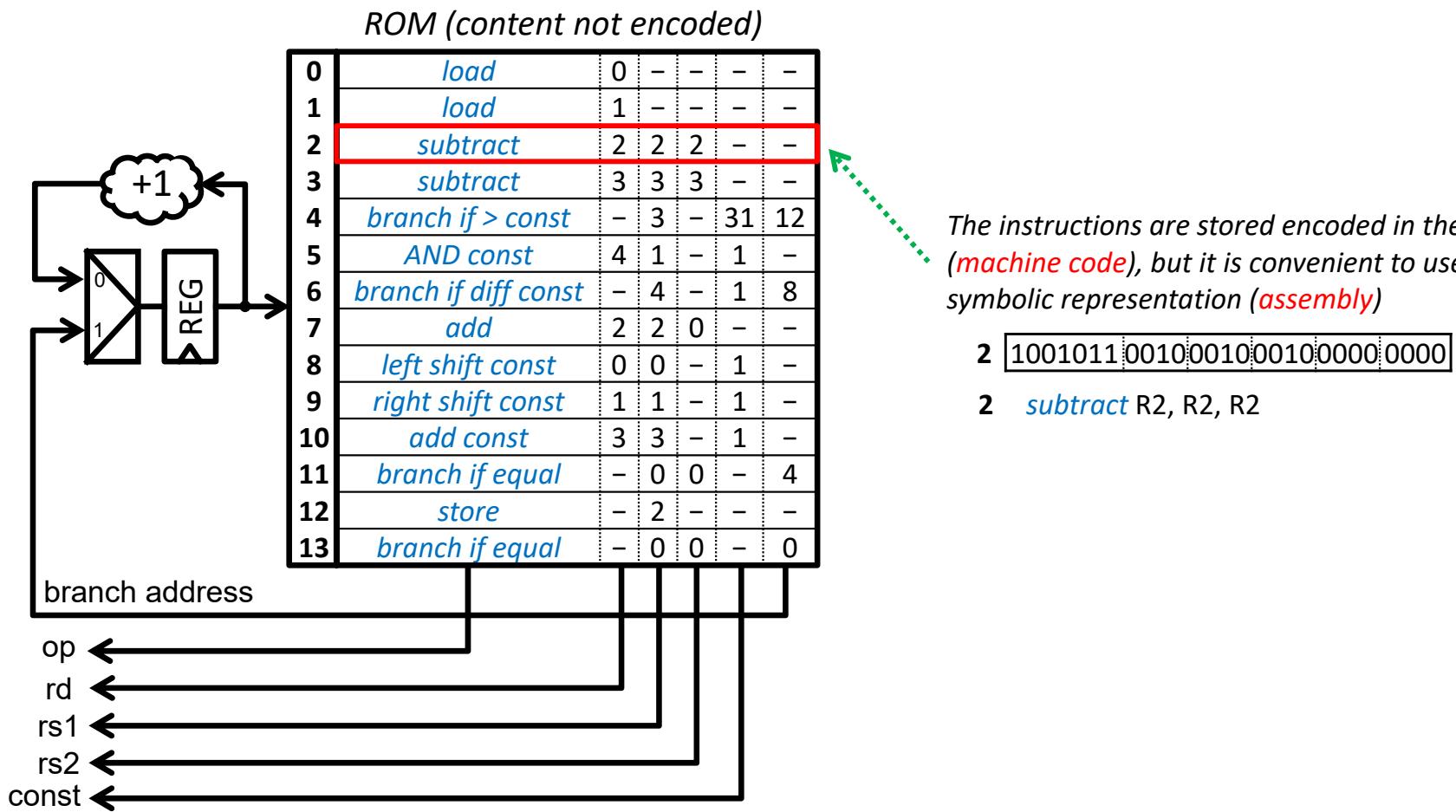
- In this controller, many elements that are common to a generic processor can be found:





Generic data path + controller

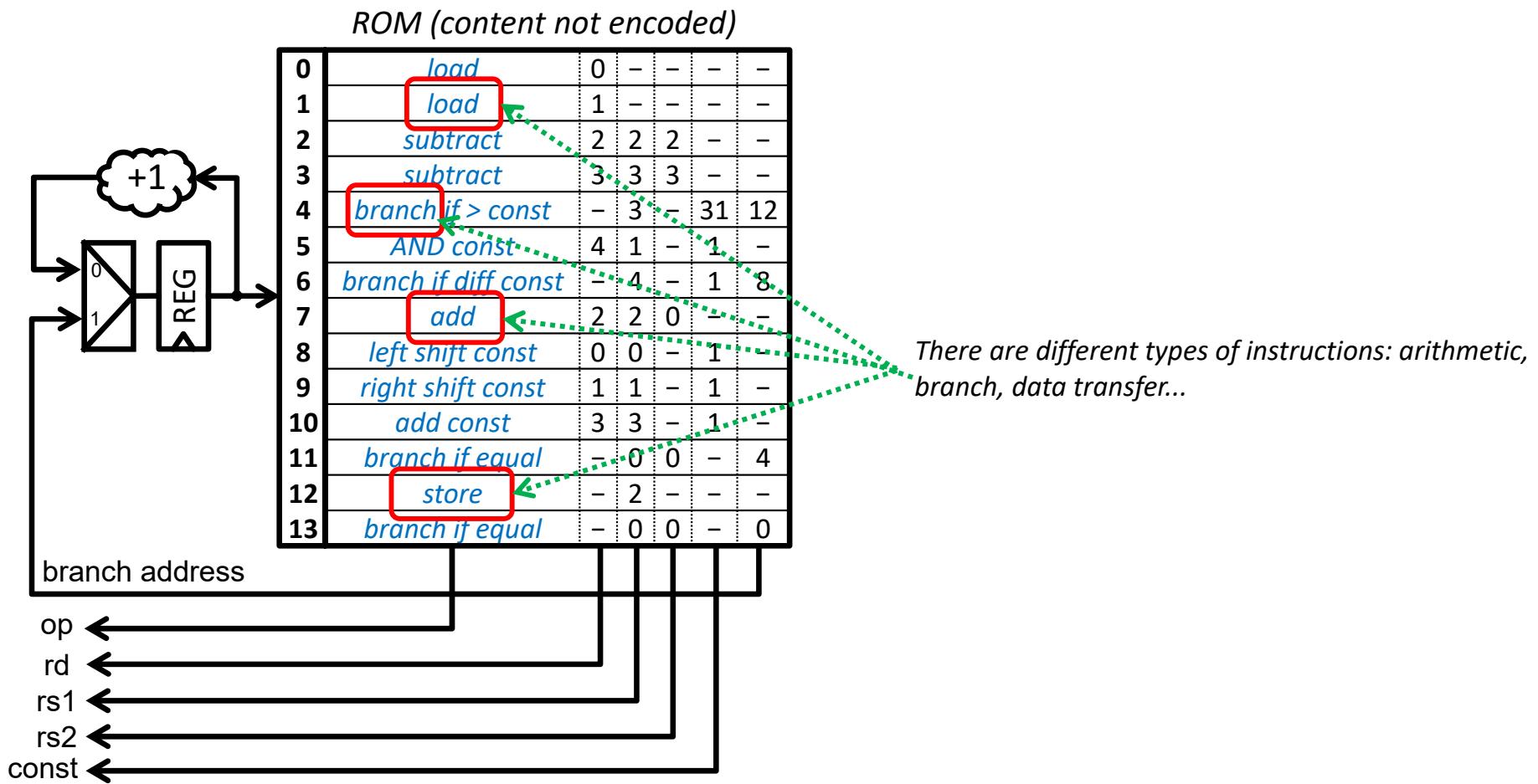
- In this controller, many elements that are common to a generic processor can be found:





Generic data path + controller

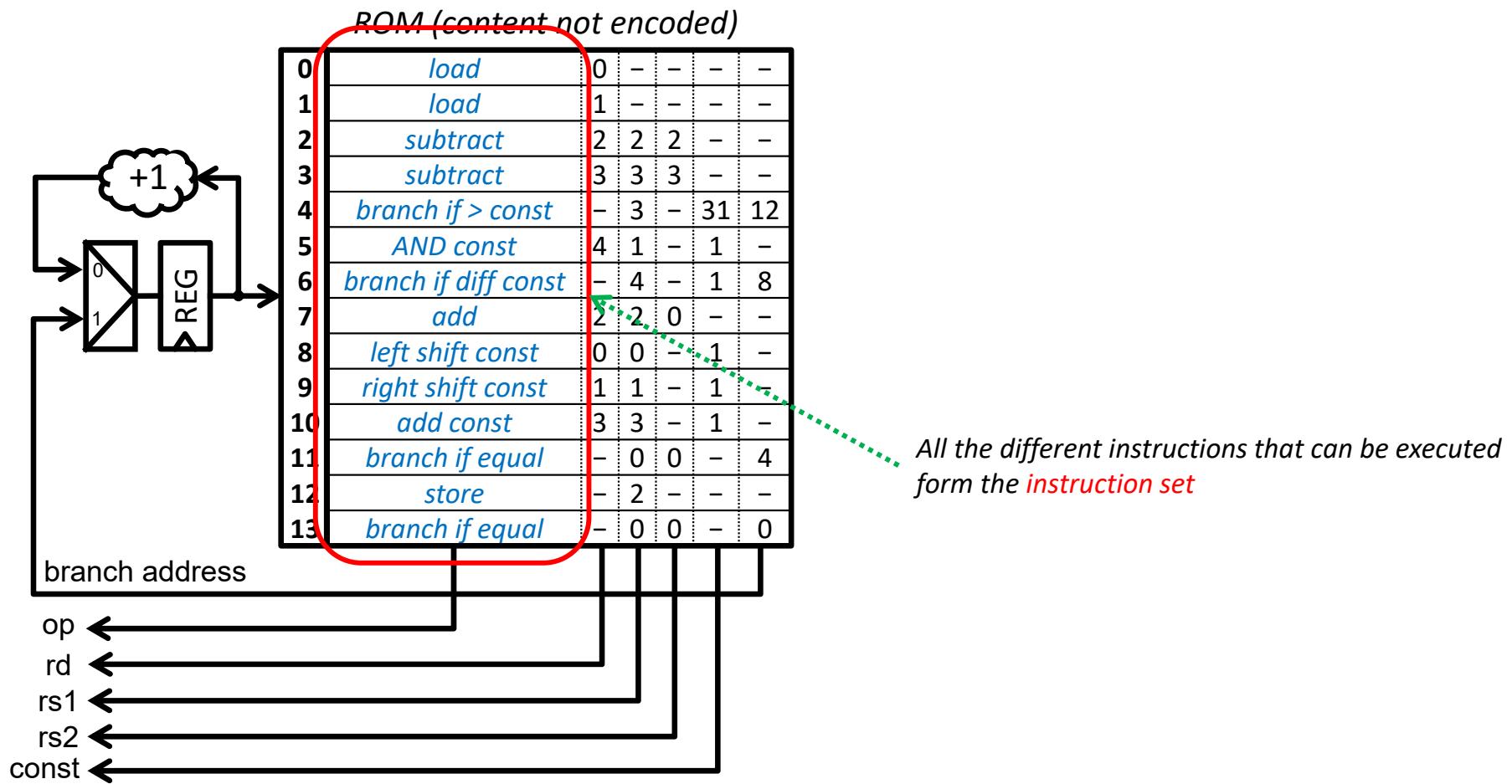
- In this controller, many elements that are common to a generic processor can be found:





Generic data path + controller

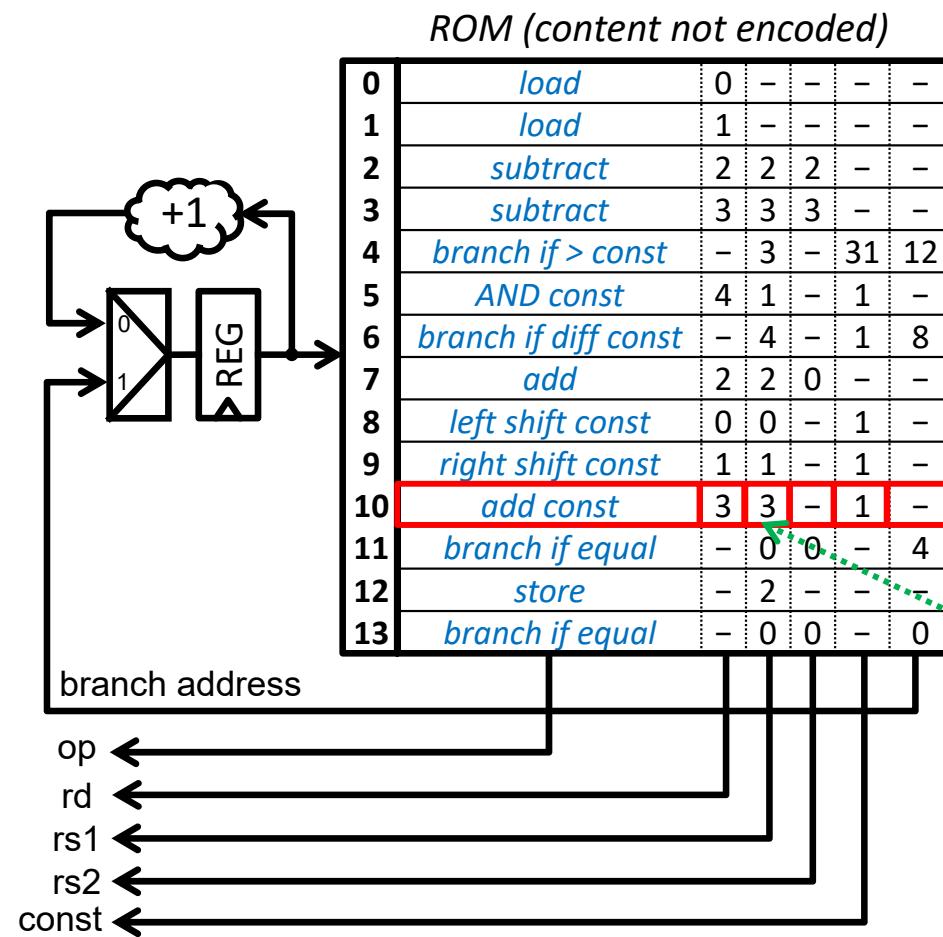- In this controller, many elements that are common to a generic processor can be found:




Instructions have a common **format** that places and encodes the information fields



Generic data path + controller

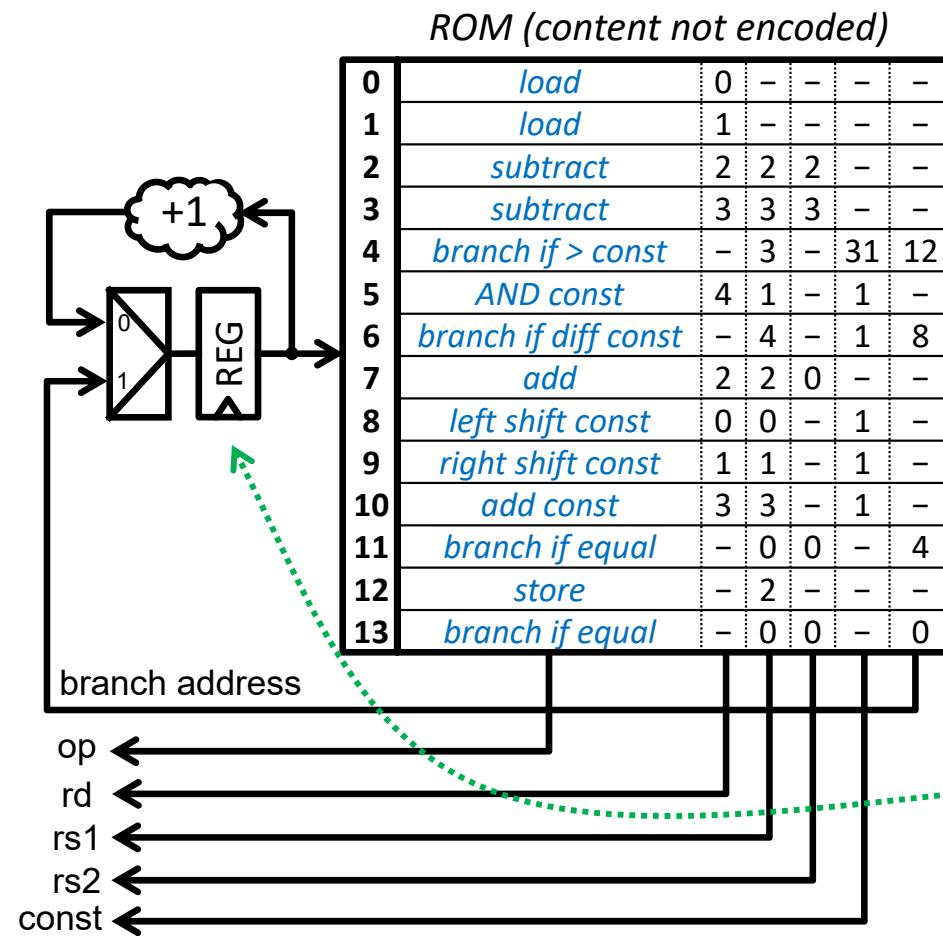- In this controller, many elements that are common to a generic processor can be found:




There is a “**program counter (PC)**” that addresses the memory



Generic data path + controller

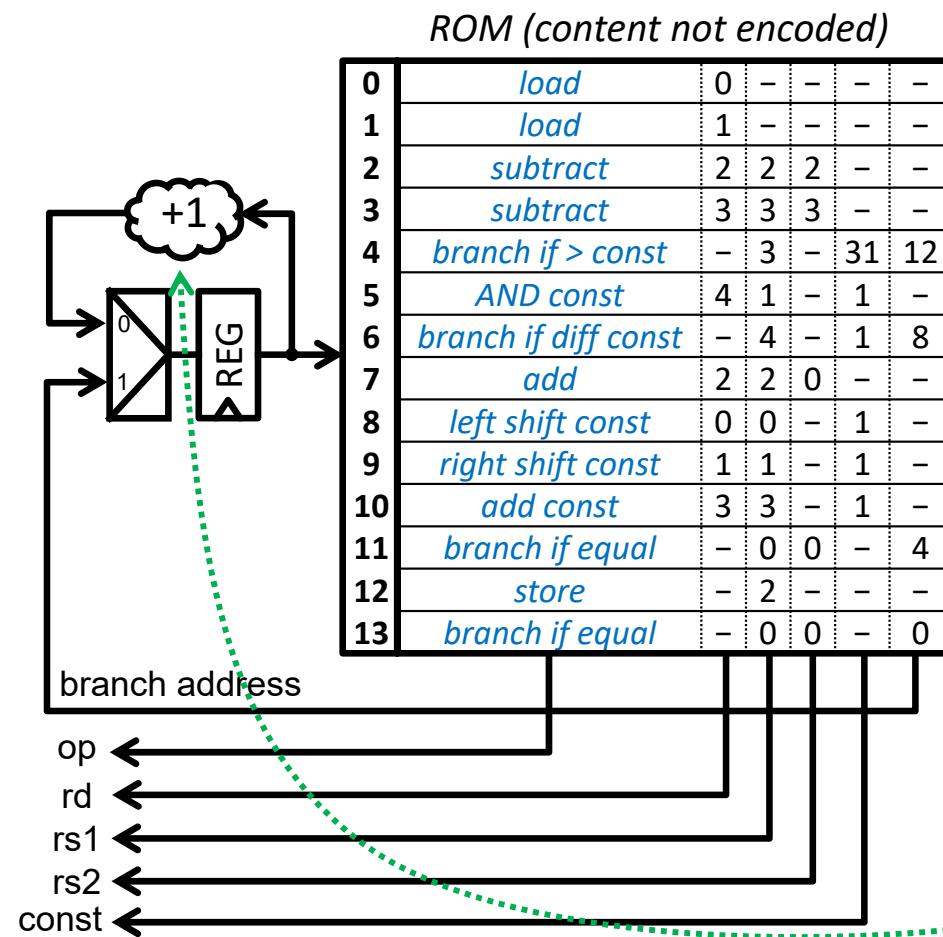- In this controller, many elements that are common to a generic processor can be found:




Usually, instructions are **executed sequentially** in the order in which they are stored

Generic data path + controller



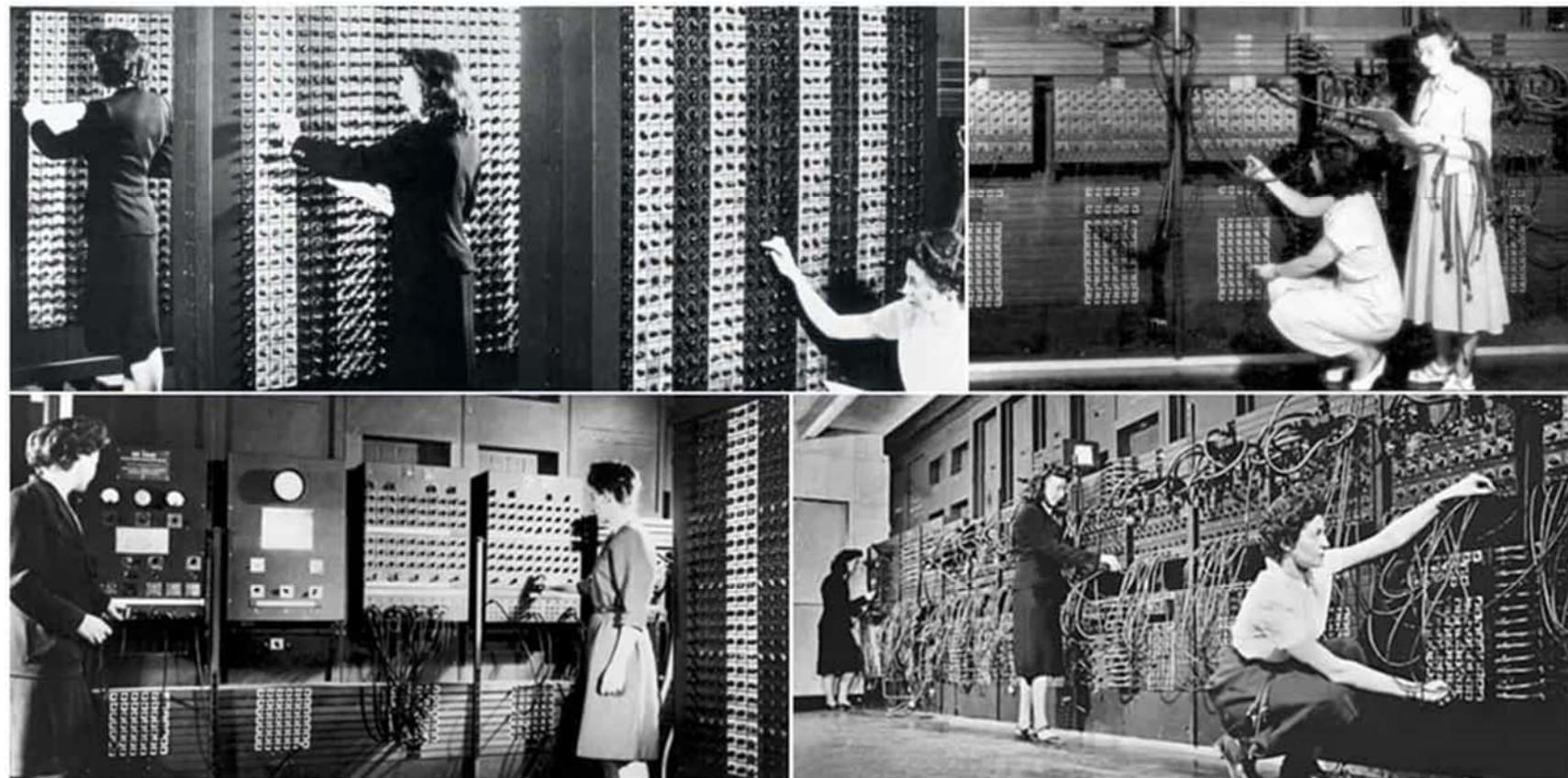- Just by **modifying the program** stored in the ROM, the data path performs a different algorithm.
 - The ENIAC (1946) was programmed by rewiring the computer




source: <https://alltogether.swe.org>



General purpose circuit: computer

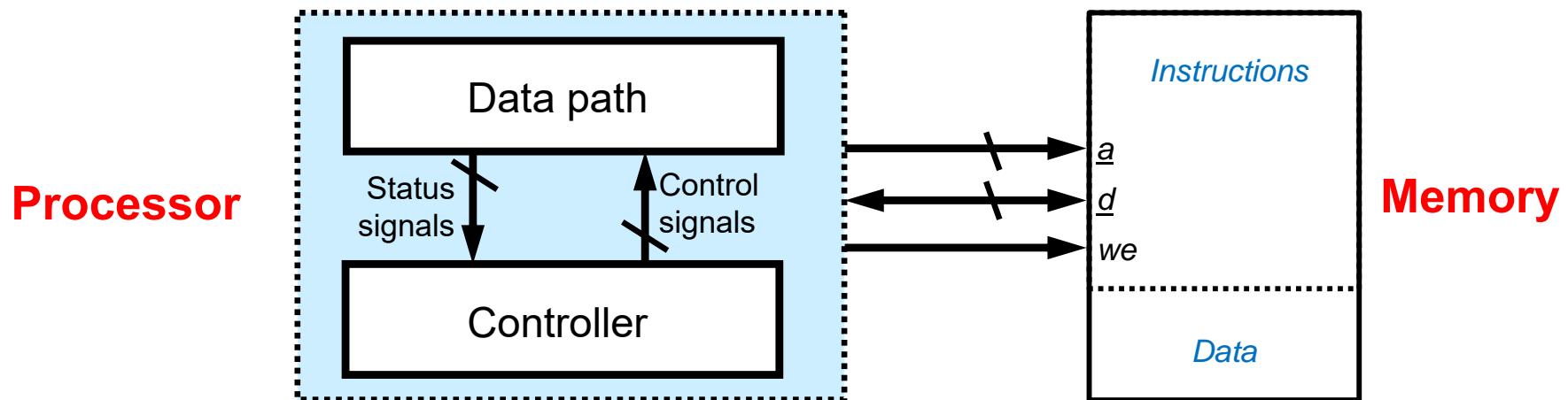- It is possible to design a **circuit even more generic** to avoid redesigning it each time **the algorithm that is performed is changed**:
 - Replacing the ROM with a RAM to facilitate the change of program.
 - Replacing the external input/output of the data path with a connection to the RAM to read/write **data stored in it**.



- New elements appear:
 - **SW**: Set of programs executed by the circuit
 - **Programmer**: person who develops software programs
 - **Compiler**: translator of algorithms into sequences of instructions

Von Neumann model (1945)

Principles



- Computer with **programs stored in memory**.
 - A **program** is a **sequence of instructions and data**.
 - **Instructions**: they rule the behavior of the computer.
 - **Data**: they are processed by the instructions.
- The memory is formed by words that are **linearly organized**.
 - All of them have the **same size**.
 - Each one is **identified by the address** that occupies in the memory.
 - It contains encoded instructions and data with no distinction.
- The program instructions are executed **sequentially**:
 - i.e., in the same **order in which they are stored** in the memory.
 - This order can only be changed after executing a branch instruction.
 - There is a **program counter** (PC) register that stores the **address** memory **occupied** by the instruction to execute.

Von Neumann model (1945)

Principles




- The **execution of an instruction** implies:
 - Fetch the **instruction** from memory, whose address is contained in the PC.
 - Decode the **instruction**.
 - Read the **source operands** indicated in the instruction.
 - Perform the **operation** indicated in the instruction on the read operands.
 - Write back the result of the operation in the target destination indicated in the instruction.
 - Update the **PC with the address** of the next instruction to execute
 - By default, this would be the PC + the size of the instruction that is being executed.
 - If the instruction is a branch, the target address will be indicated by the instruction.
- This **sequence of stages** is known as **instruction cycle**.
 - A processor performs successive instruction cycles, indefinitely, one after the other.

Von Neumann model (1945)

Organization



- The main components are:
 - Processor (CPU): controls the behavior of the computer and processes data according to the instructions of a stored program
 - Memory subsystem: stores data/instructions (program)
 - Input/output (I/O) subsystem: transfers data between the computer and the external environment
 - Interconnection subsystem: provides communication channels among the processor, the memory and the I/O.

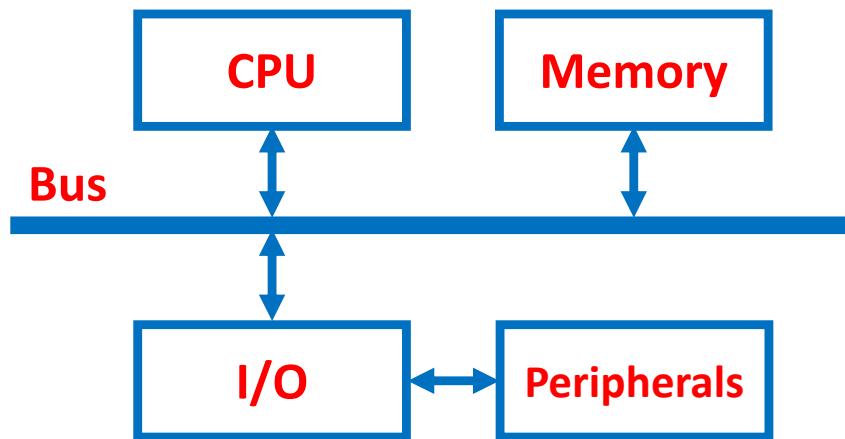

Basic concepts

Processor architecture



- The **processor architecture** or **instruction set architecture (ISA)** is the set of processor attributes that are visible by:
 - The assembly language programmer.
 - The high-level language compiler.
- It implies an **agreement between HW and SW** that comprises the following elements:
 - **Data types** supported by the instructions.
 - Memory model and **organization of the information in memory**.
 - **Processor registers** accessible by the programmer.
 - Mechanism to indicate the **operand location** of an instruction.
 - **Set of instructions** that can be executed by the processor.
 - **Format** and encoding of the machine instruction.
- The **processor architecture abstracts the complexity** of the HW design indicating **what** the processor does, without stating **how**.

Basic concepts

Processor organization




- The **processor organization** or **microarchitecture** is the **organization of the HW components** that form the architecture.
 - The same architecture can be implemented with different microarchitectures, which can be designed by different manufacturers.
- A **family** is the set of processors with the **same architecture** but **different implementations**:
 - Different technology, different performance, different price...
- There is a large number of different **architecture families**:
 - x86, ARM, MIPS, SPARC, PowerPC, RISC-V...
 - All the **processor of the same family** are compatible and **can execute exactly the same programs**.
 - **Retrocompatibility** allows the newer family members execute programs developed for the older ones.



Basic concepts

Machine code vs. assembly code

- The simplest order that a processor can execute is called **instruction**.
 - It defines the **operation** to perform and its **operands**.
 - The hardware of a computer only interprets and executes **binary encoded instructions**, i.e. **machine language**.
 - The **assembly language** is a **human-readable representation** of the **machine language**.
 - The assembly instructions use **mnemonics** to indicate the operation and the operands.
 - There usually is a **1:1 relation** between machine and assembly instructions.

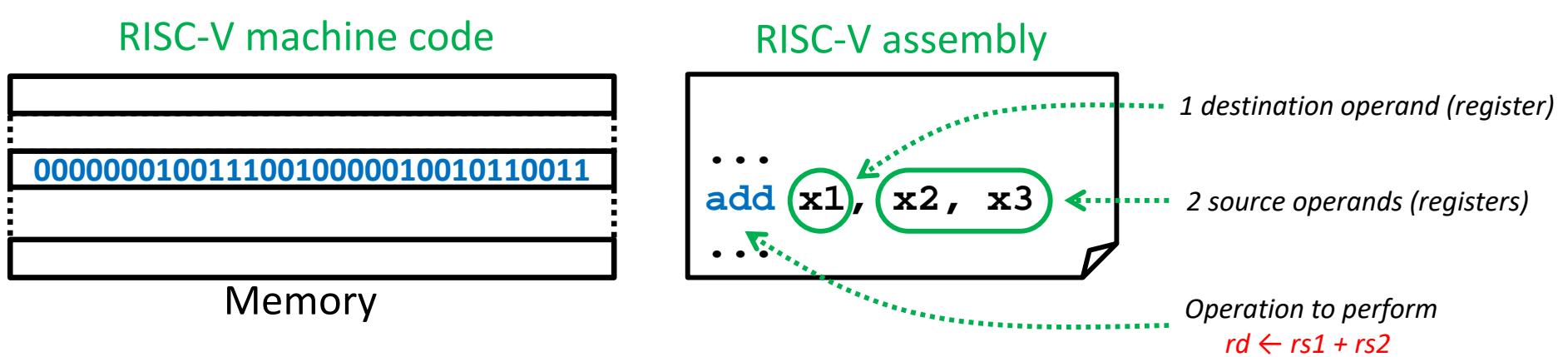

Basic concepts

Compiler vs. assembler



- **Assembler**: software that translates assembly instructions into machine code.
- **Compiler**: software that translates a high-level program (i.e. C/C++) into an assembly program.
 - Generally, the relation between high level and assembly instructions is 1:n.

C/C++ language

```
int a, b, c, d;  
...  
d = (a + b) - c;  
...
```

a → x5 c → x7
b → x6 d → x9

*Relation of C variables
with RISC-V registers*

RISC-V assembly

```
...  
lw x5, 0(x8)  
lw x6, 4(x8)  
lw x7, 8(x8)  
add x9, x5, x6  
sub x9, x9, x7  
sw x9, 12(x8)  
...
```

RISC-V machine code

00000000000001000010001010000011
00000000010001000010001100000011
00000000100001000010001110000011
00000000011000101000010010110011
01000000011101001000010010110011
00000000100101000010011000100011

--

Memory

More information: <https://creativecommons.org/licenses/by-nc-sa/4.0/>

About *Creative Commons*



■ CC license (*Creative Commons*)



- This license enables reusers to distribute, remix, adapt, and build upon the material in any medium or format for noncommercial purposes only, and only so long as attribution is given to the creator. If you remix, adapt, or build upon the material, you must license the modified material under identical terms:



Attribution:

Credit must be given to the creator.



Non commercial:

Only noncommercial uses of the work are permitted.



Share alike:

Adaptations must be shared under the same terms.