



Module 7:

Pipelined processor design

Introduction to computers II

José Manuel Mendías Cuadros

*Dpto. Arquitectura de Computadores y Automática
Universidad Complutense de Madrid*



Outline



- ✓ Introduction.
- ✓ Data path design.
- ✓ Controller design.
- ✓ Structural hazards.
- ✓ Data hazards.
- ✓ Control hazards.
- ✓ Comparison: single-cycle vs. multicycle vs. pipelined.
- ✓ Advanced microarchitectures.
- ✓ Technology.

These slides are based on:

- S.L. Harris and D. Harris. *Digital Design and Computer Architecture. RISC-V Edition.*
- D.A. Patterson and J.L. Hennessy. *Computer Organization and Design. RISC-V Edition.*



Introduction


- **No modern processor is single-cycle.**
 - This microarchitecture was only used in the **first computers**.
- **No current processor is multicycle.**
 - This microarchitecture was **used until the late 80s**:
 - Mainframes: IBM/360, DEC VAX
 - Microprocessors: 8088/86 (IBM PC), 68000 (Apple Macintosh), Z80 (Spectrum)
 - Nowadays, it is only used in **low-performance microcontrollers**:
 - 8051, 68HC11, PIC-16
- Since the 90s, **all processors are pipelined.**
 - **Current processors** use **even more advanced microarchitectures** but based on the pipelining concept.



Introduction

Pipelining (i)

 - At home, it is usual to have a **sequential laundry**:
 - 4 stages with **similar duration**: wash, dry, iron and store.




- Each **appliance** is inactive during **75% of the time**.
- 1 load takes 4 units of time.
- 5 loads take $4 \times 5 = 20$ units of time.
- n loads take $4 \cdot n$ units of time.



Introduction

Pipelining (ii)

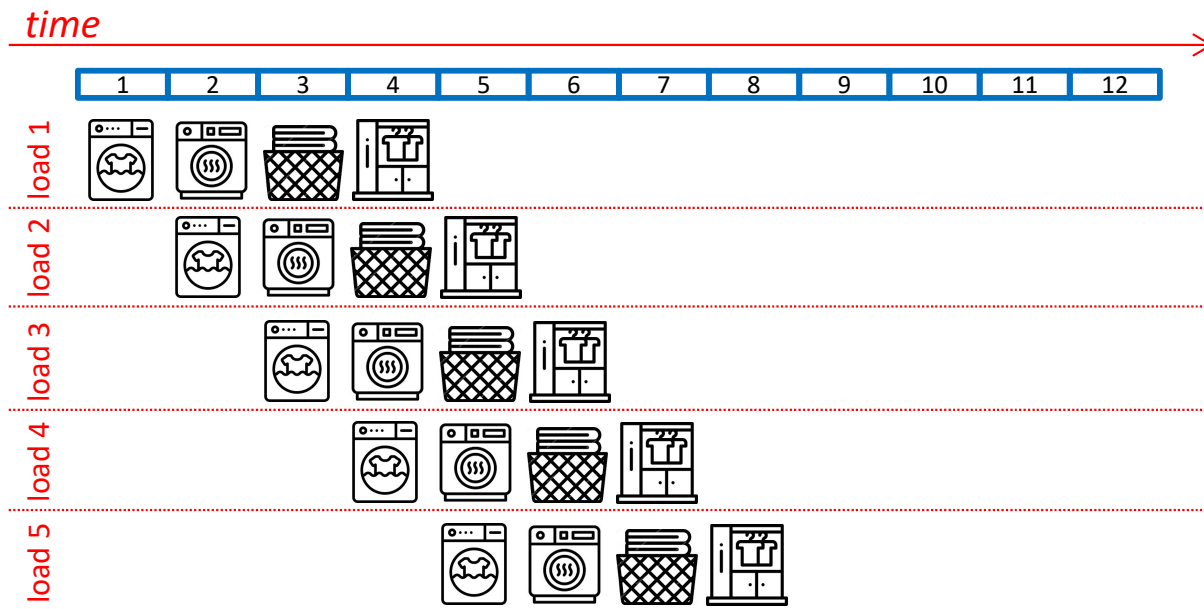- In an **industrial laundry**, the process is more efficient:
 - A new load is started even if the previous one has not finished



$$Speedup = \frac{4 \cdot n}{4 + (n - 1)}$$

$$\lim_{n \rightarrow \infty} \frac{4 \cdot n}{4 + (n - 1)} = 4$$


- Now, **appliances** are used **100%** of the time.
- 1 load still takes 4 units of time.
- 5 loads now take $4 + (5-1) = 8$ units of time.
- n loads take $4 + (n-1)$ units of time.



Introduction

Pipelining (iii)

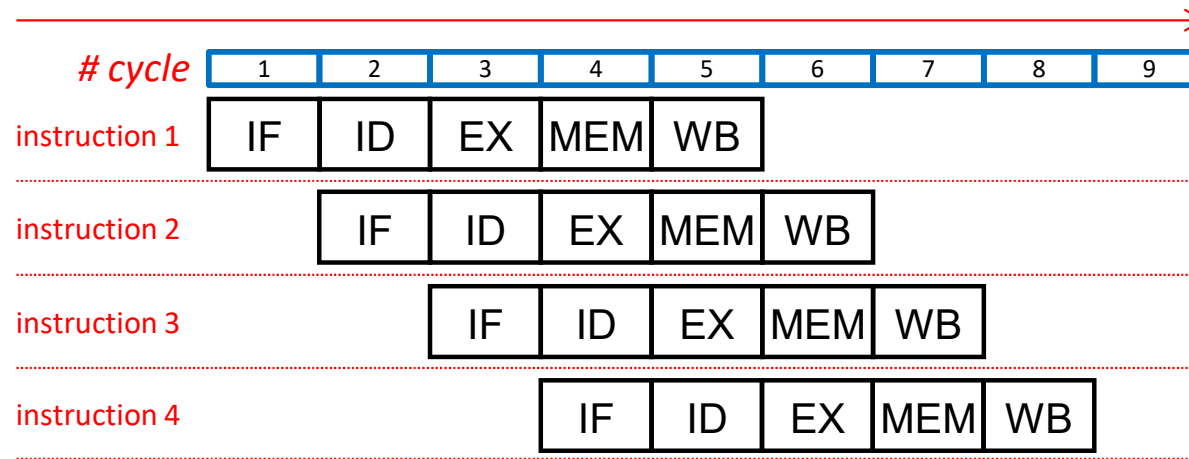- A **pipelined processor** behaves as in the industrial laundry example, overlapping the execution of several instructions.




- Each cycle, a new instruction is fetched before the previous one has finished.
- Each **instruction goes through 5 stages, taking 5 cycles to execute:**
 - The **latency** of this processor is **5 cycles**.
- The **execution time** of a program will be **much lower** because:
 - Several instructions are executed simultaneously.
 - The **cycle time** can be **shorter** (as in the multicycle processor).
 - Ideally, **CPI = 1** (as in the single-cycle processor).



Data path design

Reduced RISC-V data path (i)

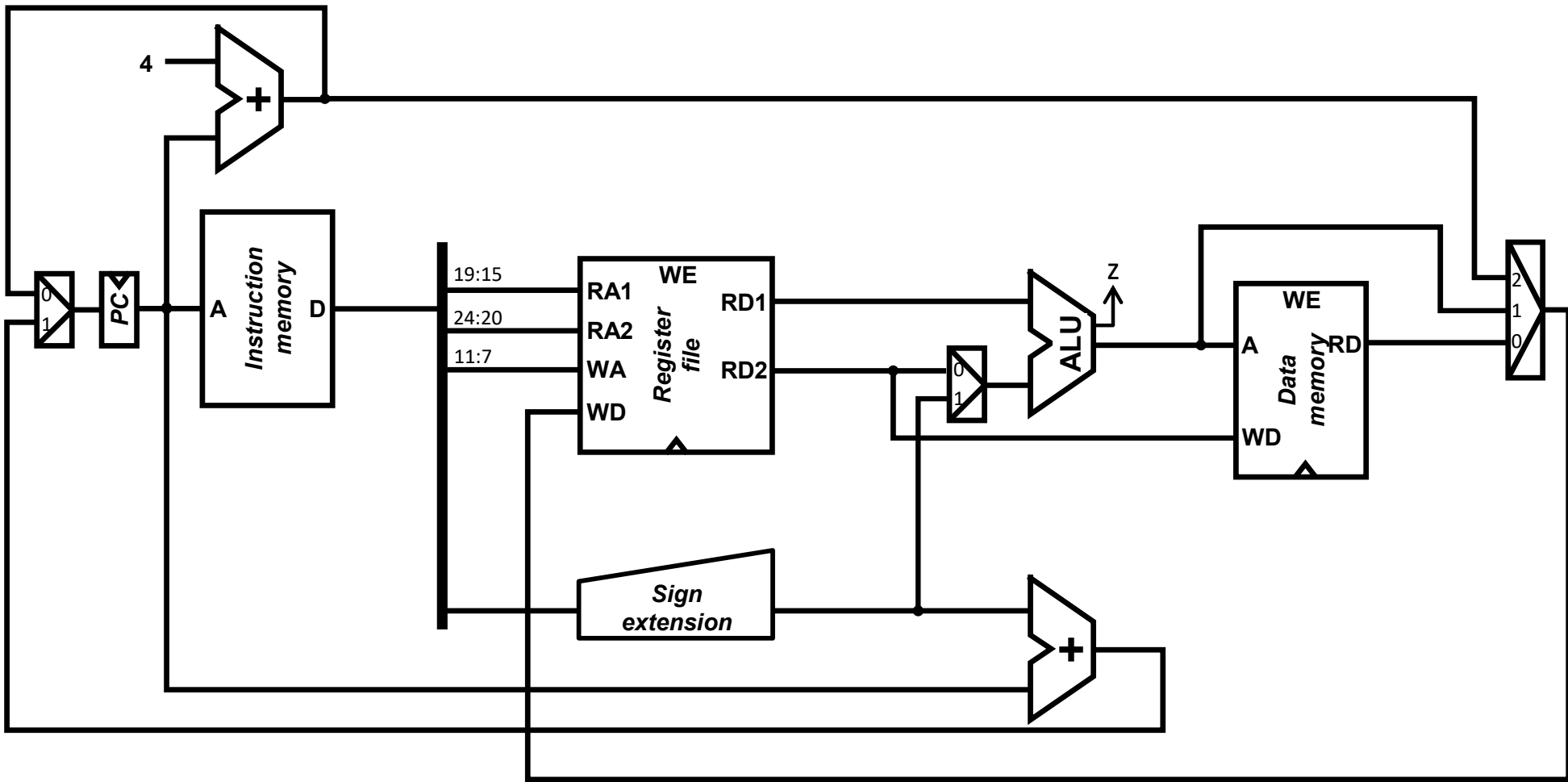- The **data path** of the pipelined processor is:
 - single-cycle processor data path + pipeline registers






Data path design

Reduced RISC-V data path (ii)

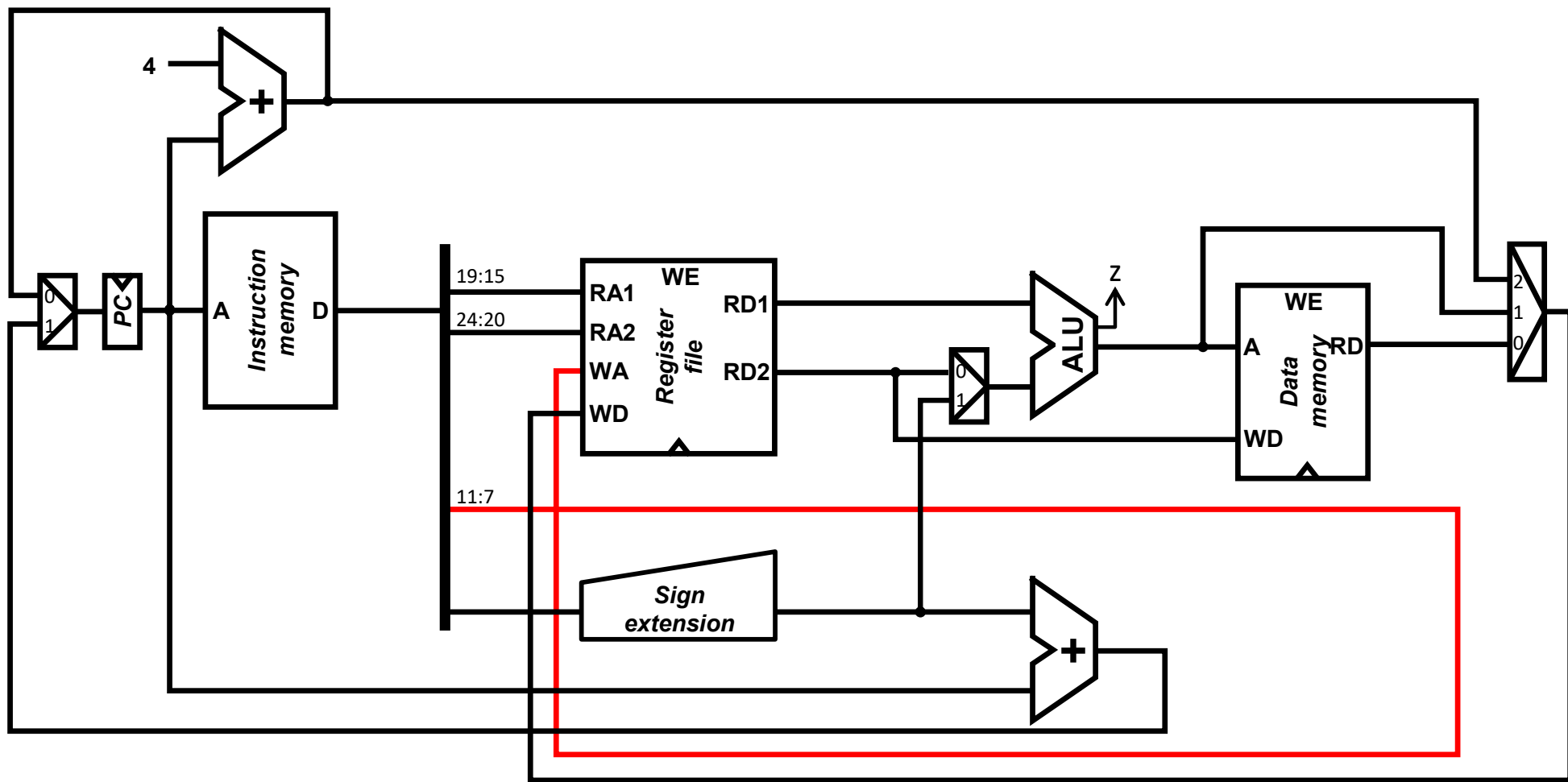- The **data path** of the pipelined processor is:
 - single-cycle processor data path + pipeline registers





Data path design

Reduced RISC-V data path (iii)


IF
Instruction fetch

ID
Instruction decode and
register file read

EX
Execution or
address calculation

MEM
Data memory
access

WB
Write back

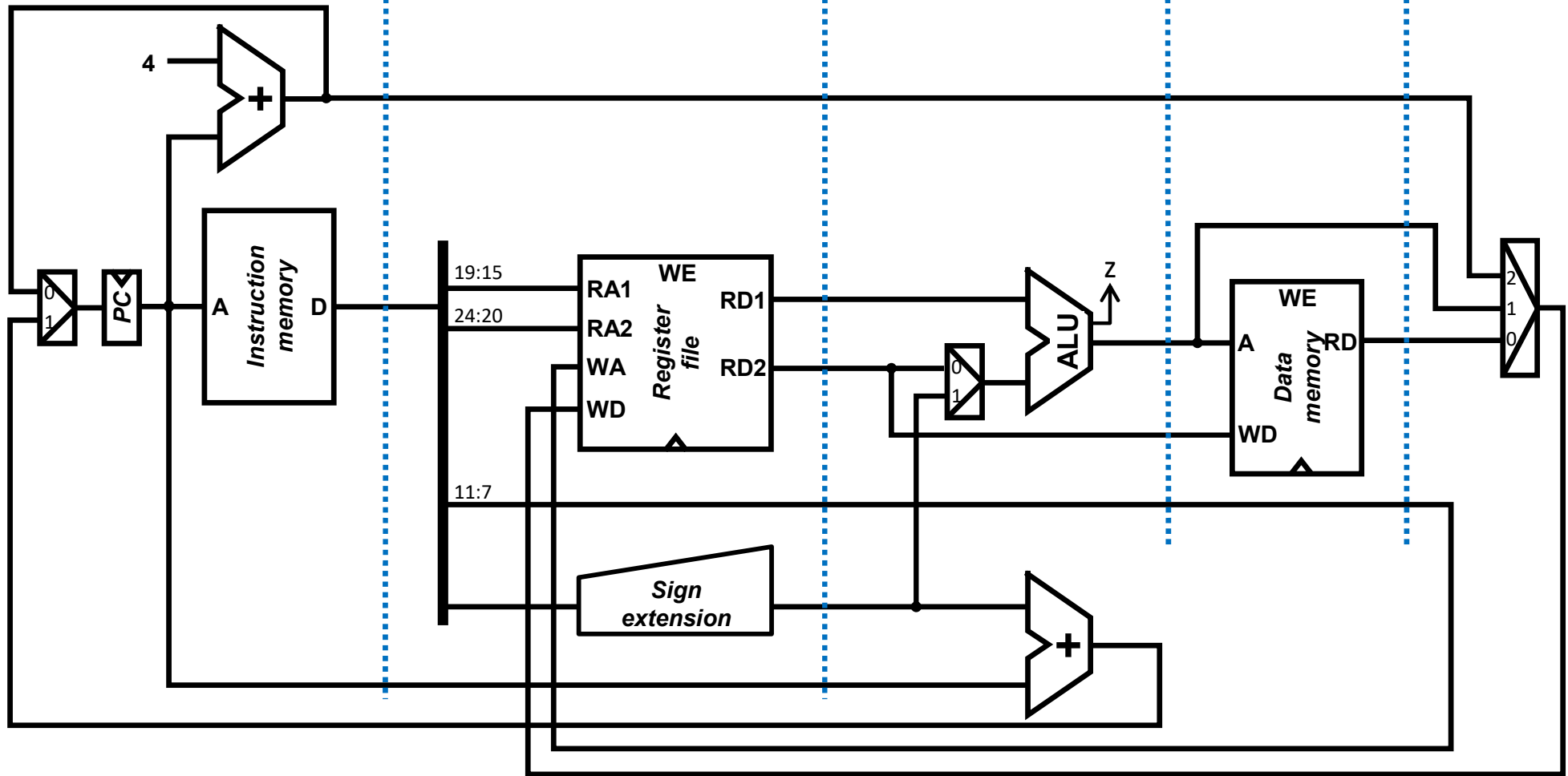




Data path design

Reduced RISC-V data path (iv)

IF Instruction fetch
ID Instruction decode and register file read
EX Execution or address calculation
MEM Data memory access
WB Write back

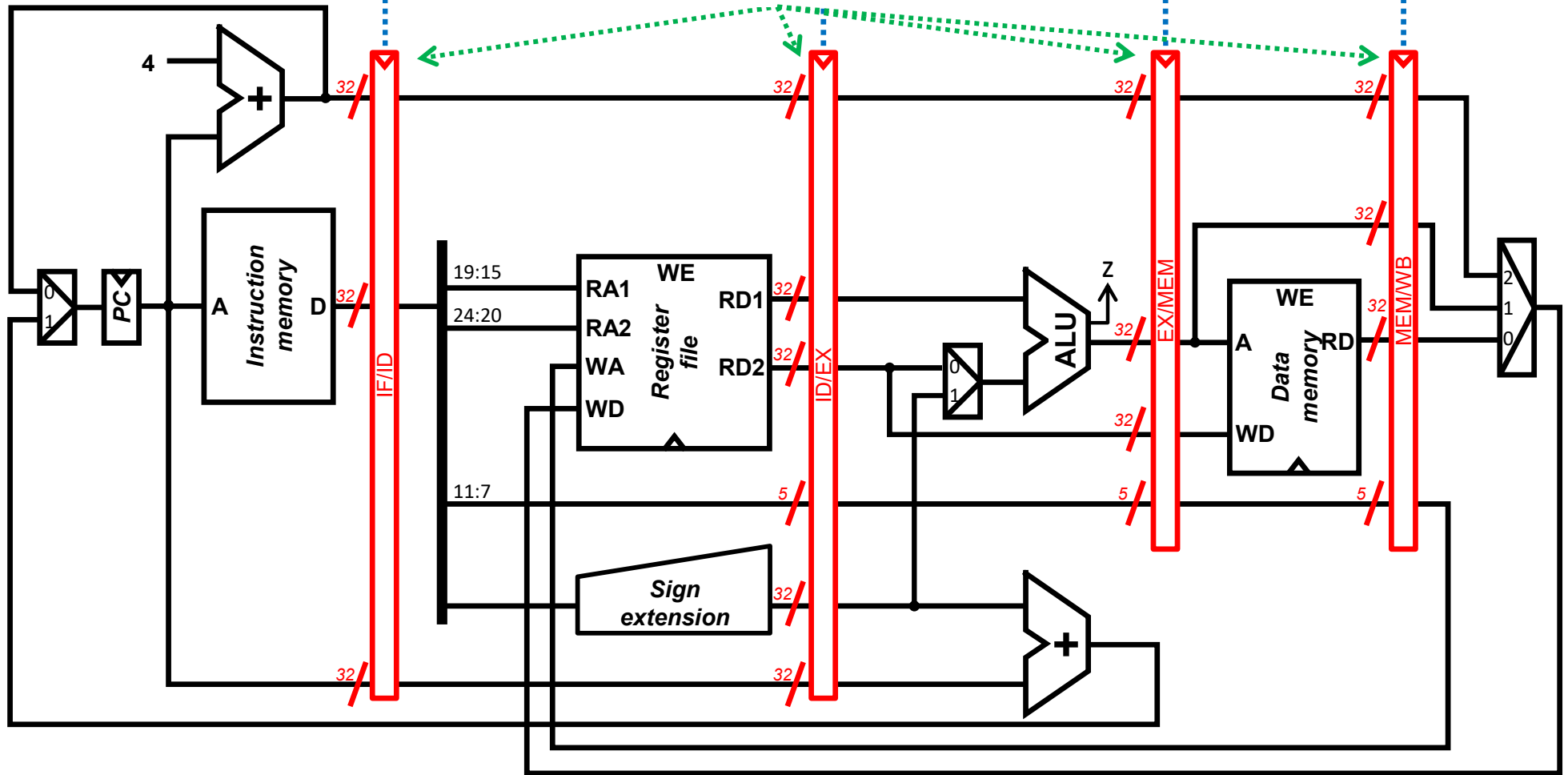Pipeline registers are added to separate stages







Data path design

lw instruction: IF stage

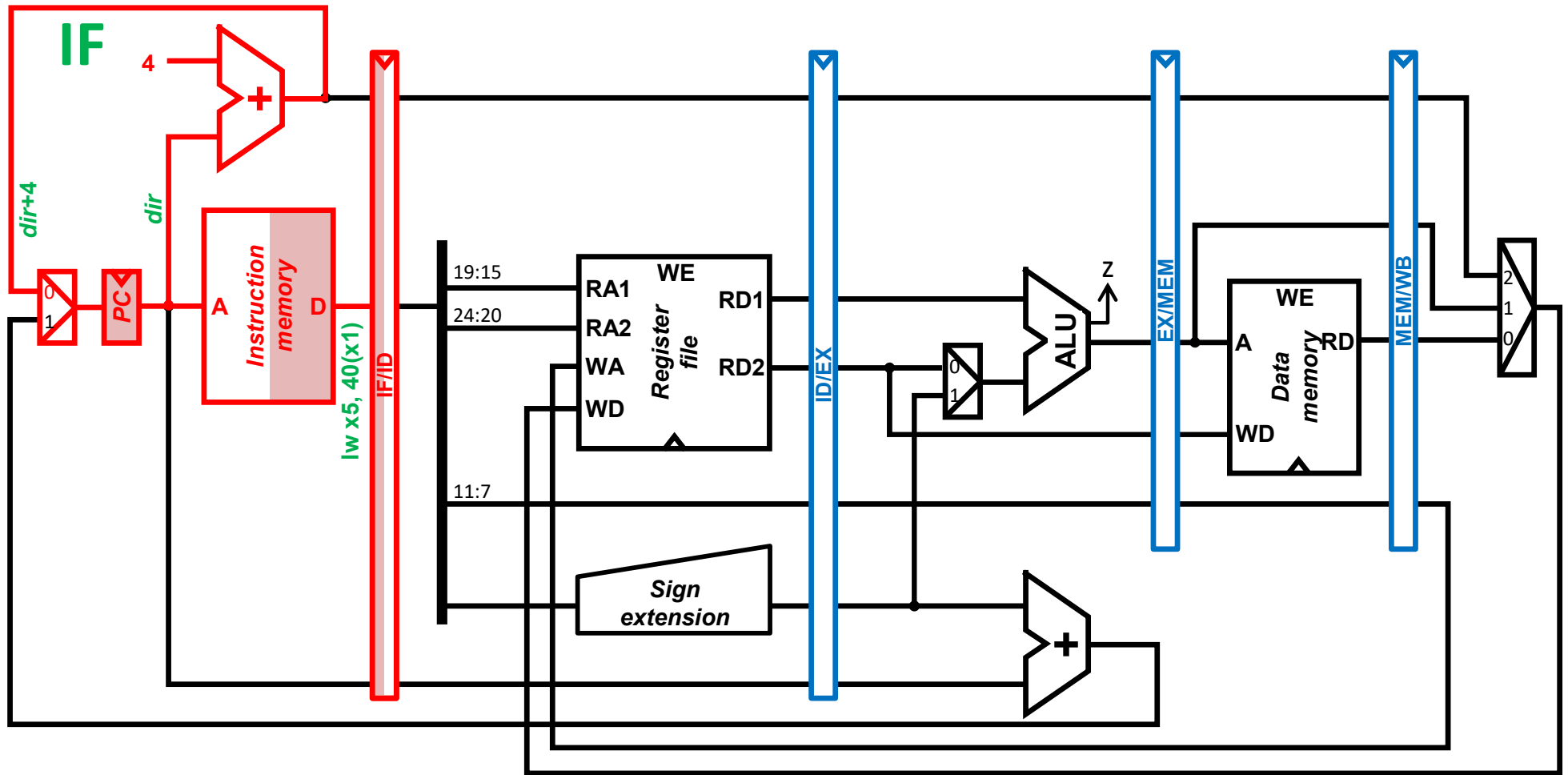 The **lw** load instruction takes 5 cycles using resources in all the stages







Data path design

lw instruction: ID stage

The **lw** load instruction takes 5 cycles using resources in all the stages



lw x5, 40(x1)

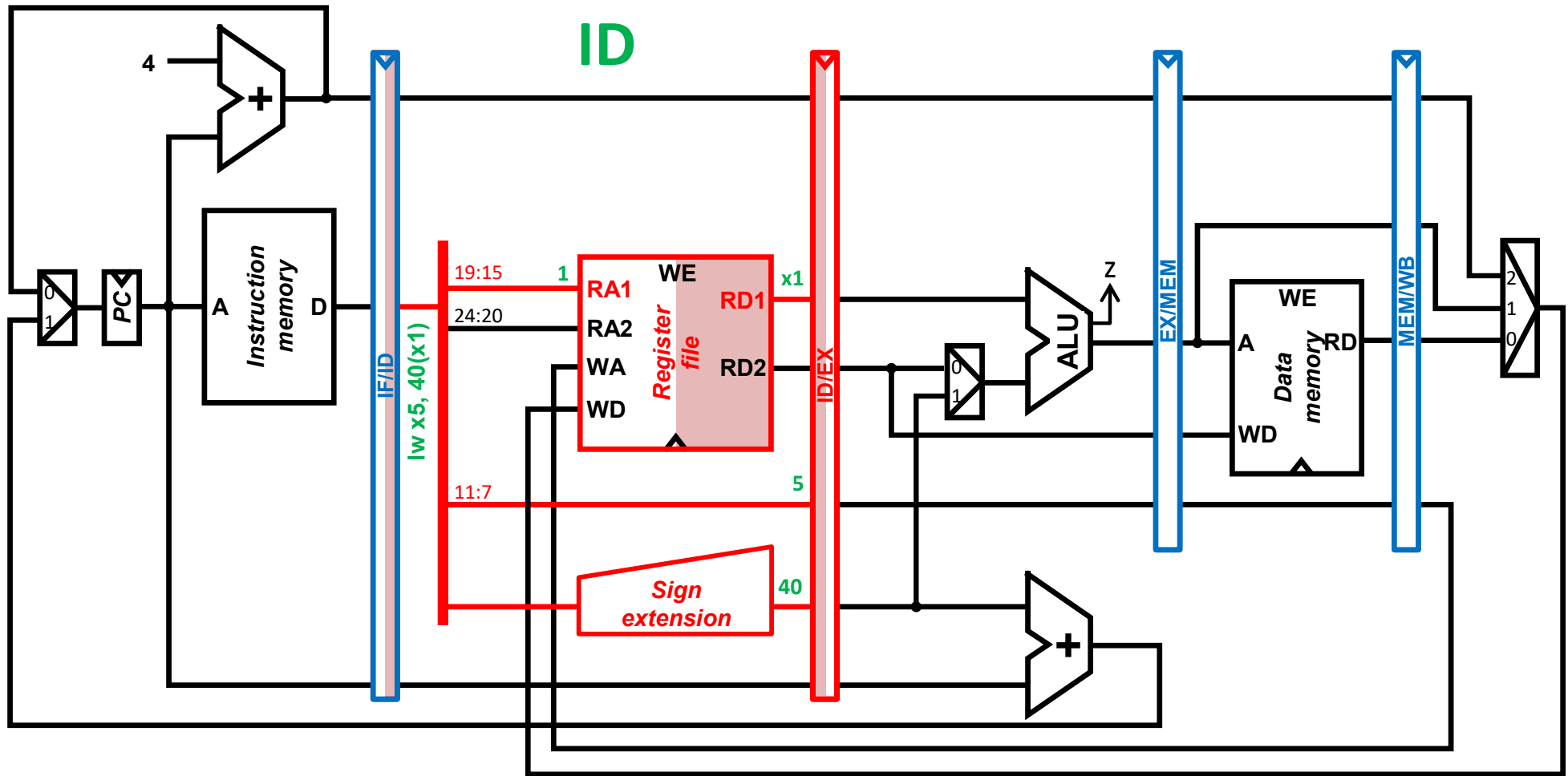
 




Data path design

lw instruction: EX stage

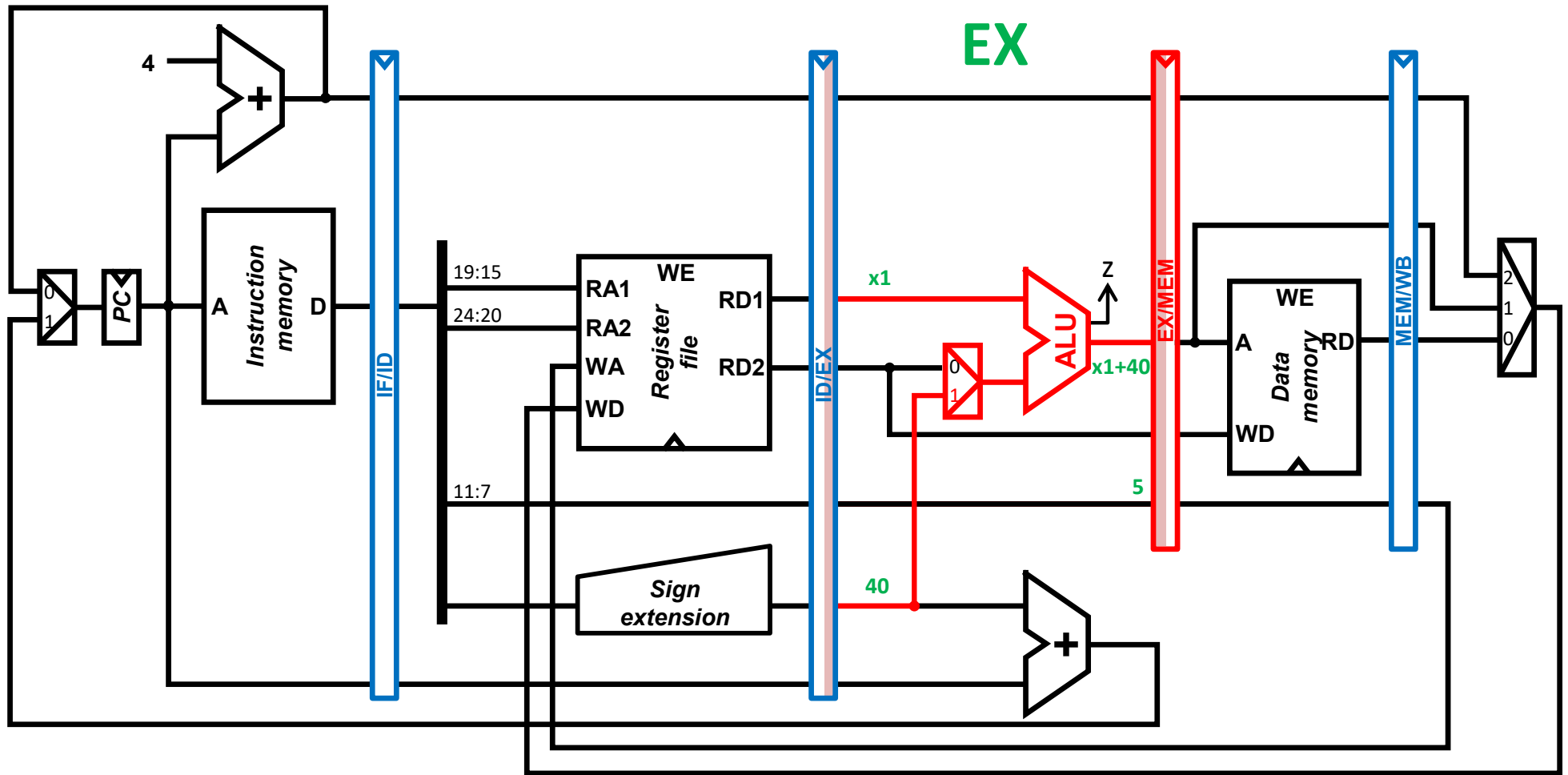 The **lw** load instruction takes 5 cycles using resources in all the stages







Data path design

lw instruction: MEM stage

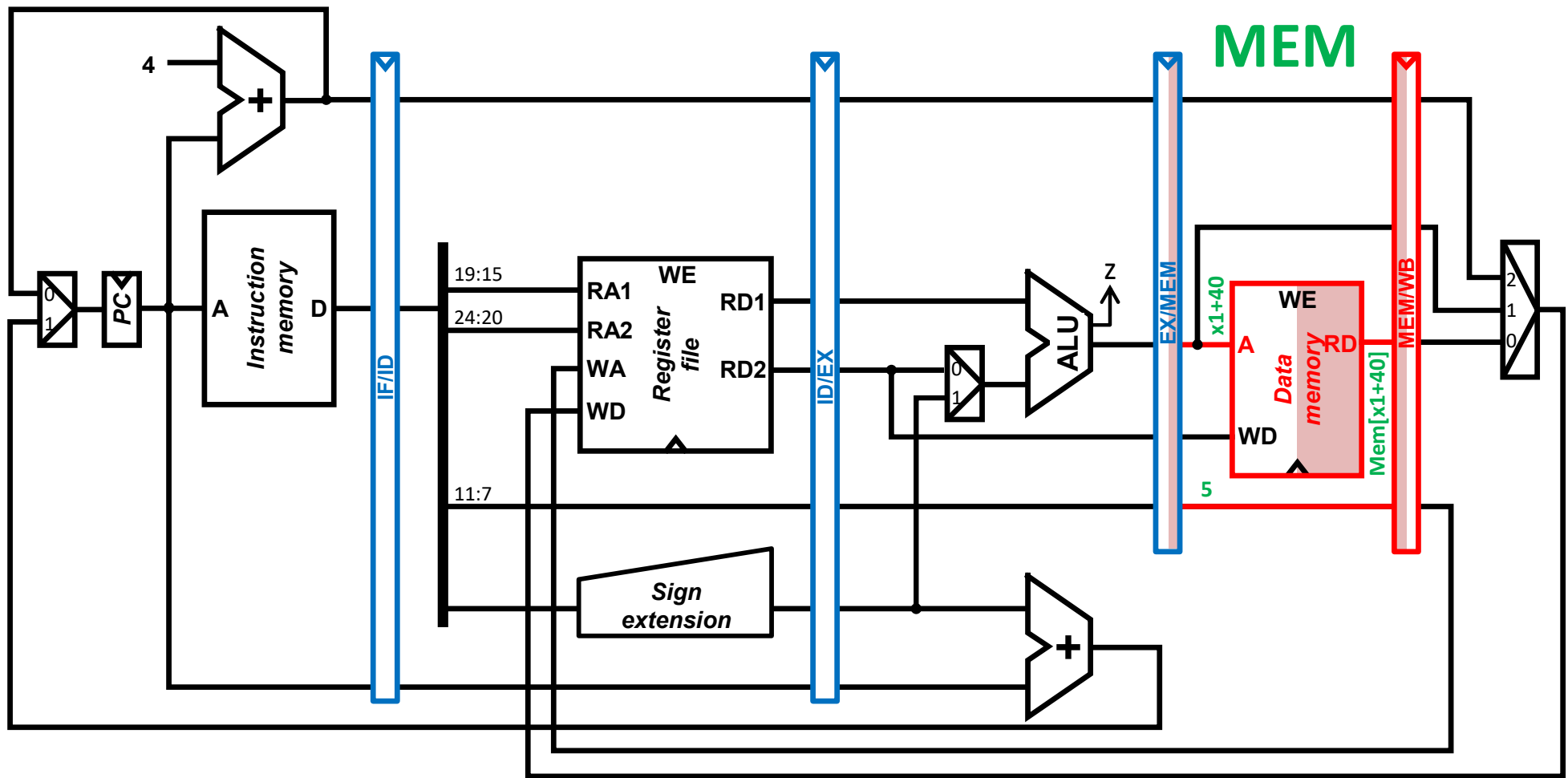 The `lw` load instruction takes 5 cycles using resources in all the stages







Data path design

lw instruction: WB stage

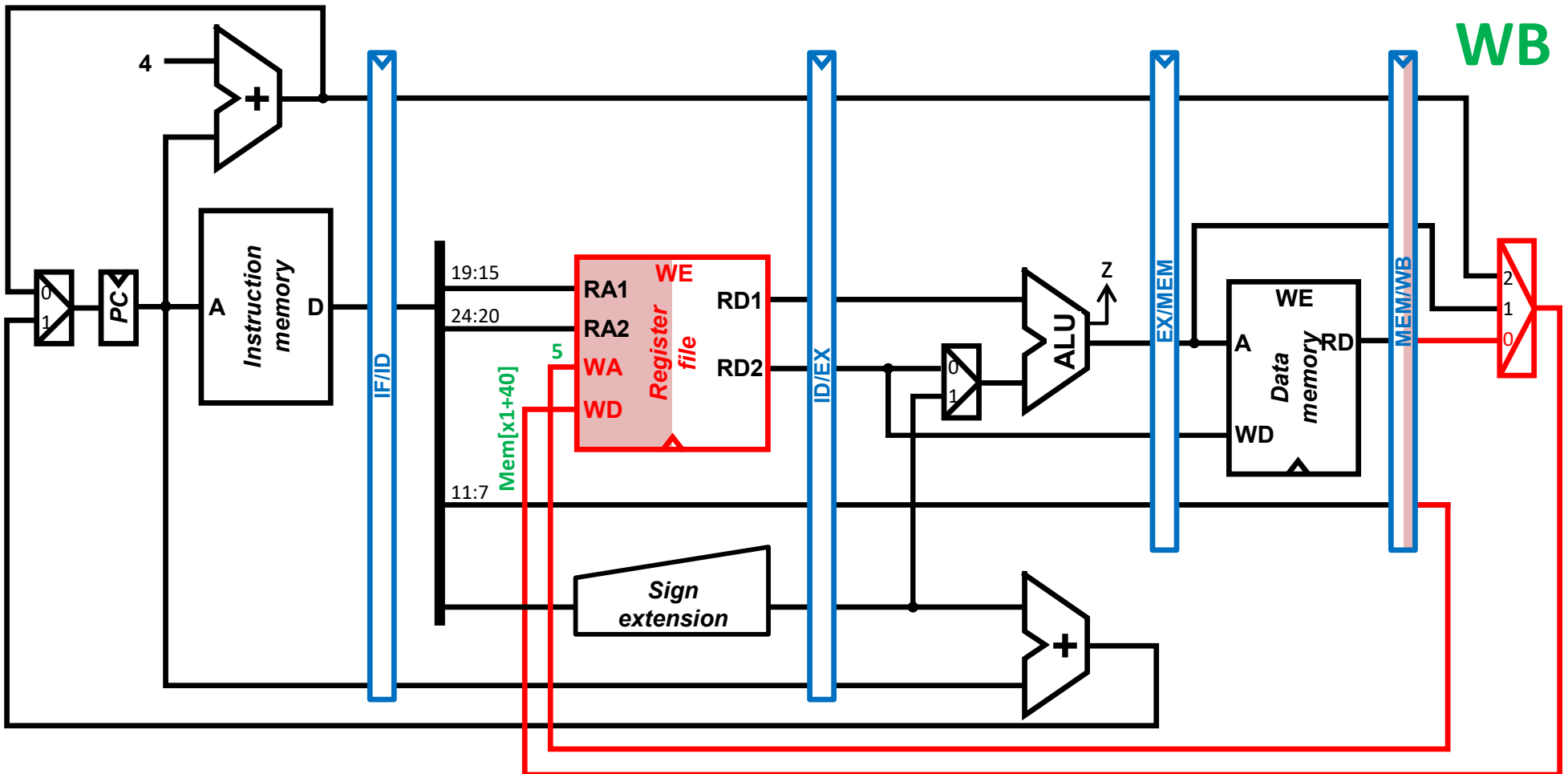 The **lw** load instruction takes 5 cycles using resources in all the stages







Data path design

sw instruction: IF stage

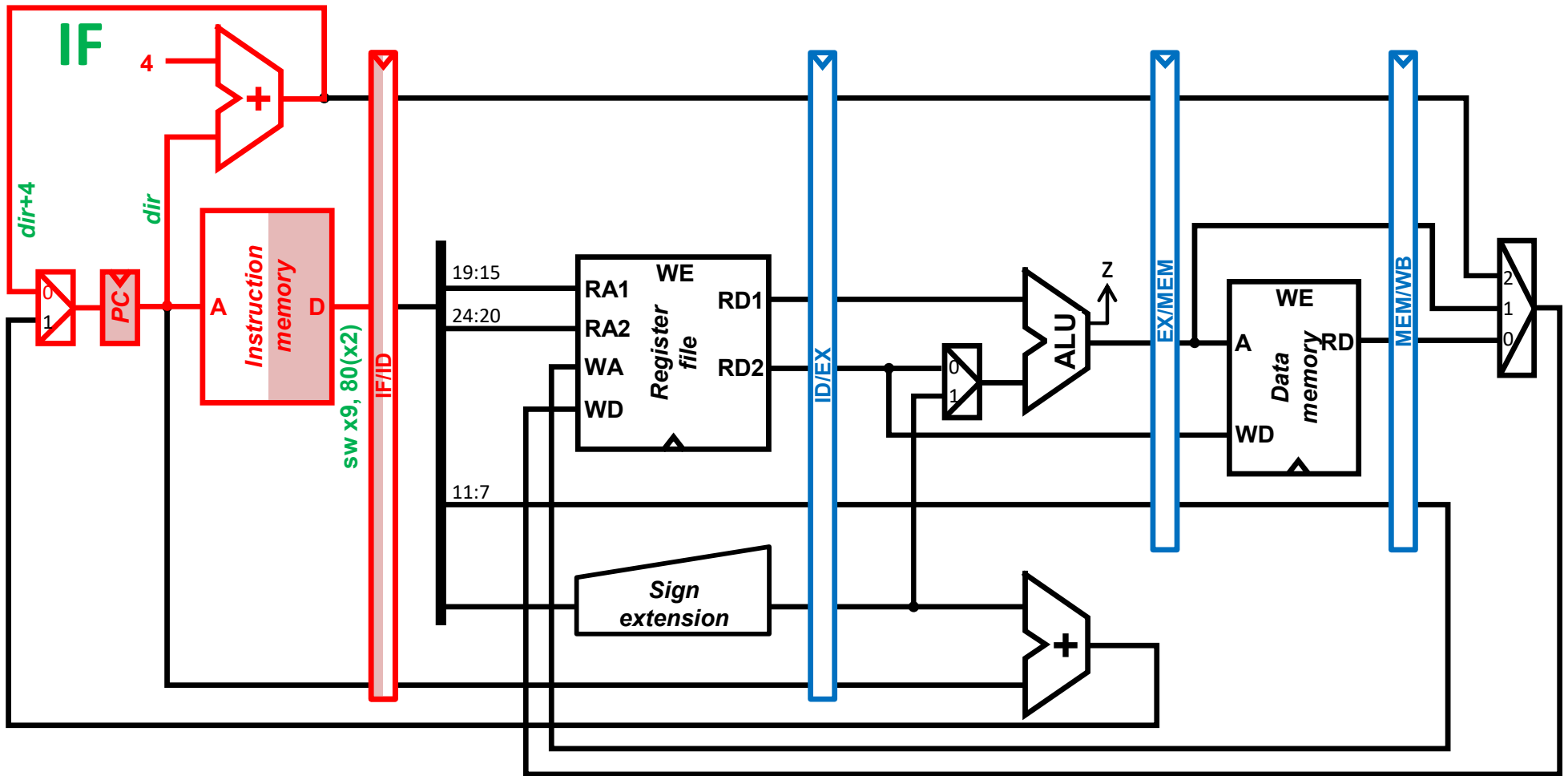 The **sw** instruction takes 5 cycles without using the RF in the WB stage







Data path design

sw instruction: ID stage

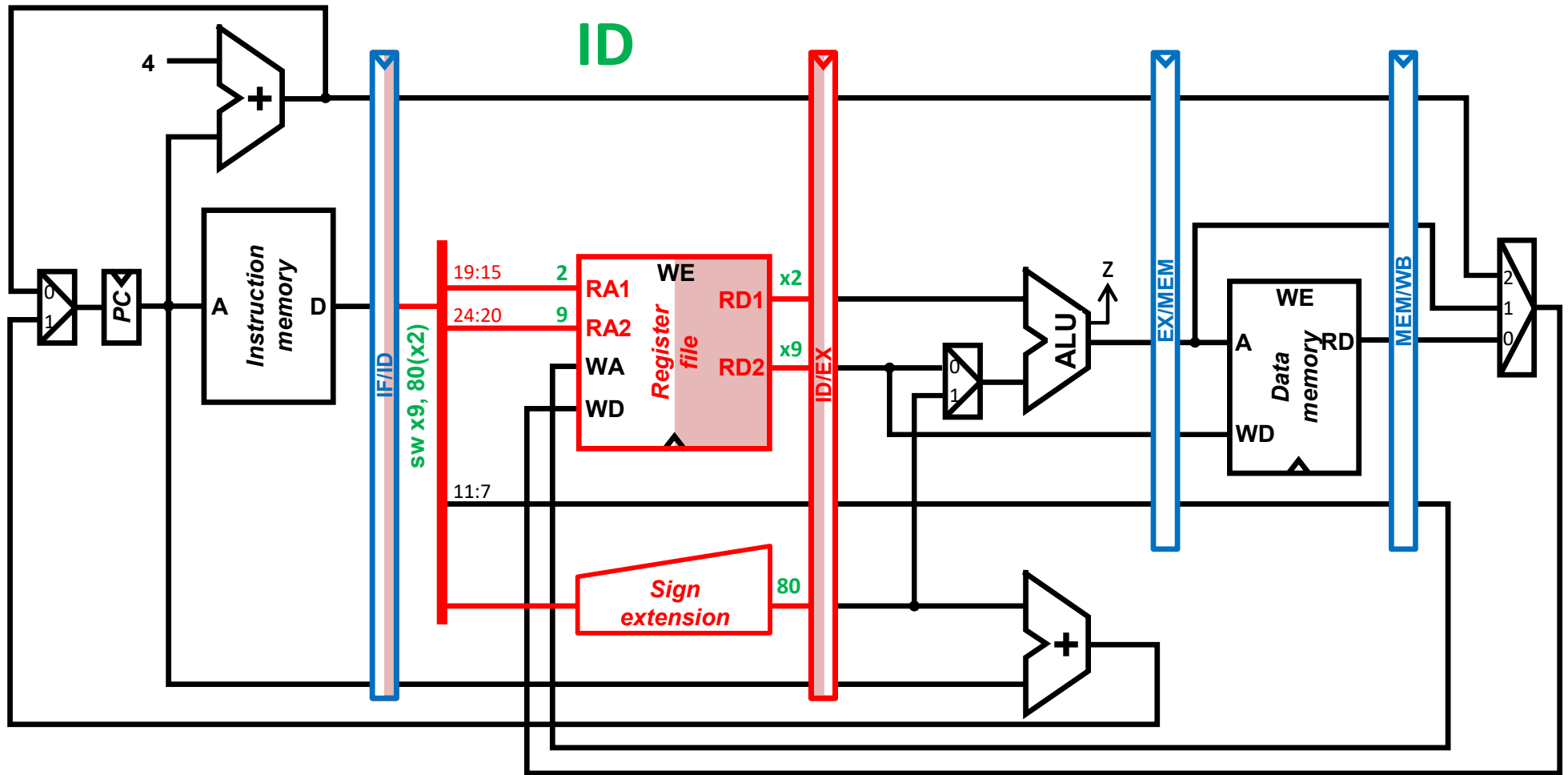 The **sw** instruction takes 5 cycles without using the RF in the WB stage







Data path design

sw instruction: EX stage

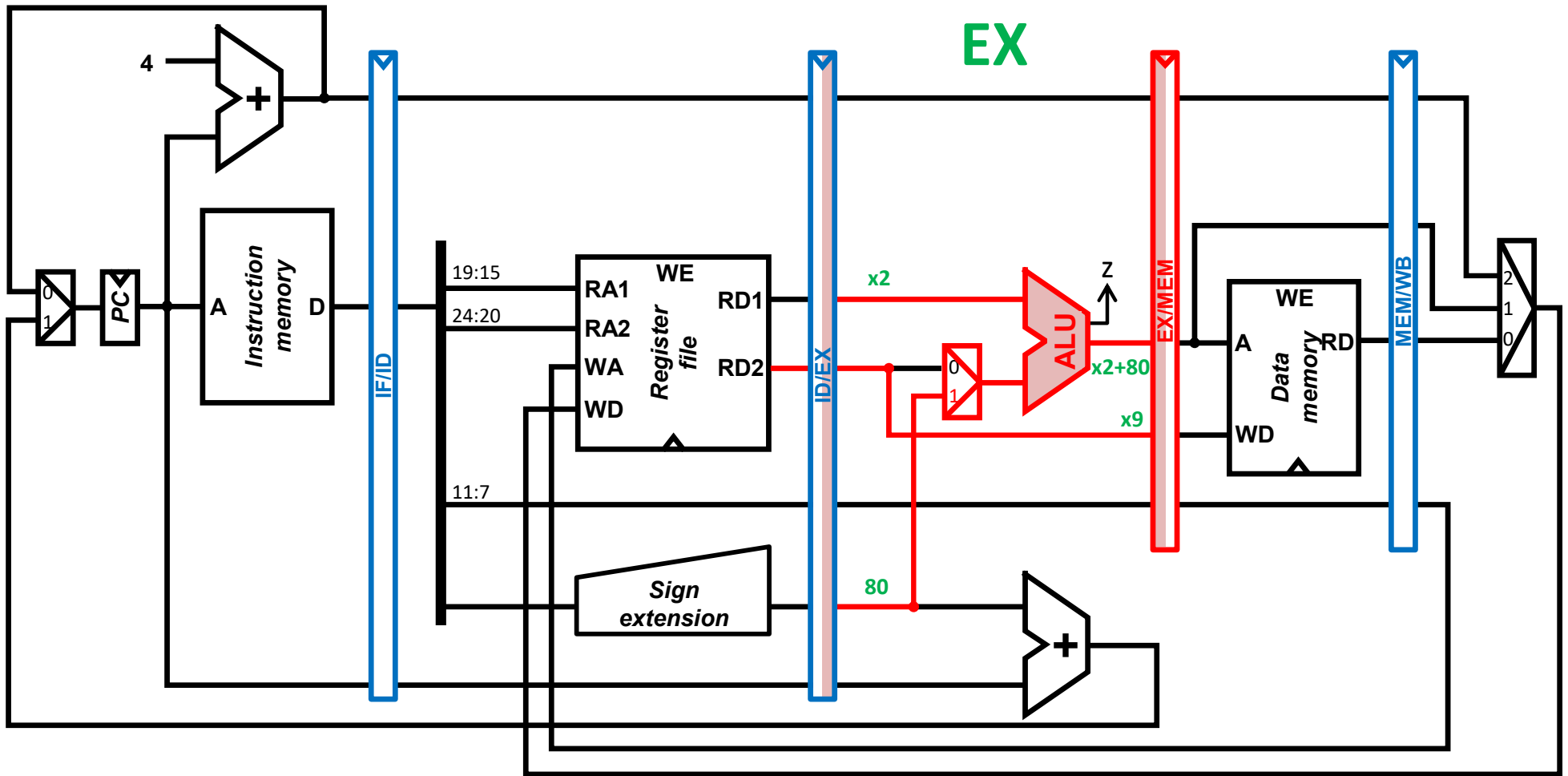 The **sw** instruction takes 5 cycles
without using the RF in the WB stage







Data path design

sw instruction: WB stage

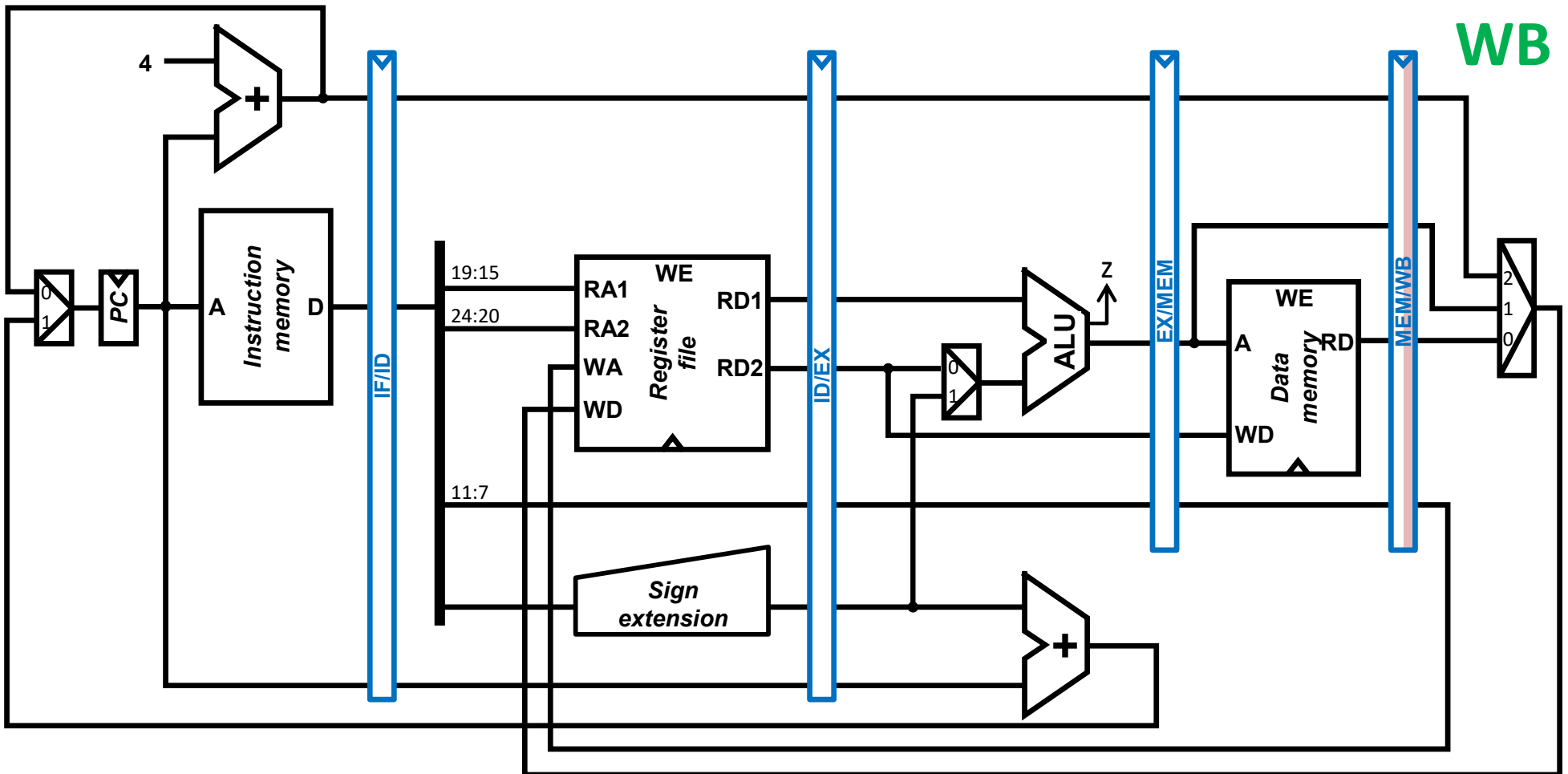 The **sw** instruction takes 5 cycles
without using the RF in the WB stage







Data path design

add-like instruction: IF stage

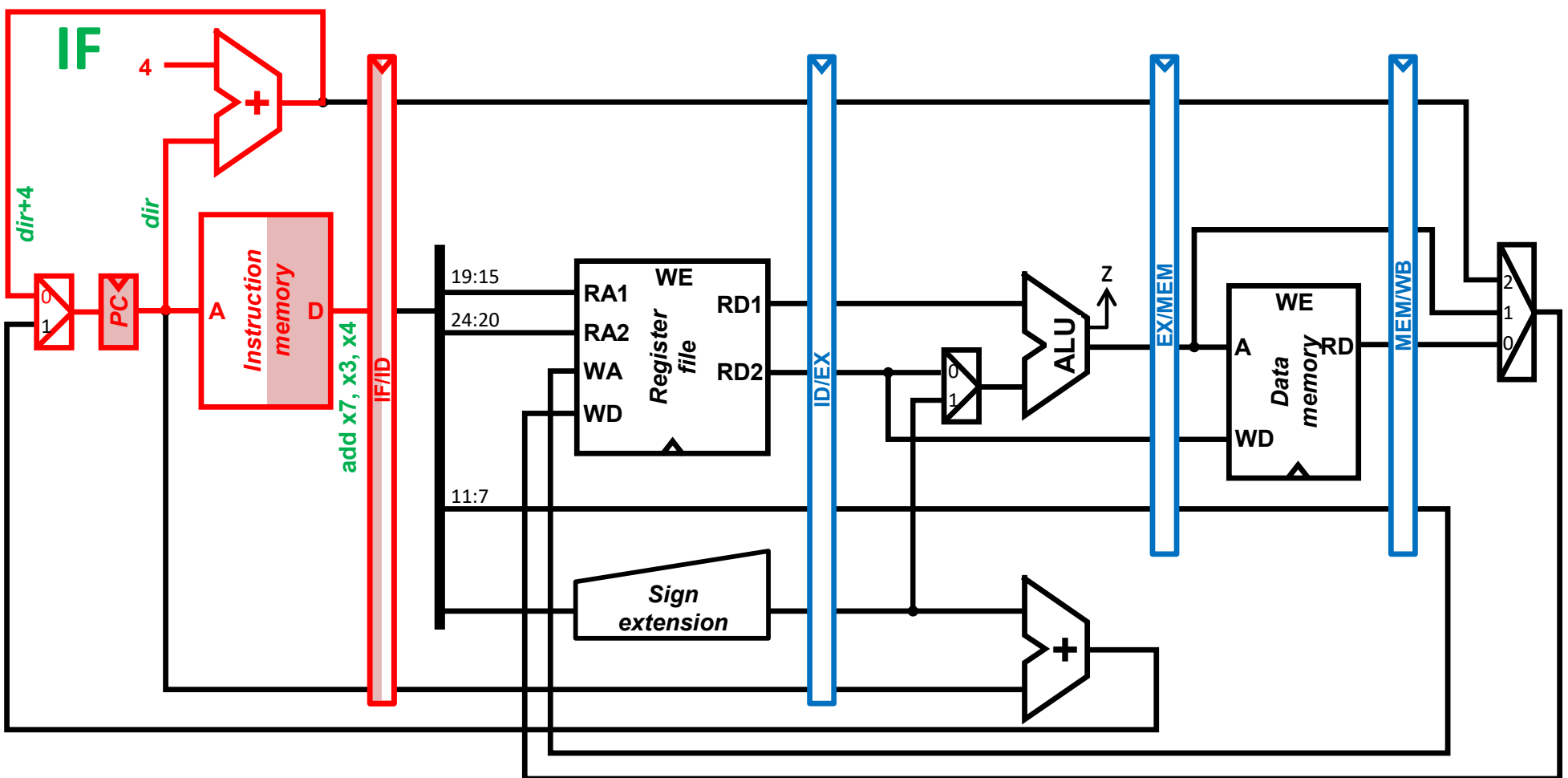 The `add` instruction takes 5 cycles without using the memory in the MEM stage







Data path design

add-like instruction: ID stage

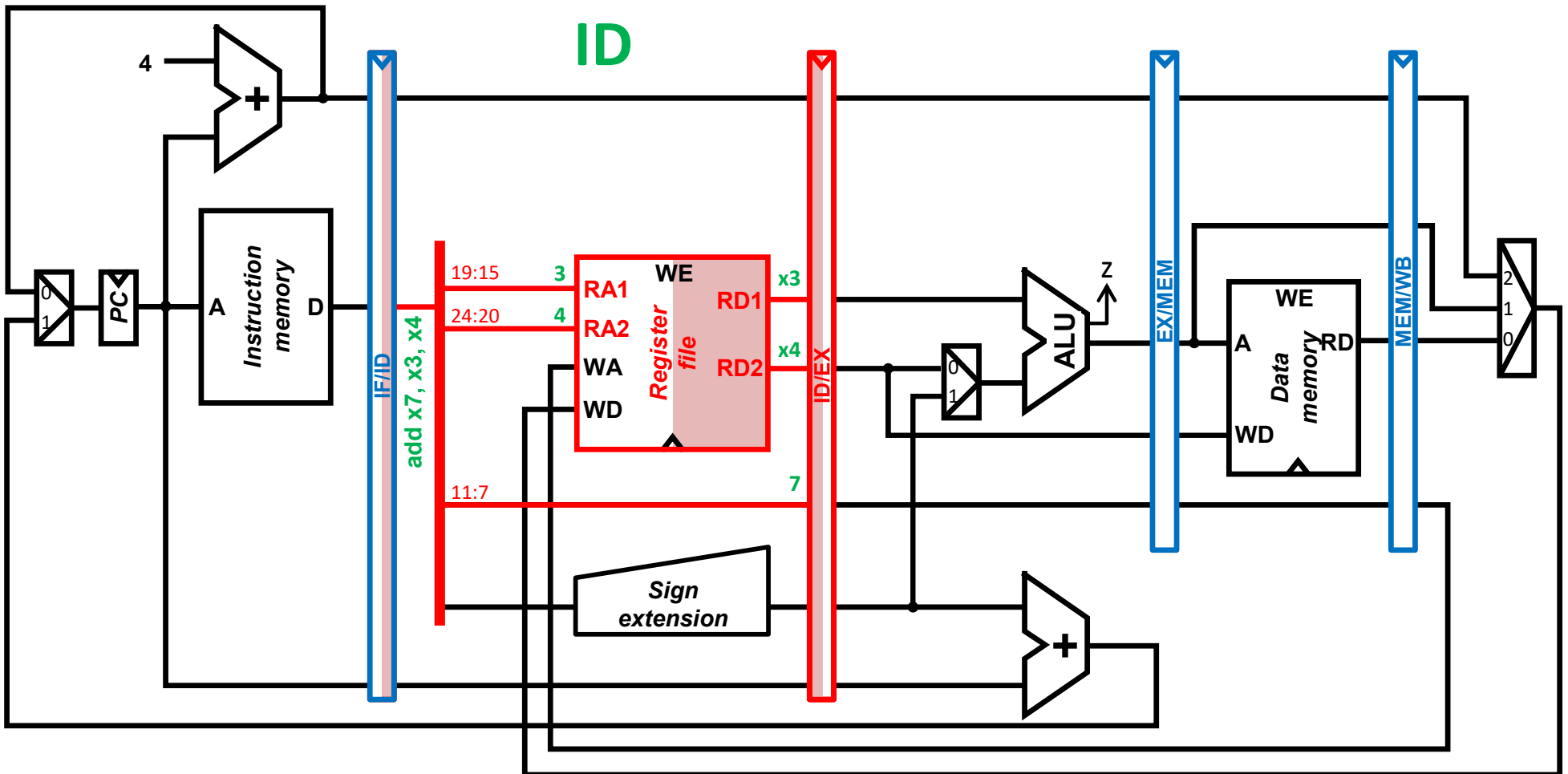 The `add` instruction takes 5 cycles without using the memory in the MEM stage







Data path design

add-like instruction: EX stage

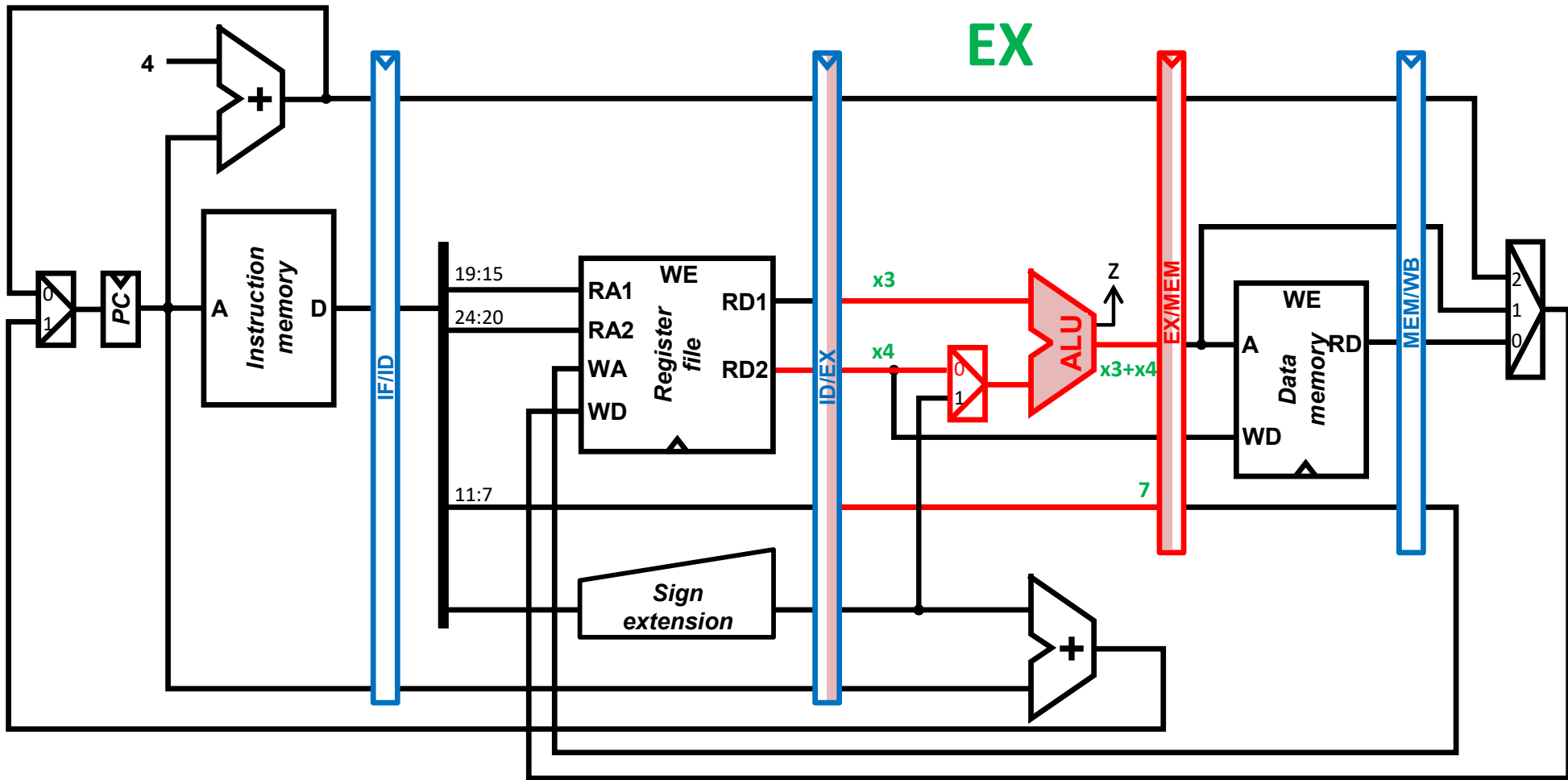 The **add** instruction takes 5 cycles
without using the memory in the MEM stage






Data path design

add-like instruction: WB stage

The **add** instruction takes 5 cycles without using the memory in the MEM stage



`add x7, x3, x4`


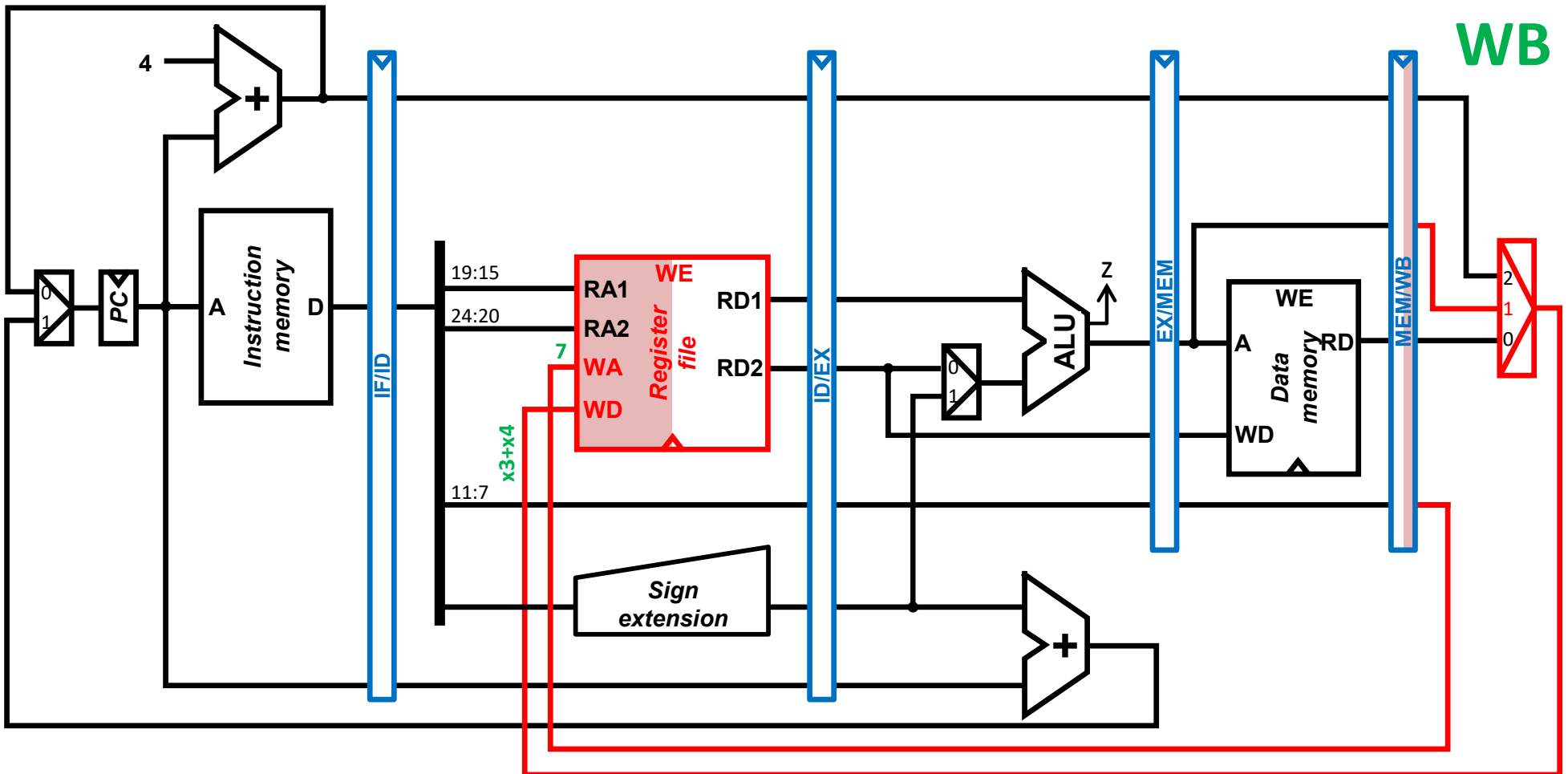




Data path design

addi-like instruction: IF stage

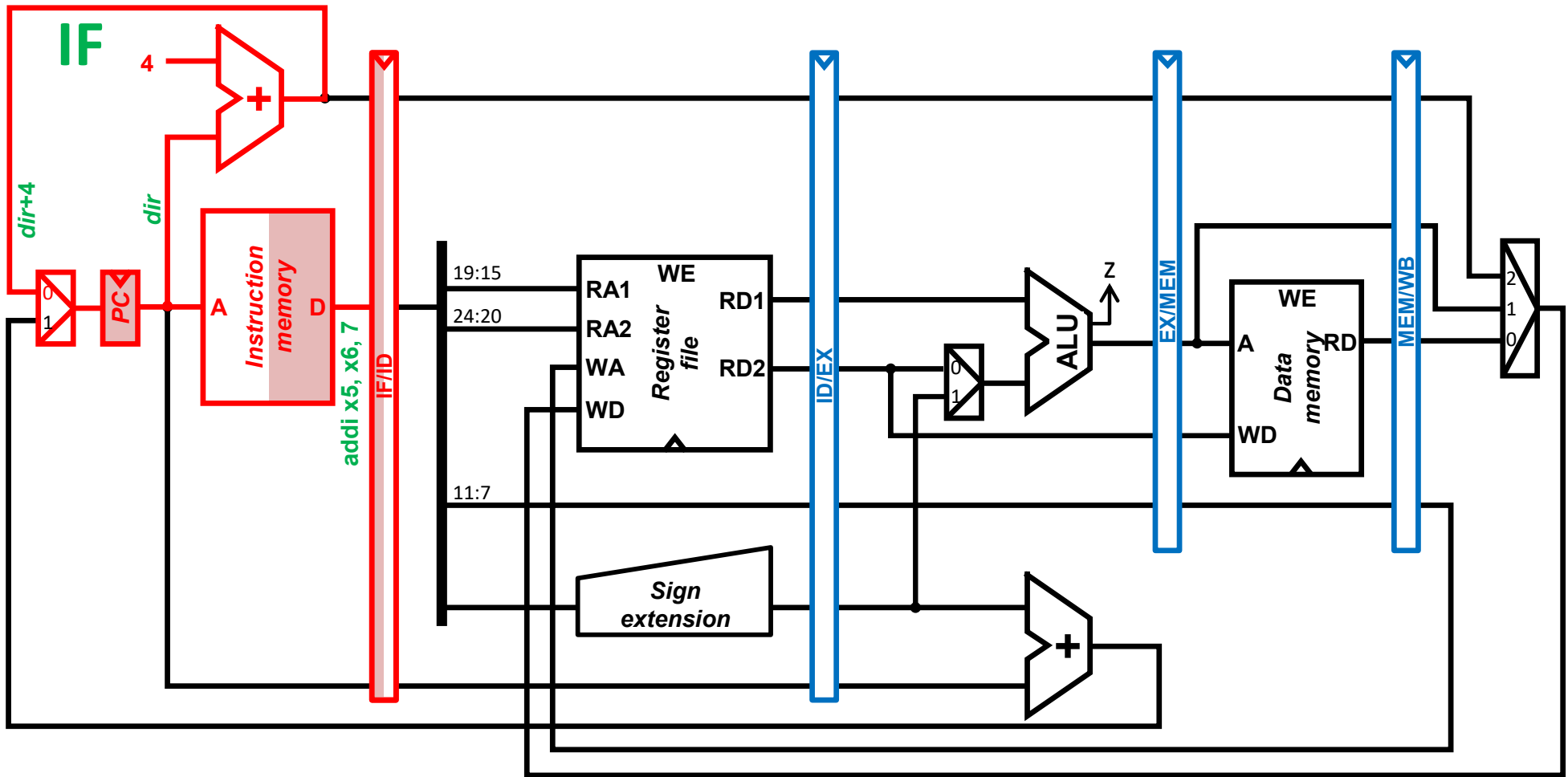 The `addi` instruction takes 5 cycles without using the memory in the MEM stage







Data path design

addi-like instruction: ID stage

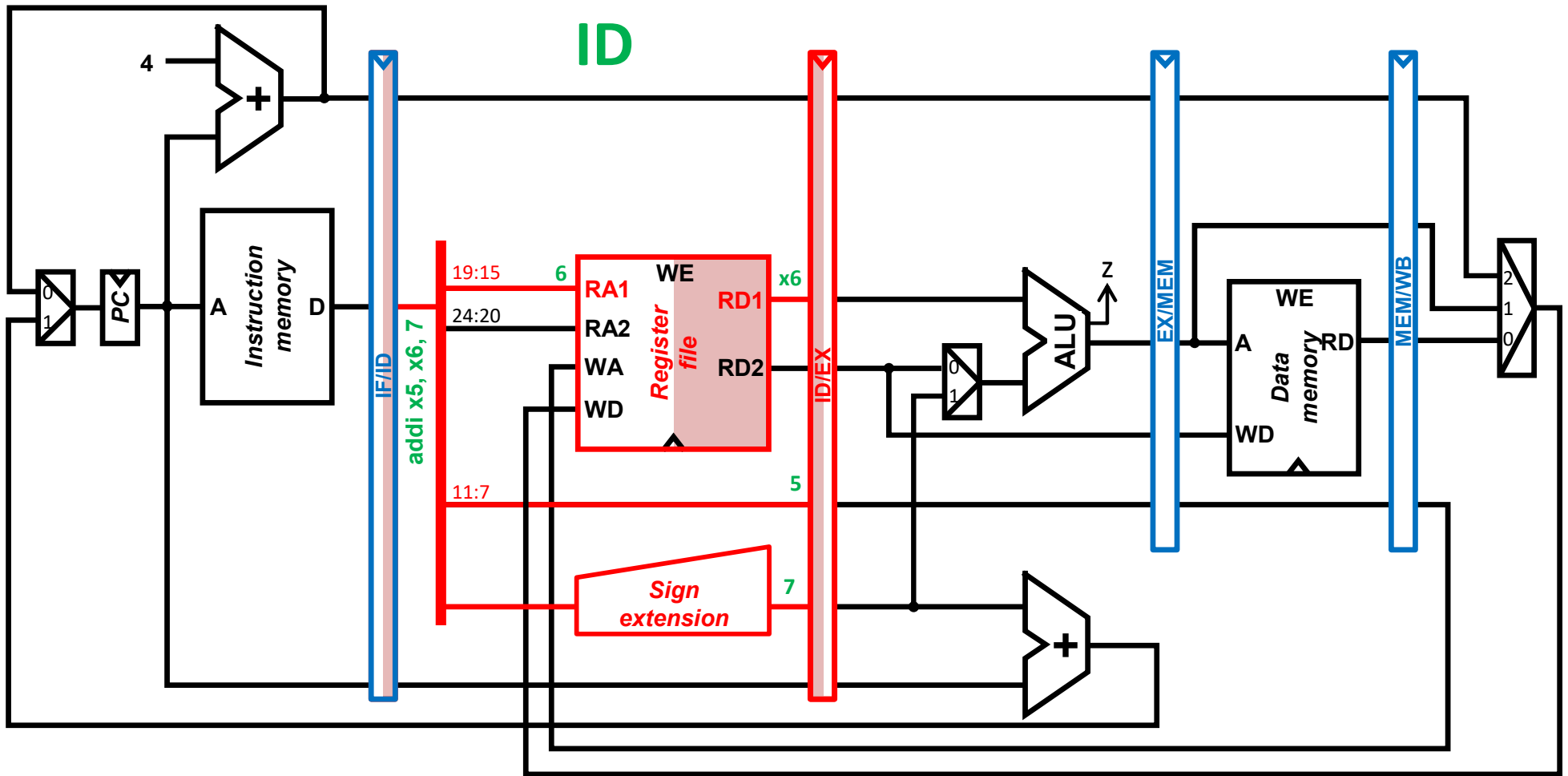 The `addi` instruction takes 5 cycles without using the memory in the MEM stage







Data path design

addi-like instruction: EX stage

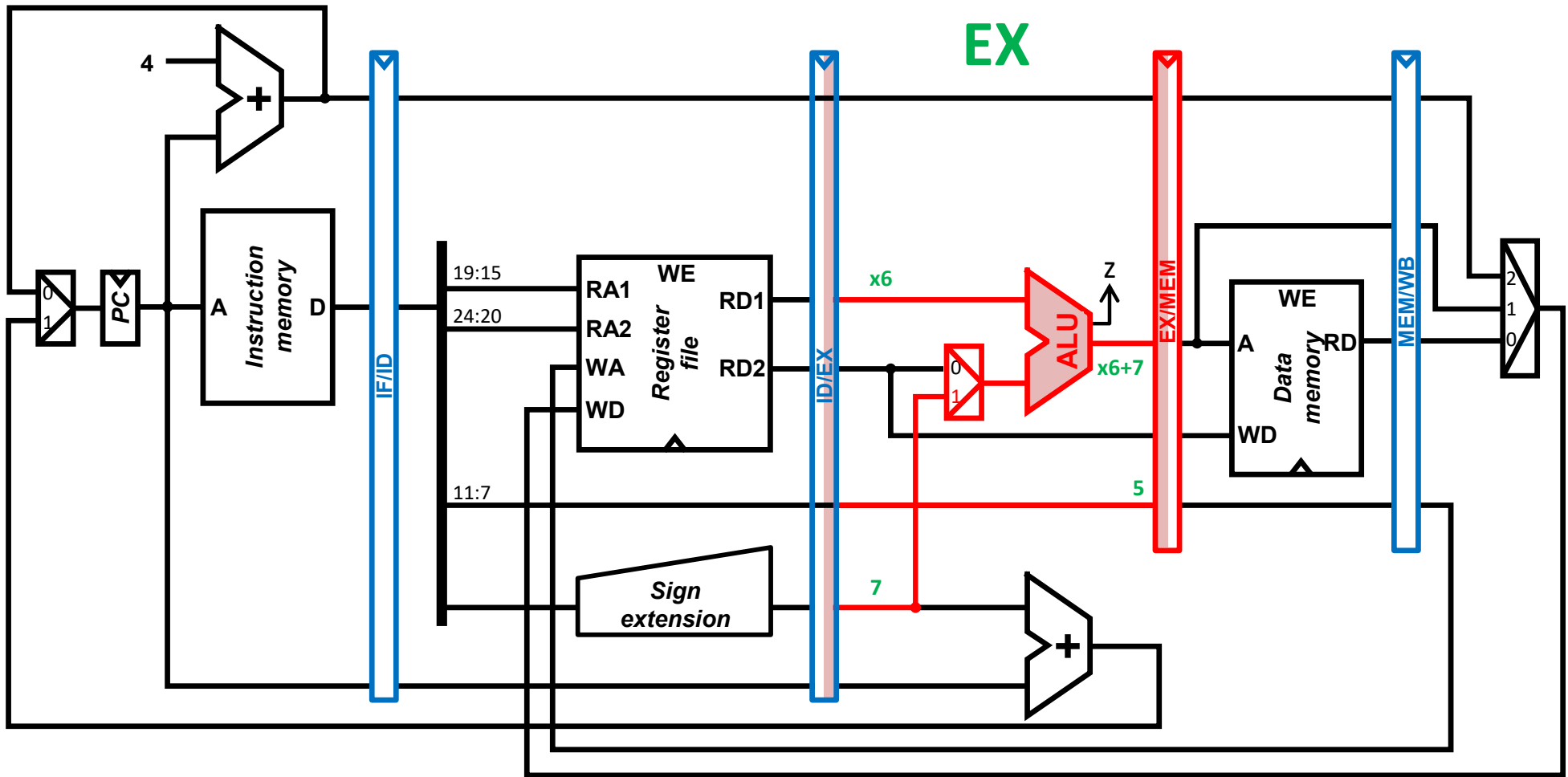 The `addi` instruction takes 5 cycles without using the memory in the MEM stage







Data path design

addi-like instruction: MEM stage

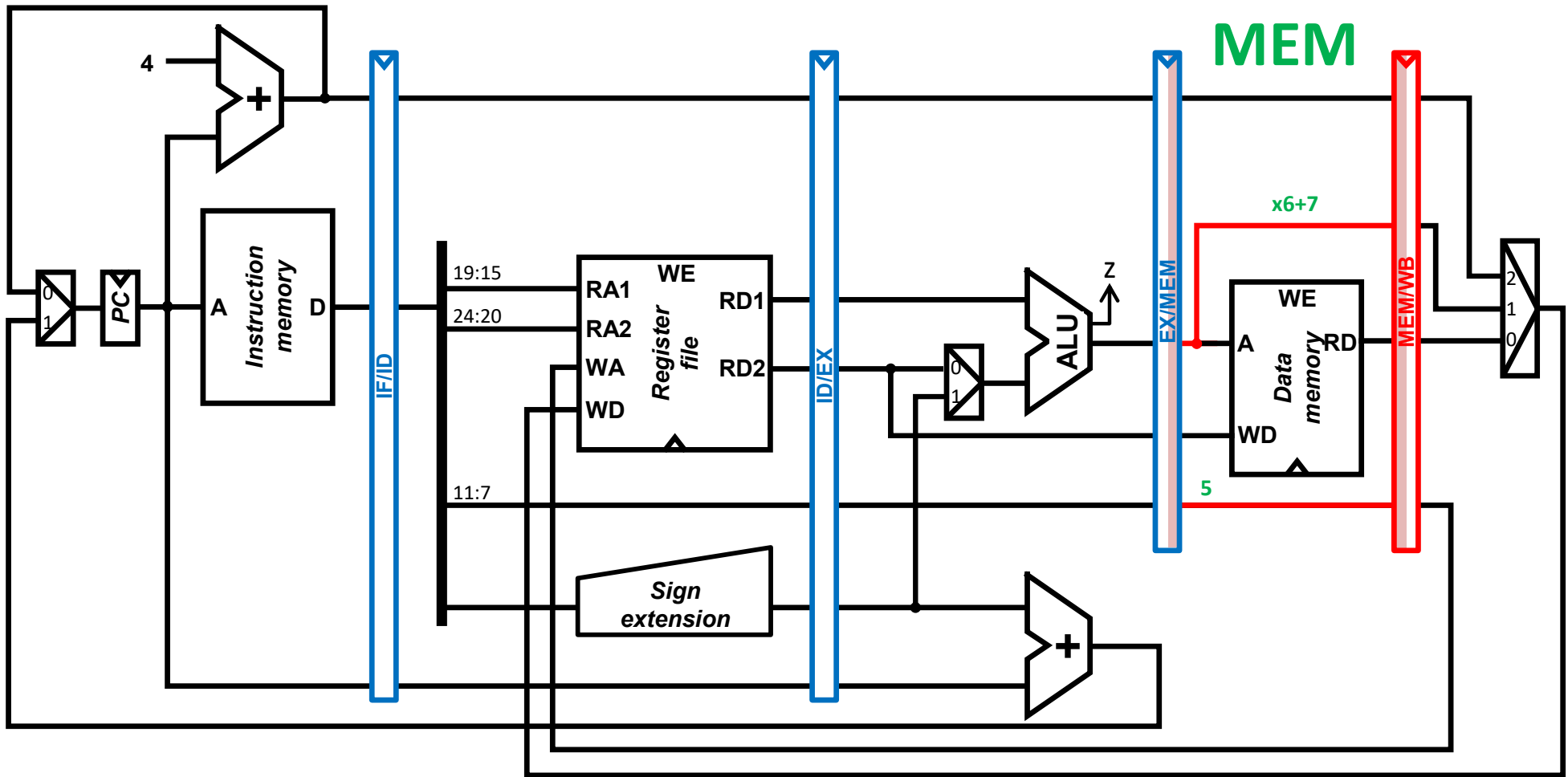 The `addi` instruction takes 5 cycles without using the memory in the MEM stage








Data path design

addi-like instruction: WB stage

  The `addi` instruction takes 5 cycles without using the memory in the MEM stage



WB


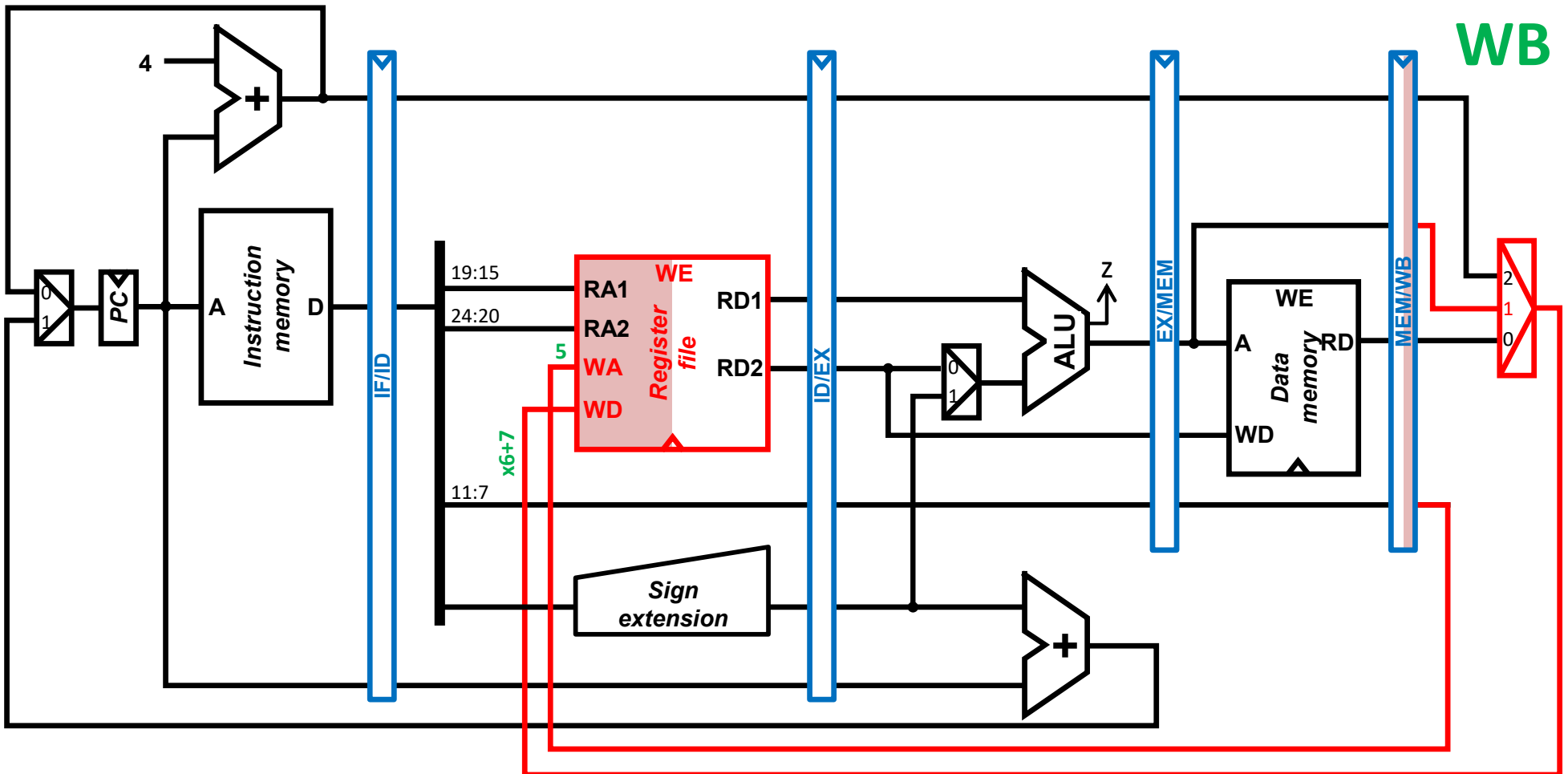




Data path design

beq instruction: ID stage

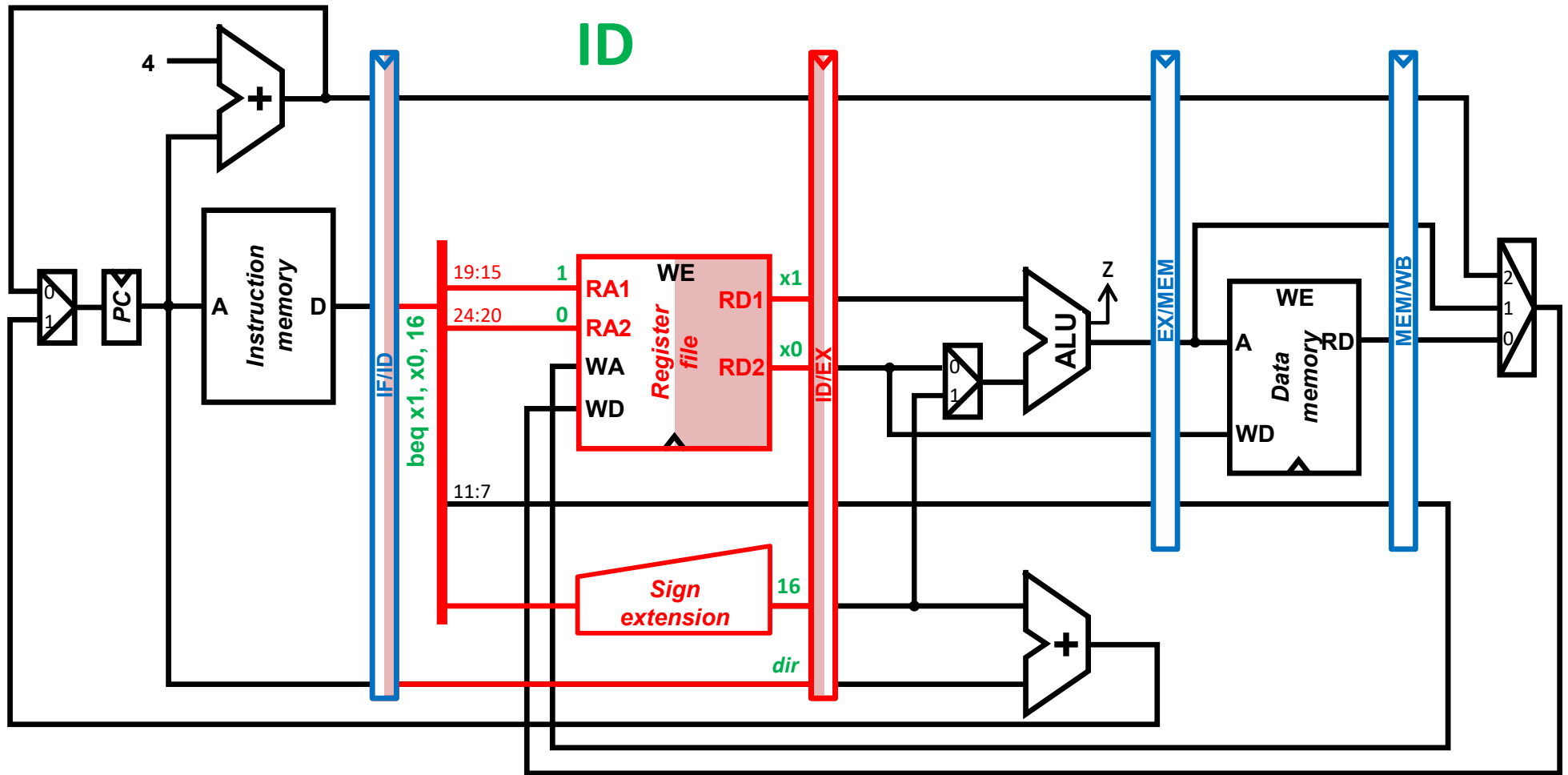 The **beq** instruction takes 5 cycles without using the memory in the MEM stage or the RF in the WB stage







Data path design

beq instruction: EX stage

 The **beq** instruction takes 5 cycles without using the memory in the MEM stage or the RF in the WB stage



beq x1, x0, 16


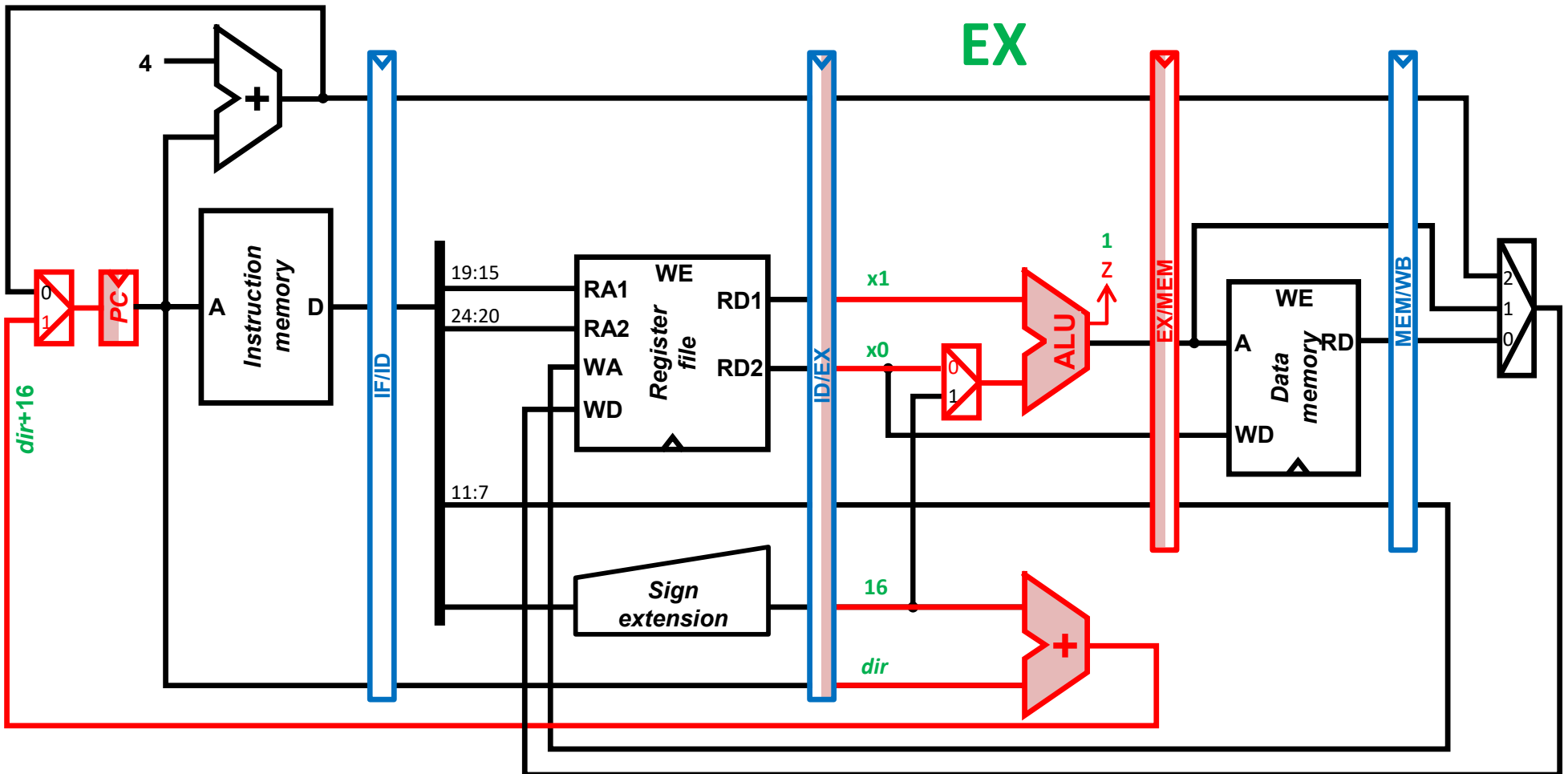




Data path design

beq instruction: MEM stage

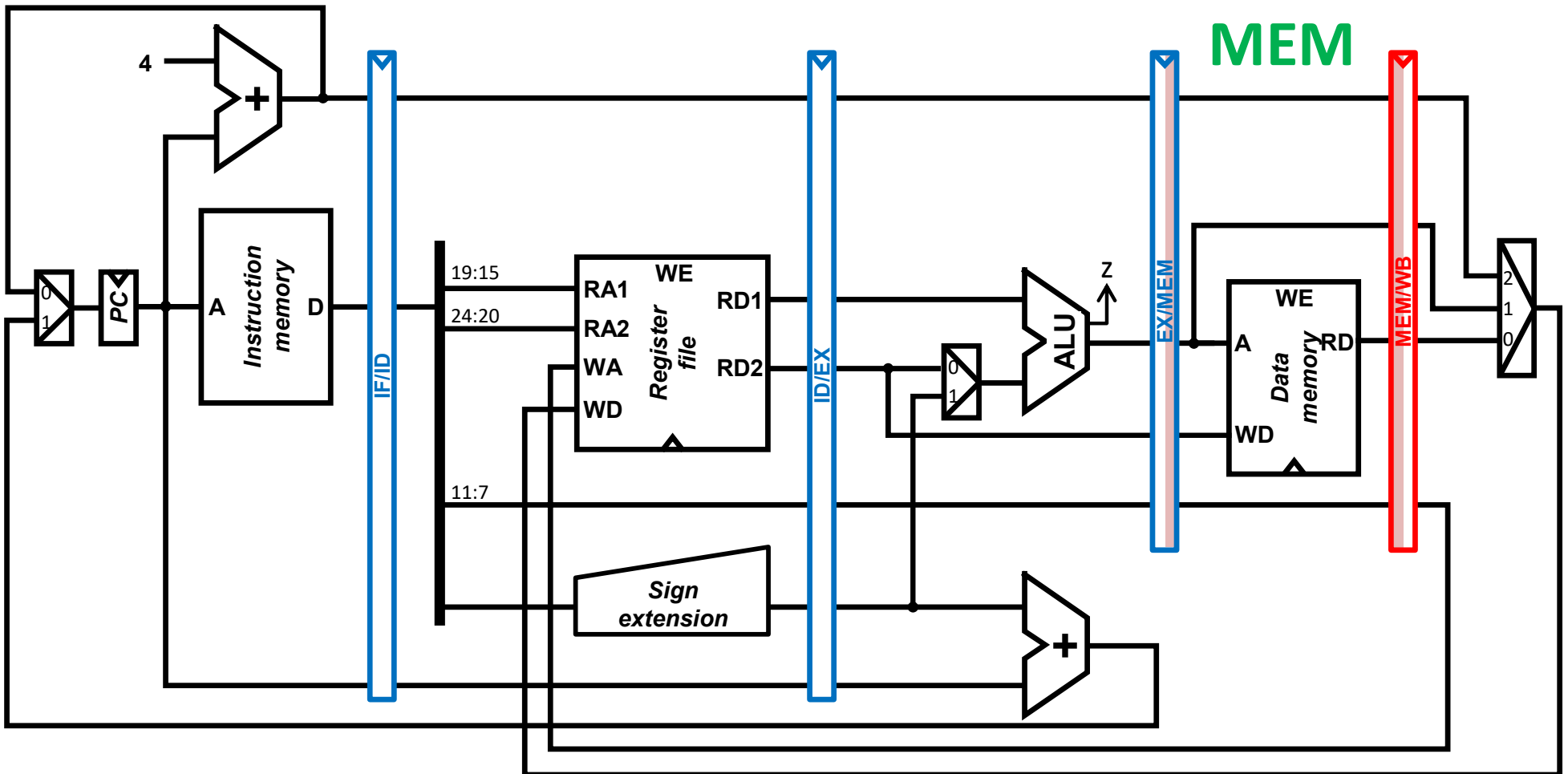 The **beq** instruction takes 5 cycles without using the memory in the MEM stage or the RF in the WB stage







Data path design

jal instruction: ID stage

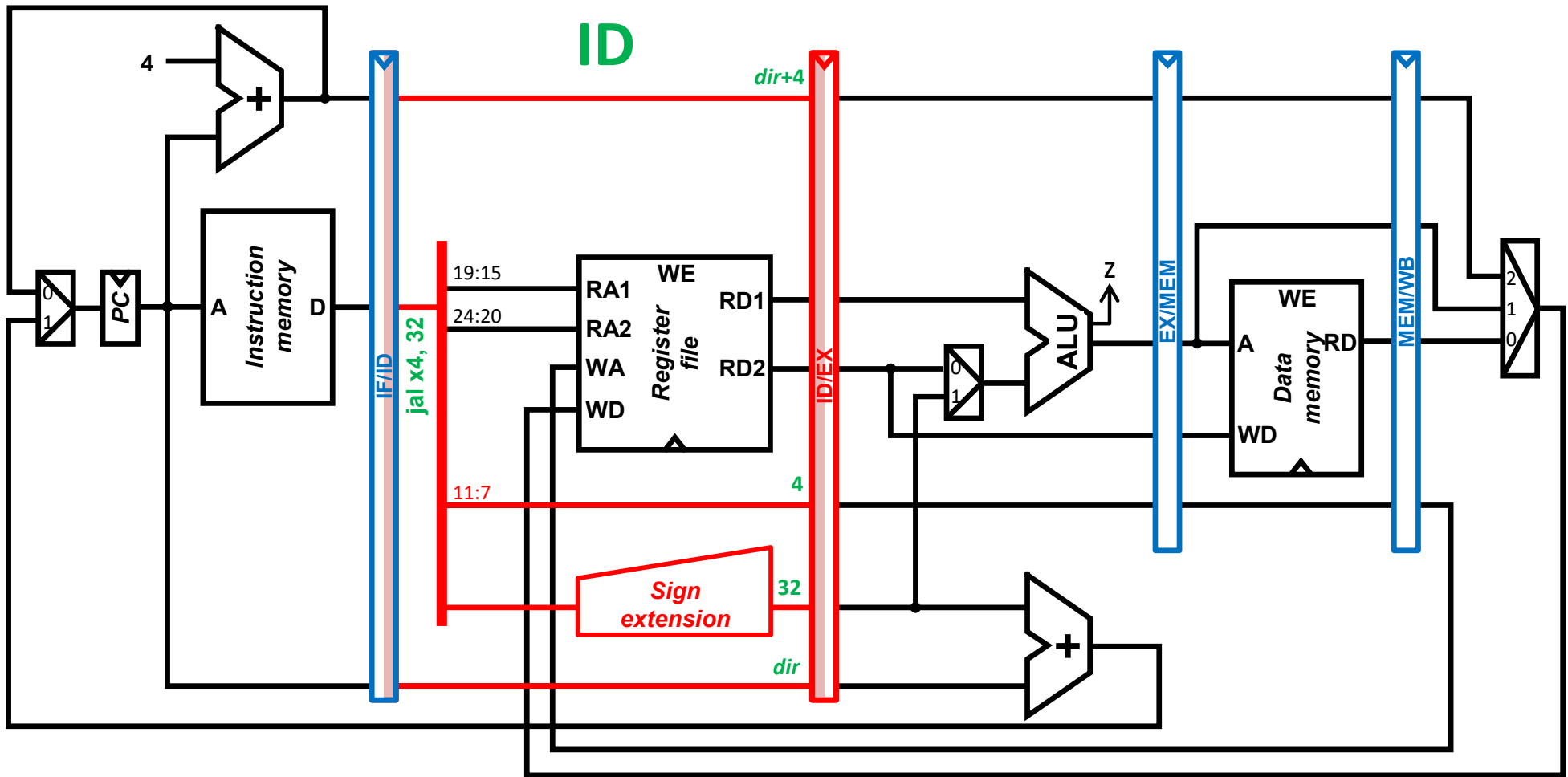 The `jal` instruction takes 5 cycles without using the RF in the ID stage, the ALU in the EX stage or the memory in the MEM stage







Data path design

jal instruction: EX stage

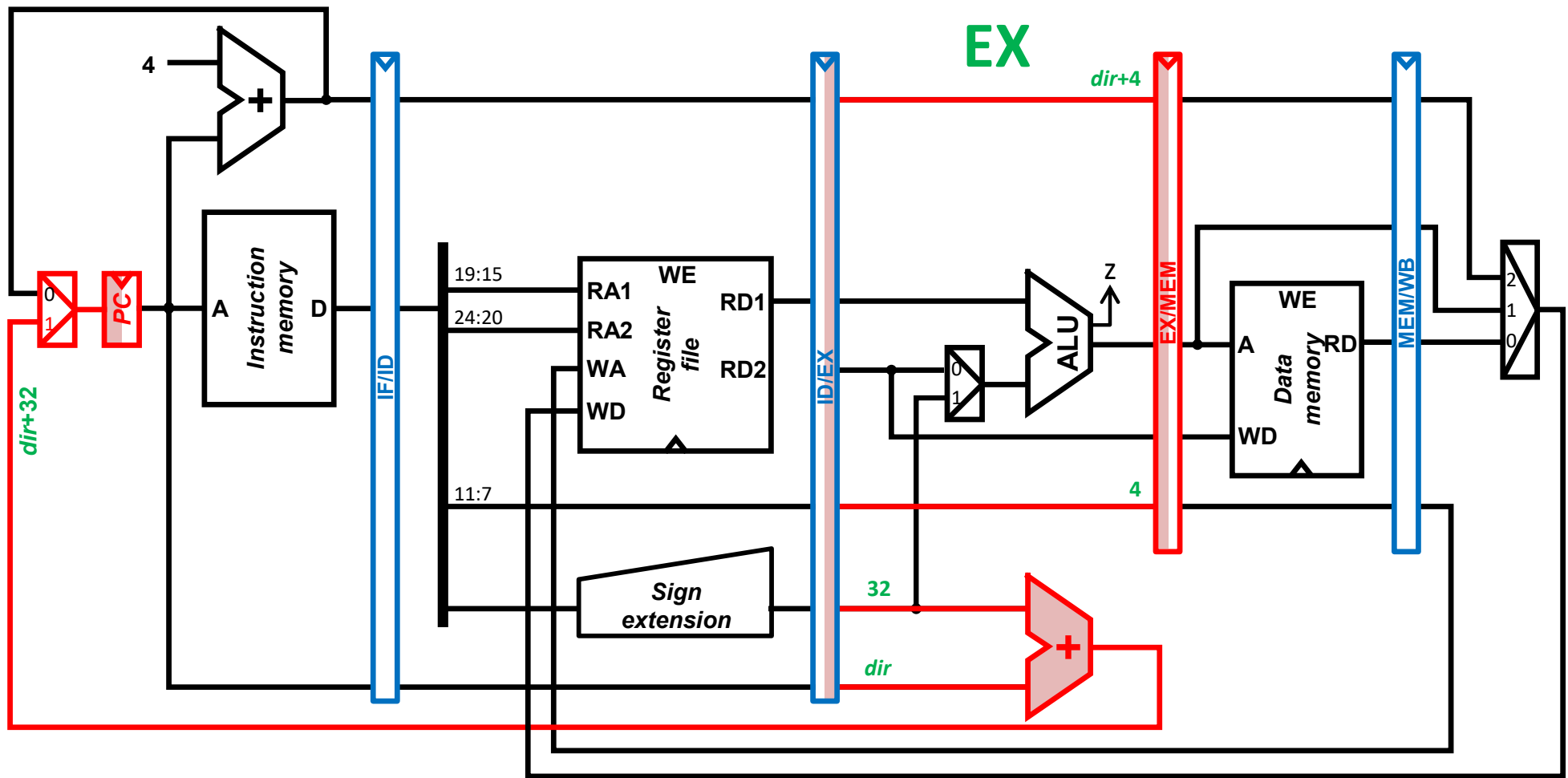 The `jal` instruction takes 5 cycles without using the RF in the ID stage, the ALU in the EX stage or the memory in the MEM stage







Data path design

jal instruction: MEM stage

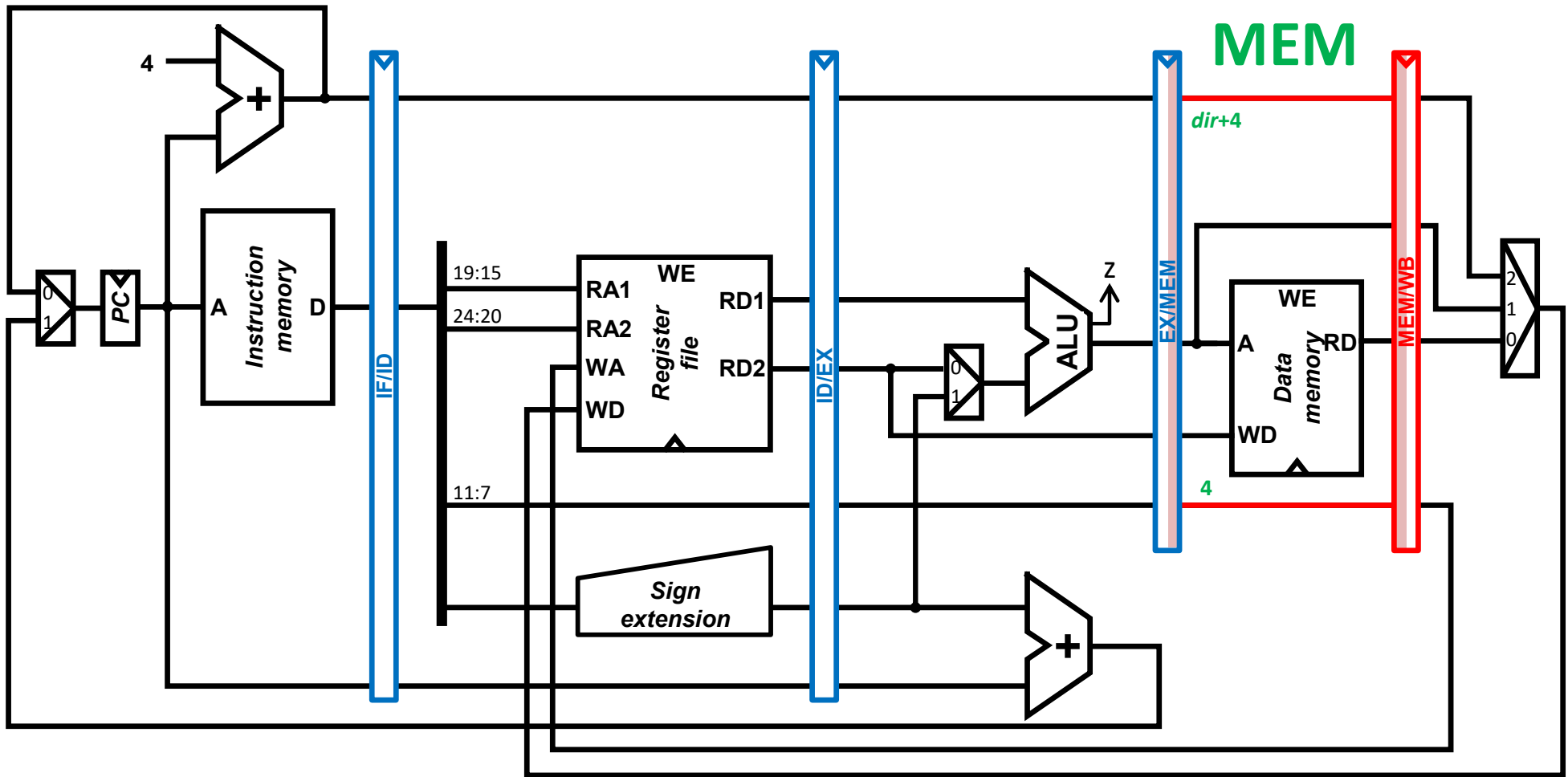 The jal instruction takes 5 cycles without using the RF in the ID stage, the ALU in the EX stage or the memory in the MEM stage







Data path design

jal instruction: WB stage

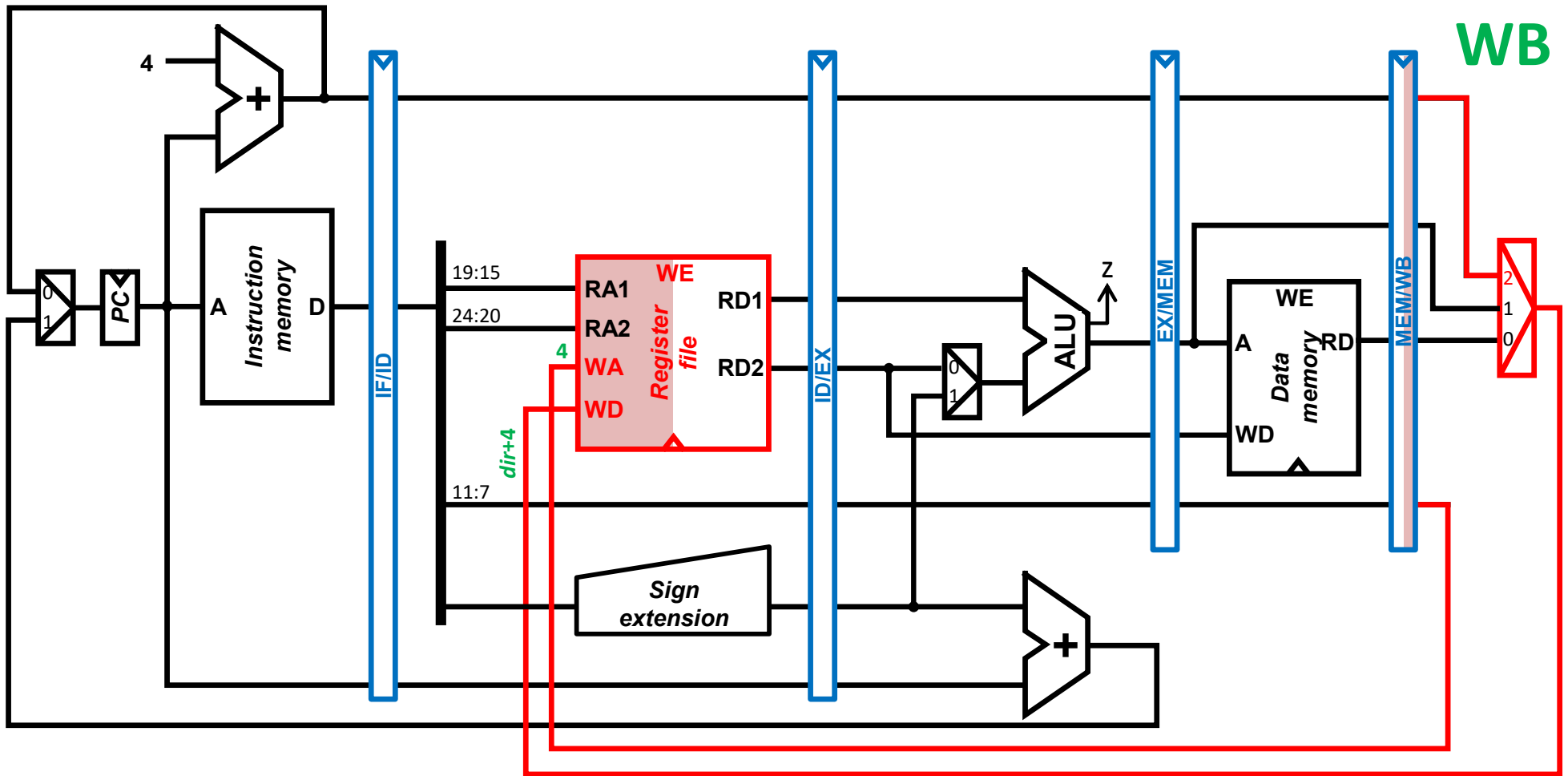 The `jal` instruction takes 5 cycles without using the RF in the ID stage, the ALU in the EX stage or the memory in the MEM stage






Data path design

Execution diagrams (i)

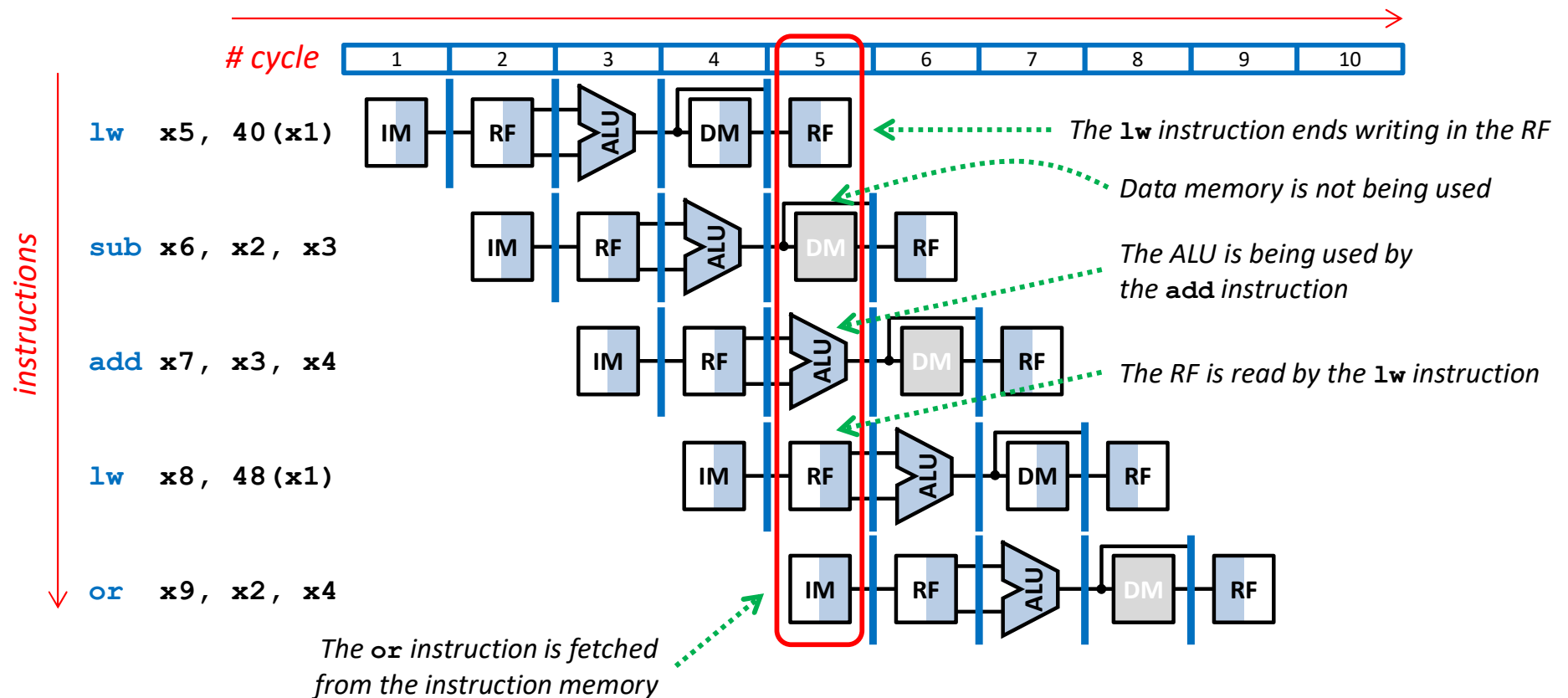- An **execution diagram** allows visualizing the execution of a program in the pipeline:
 - For a **given cycle**, it visualizes the **instructions in execution**, in which **pipeline stage** each of them is and the **resources** that are used.






Data path design

Execution diagrams (ii)

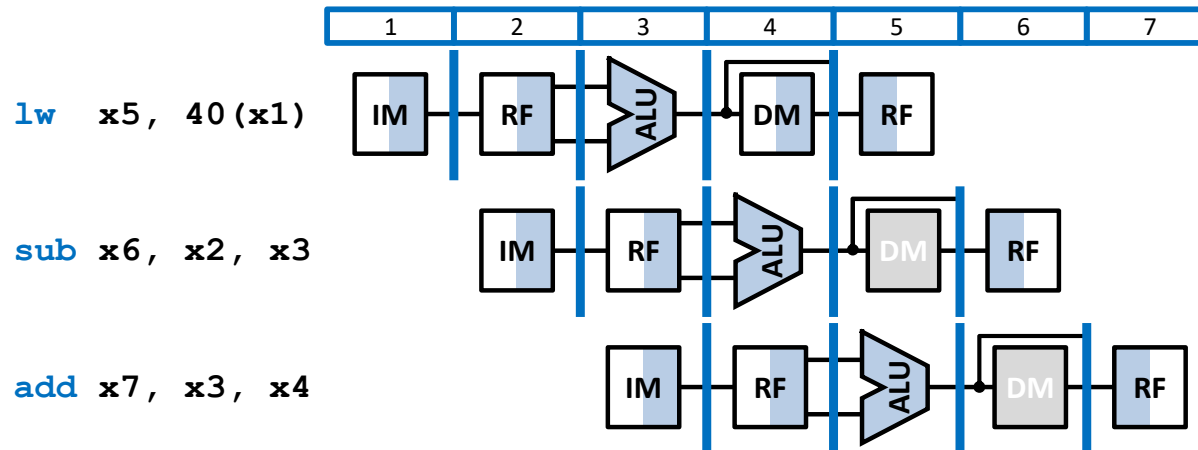- Alternatively, it is common to use **simplified execution diagrams** that show, in each **cycle**, the **stage** in which each instruction is.




	1	2	3	4	5	6	7
<code>lw x5, 40(x1)</code>	IF	ID	EX	M	WB		
<code>sub x6, x2, x3</code>		IF	ID	EX	M	WB	
<code>add x7, x3, x4</code>			IF	ID	EX	M	WB



Data path design

Simulation: 1st. cycle


lw x5, 40(x1)

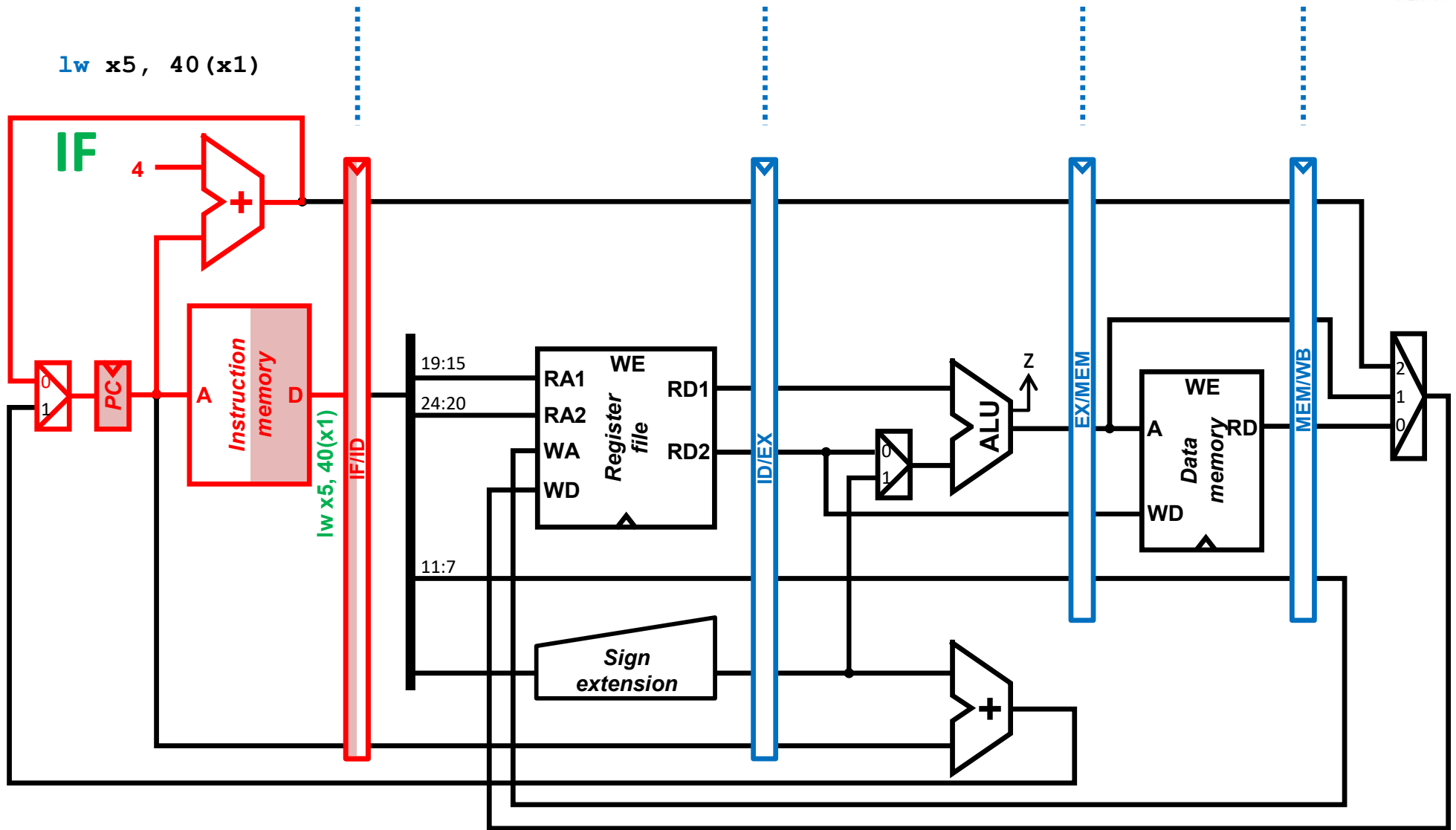



Data path design


Simulation: 2nd. cycle

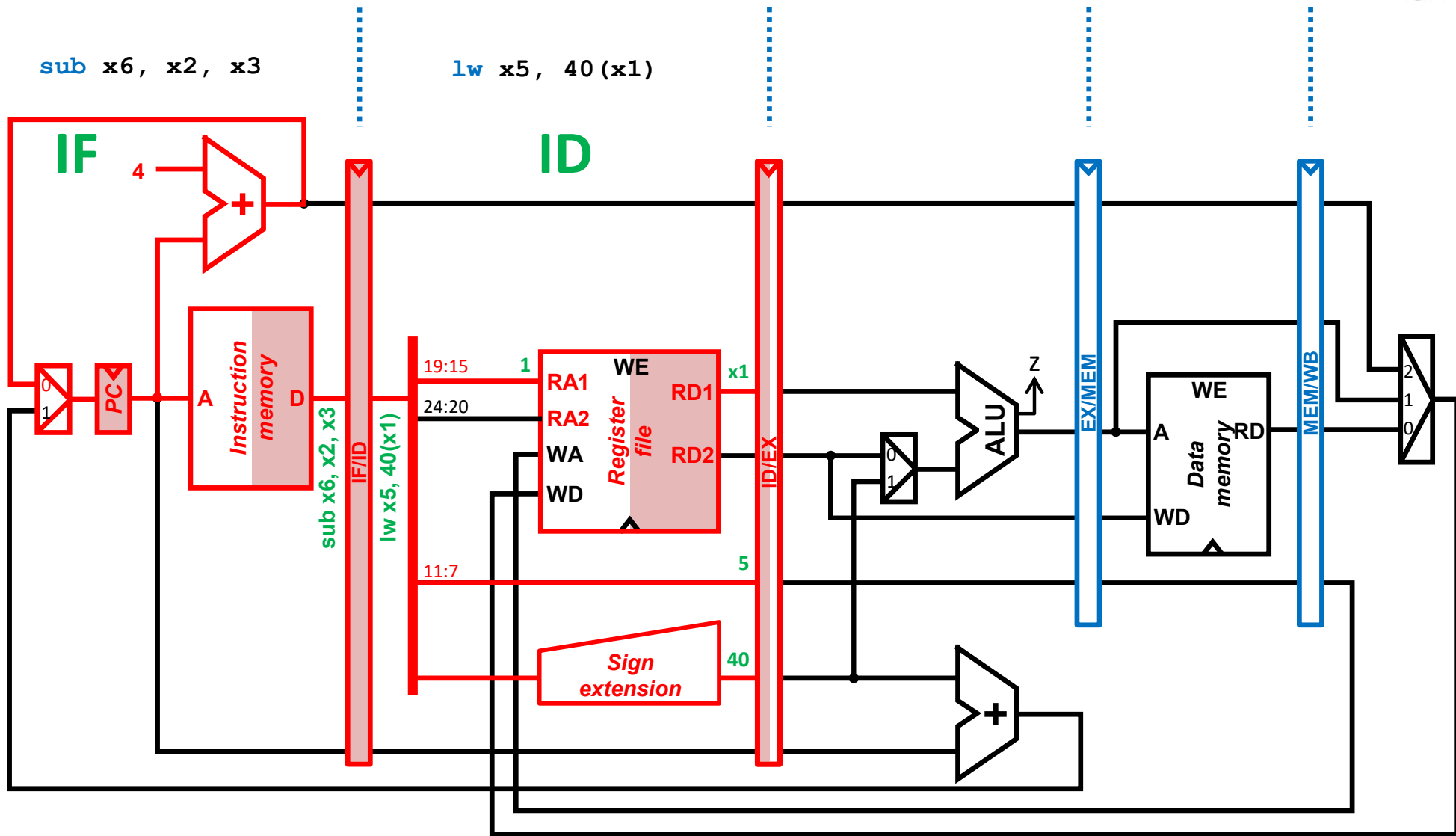



Data path design


Simulation: 3rd. cycle

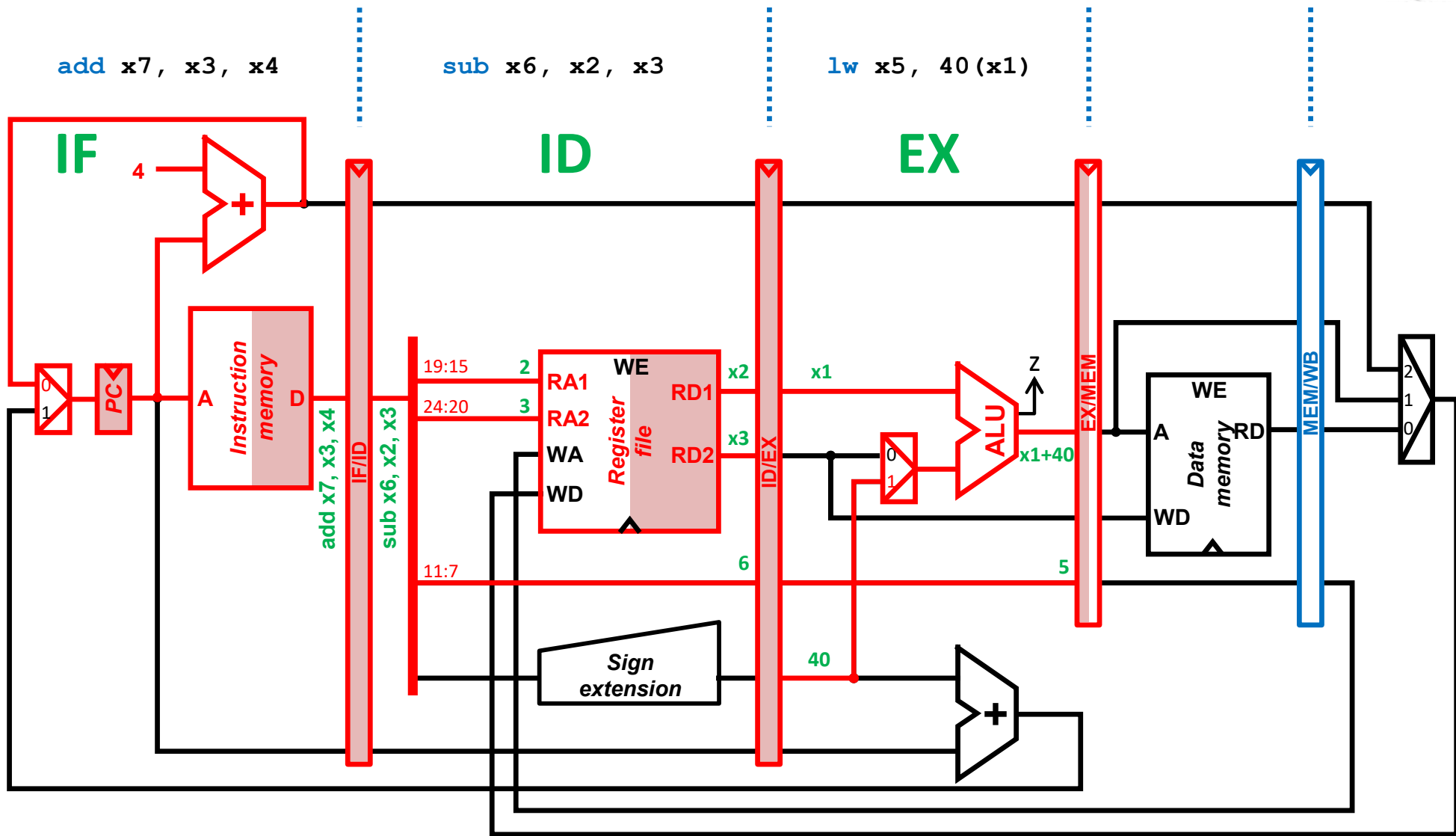



Data path design


Simulation: 4th. cycle

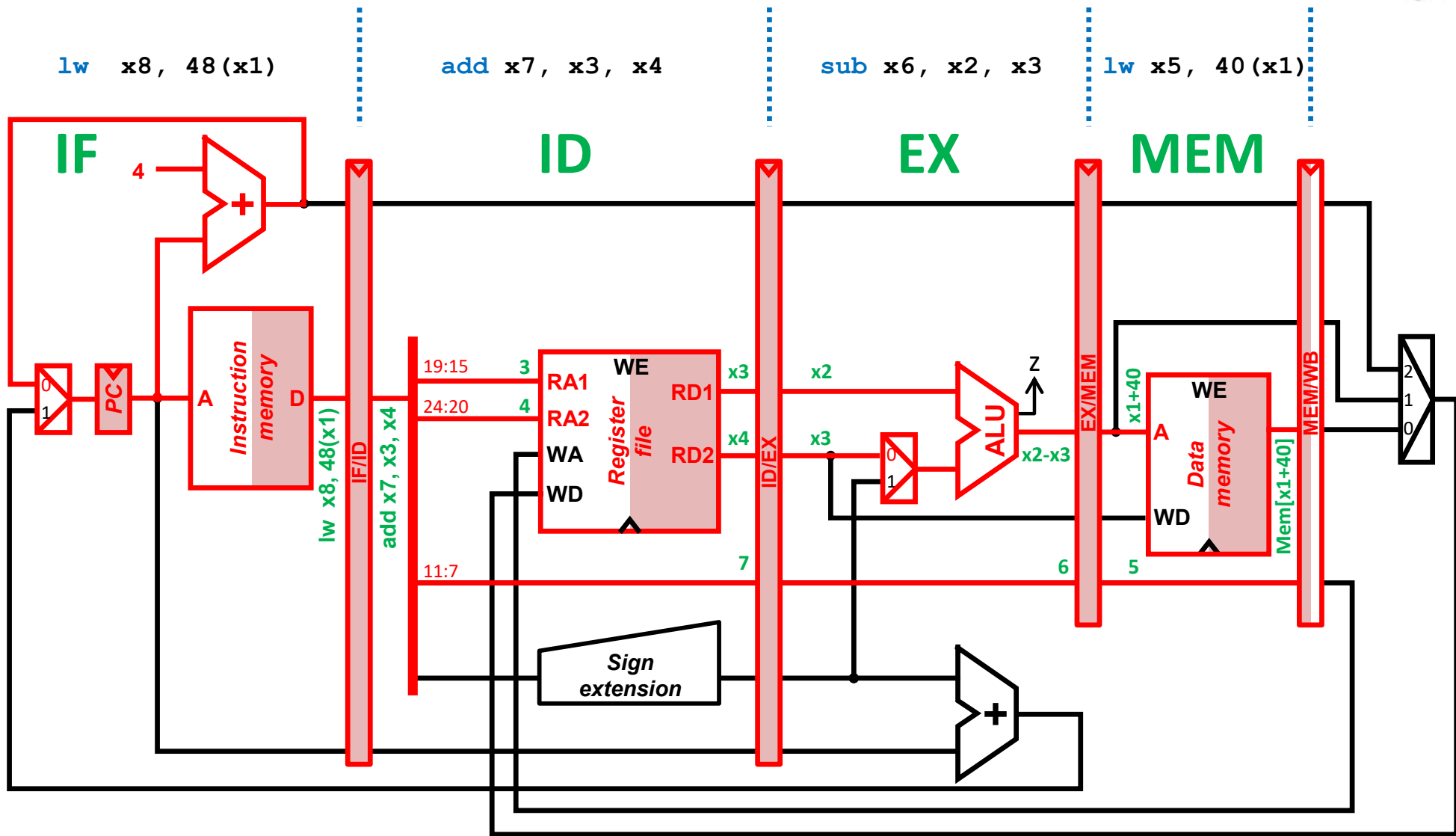



Data path design


Simulation: 5th. cycle

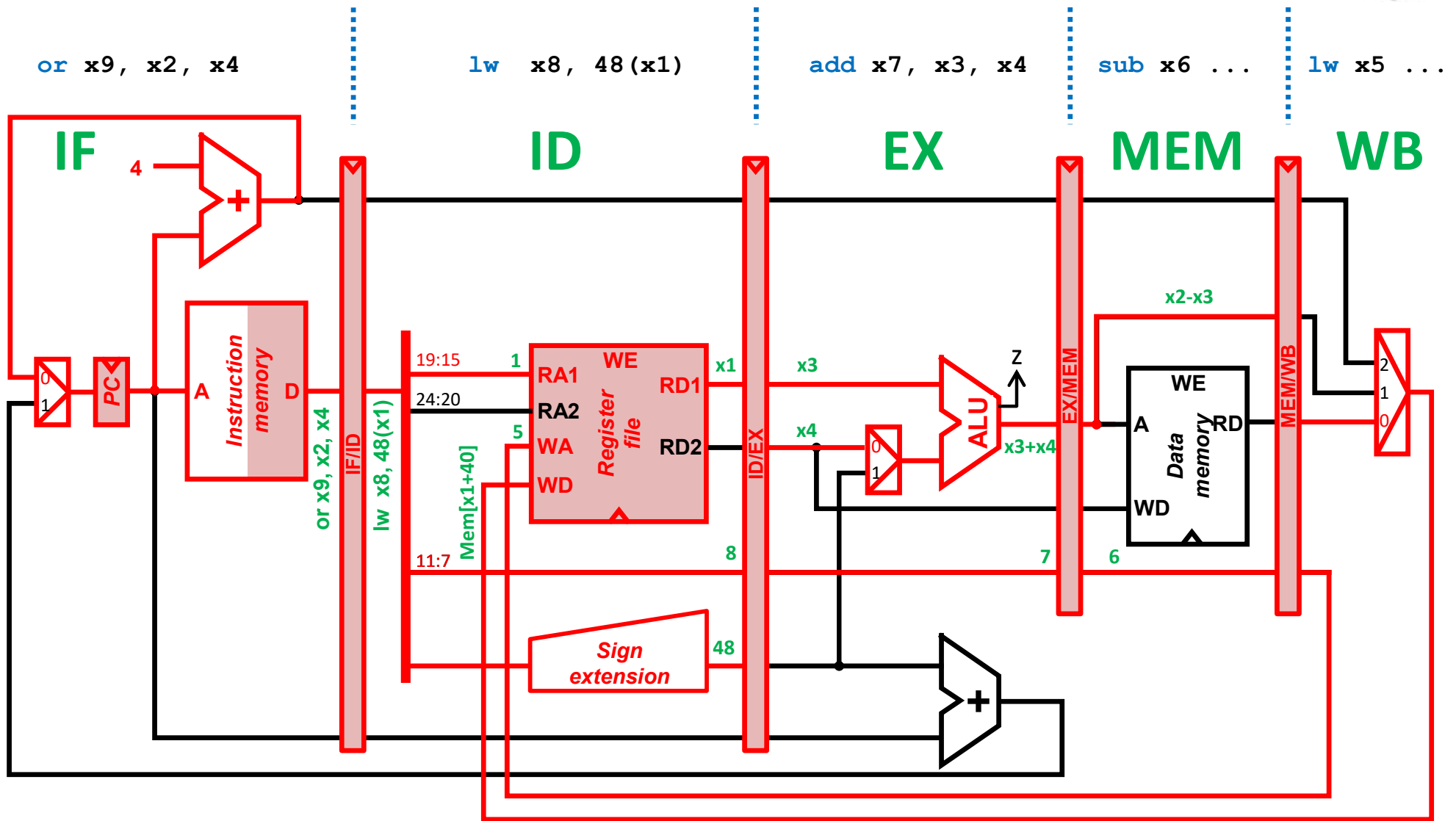



Data path design


Control signals

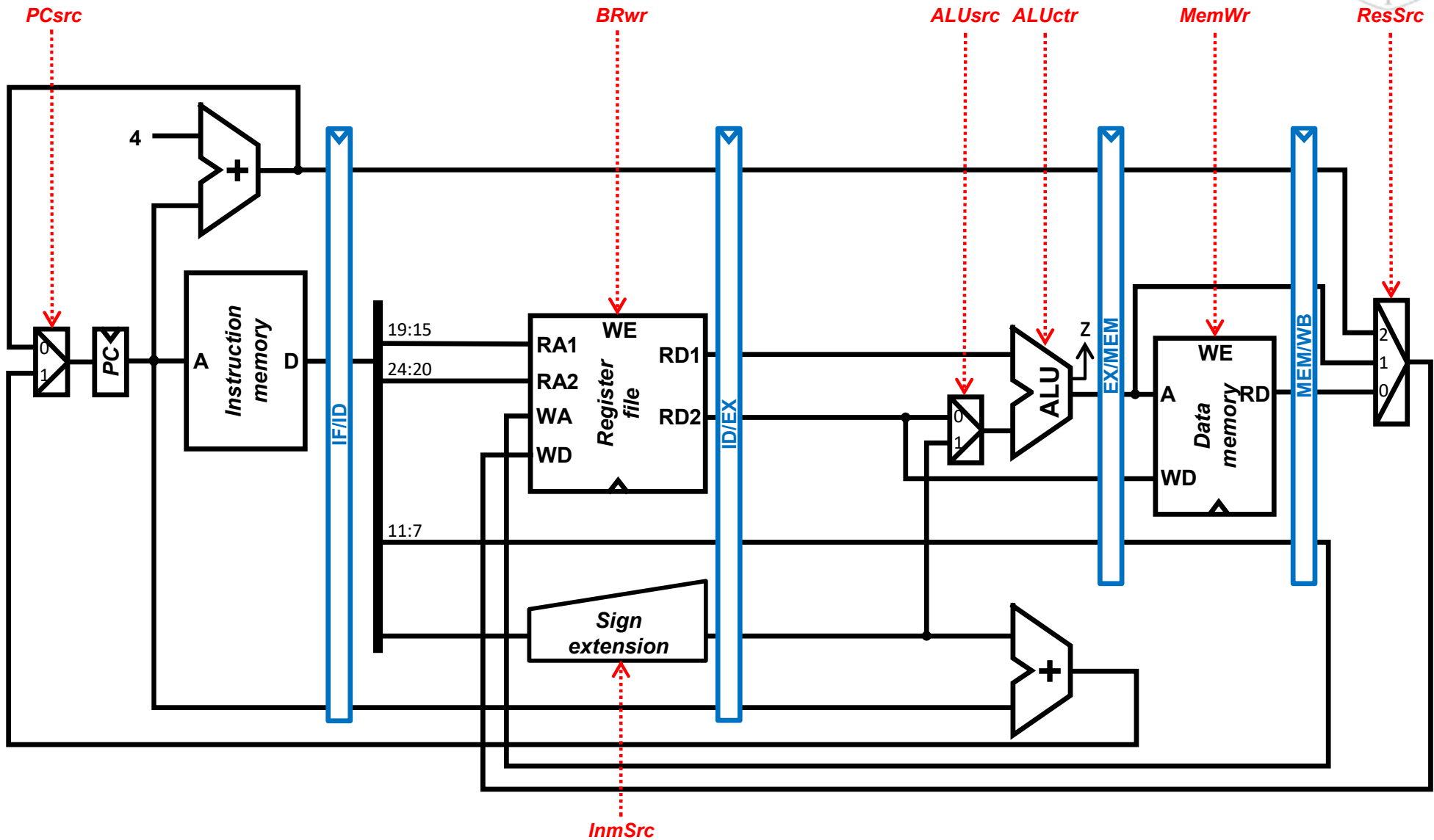



Data path design

Control signals

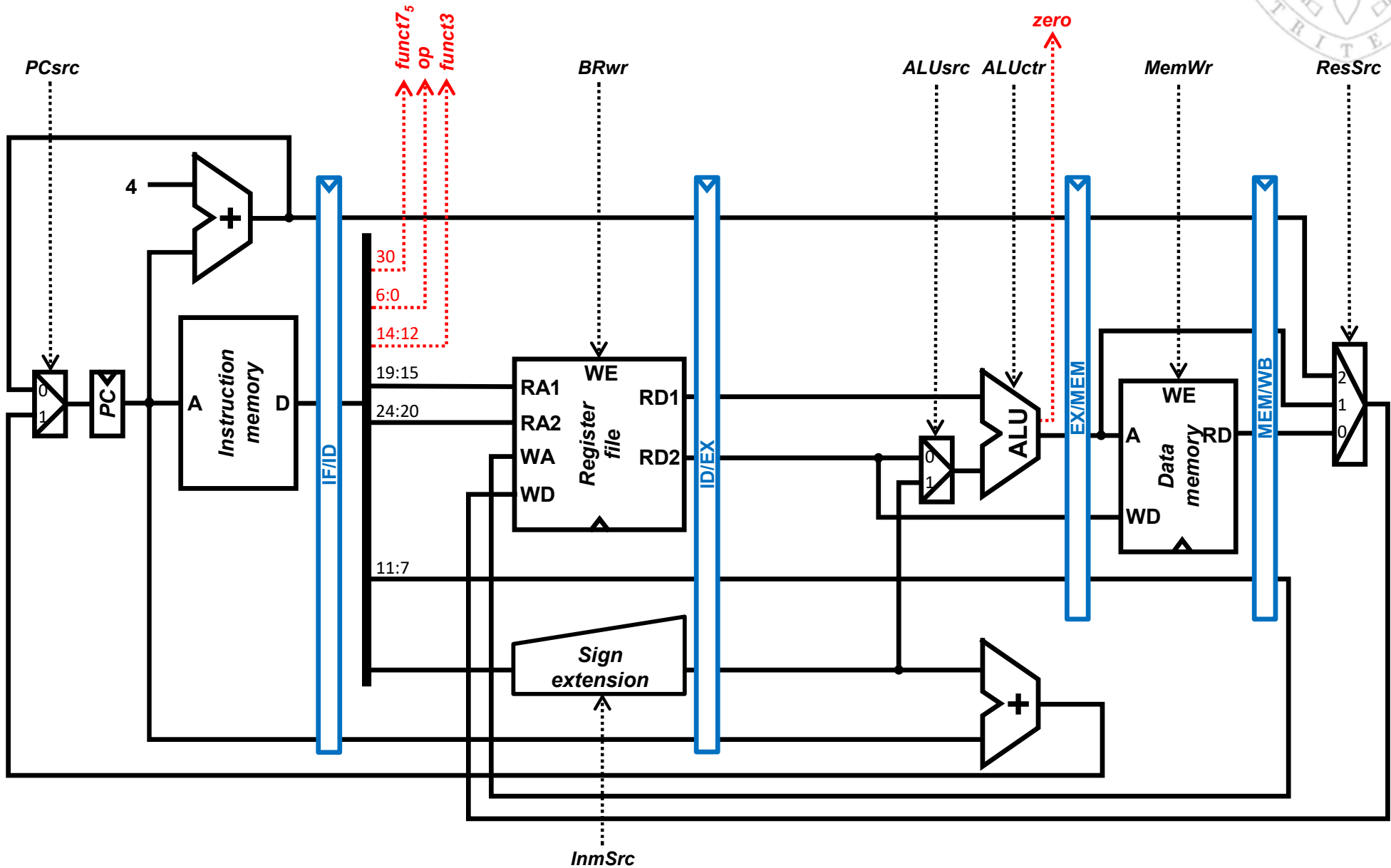



Controller design


Connection with the controller

27/10/23 version

module 7:
Pipelined processor design

FC-2

50

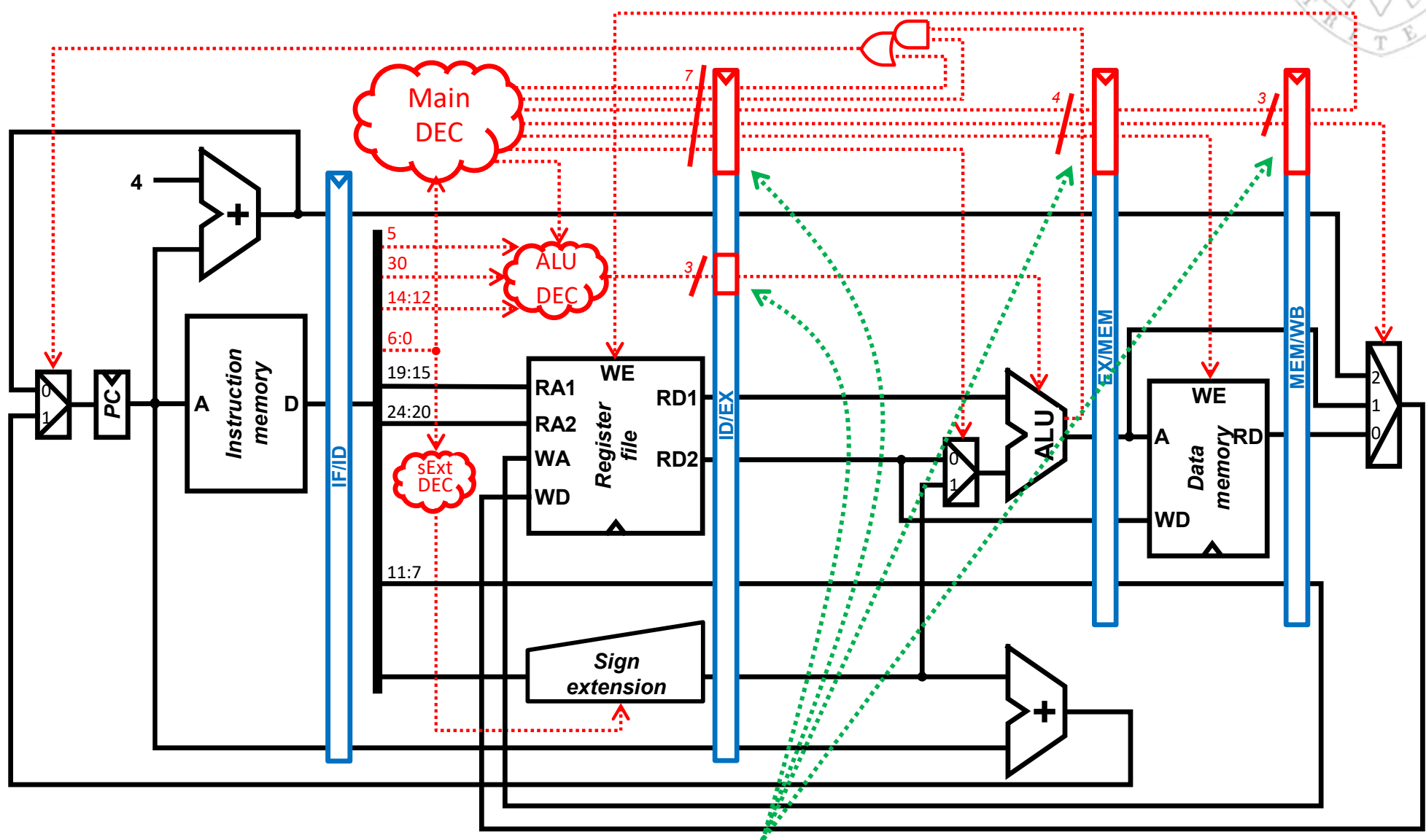


Pipeline registers are extended to transmit the control signals that are needed through the stages



Pipelined processor


Connection of the clock and the reset

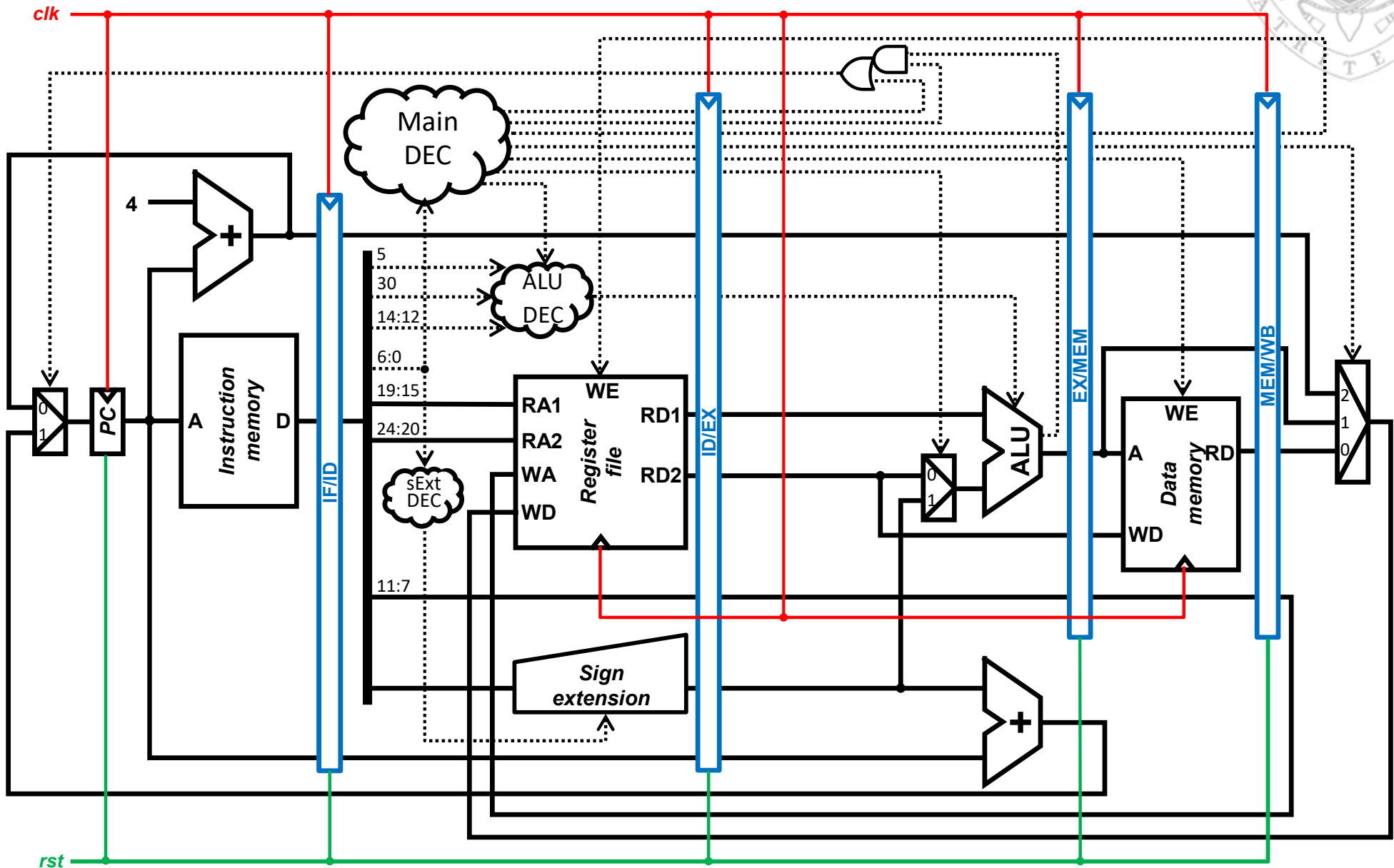



Pipelined processor

Full system structure

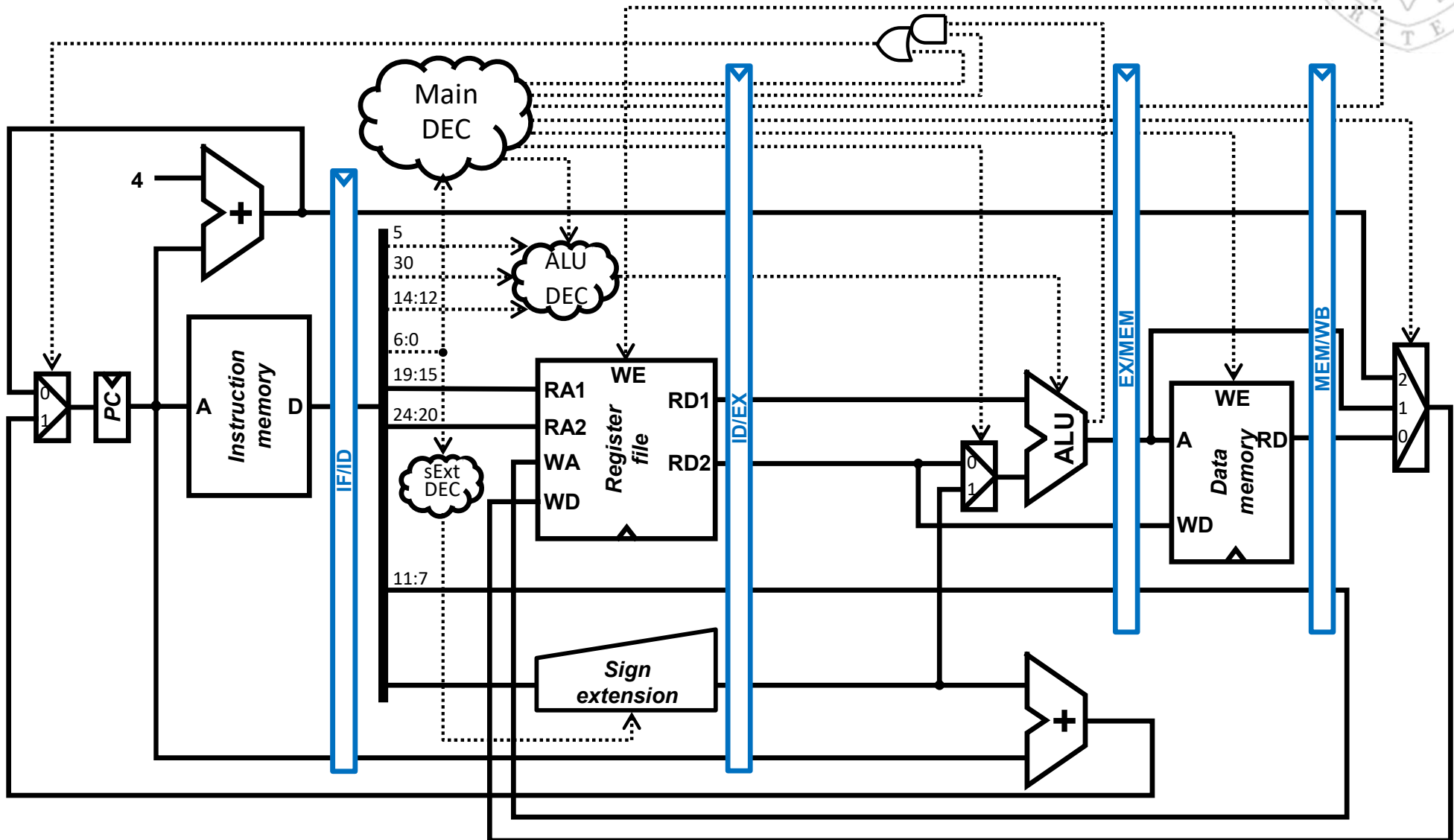

Hazards




- In a **pipelined processor**, **hazards** may appear between the instructions that are executed simultaneously.
 - These never happen in the **single-cycle and multicycle processors** because in those cases each instruction is executed after the previous one has ended.
- **Types of hazards:**
 - **Structural**: an instruction **needs a hardware resource** that **is being used** by a previous instruction.
 - **Data**: an instruction **must read a data** from a register that **has not been written yet** by a previous instruction.
 - **Control**: the **next instruction** must be **fetches** from memory, but its address **has not been decided/calculated yet** by a previous branch instruction.



Structural hazards


- This pipelined processor **does not have structural hazards** because:
 - There are no shared resources.
 - The PC can be incremented (IF stage), the effective address calculated (EX stage) and the branch condition checked (EX stage) simultaneously.
 - Memory is split in two.
 - Instructions (IF stage) and data (MEM stage) can be read simultaneously.
 - The register file has a triple port.
 - 2 registers can be read (ID stage) and 1 written (WB stage) simultaneously.
 - All instructions go through the 5 stages.
 - Adding inactive stages when needed to avoid hazards.

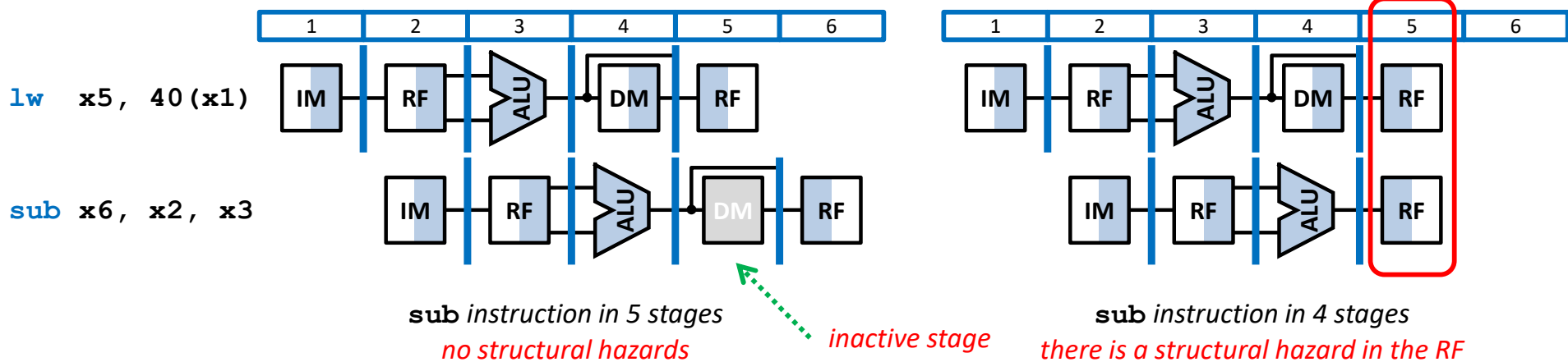



Data hazards

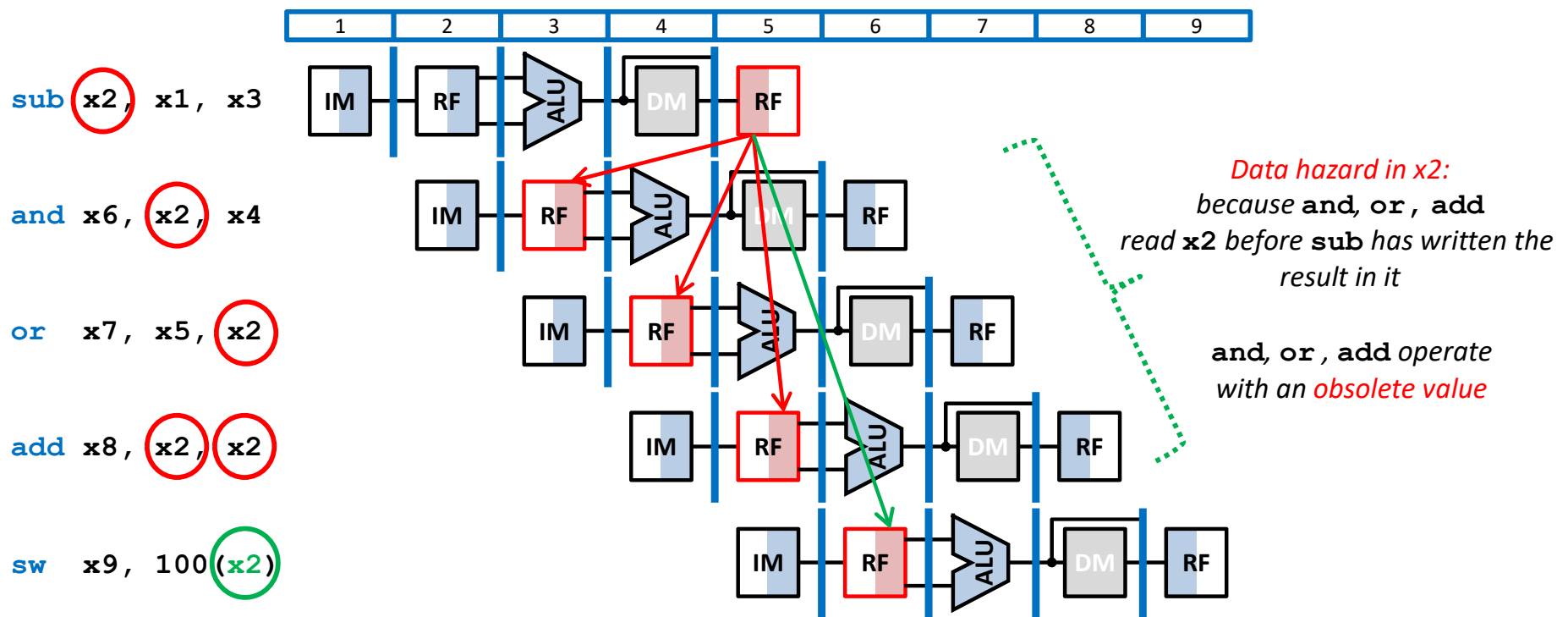- This pipelined processor has data hazards when executing an instruction that needs to read a register written by any of the 3 previous instructions.




*No data hazards in x2:
The value of x2 calculated by the sub instruction
has been already written in the register file*



Control hazards

- This pipelined processor **has control hazards** when executing branch instructions, because the next instruction must be fetched:
 - Before deciding if the branch is taken or not (**beq** instruction)
 - Before having calculated the destination address, in the case the branch is taken (**beq** and **jal** instructions)
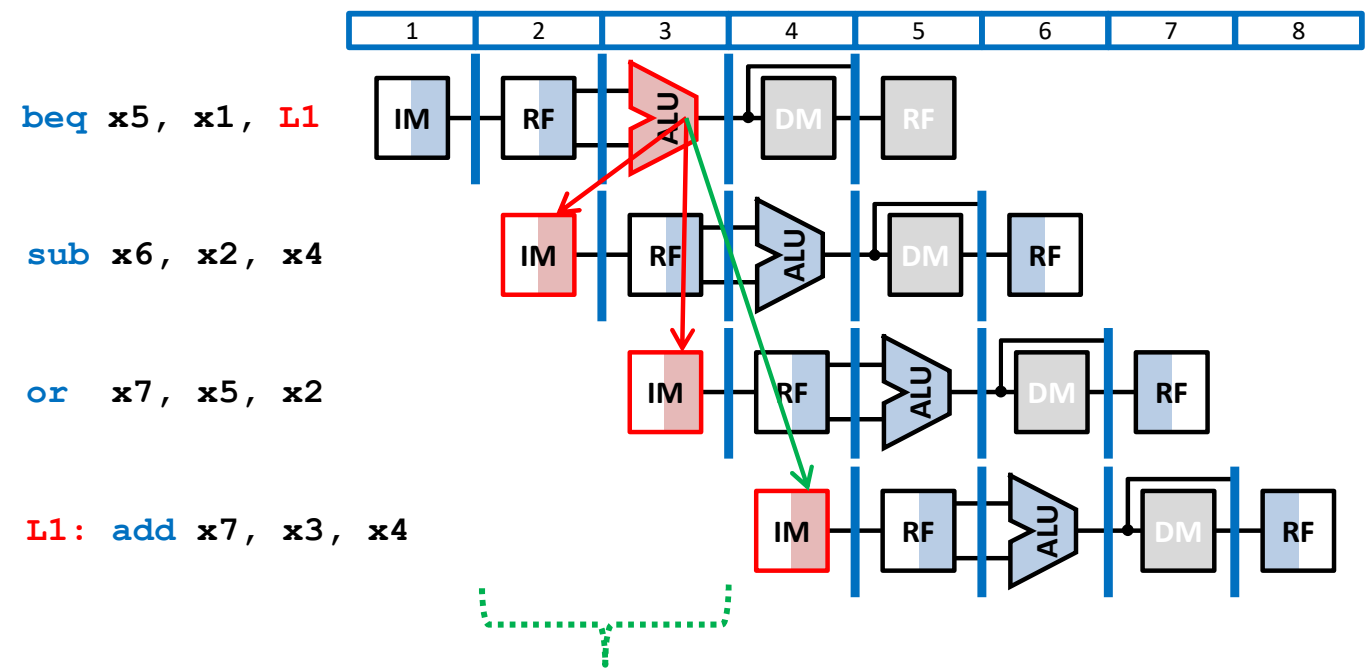
```
...  
beq x5, x1, L1  
sub x6, x2, x4  
or x7, x5, x2  
...  
L1:  
add x7, x3, x4  
...
```




There is a control hazard because instructions are fetched before **beq** decides if the branch is taken or not



Data hazards

SW solution: inserting nop (i)

 - They can be solved by software, inserting 1, 2 or 3 **nop** instructions between the instruction that writes the register and the one that reads it.






Control hazards

SW solution: inserting nop (ii)

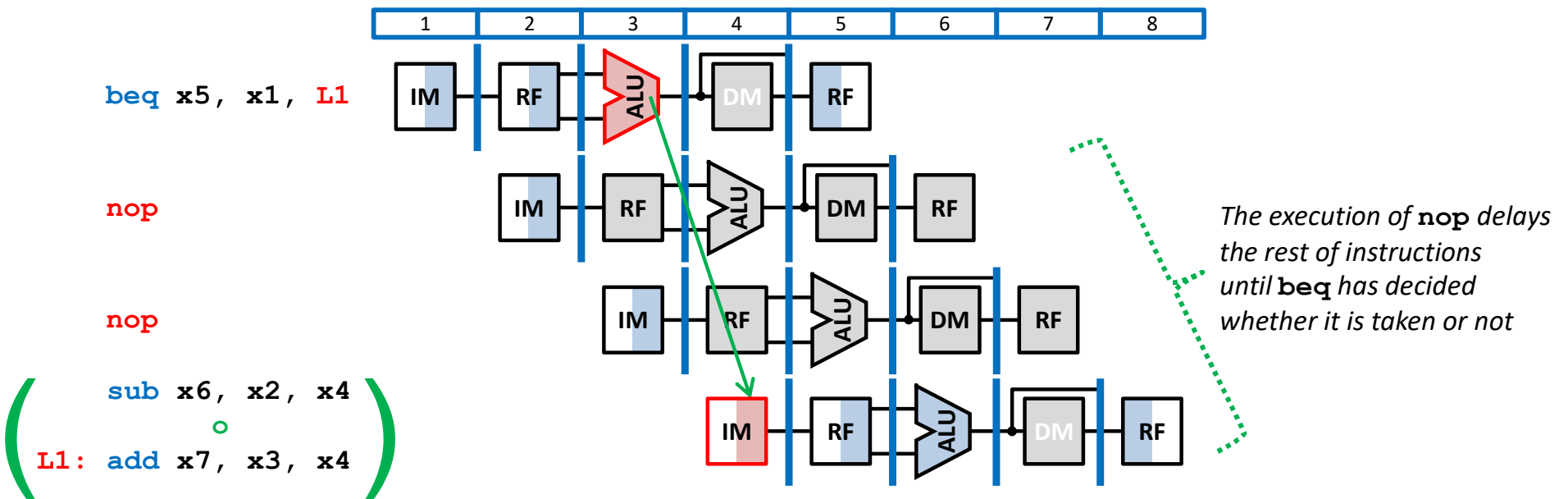- They can be solved by software, inserting **2 nop instructions** after each branch instruction.






Data and control hazards

SW solution: inserting nop (iii)

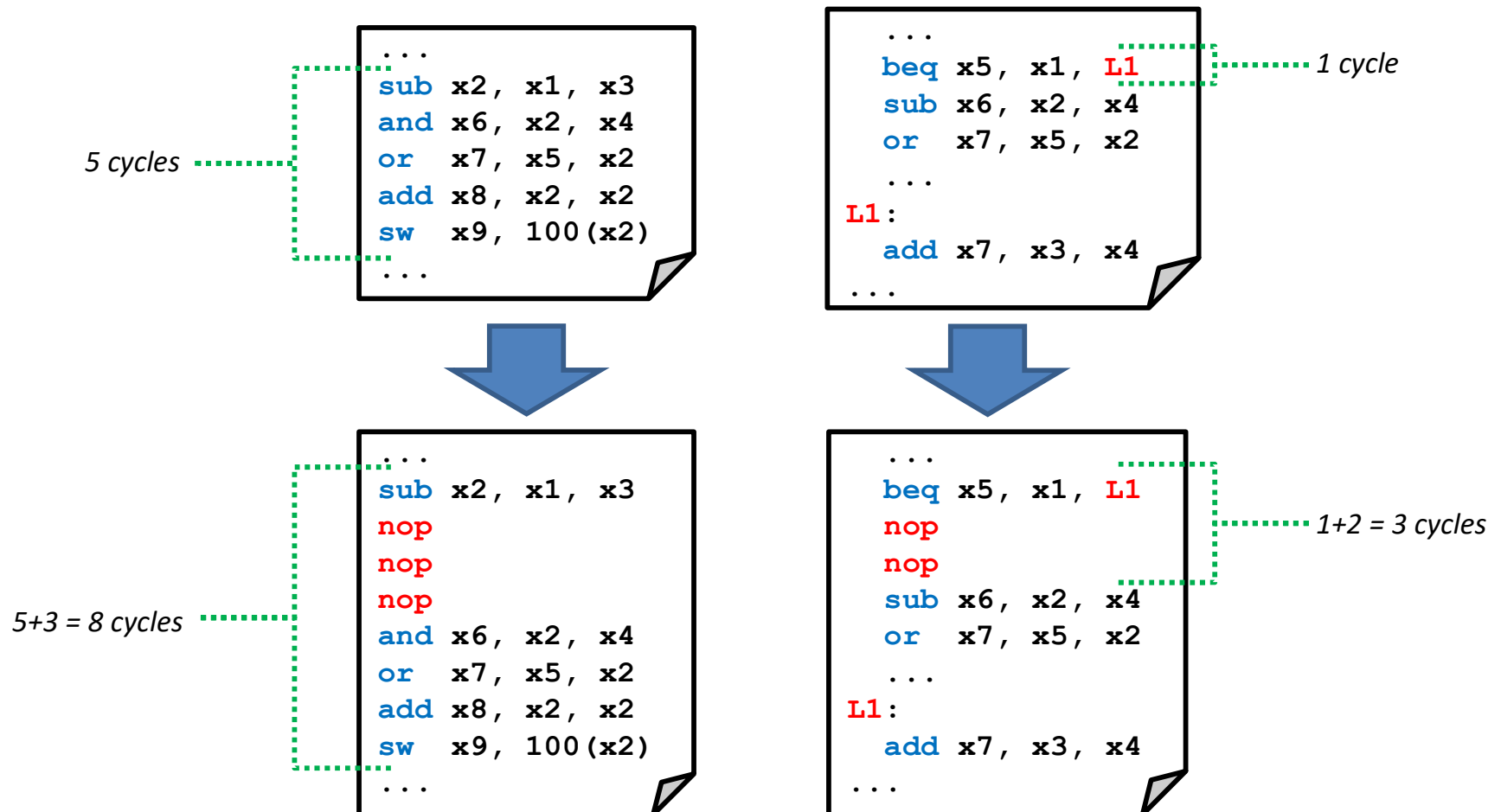- The software solution has **important disadvantages**:
 - It makes programming harder because it requires inserting `nop` instructions.
 - The execution of each `nop` increases the execution time in 1 cycle.






Data hazards

HW solution: forwarding (i)

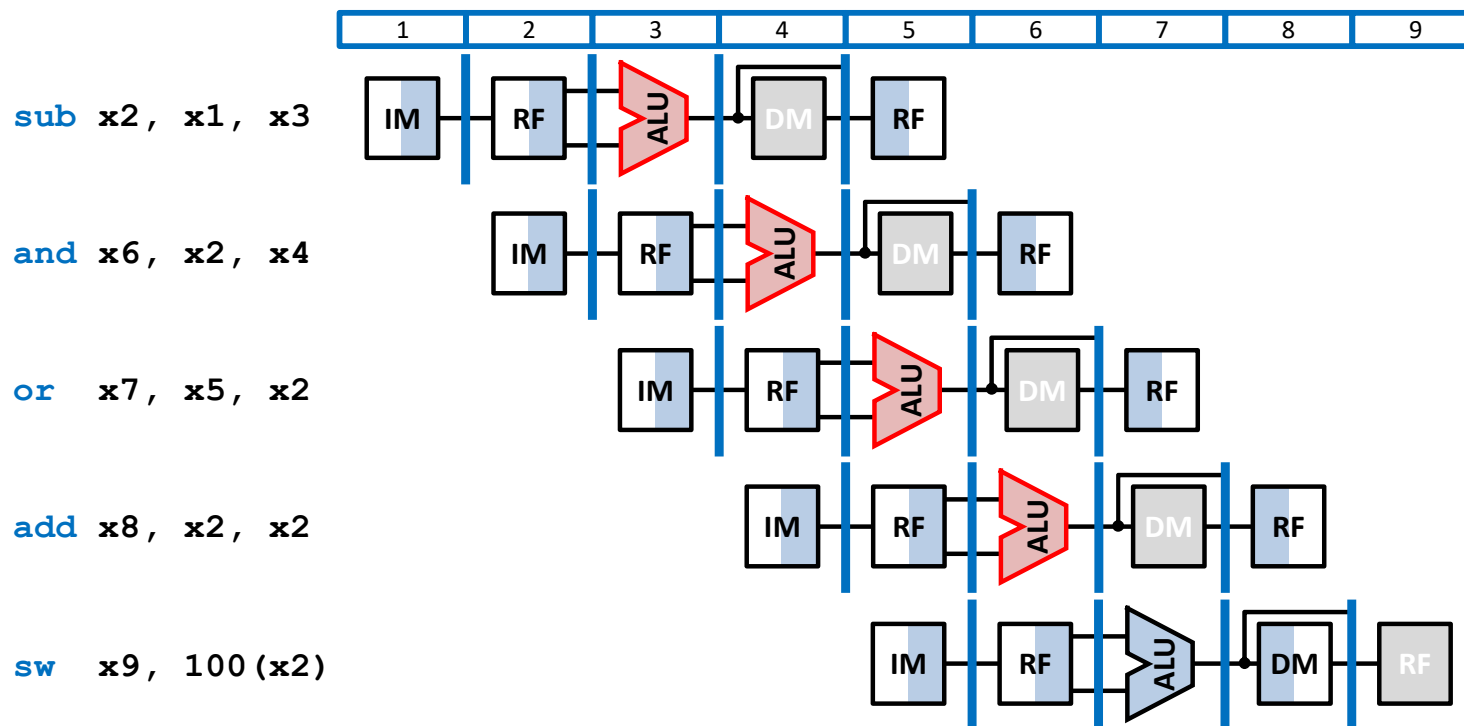- There is a **hardware solution** that **avoids this overhead** given that:
 - The `sub` instruction uses the ALU in cycle 3 to calculate the subtraction.
 - The following instructions need the data in cycles 4, 5 and 6.
 - The data is available since cycle 4**, and therefore **it can be forwarded** without waiting to read it from the RF.






Data hazards

HW solution: forwarding (ii)

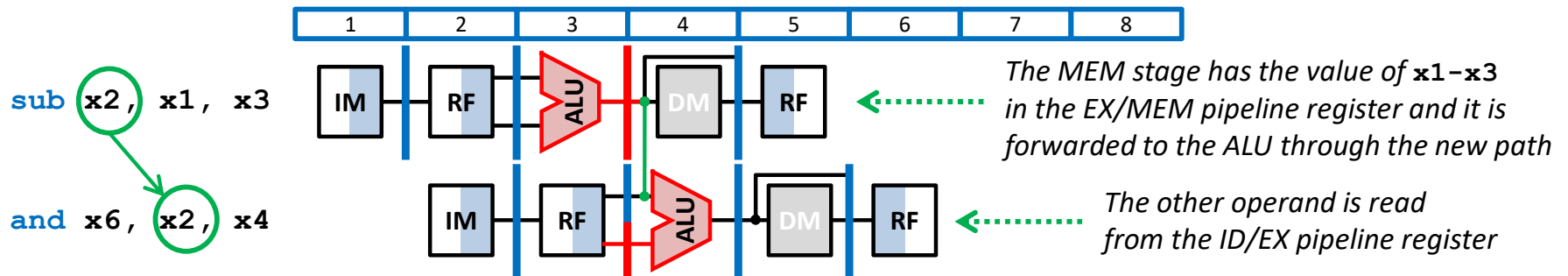- Each hazard is solved in a different way:
 - sub - and**: signal paths are added to forward the data from the MEM stage to each of the ALU inputs (EX stage)






Data hazards

HW solution: forwarding (ii)

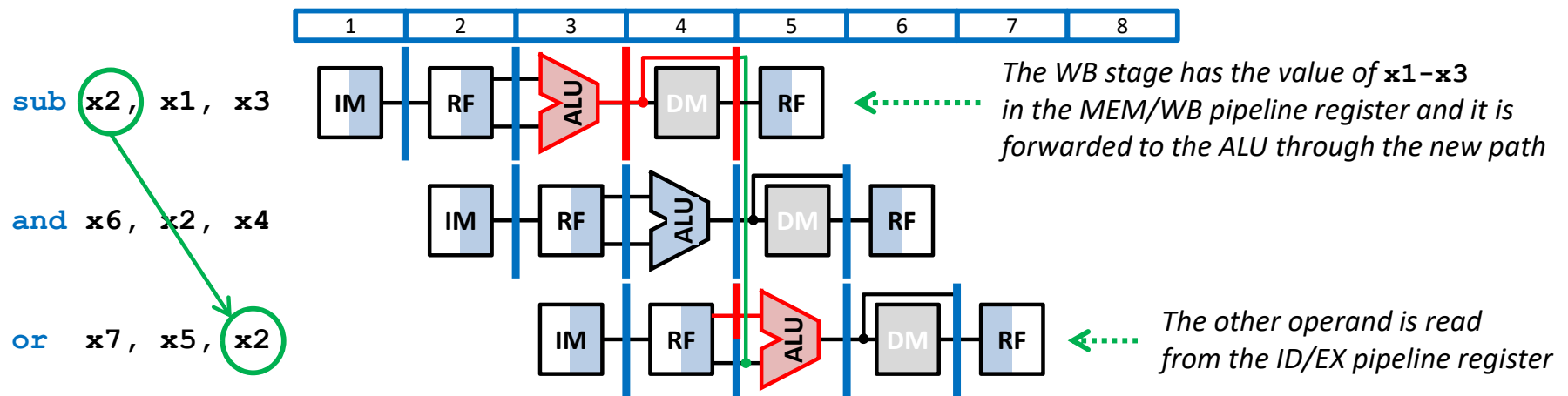- Each hazard is solved in a different way:
 - sub - and**: signal paths are added to forward the data from the MEM stage to each of the ALU inputs (EX stage)
 - sub - or**: signal paths are added to forward the data from the WB stage to each of the ALU inputs (EX stage)






Data hazards

HW solution: forwarding (ii)

- Each hazard is solved in a different way:
 - sub - and**: signal paths are added to forward the data from the MEM stage to each of the ALU inputs (EX stage)
 - sub - or**: signal paths are added to forward the data from the WB stage to each of the ALU inputs (EX stage)
 - sub - add**: it is solved by writing the RF at the end of the clock cycle first half, so that it can be read in the second half.

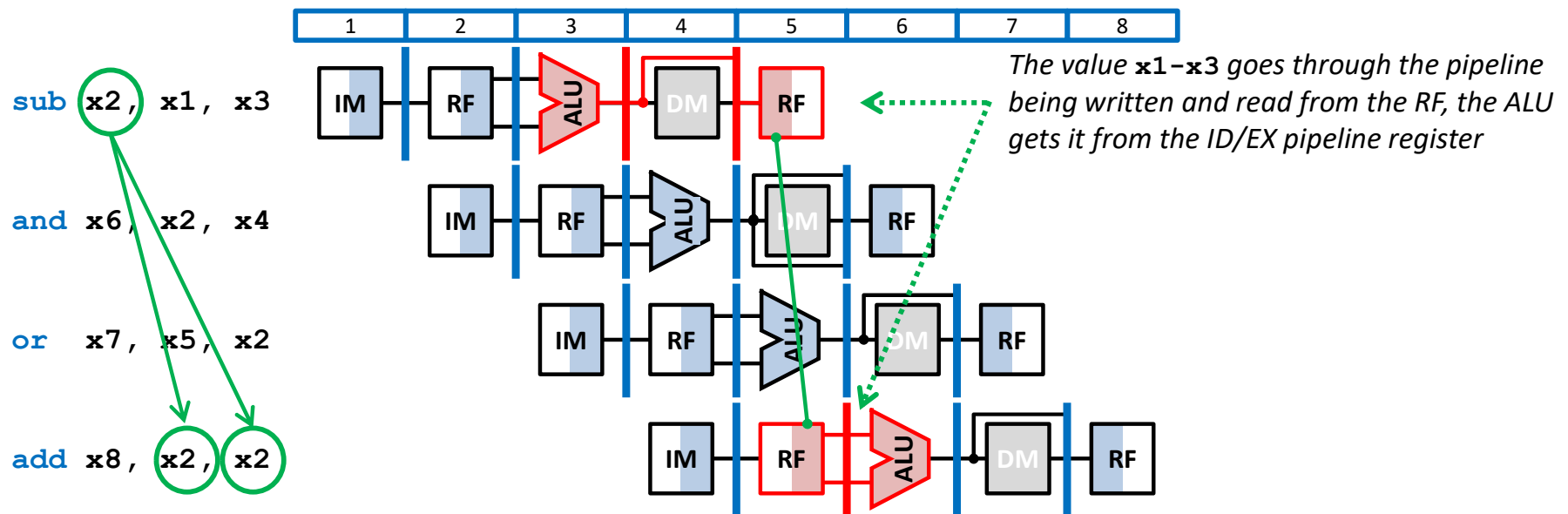





Data hazards

HW solution: forwarding (iii)

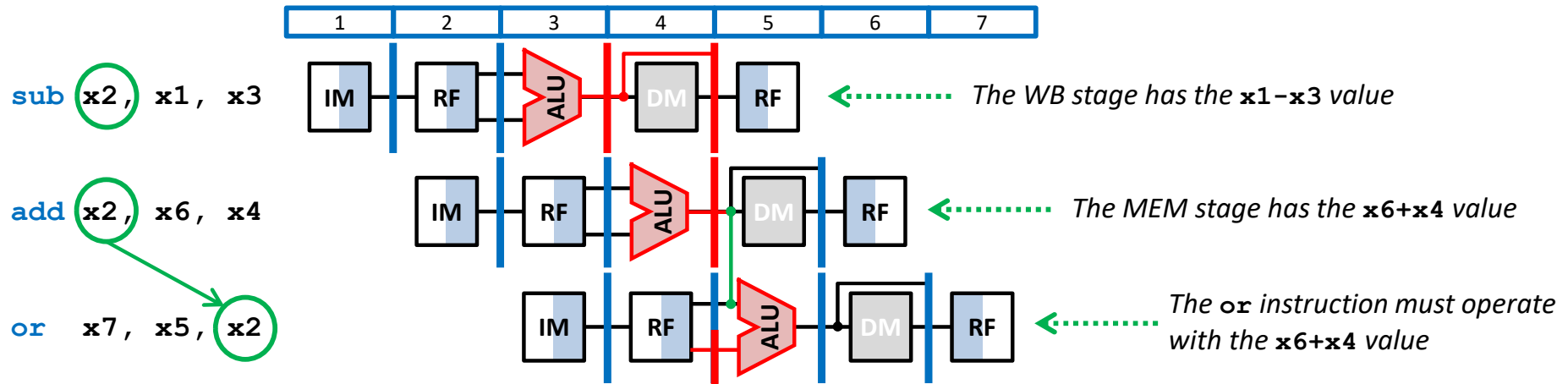- In the case a register can be forwarded from MEM and WB:
 - It has to be done from the MEM stage, since this has the most recent value of the register causing the hazard.



- The x_0 register is never forwarded:

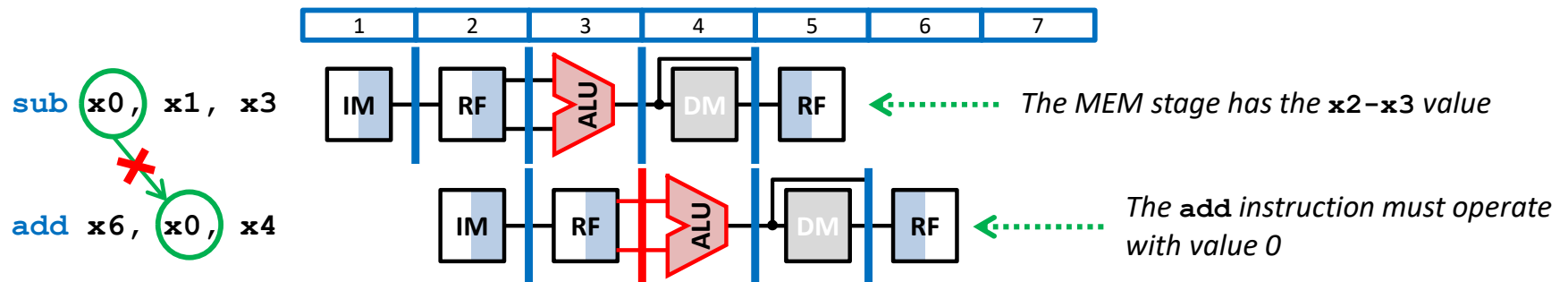




Data hazards


HW solution: forwarding (iv)

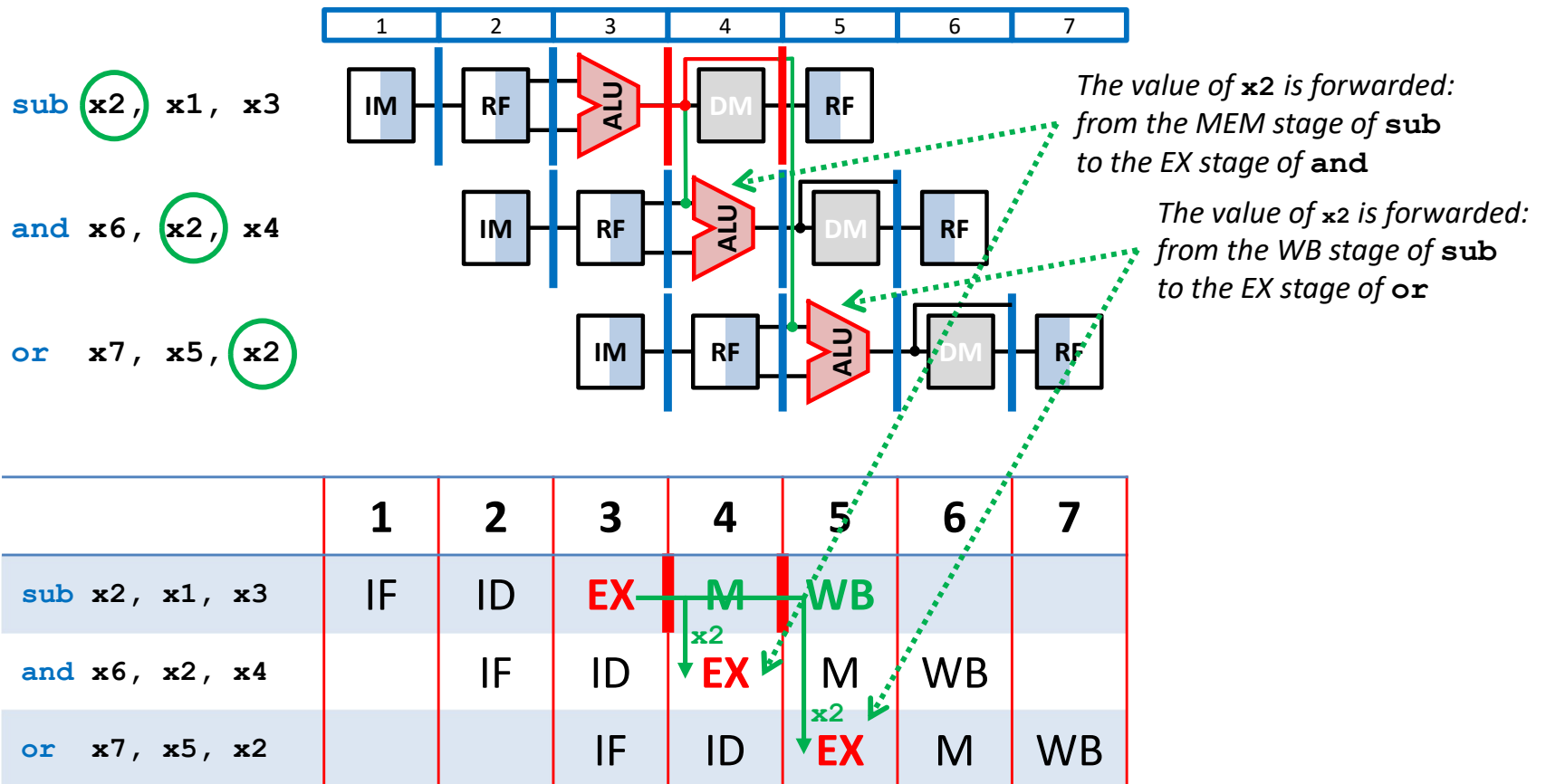- In the **simplified execution diagrams**, forwarding is indicated as dependencies between stages:




Pipelined processor

+ forwarding: data path

 

27/10/23 version

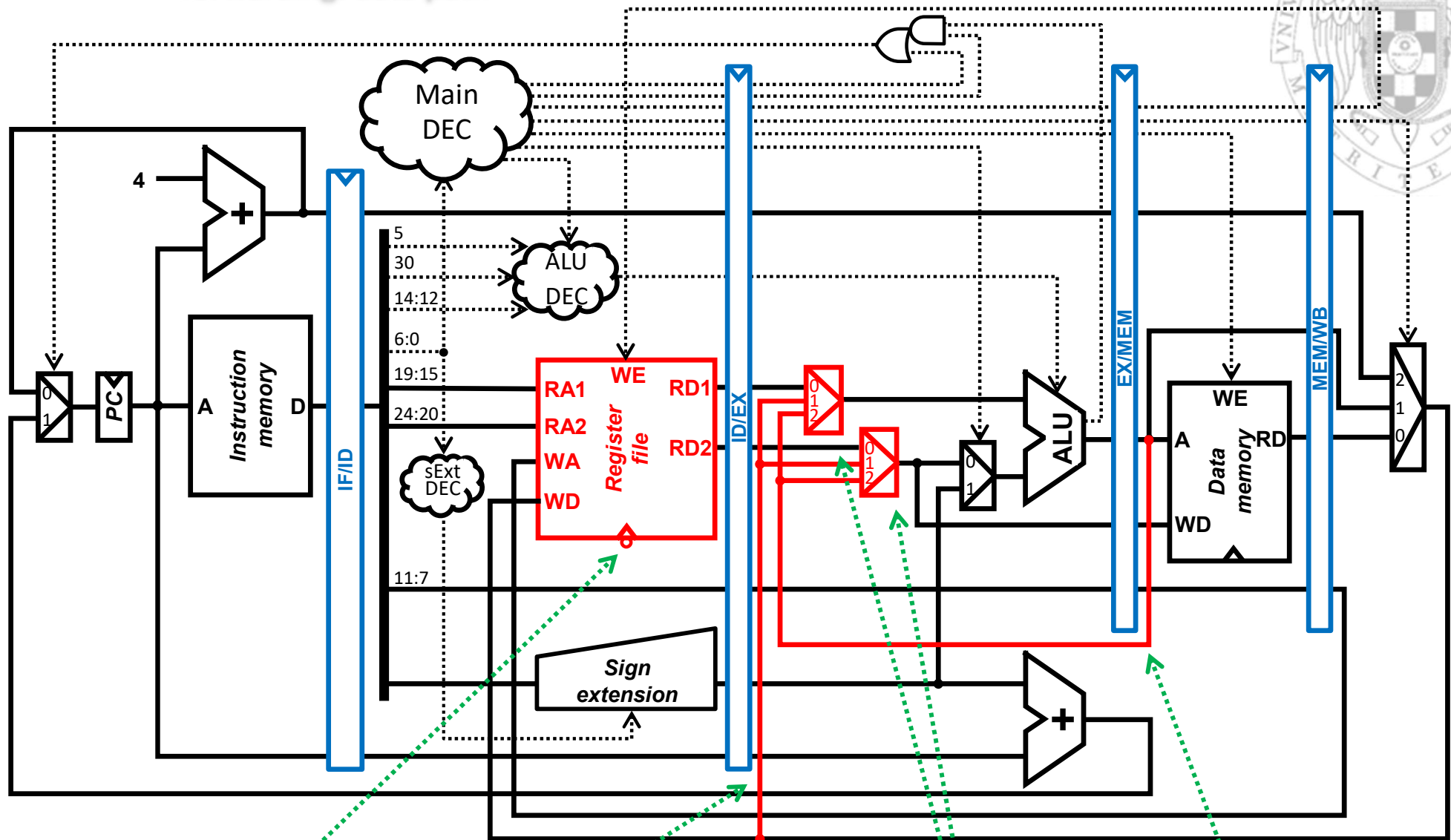

module 7:
Pipelined processor design

FC-2

66

By inverting the clock input,
The RF loads at the falling edge
(half cycle of the rising edge)

A forwarding path is added
from the WB stage to the EX stage

A forwarding path is added
from the MEM stage to the EX stage
MUX are added to the ALU inputs



Pipelined processor


Forwarding simulation: 3rd. cycle

27/10/23 version

module 7:
Pipelined processor design

FC-2


67

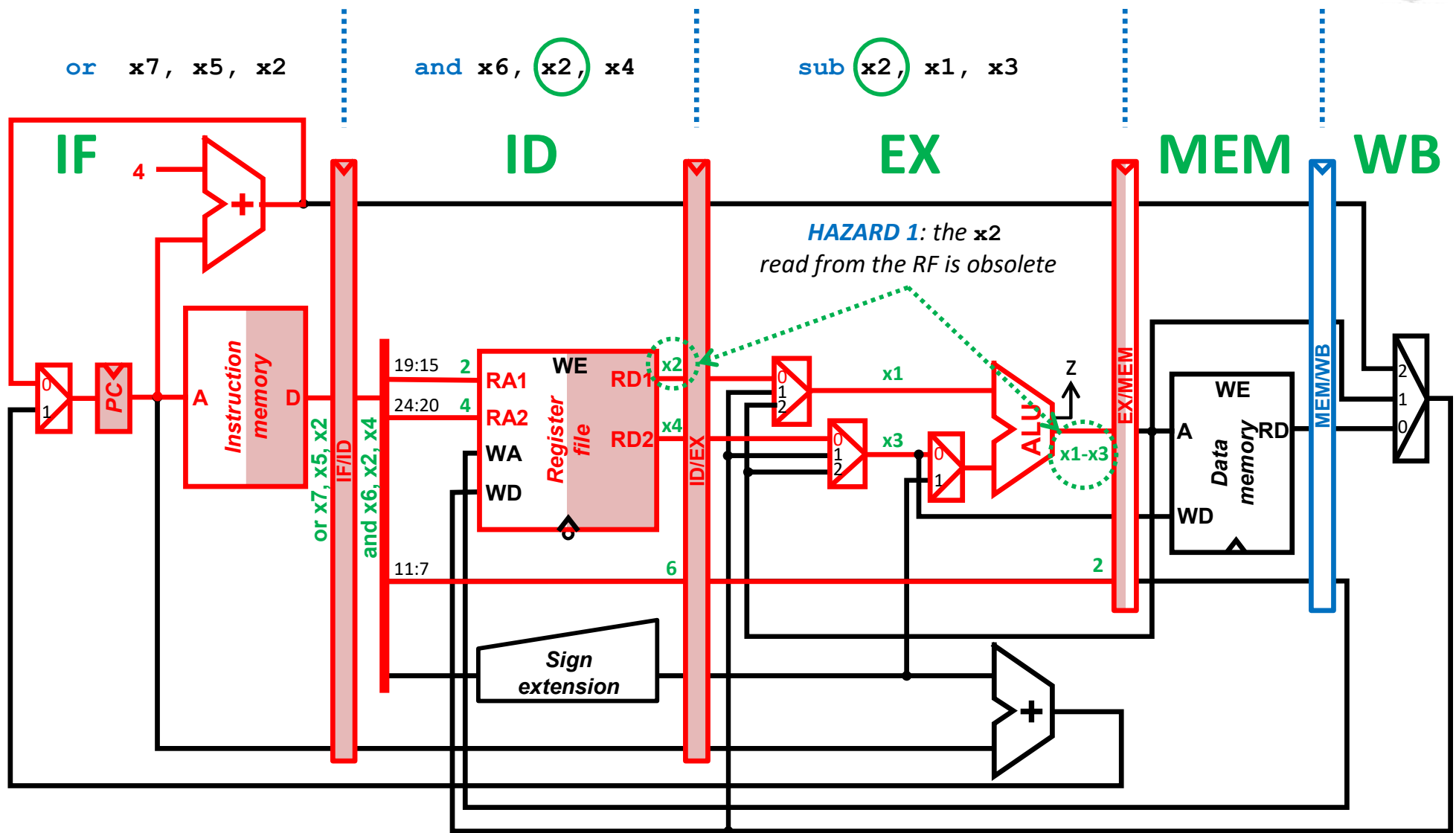



Pipelined processor


Forwarding simulation: 4th. cycle

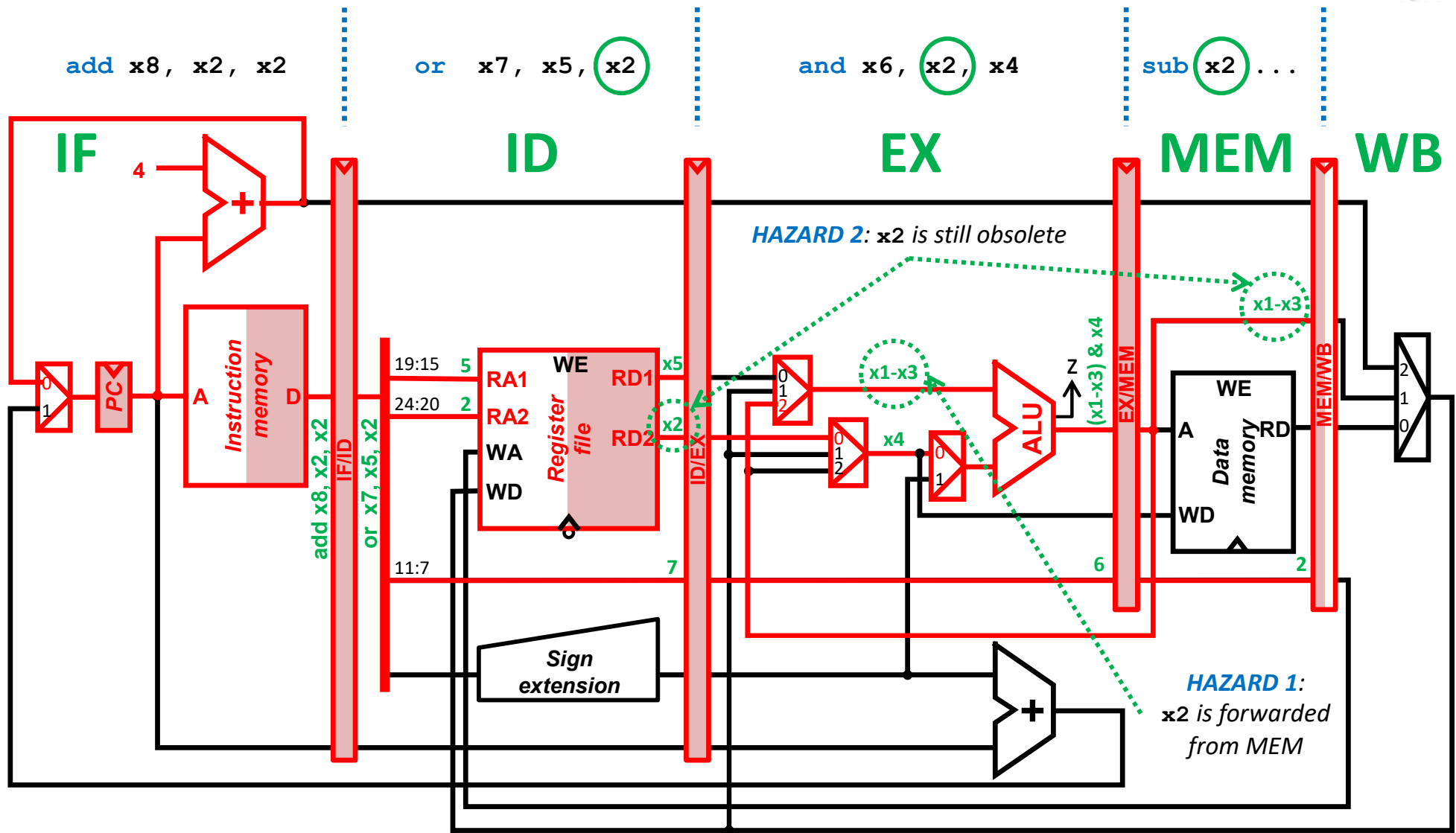



Pipelined processor

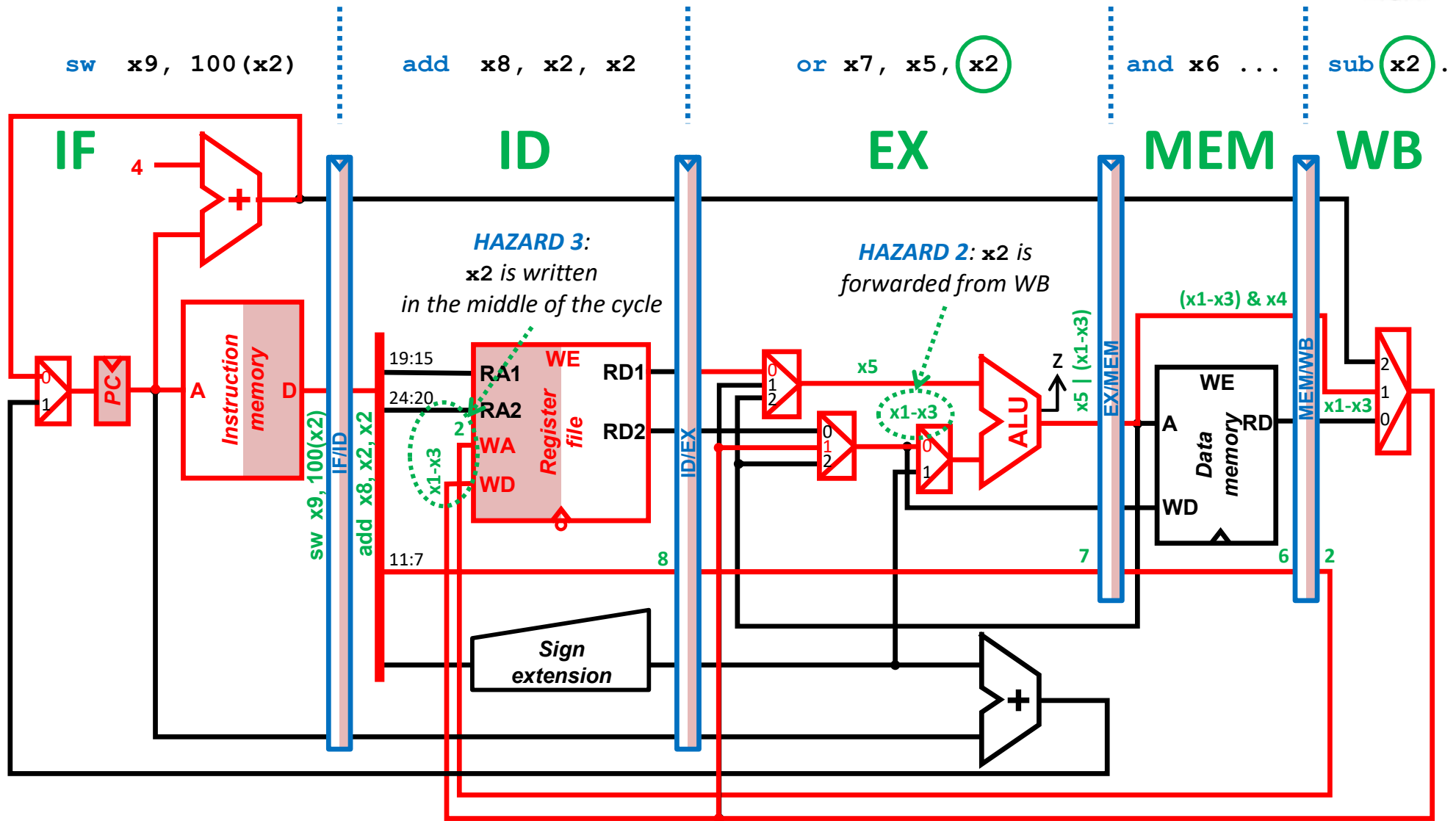
Forwarding simulation: 5th. cycle (1st. half)





Pipelined processor

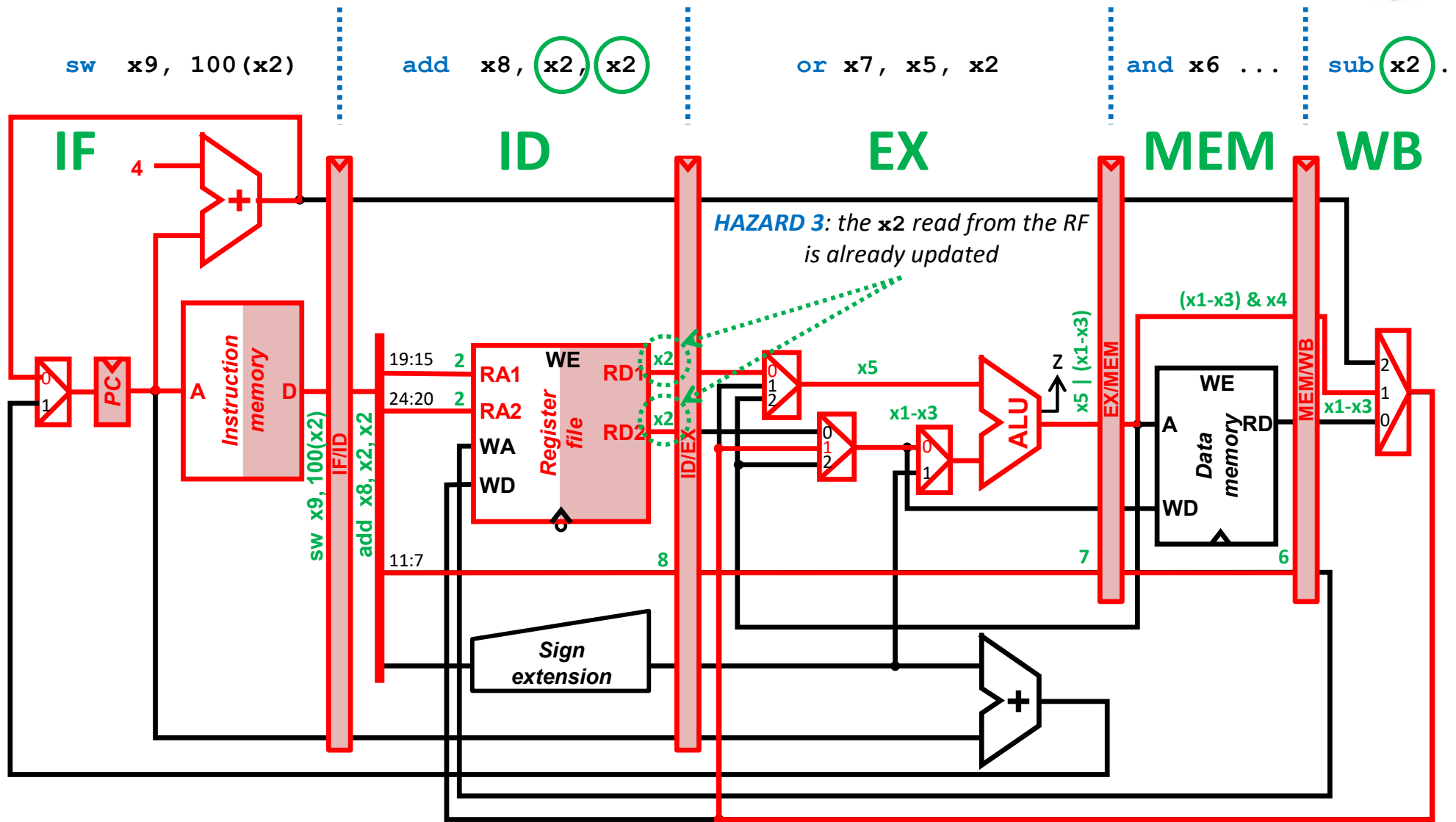Forwarding simulation: 5th. cycle (2nd. half)



Pipelined processor


Forwarding unit



- The **forwarding unit** is a **combinational circuit** that **controls the forwarding MUX** so that the ALU can operate with data:
 - Read from the RF and available in the ID/EX forwarding register.
 - Available in pipeline registers of the following stages (EX/MEM or MEM/WB)
- In order to behave correctly, **it must know**:
 - **Rs1E**: number of source register 1 of the instruction in the EX stage.
 - **Rs2E**: number of source register 2 of the instruction in the EX stage.
 - **RdM**: number of the destination register of the instruction in the MEM stage.
 - **BRwrM**: whether the instruction in the MEM stage writes in the RF or not.
 - **RdW**: number of the destination register of the instruction in the WB stage.
 - **BRweW**: whether the instruction in the WB stage writes in the RF or not.


Pipelined processor

+ Forwarding unit: control signals

 

27/10/23 version

module 7:
Pipelined processor design

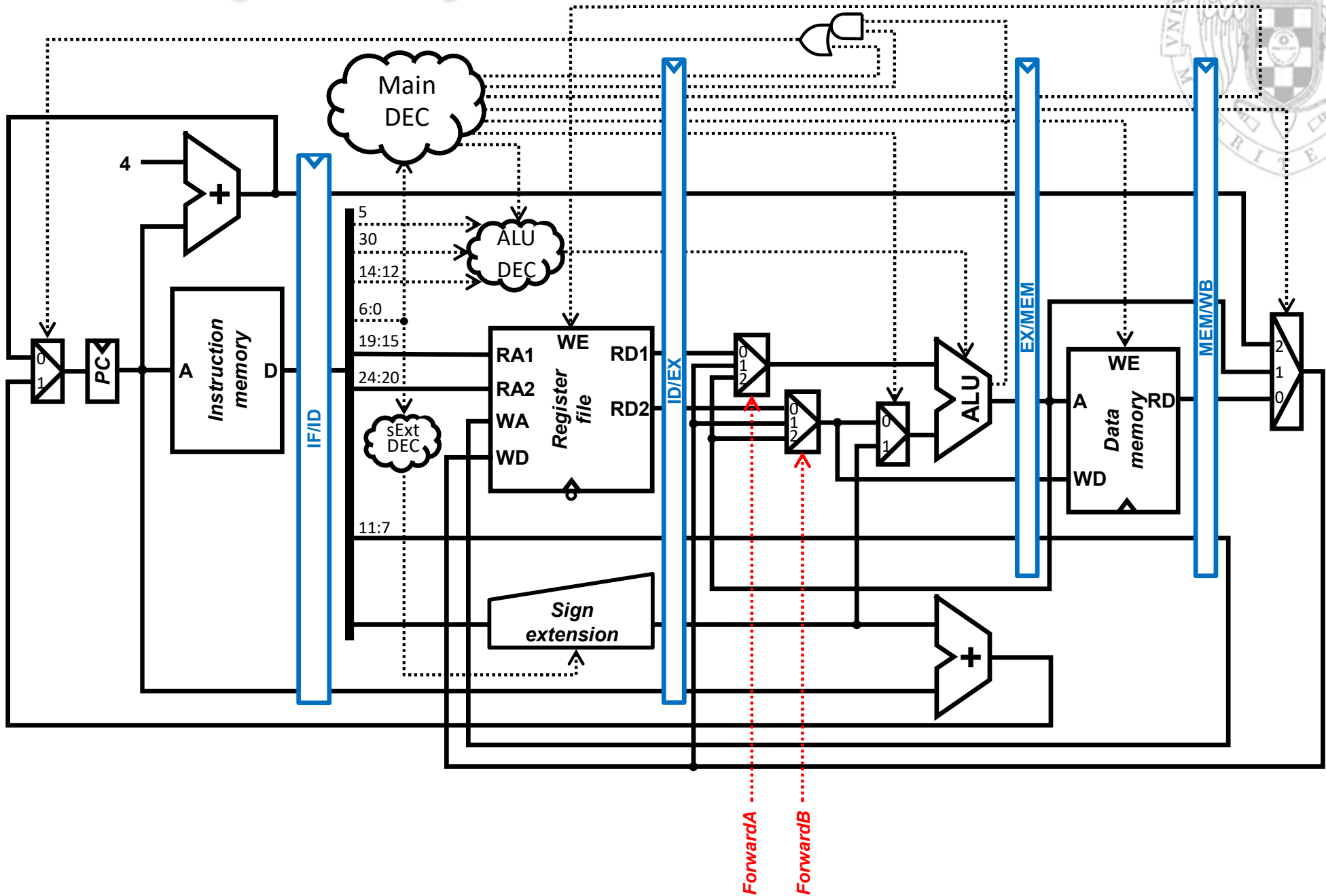


Pipelined processor

+ Forwarding unit: status signals

27/10/23 version

module 7:
Pipelined processor design

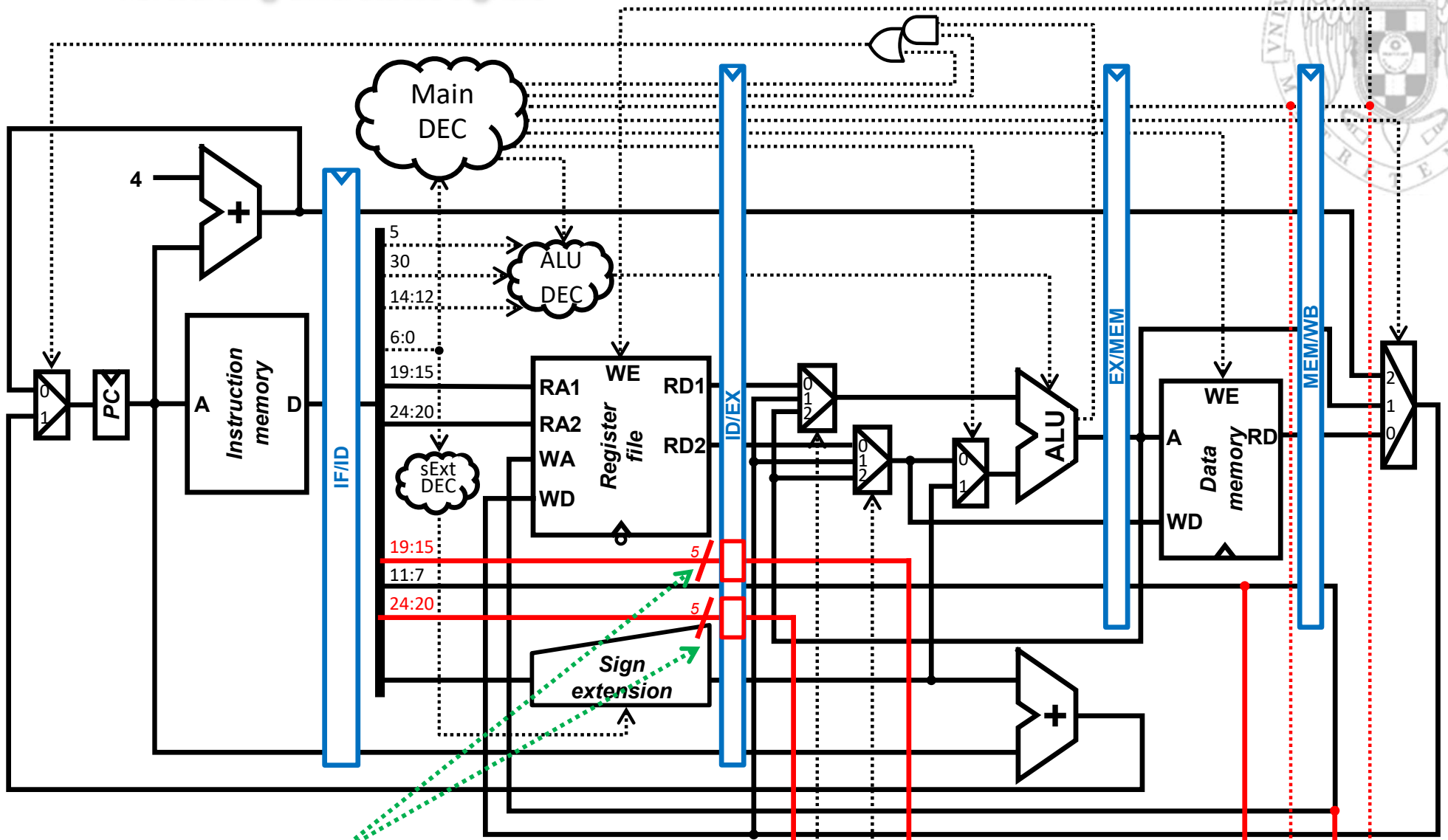


The pipeline register is extended to transmit the number of the source registers to the EX stage

Source registers of the instruction in the EX stage


Same for the MEM stage

 Destination register and write to RF signal of the instruction in the WB stage



Pipelined processor

+ Forwarding unit

 


27/10/23 version

module 7:
Pipelined processor design

FC-2

74

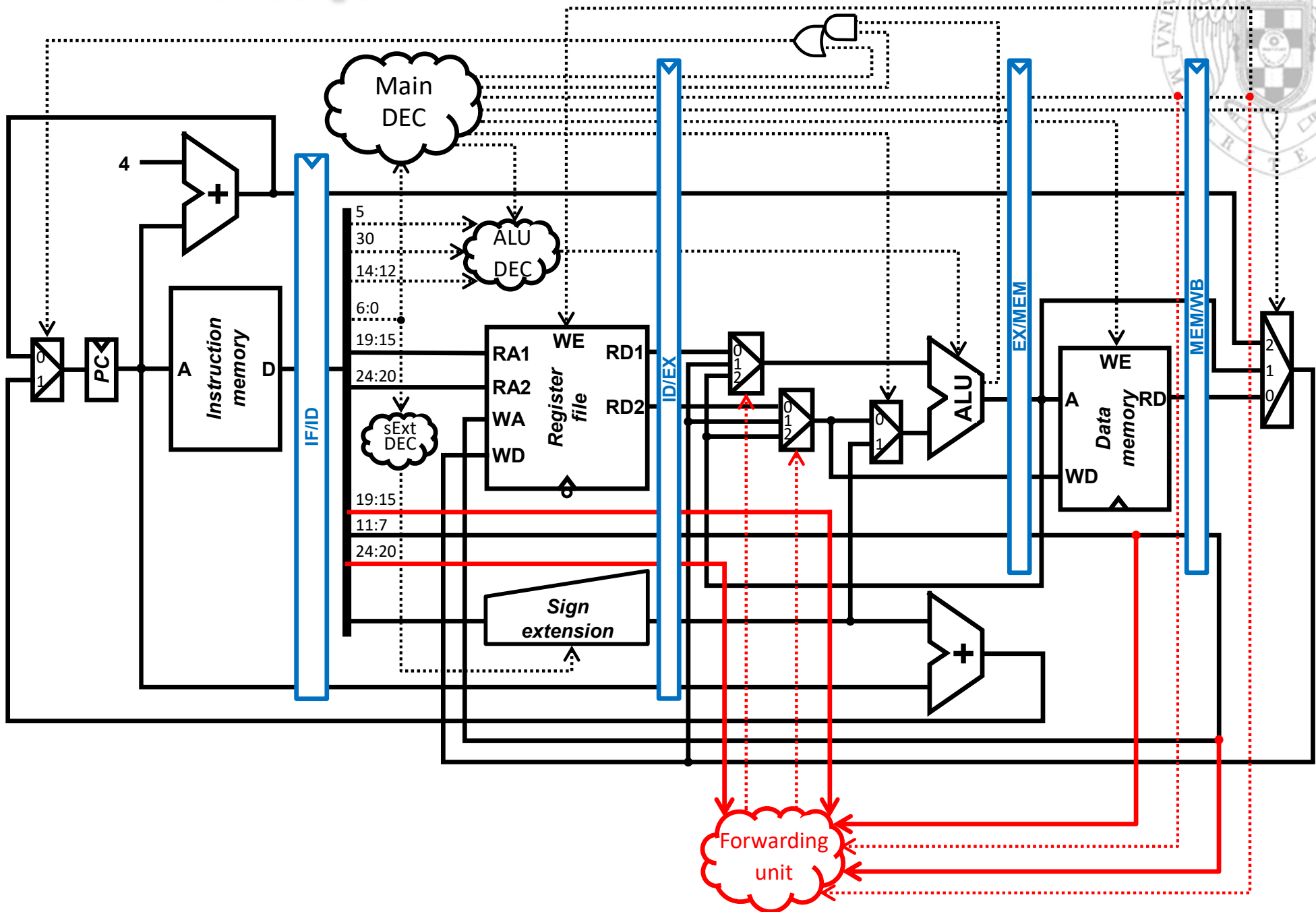



Pipelined processor

Forwarding unit design (i)

- A **data** must be **forwarded to the input A of the ALU**:
 - From the **MEM stage**, if the destination register of the MEM stage (RdM) will be written ($BRwrM$) and coincides with the source register of the EX stage ($Rs1E$).

$ForwardA \leftarrow if (BRwrM \ \& \ (Rs1E = RdM)) \ then \ (10) \ \leftarrow \dots \ Forwarding \ from \ MEM$



Pipelined processor

Forwarding unit design (i)

- A **data** must be **forwarded to the input A of the ALU**:
 - From the **MEM stage**, if the destination register of the MEM stage (RdM) will be written ($BRwrM$) and coincides with the source register of the EX stage ($Rs1E$).
 - From the **WB stage**, if the destination register of the WB stage (RdW) will be written ($BRwrW$) and coincides with the source register of the EX stage ($Rs1E$).
 - This condition is only checked if the previous one is not met, because when the data can be forwarded from both stages, it has to be taken from the MEM stage.

```
ForwardA ← if (          BRwrM & (Rs1E = RdM) ) then ( 10 ) ←..... Forwarding from MEM
               elsif(     BRwrW & (Rs1E = RdW) ) then ( 01 ) ←..... Forwarding from WB
```



Pipelined processor

Forwarding unit design (i)

- A **data** must be **forwarded to the input A of the ALU**:
 - From the **MEM stage**, if the destination register of the MEM stage (RdM) will be written ($BRwrM$) and coincides with the source register of the EX stage ($Rs1E$).
 - From the **WB stage**, if the destination register of the WB stage (RdW) will be written ($BRwrW$) and coincides with the source register of the EX stage ($Rs1E$).
 - This condition is only checked if the previous one is not met, because when the data can be forwarded from both stages, it has to be taken from the MEM stage.
 - Register **x0** is never forwarded because it has a constant value of 0.

```
ForwardA ← if ( (Rs1E ≠ 0) & BRwrM & (Rs1E = RdM) ) then ( 10 ) ←..... Forwarding from MEM
           elsif( (Rs1E ≠ 0) & BRwrW & (Rs1E = RdW) ) then ( 01 ) ←..... Forwarding from WB
```



Pipelined processor

Forwarding unit design (i)

- A **data** must be **forwarded to the input A of the ALU**:
 - From the **MEM stage**, if the destination register of the MEM stage (RdM) will be written (BRwrM) and coincides with the source register of the EX stage (Rs1E).
 - From the **WB stage**, if the destination register of the WB stage (RdW) will be written (BRwrW) and coincides with the source register of the EX stage (Rs1E).
 - This condition is only checked if the previous one is not met, because when the data can be forwarded from both stages, it has to be taken from the MEM stage.
 - Register x0 is never forwarded because it has a constant value of 0.
- Otherwise, do not forward.

```

ForwardA ← if ( (Rs1E ≠ 0) & BRwrM & (Rs1E = RdM) ) then ( 10 ) ← Forwarding from MEM
           elsif( (Rs1E ≠ 0) & BRwrW & (Rs1E = RdW) ) then ( 01 ) ← Forwarding from WB
           else ( 00 ) ← Do not forward
  
```

- Same for the forwarding unit to the **input B of the ALU**
 - Replacing RS1E with RS2E.



Pipelined processor

Forwarding unit design (ii)

ForwardA \leftarrow if ((Rs1E \neq 0) & BRwrM & (Rs1E = RdM)) then (10)
elsif((Rs1E \neq 0) & BRwrW & (Rs1E = RdW)) then (01)
else (00)

Truth table

Rs1E \neq 0	BRwrM	BRwrW	Rs1E = RdM	Rs1E = RdW	ForwardA
0	X	X	X	X	00 (no forwarding)
1	0	1	X	0	00 (no forwarding)
1	0	1	X	1	01 (WB forwarding)
1	1	X	0	X	00 (no forwarding)
1	1	X	1	X	10 (MEM forwarding)



Pipelined processor

Forwarding unit design (ii)

$ForwardA \leftarrow$ if ($Rs1E \neq 0$) & BRwrM & ($Rs1E = RdM$) then (10)
 elsif(($Rs1E \neq 0$) & BRwrW & ($Rs1E = RdW$)) then (01)
 else (00)

$ForwardB \leftarrow$ if ($Rs2E \neq 0$) & BRwrM & ($Rs2E = RdM$) then (10)
 elsif(($Rs2E \neq 0$) & BRwrW & ($Rs2E = RdW$)) then (01)
 else (00)

Truth table

Rs1E ≠ 0	BRwrM	BRwrW	Rs1E = RdM	Rs1E = RdW	ForwardA
0	X	X	X	X	00 (no forwarding)
1	0	1	X	0	00 (no forwarding)
1	0	1	X	1	01 (WB forwarding)
1	1	X	0	X	00 (no forwarding)
1	1	X	1	X	10 (MEM forwarding)


Truth table

Rs2E ≠ 0	BRwrM	BRwrW	Rs2E = RdM	Rs2E = RdW	ForwardB
0	X	X	X	X	00 (no forwarding)
1	0	1	X	0	00 (no forwarding)
1	0	1	X	1	01 (WB forwarding)
1	1	X	0	X	00 (no forwarding)
1	1	X	1	X	10 (MEM forwarding)



Pipelined processor

Forwarding unit design (iii)

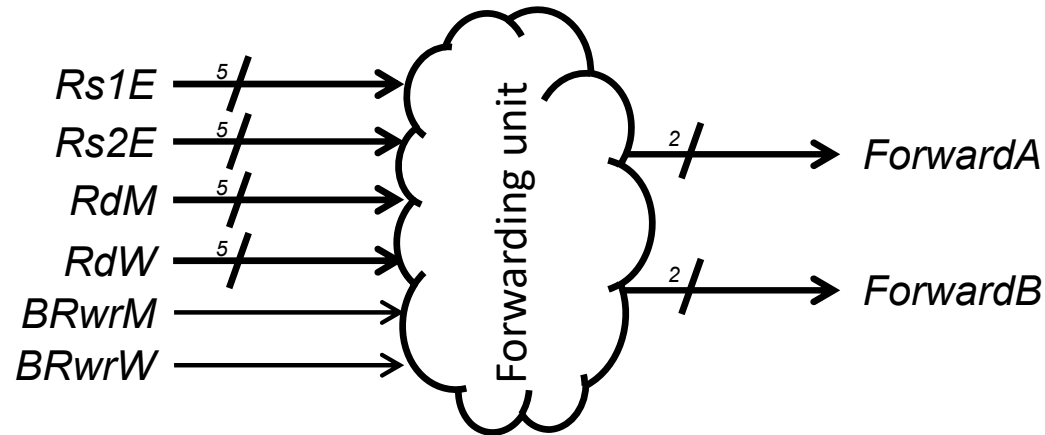

Truth table

Rs1E # 0	BRwrM	BRwrW	Rs1E = RdM	Rs1E = RdW	ForwardA
0	X	X	X	X	00 (no forwarding)
1	0	1	X	0	00 (no forwarding)
1	0	1	X	1	01 (WB forwarding)
1	1	X	0	X	00 (no forwarding)
1	1	X	1	X	10 (MEM forwarding)



Truth table

Rs2E # 0	BRwrM	BRwrW	Rs2E = RdM	Rs2E = RdW	ForwardB
0	X	X	X	X	00 (no forwarding)
1	0	1	X	0	00 (no forwarding)
1	0	1	X	1	01 (WB forwarding)
1	1	X	0	X	00 (no forwarding)
1	1	X	1	X	10 (MEM forwarding)



Pipelined processor

Forwarding unit design (iv)

  

Truth table

Rs1E ≠ 0	BRwrM	BRwrW	Rs1E = RdM	Rs1E = RdW	ForwardA
0	X	X	X	X	00 (no forwarding)
1	0	1	X	0	00 (no forwarding)
1	0	1	X	1	01 (WB forwarding)
1	1	X	0	X	00 (no forwarding)
1	1	X	1	X	10 (MEM forwarding)

Truth table


Rs2E ≠ 0	BRwrM	BRwrW	Rs2E = RdM	Rs2E = RdW	ForwardB
0	X	X	X	X	00 (no forwarding)
1	0	1	X	0	00 (no forwarding)
1	0	1	X	1	01 (WB forwarding)
1	1	X	0	X	00 (no forwarding)
1	1	X	1	X	10 (MEM forwarding)




Data hazards

HW solution: **1w** hazard

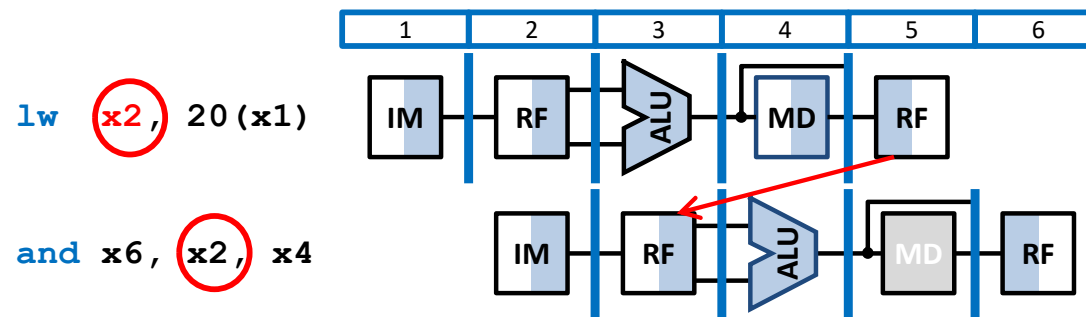- There is a kind of **data hazard** that requires a **special treatment**:
 - When a **1w** instruction loads a register that is read by the following instruction.



 - The required data **cannot be forwarded** because:
 - The **1w** instruction reads the data from memory in cycle 4.
 - The following instruction needs that data in the same cycle.






Data hazards

HW solution: 1w hazard, stalling (i)

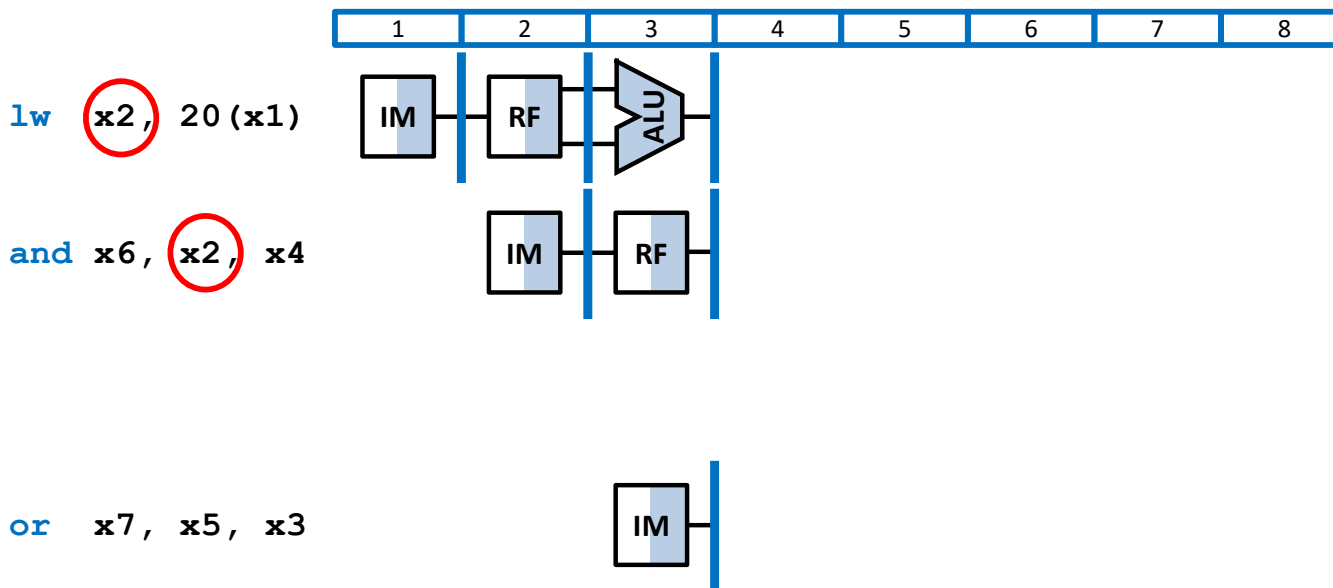- The **solution** implies **stalling** the pipeline during one cycle in order to delay the instruction that requires the data, so that it can be forwarded.
 - **Cycle 3:** **and** (in ID), the hazard is detected.






Data hazards

HW solution: ~~lw~~ hazard, stalling (i)

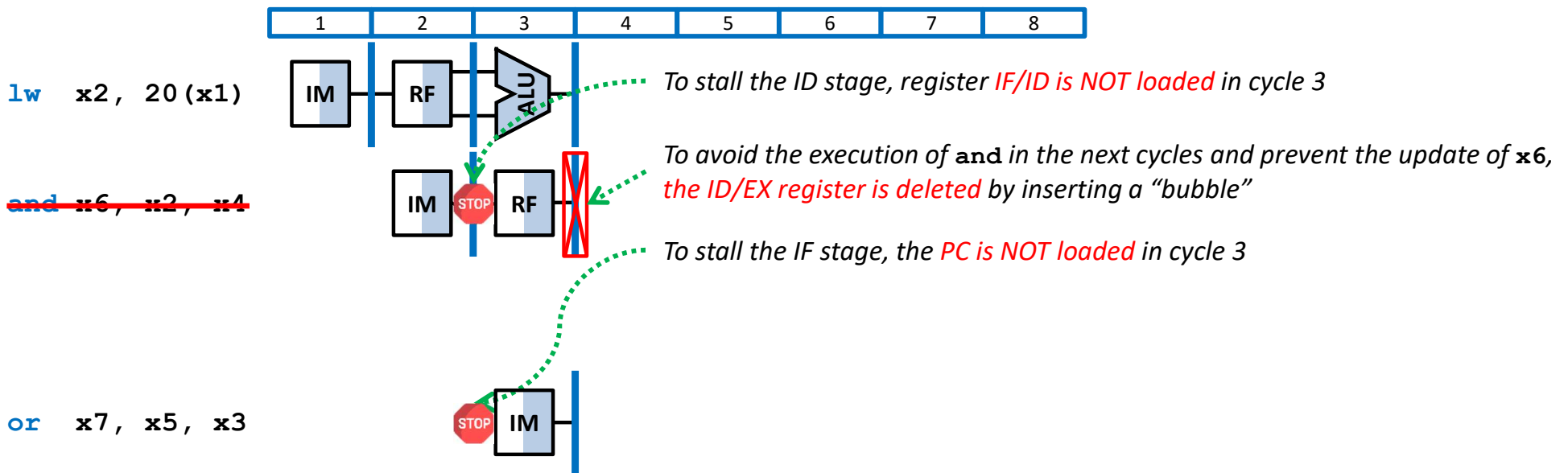- The **solution** implies **stalling** the pipeline during one cycle in order to delay the instruction that requires the data, so that it can be forwarded.
- **Cycle 3:** `and` (in ID), the hazard is detected. Instructions **`and`**, **`or`** are stalled and a nop “bubble” is inserted in the EX stage.






Data hazards

HW solution: `lw` hazard, stalling (i)

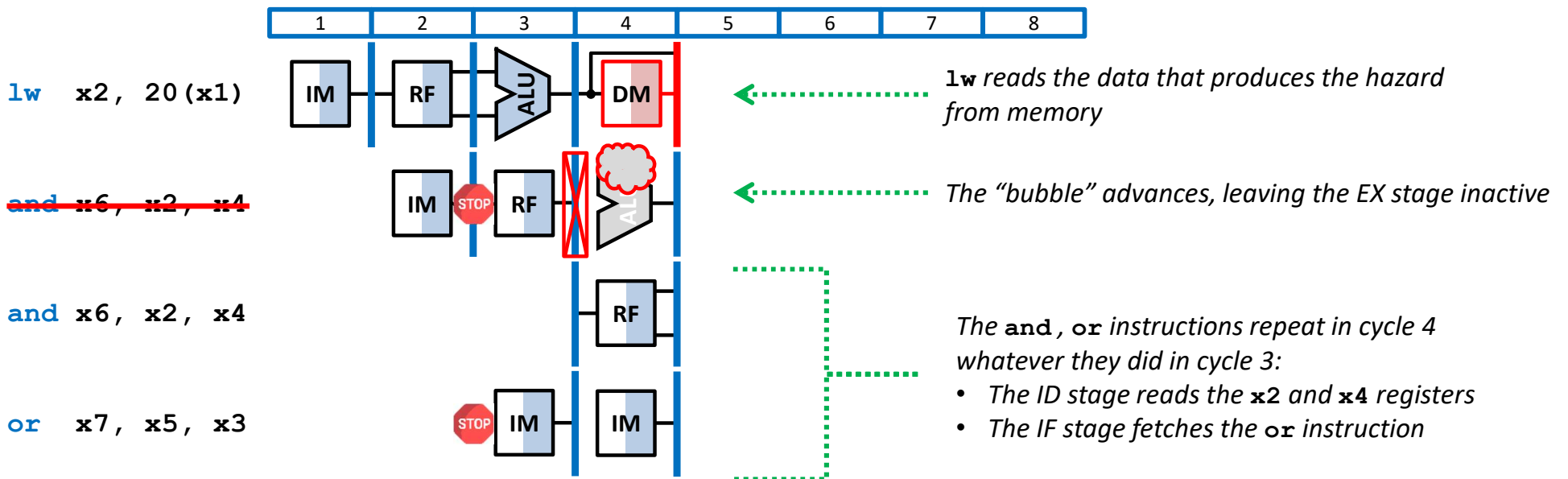- The **solution** implies **stalling** the pipeline during one cycle in order to delay the instruction that requires the data, so that it can be forwarded.
- **Cycle 3:** `and` (in ID), the hazard is detected. Instructions `and`, `or` are stalled and a nop “bubble” is inserted in the EX stage.
- **Cycle 4:** `lw` reads the data from memory; `and`, `or` resume.






Data hazards

HW solution: **lw** hazard, stalling (i)

- The **solution** implies **stalling** the pipeline during one cycle in order to delay the instruction that requires the data, so that it can be forwarded.
- **Cycle 3:** **and** (in ID), the hazard is detected. Instructions **and** , **or** are stalled and a nop “bubble” is inserted in the EX stage.
- **Cycle 4:** **lw** reads the data from memory; **and** , **or** resume.
- **Cycle 5:** the **data is forwarded** from the WB stage of **lw** to the EX stage of **and**.

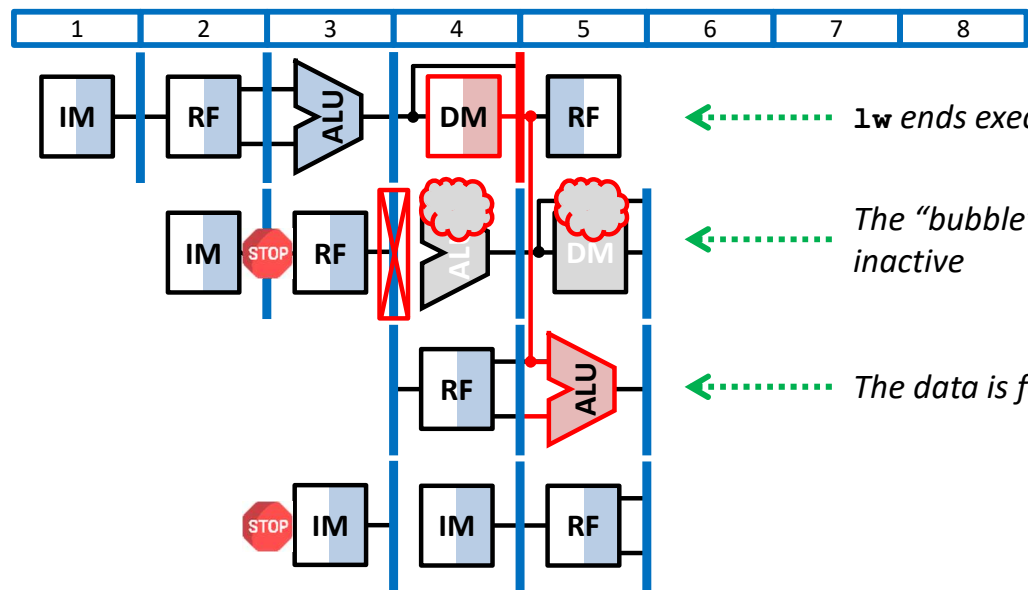




Data hazards

HW solution: **lw** hazard, stalling (i)

- The **solution** implies **stalling** the pipeline during one cycle in order to delay the instruction that requires the data, so that it can be forwarded.
- **Cycle 3:** **and** (in ID), the hazard is detected. Instructions **and**, **or** are stalled and a nop “bubble” is inserted in the EX stage.
- **Cycle 4:** **lw** reads the data from memory; **and**, **or** resume.
- **Cycle 5:** the **data is forwarded** from the WB stage of **lw** to the EX stage of **and**.
- **Next cycles:** the pipeline behaves as expected.
- There is a **one cycle penalty** due to the **lw** hazard.

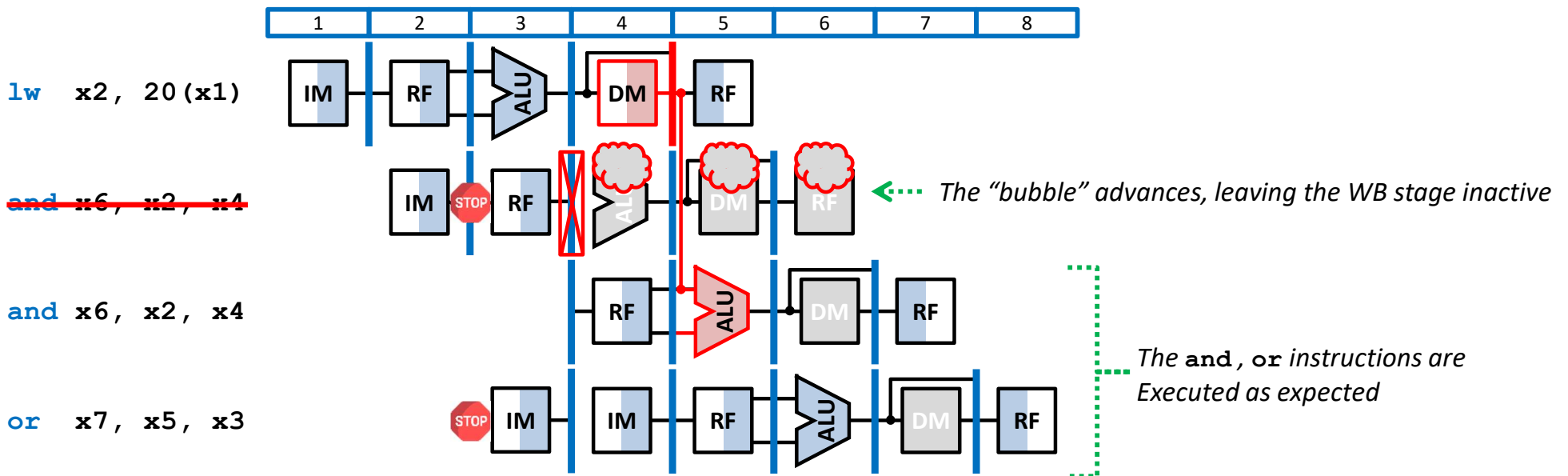




Data hazards

HW solution: `lw` hazard, stalling (ii)

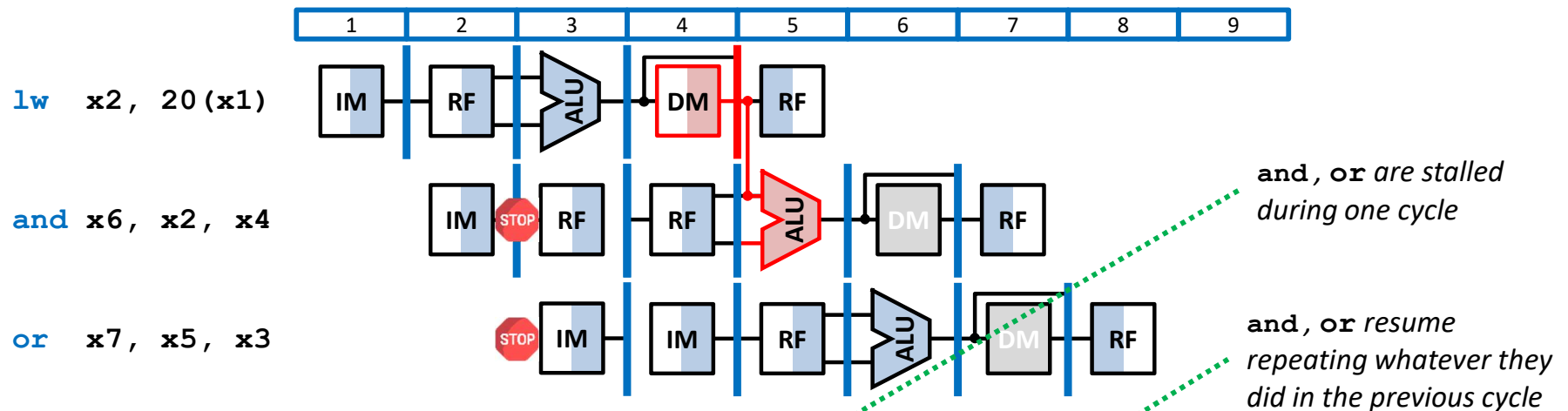- In the **simplified execution diagrams**, stalls are indicated marking the stages that are stalled (“bubbles” are implicit):




	1	2	3	4	5	6	7	8	9
<code>lw x2, 20(x1)</code>	IF	ID	EX	M	WB				
<code>and x6, x2, x4</code>		IF	IDs	ID	EX	M	WB		
<code>or x7, x5, x3</code>			IFs	IF	ID	EX	M	WB	
<code>add x8, x2, x2</code>					IF	ID	EX	M	WB

The next instruction is fetched after resuming `and`, `or`



Pipelined processor

Stall simulation: 3rd. cycle

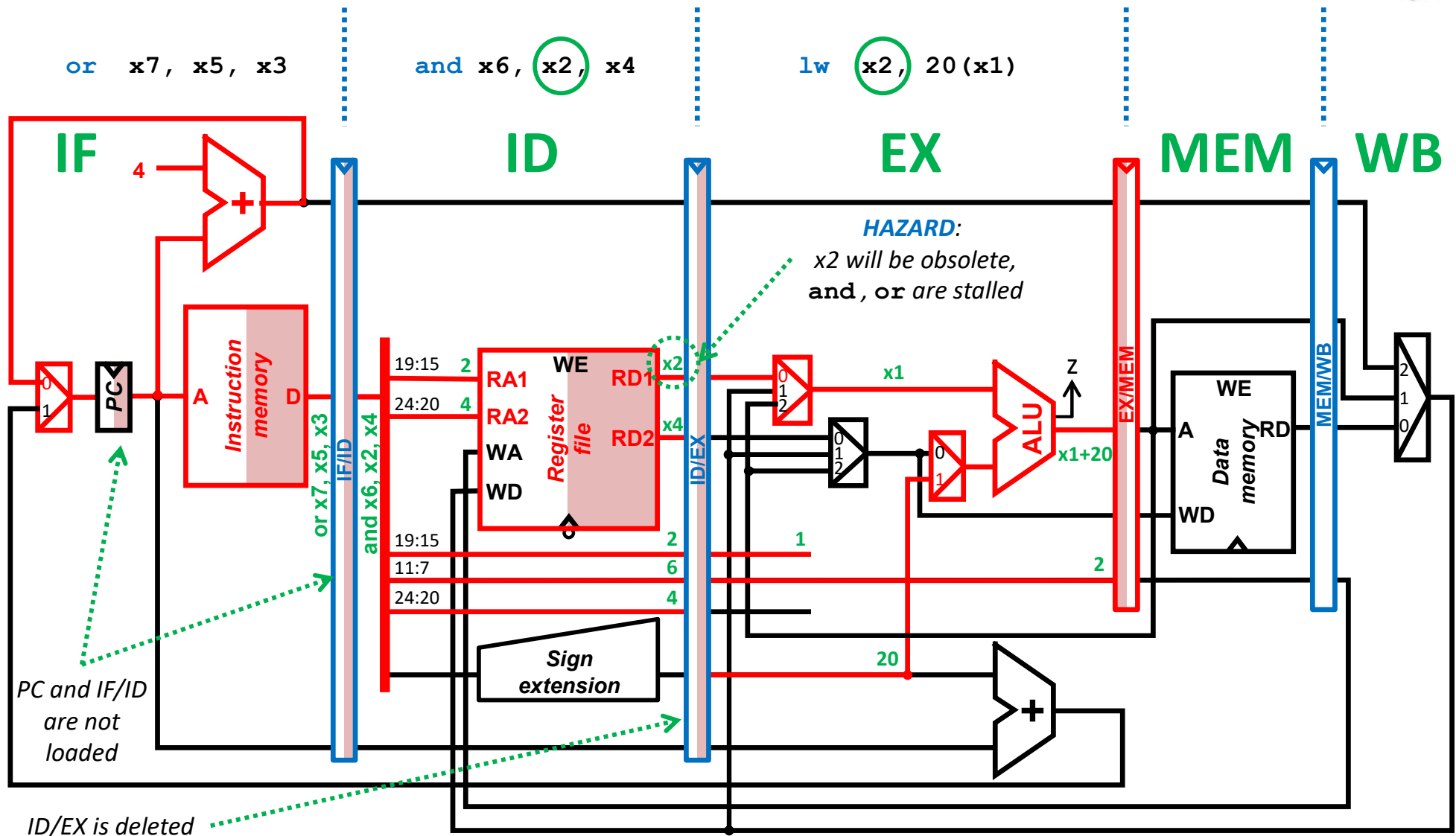


ID/EX is deleted



Pipelined processor


Stall simulation : 4th. cycle

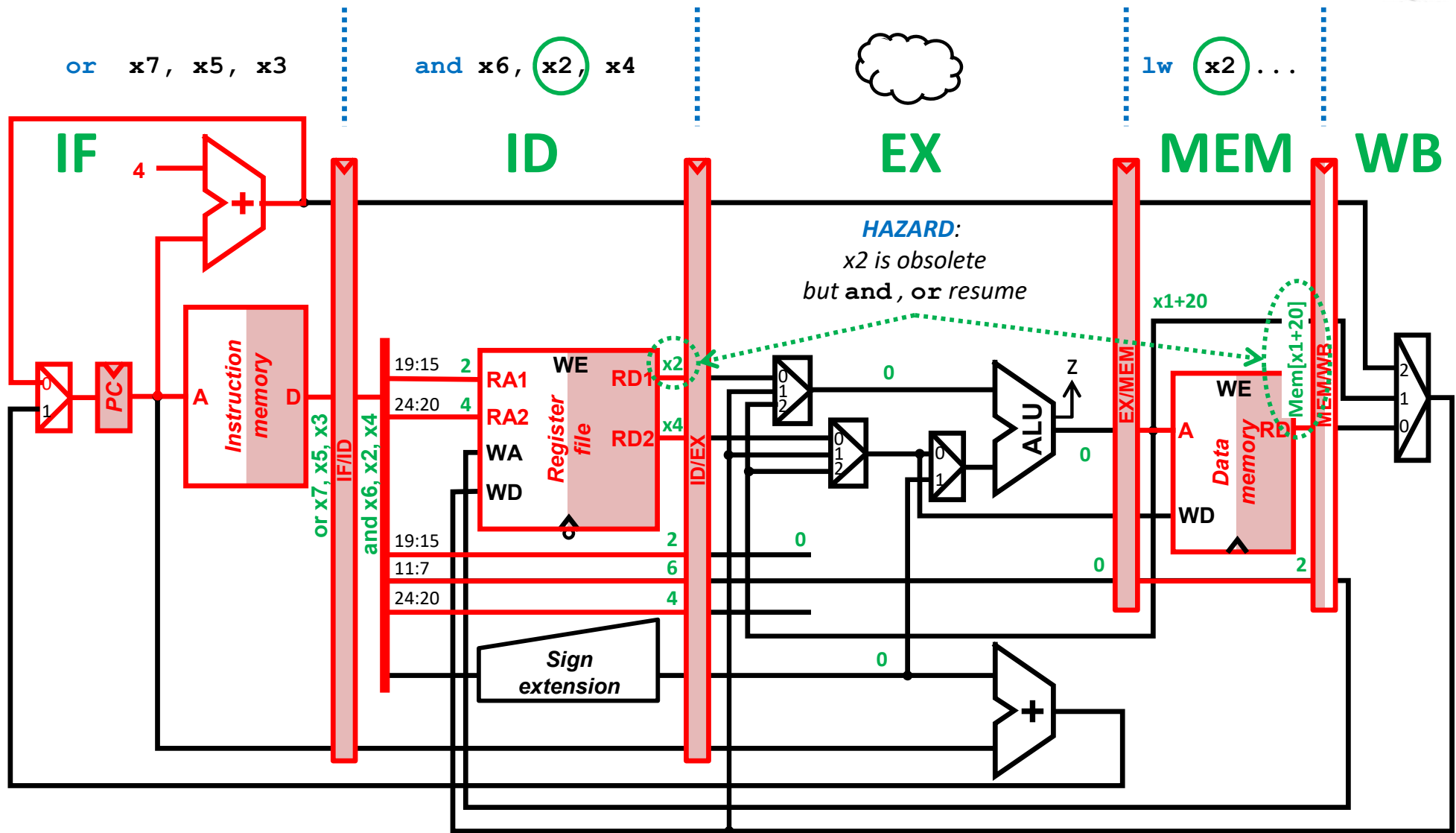



Pipelined processor

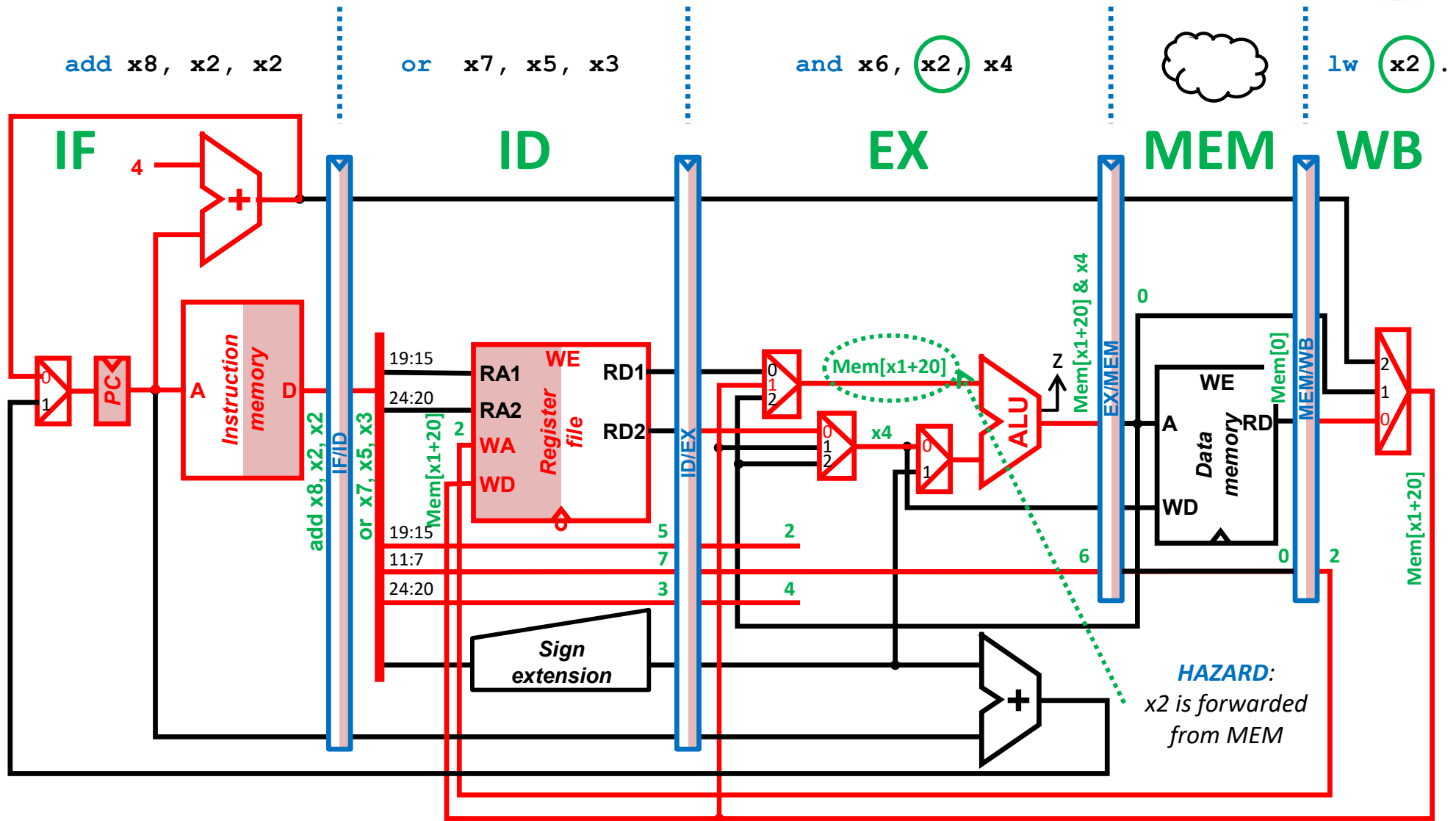
Stall simulation : 5th. cycle (1st. half)





Pipelined processor

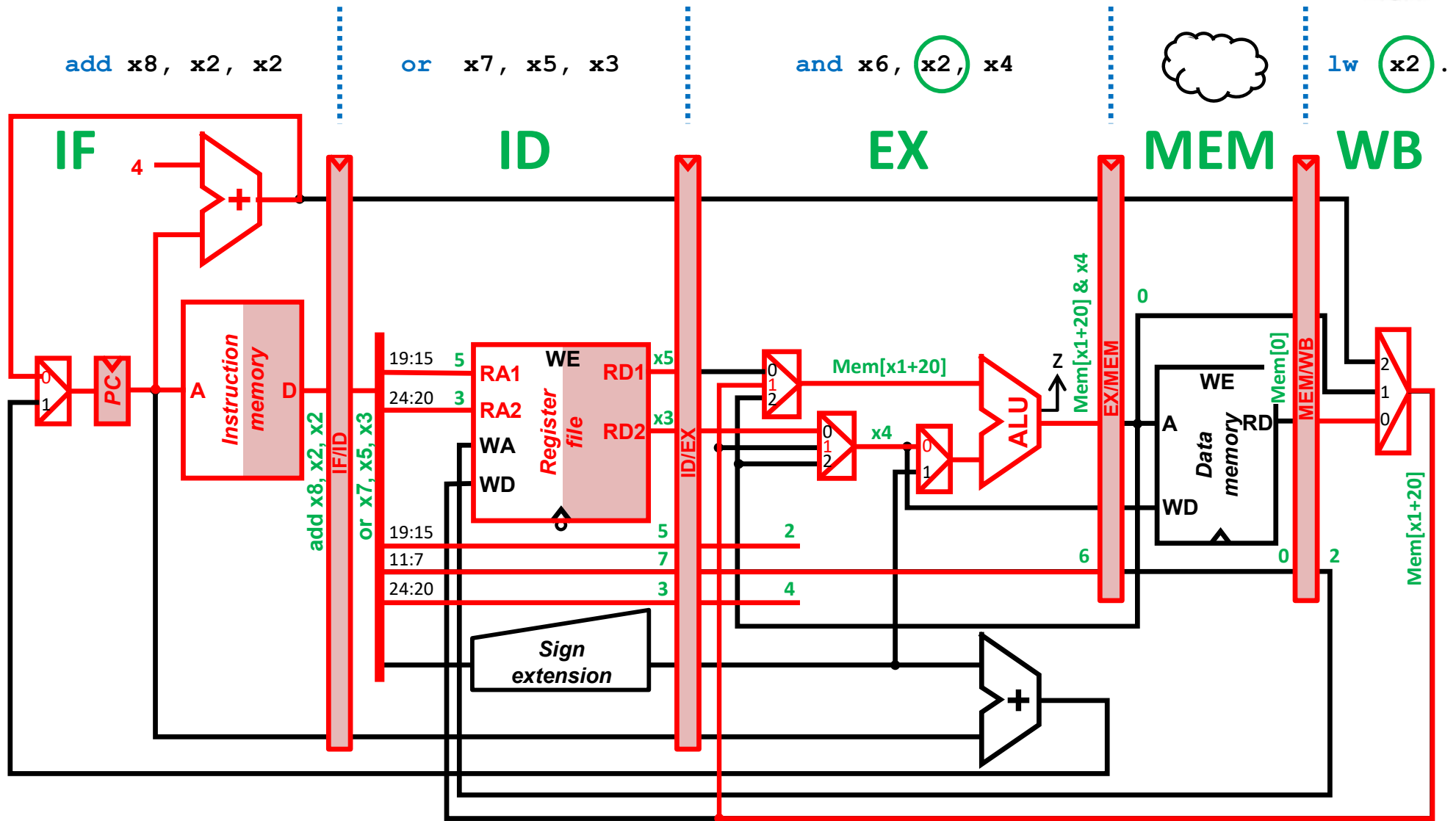
Stall simulation : 5th. cycle (2nd. half)





Pipelined processor

Stall simulation : 6th. cycle

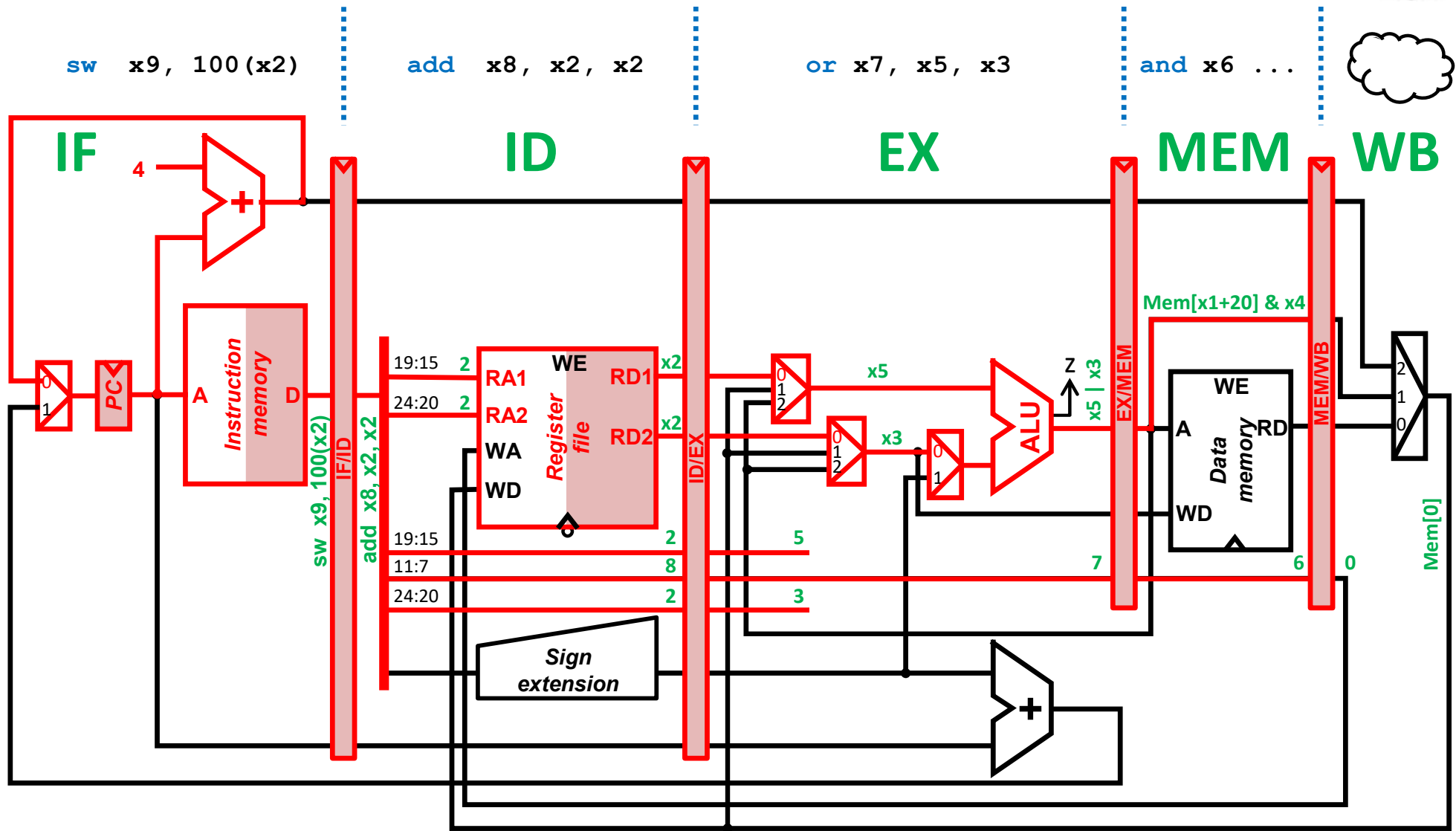

Pipelined processor


Hazard unit



- The **hazard unit** is a **combinational circuit** that determines if the **IF and ID stages of the pipeline have to be stalled**, controlling whether:
 - The PC and the IF/ID pipeline register have to be loaded or not.
 - The ID/EX pipeline register must be deleted or not.
- In order to behave correctly, **it must know**:
 - If there is a **1w instruction** in the EX stage.
 - Checking if **ResSrcE = 0** and **BRwrE = 1** (only **1w** meets this)
 - **RdE**: number of the destination register of the **1w** instruction in the EX stage.
 - **Rs1D**: number of source register 1 of the instruction in the ID stage.
 - **Rs2D**: number of source register 2 of the instruction in the ID stage.

Pipelined processor

+ Hazard unit

 


27/10/23 version

module 7:
Pipelined processor design

FC-2

99

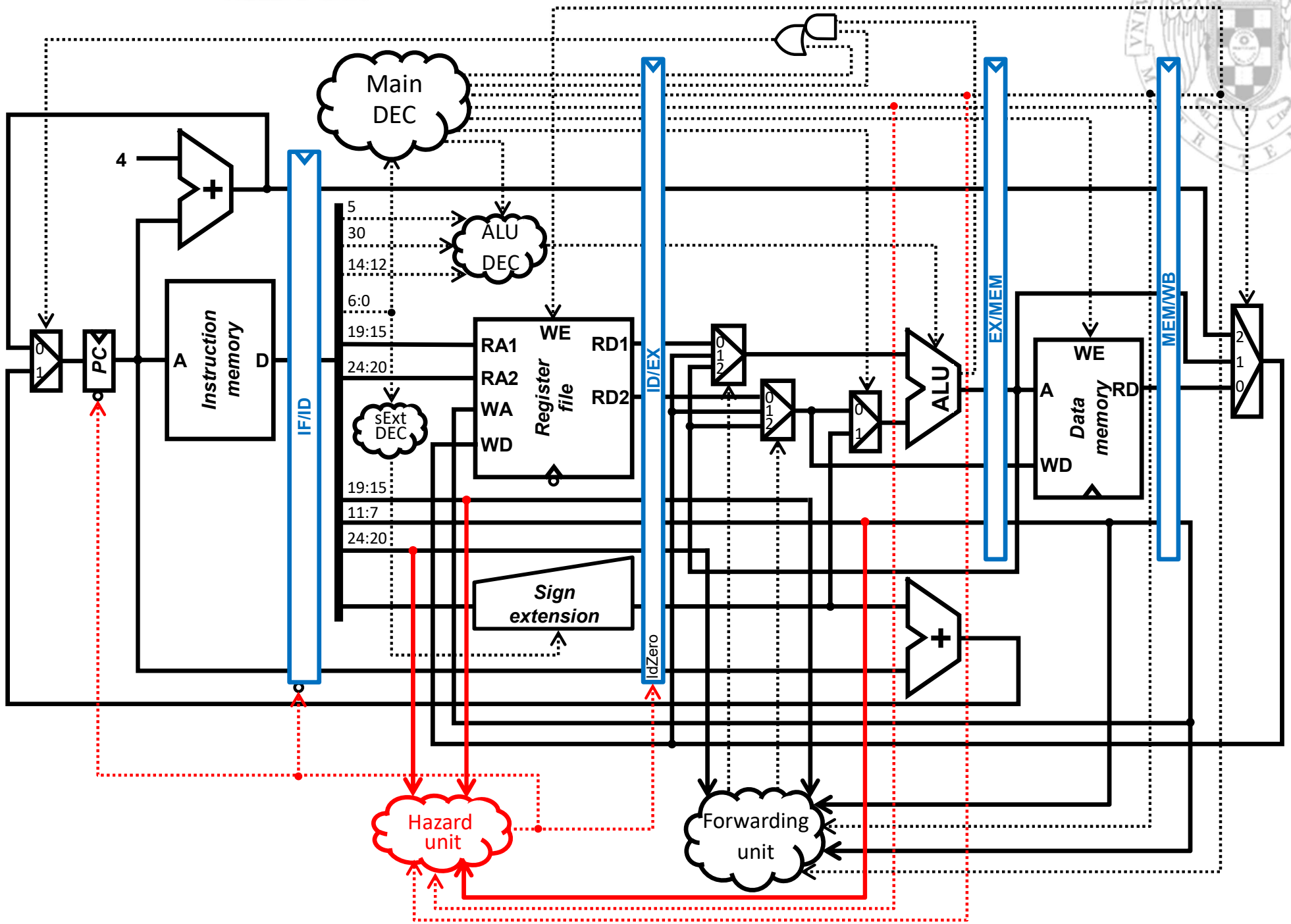



Pipelined processor

Hazard unit design (i)

- The pipeline must be stalled during one cycle due to a **1w** hazard if:
 - There is a **1w** instruction in the EX stage
 - Checking if ResSrcE = 0 and BRwrE = 1 (only **1w** meets this)

```
Stall ← if ( (ResSrcE = 0) & BRwrE ) then ( 1 ) ←..... Stall the pipeline
```



Pipelined processor

Hazard unit design (i)

- The pipeline must be stalled during one cycle due to a **lw** hazard if:
 - There is a **lw** instruction in the EX stage
 - Checking if $\text{ResSrcE} = \underline{0}$ and $\text{BRwrE} = 1$ (only **lw** meets this)
 - The destination register of the EX stage (RdE) coincides with one of the source registers of the ID stage (Rs1D and/or Rs2D).

Stall \leftarrow if (($\text{ResSrcE} = \underline{0}$) & BRwrE & (($\text{Rs1D} = \text{RdE}$) | ($\text{Rs2D} = \text{RdE}$))) then (1) \leftarrow Stall the pipeline



Pipelined processor

Hazard unit design (i)

- The pipeline must be stalled during one cycle due to a **1w** hazard if:
 - There is a **1w** instruction in the EX stage
 - Checking if $\text{ResSrcE} = \underline{0}$ and $\text{BRwrE} = 1$ (only **1w** meets this)
 - The destination register of the EX stage (RdE) coincides with one of the source registers of the ID stage (Rs1D and/or Rs2D).
- Otherwise, the pipeline is not stalled.

```
Stall ← if ( (ResSrcE = 0) & BRwrE & ((Rs1D = RdE) | (Rs2D = RdE)) ) then ( 1 ) ←..... Stall the pipeline
      else ( 0 ) ←..... Do not stall the pipeline
```



Pipelined processor

Hazard unit design (i)

- The pipeline must be stalled during one cycle due to a **1w** hazard if:
 - There is a **1w** instruction in the EX stage
 - Checking if $\text{ResSrcE} = \underline{0}$ and $\text{BRwrE} = 1$ (only **1w** meets this)
 - The destination register of the EX stage (RdE) coincides with one of the source registers of the ID stage (Rs1D and/or Rs2D).
- Otherwise, the pipeline is not stalled.
- When a stall happens:
 - Disable the load of the PC and the ID/IF pipeline register.

```

Stall  ← if ( (ResSrcE = 0) & BRwrE & ((Rs1D = RdE) | (Rs2D = RdE)) ) then ( 1 ) ←..... Stall the pipeline
        else
        ( 0 ) ←..... Do not stall the pipeline
StallF ← Stall
StallD ← Stall

```



Pipelined processor

Hazard unit design (i)

- The pipeline must be stalled during one cycle due to a **1w** hazard if:
 - There is a **1w** instruction in the EX stage
 - Checking if $\text{ResSrcE} = \underline{0}$ and $\text{BRwrE} = 1$ (only **1w** meets this)
 - The destination register of the EX stage (RdE) coincides with one of the source registers of the ID stage (Rs1D and/or Rs2D).
- Otherwise, the pipeline is not stalled.
- When a stall happens:
 - Disable the load of the PC and the ID/IF pipeline register.
 - Delete the ID/EX pipeline register.

```

Stall ← if ( (ResSrcE = 0) & BRwrE & ((Rs1D = RdE) | (Rs2D = RdE)) ) then ( 1 ) ←..... Stall the pipeline
      else
      ( 0 ) ←..... Do not stall the pipeline

```

StallF ← Stall

StallD ← Stall

FlushE ← Stall



Pipelined processor



Hazard unit design (ii)

$Stall \leftarrow if ((ResSrcE = 0) \& BRwrE \& ((Rs1D = RdE) | (Rs2D = RdE))) then (1)$
else (0)

$StallF \leftarrow Stall$

$StallD \leftarrow Stall$

$FlushE \leftarrow Stall$

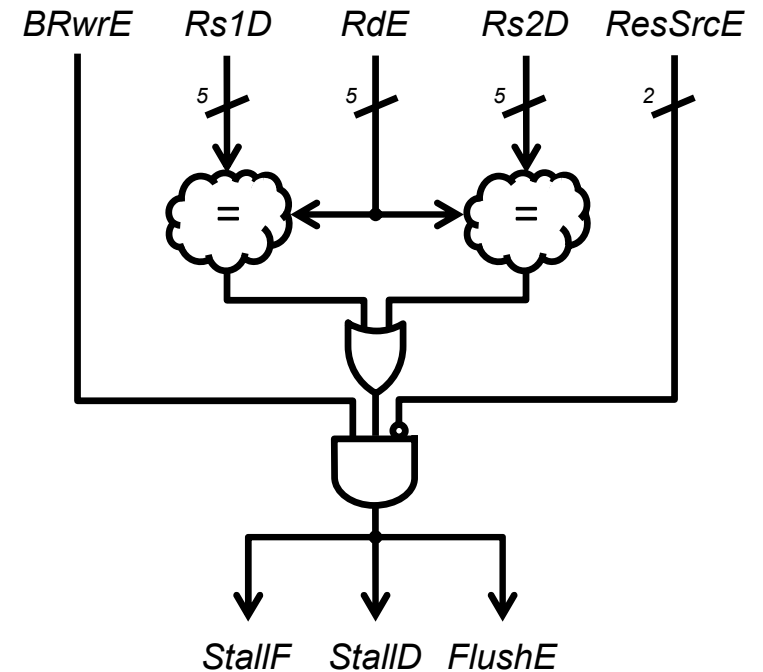 




Data hazards

HW solution: additional optimizations (i)

- The proposed solution sometimes performs **unnecessary stalls**.
- When **x0** is the destination register of the memory load.
 - Since instructions as **lw x0, 20(x1)** are meaningless, it is not worth adding the hardware logic to handle these cases.
- When a **lw** instruction is followed by a **sw** instruction that stores the register loaded from memory by the former.
 - It is a more common case because it is used e.g. to copy arrays.
 - The **data, available since cycle 5, could be forwarded** without stalling.

 



Data hazards

HW+SW solution: code reordering

- Given an assembly program, stalls due to data hazards by `lw` instructions are unavoidable by HW.
 - But they can be avoided by reordering the code, so that a `lw` instruction is never followed by another one that uses the loaded register.
 - This is one of the optimizations applied by the compilers.

```

...
int a, b, c;
int d, e;
...
c = a + b;
e = d + b;
...

```

```

a → x1    d → x4
b → x2    e → x5
c → x3

```

Assignment of variables

direct compilation

```

...
lw  x1, 0(x31)
lw  x2, 4(x31)
add x3, x1, x2
sw  x3, 8(x31)
lw  x4, 12(x31)
add x5, x4, x2
sw  x5, 16(x31)
...

```

2 stalls

optimized compilation

```

...
lw  x1, 0(x31)
lw  x2, 4(x31)
lw  x4, 12(x31)
add x3, x1, x2
sw  x3, 8(x31)
add x5, x4, x2
sw  x5, 16(x31)
...

```


0 stalls



Control hazards

HW solution: stalling

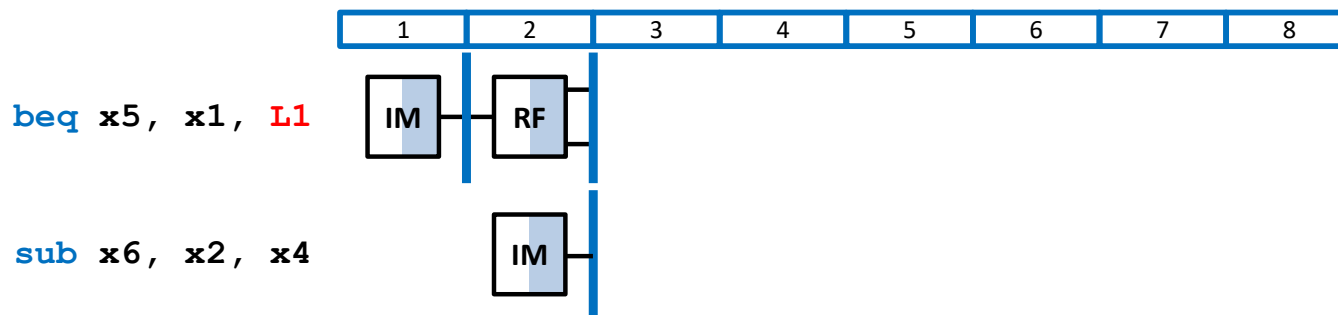- One solution consists in stalling the pipeline during 2 cycles to delay fetching new instructions until the branch is decided.
 - Cycle 2: `beq` (in ID), the control hazard is detected.






Control hazards

HW solution: stalling

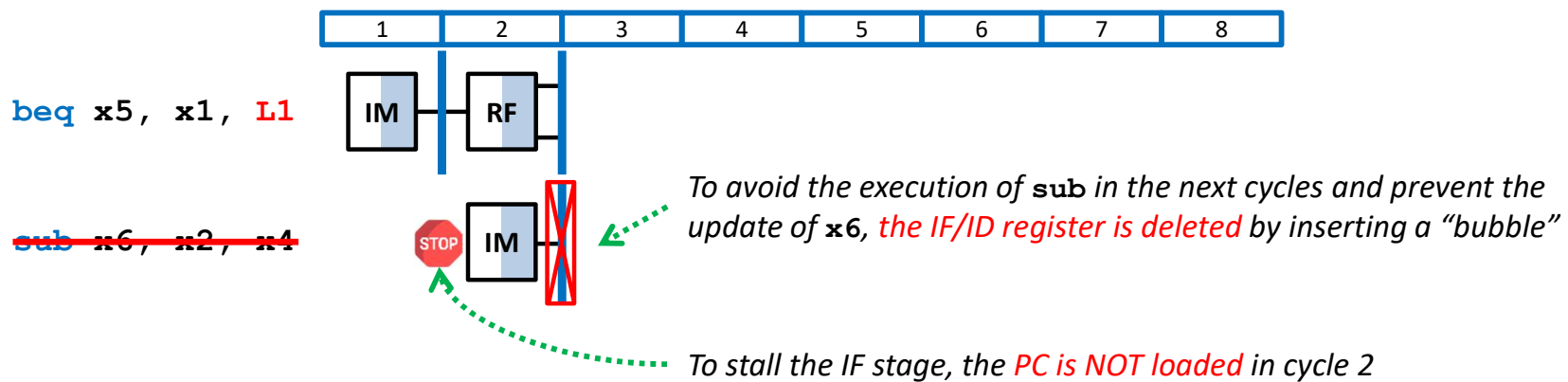- One solution consists in **stalling** the pipeline **during 2 cycles** to delay fetching new instructions until the branch is decided.
 - **Cycle 2:** `beq` (in ID), the control hazard is detected. The `sub` instruction is **stalled** and a nop “bubble” is inserted in the ID stage.






Control hazards

HW solution: stalling

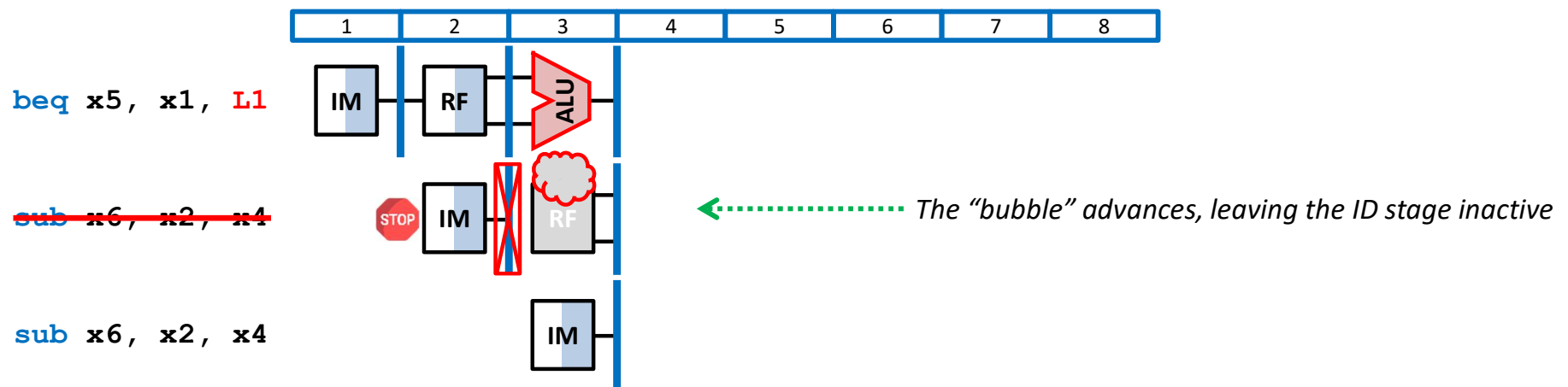- One solution consists in **stalling** the pipeline **during 2 cycles** to delay fetching new instructions until the branch is decided.
 - **Cycle 2:** `beq` (in ID), the control hazard is detected. The `sub` instruction is **stalled** and a nop “bubble” is inserted in the ID stage.
 - **Cycle 3:** `beq` (in EX) decides the branch, but the hazard continues.






Control hazards

HW solution: stalling

- One solution consists in **stalling** the pipeline **during 2 cycles** to delay fetching new instructions until the branch is decided.
 - **Cycle 2:** `beq` (in ID), the control hazard is detected. The `sub` instruction is **stalled** and a nop “bubble” is inserted in the ID stage.
 - **Cycle 3:** `beq` (in EX) decides the branch, but the hazard continues. The `sub` instruction **remains stalled** and another “bubble” is inserted.

 




Control hazards

HW solution: stalling

- One solution consists in **stalling** the pipeline **during 2 cycles** to delay fetching new instructions until the branch is decided.
 - Cycle 2:** `beq` (in ID), the control hazard is detected. The `sub` instruction is **stalled** and a nop “bubble” is inserted in the ID stage.
 - Cycle 3:** `beq` (in EX) decides the branch, but the hazard continues. The `sub` instruction **remains stalled** and another “bubble” is inserted.
 - Cycle 4:** `beq` (in MEM), **the appropriate instruction is fetched**.

 




Control hazards

HW solution: stalling

- One solution consists in **stalling** the pipeline **during 2 cycles** to delay fetching new instructions until the branch is decided.
 - Cycle 2:** `beq` (in ID), the control hazard is detected. The `sub` instruction is **stalled** and a nop “bubble” is inserted in the ID stage.
 - Cycle 3:** `beq` (in EX) decides the branch, but the hazard continues. The `sub` **instruction remains stalled** and another “bubble” is inserted.
 - Cycle 4:** `beq` (in MEM), **the appropriate instruction is fetched**.
 - There is a **penalty of two cycles** per **branch instruction**.

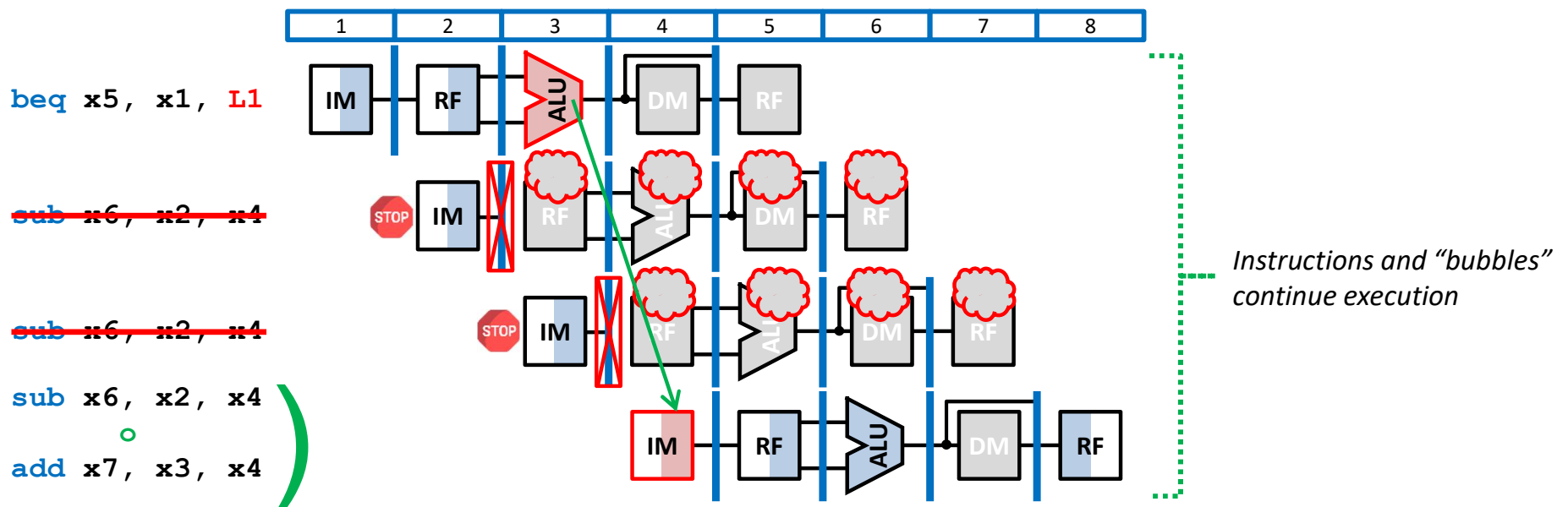



Control hazards



HW solution: branch prediction (i)

- There is a better solution for `beq` instructions, which consists in predicting that the branch will not be taken.
 - The `beq` instruction and the following ones are fetched as normal.
 - When the branch address/decision is known (`beq` will be in the EX stage):
 - If the branch is not taken, do nothing.
 - If the branch is taken, the last 2 fetched instructions are flushed, inserting nop “bubbles” in the ID and EX stages.
 - In the next cycle (`beq` will be in MEM), the appropriate instruction is fetched.
 - There is a penalty of two cycles per taken branch instruction. No penalty if the branch is not taken.
- The opposite operation, i.e. , to predict that the branch is taken, is much more complex since this also requires to predict the destination address.



Control hazards



HW solution: branch prediction (ii)

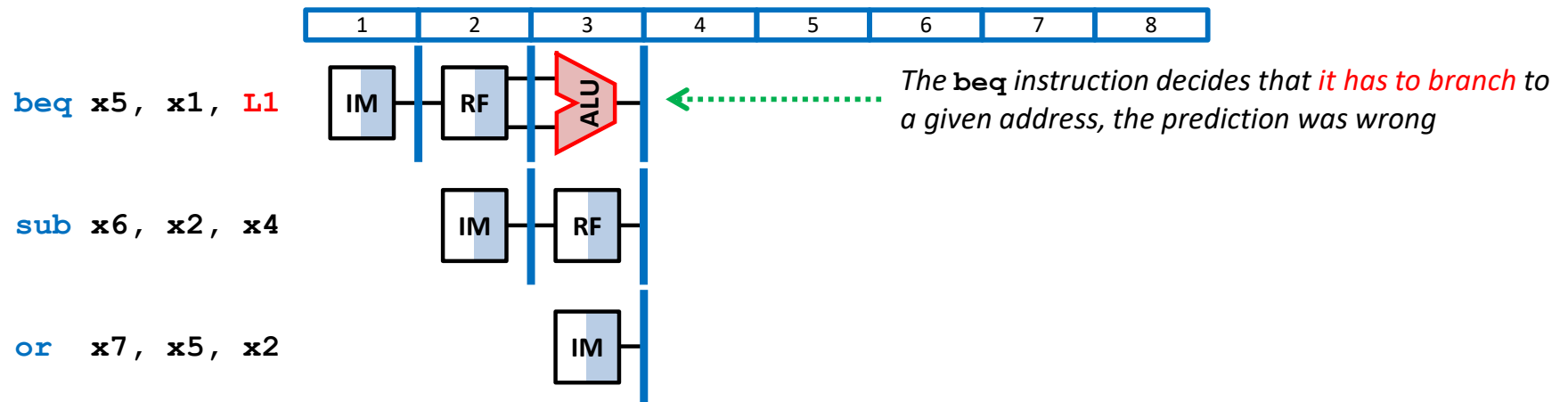 



Control hazards



HW solution: branch prediction (ii)

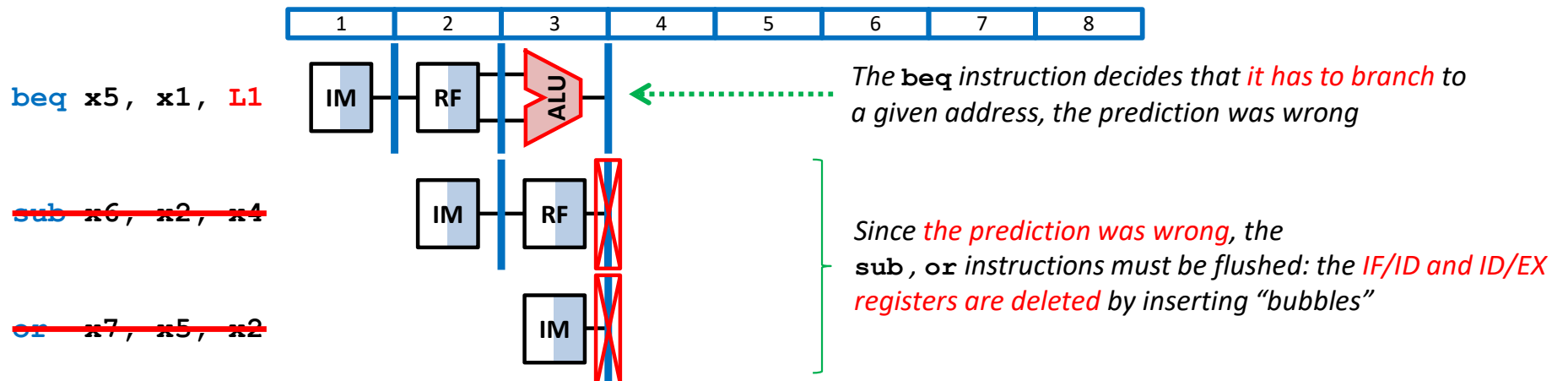 



Control hazards



HW solution: branch prediction (ii)

 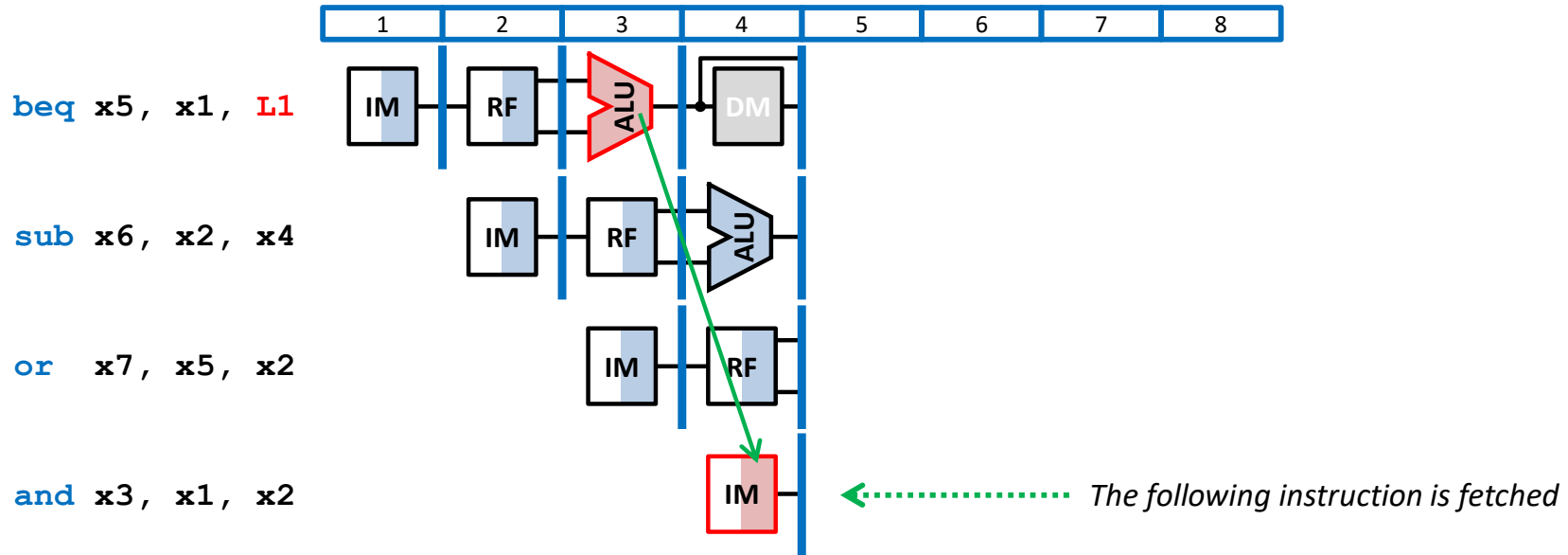



Control hazards

HW solution: branch prediction (ii)

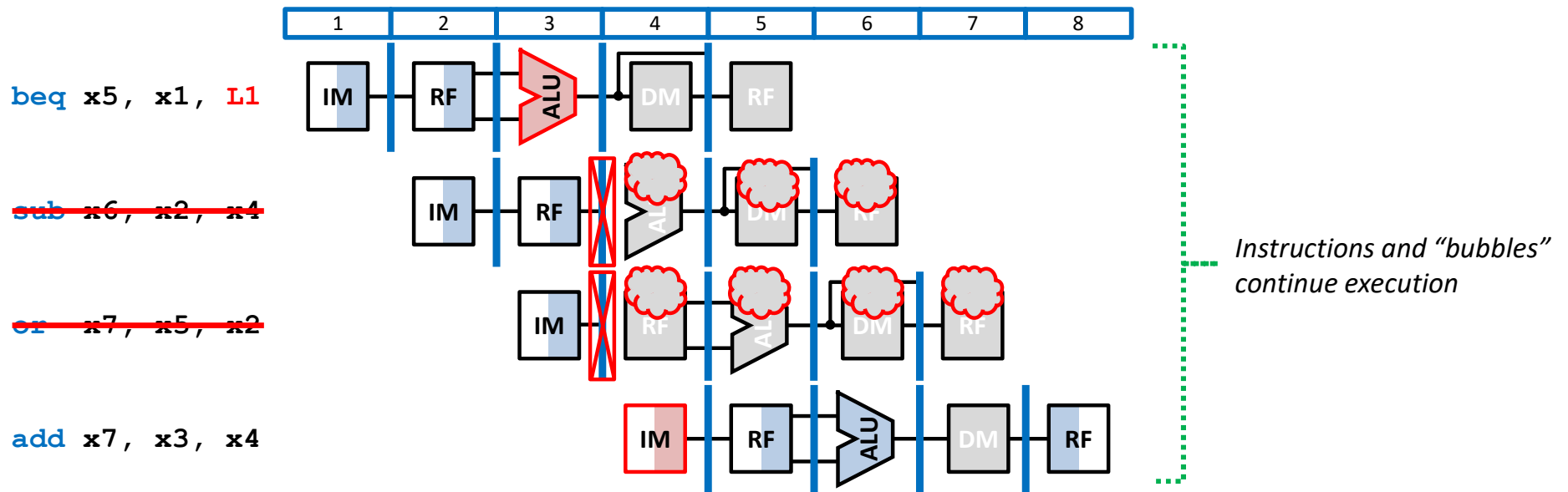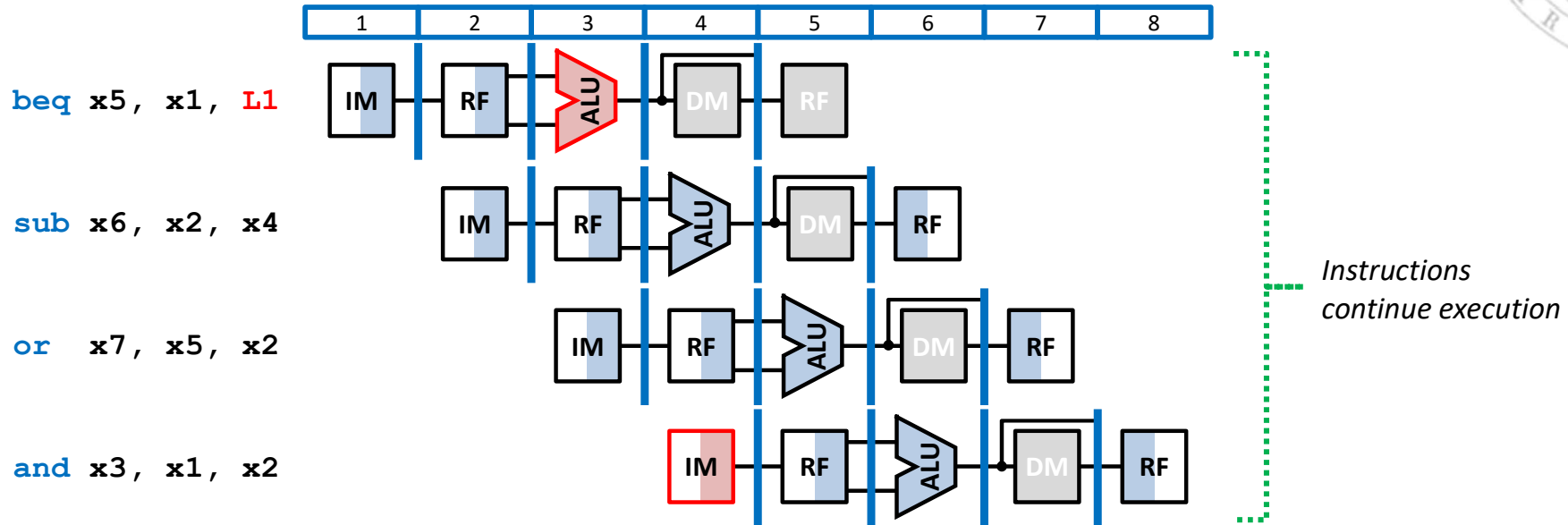


L1: `add x7, x3, x4`



Control hazards

HW solution: branch prediction (iii)

- For **jal** instructions (which always branch), **predicting that the branch is not taken** is always wrong, but it is used because:
 - The **penalty is the same** as stalling the pipeline.
 - **No additional logic** to the one needed for **beq** is needed.
 - Implicitly, this **solves a special kind of data hazard**.
 - The **jal** instruction stores PC+4 in **x1** during the WB stage, a value that is not in the ALU and therefore it cannot be forwarded using the designed data path.
 - Thanks to the 2-cycle delay, the updated value of **x1** can be read from the RF.

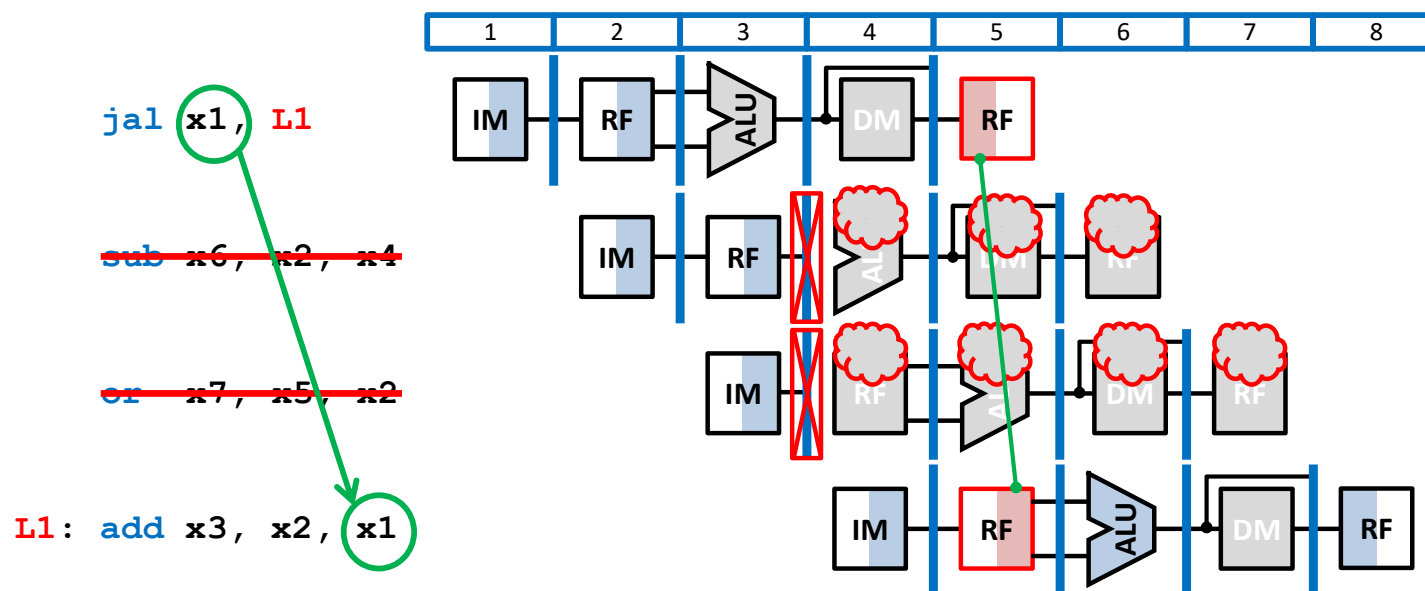




Control hazards


HW solution: branch prediction (iv)

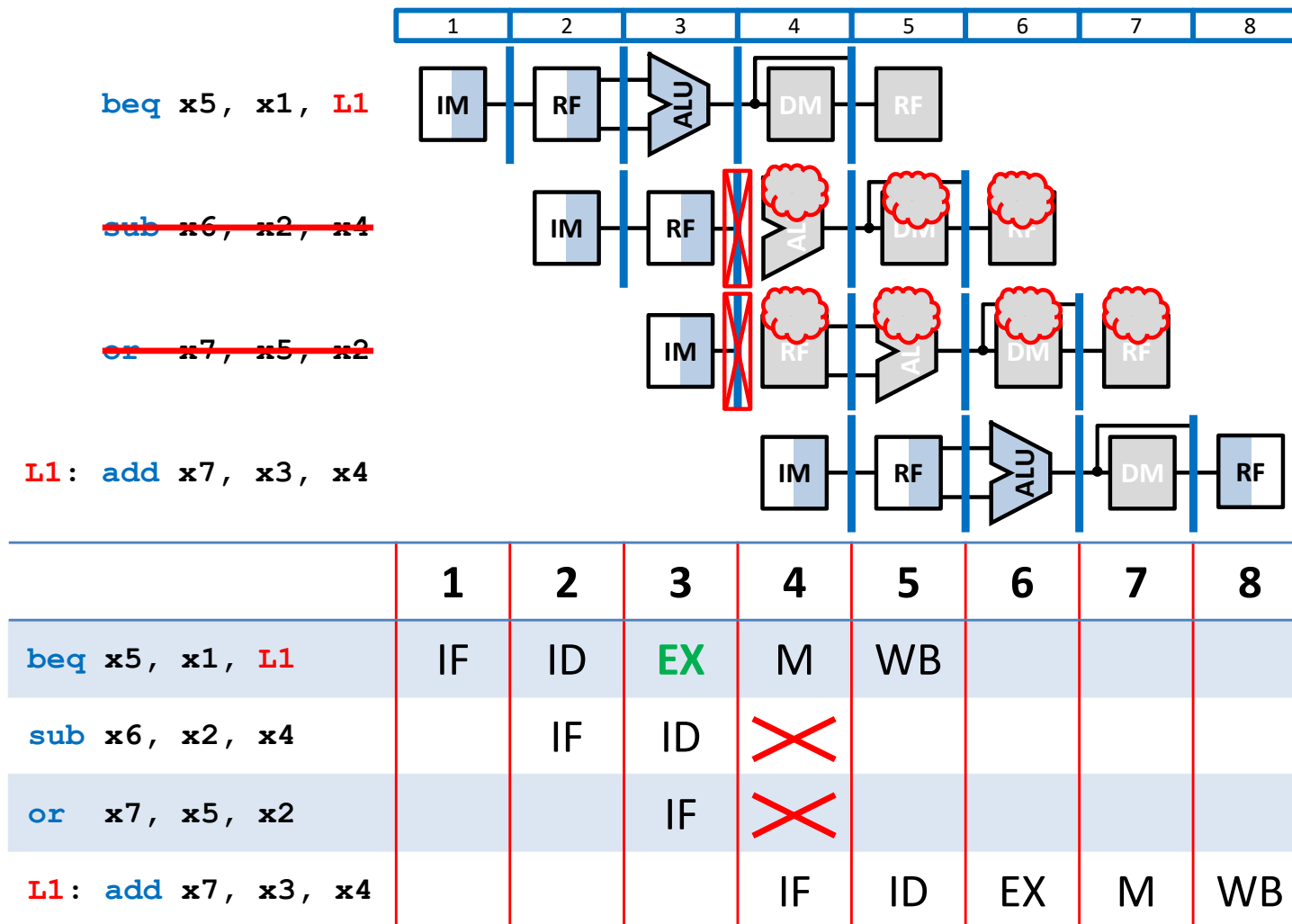- In the **simplified execution diagrams**, the flushed instructions are marked explicitly:




Pipelined processor

+ branch prediction: data path

 

27/10/23 version

module 7:
Pipelined processor design

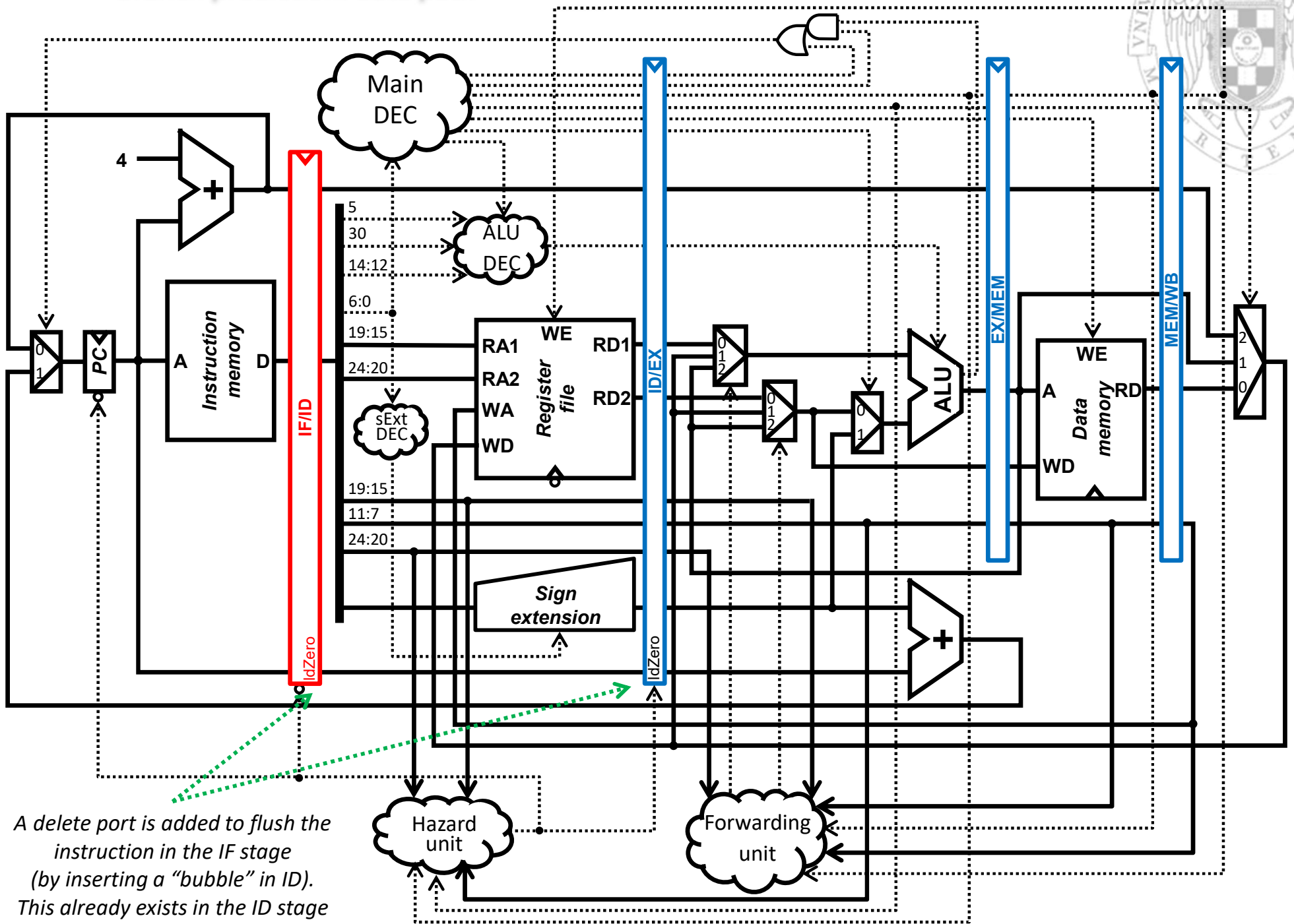


A delete port is added to flush the instruction in the IF stage (by inserting a "bubble" in ID). This already exists in the ID stage



Pipelined processor

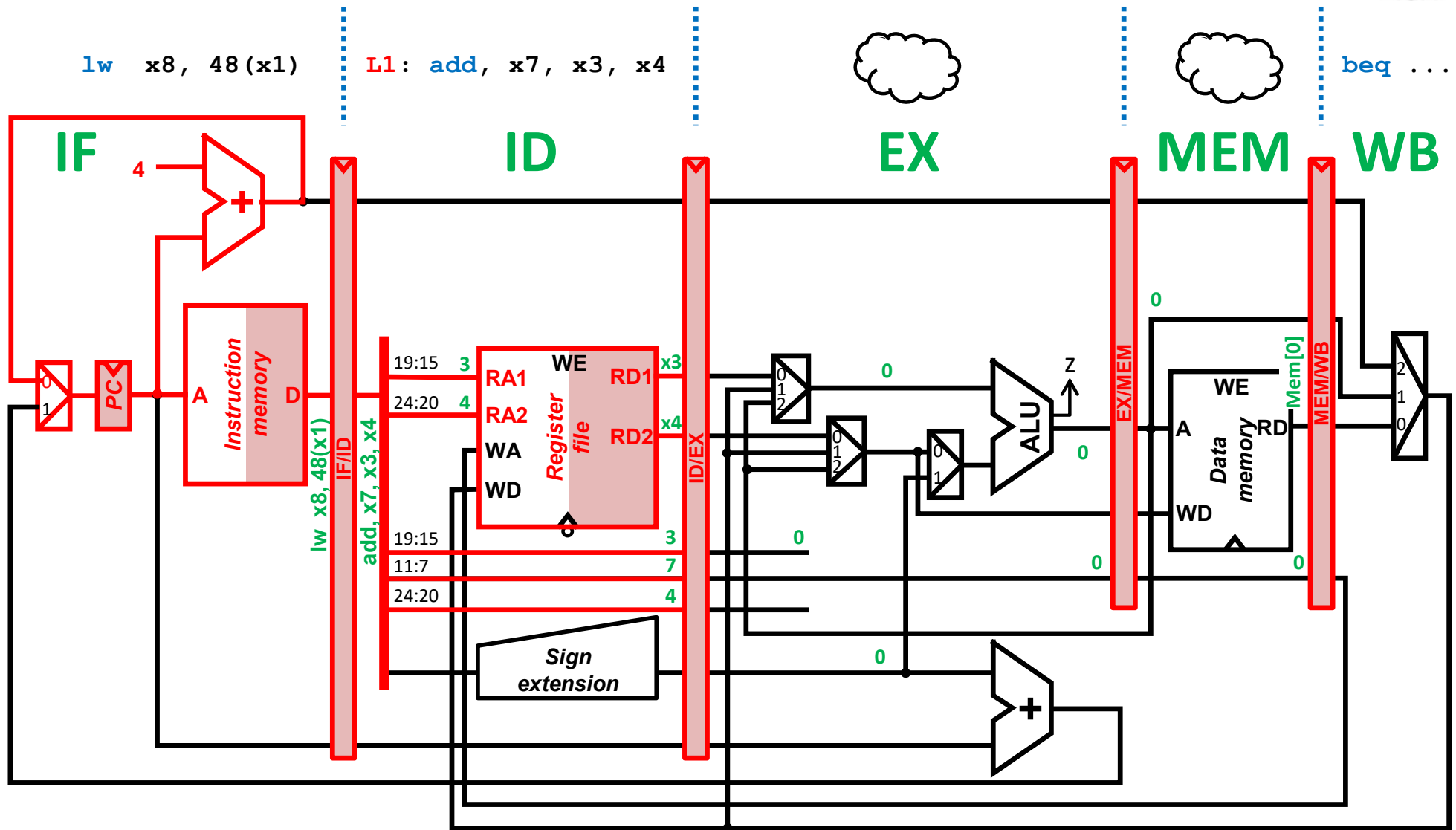Wrong branch prediction simulation: 5th. cycle





Pipelined processor

Extended hazard unit design (i)

- The **hazard unit** is extended in order to flush the instructions in the IF and ID stages if a branch has to be taken:
 - The IF/ID and ID/EX pipeline registers are deleted.
- In order to behave correctly, **it must know**:
 - **PCsrcE**: it is only active if the instruction in the EX stage is a branch and it has to be taken.

```
Stall ← if ( (ResSrcE = 0) & BRwrE & ((Rs1D = RdE) | (Rs2D = RdE)) ) then ( 1 )  
      else ( 0 )
```

```
StallF ← Stall
```

```
StallD ← Stall
```

```
FlushE ← Stall | PCsrcE
```

←..... The ID/EX pipeline register is deleted

```
FlushD ← PCsrcE
```

←..... The IF/ID pipeline register is deleted



Pipelined processor

Extended hazard unit design (ii)

```

Stall ← if ( (ResSrcE = 0) & BRwrE & ((Rs1D = RdE) | (Rs2D = RdE)) ) then ( 1 )
      else ( 0 )



```

StallF ← Stall

StallD ← Stall


FlushE ← Stall | PCsrcE

FlushD ← PCsrcE

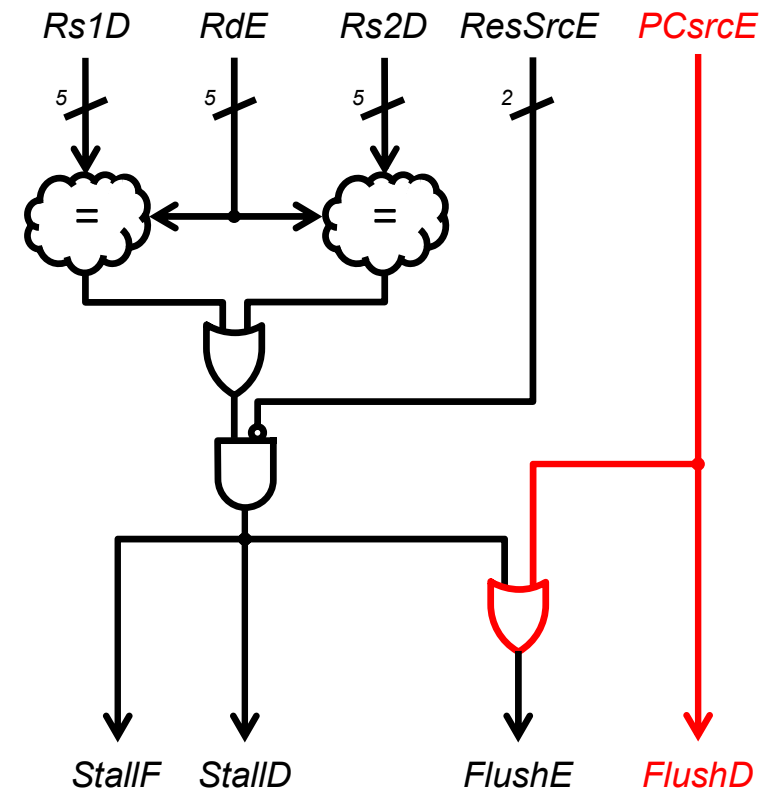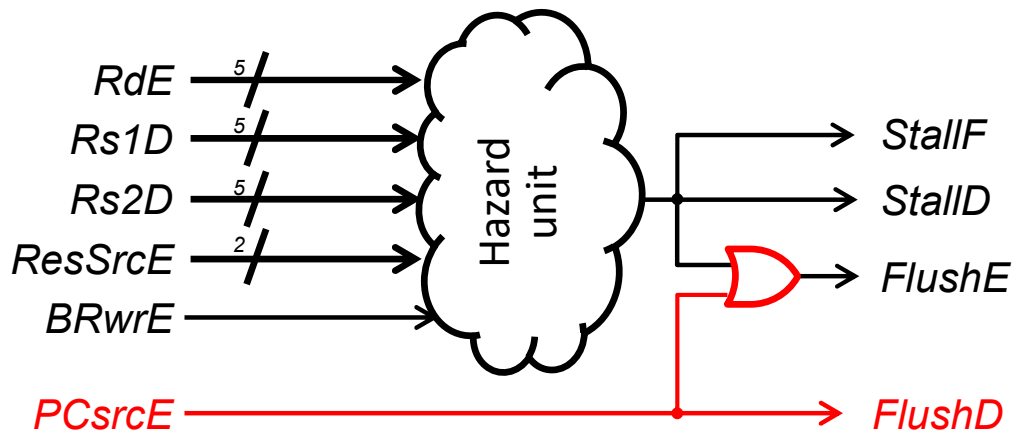


Pipelined processor

+ branch prediction: control signals

 

27/10/23 version


module 7:
Pipelined processor design

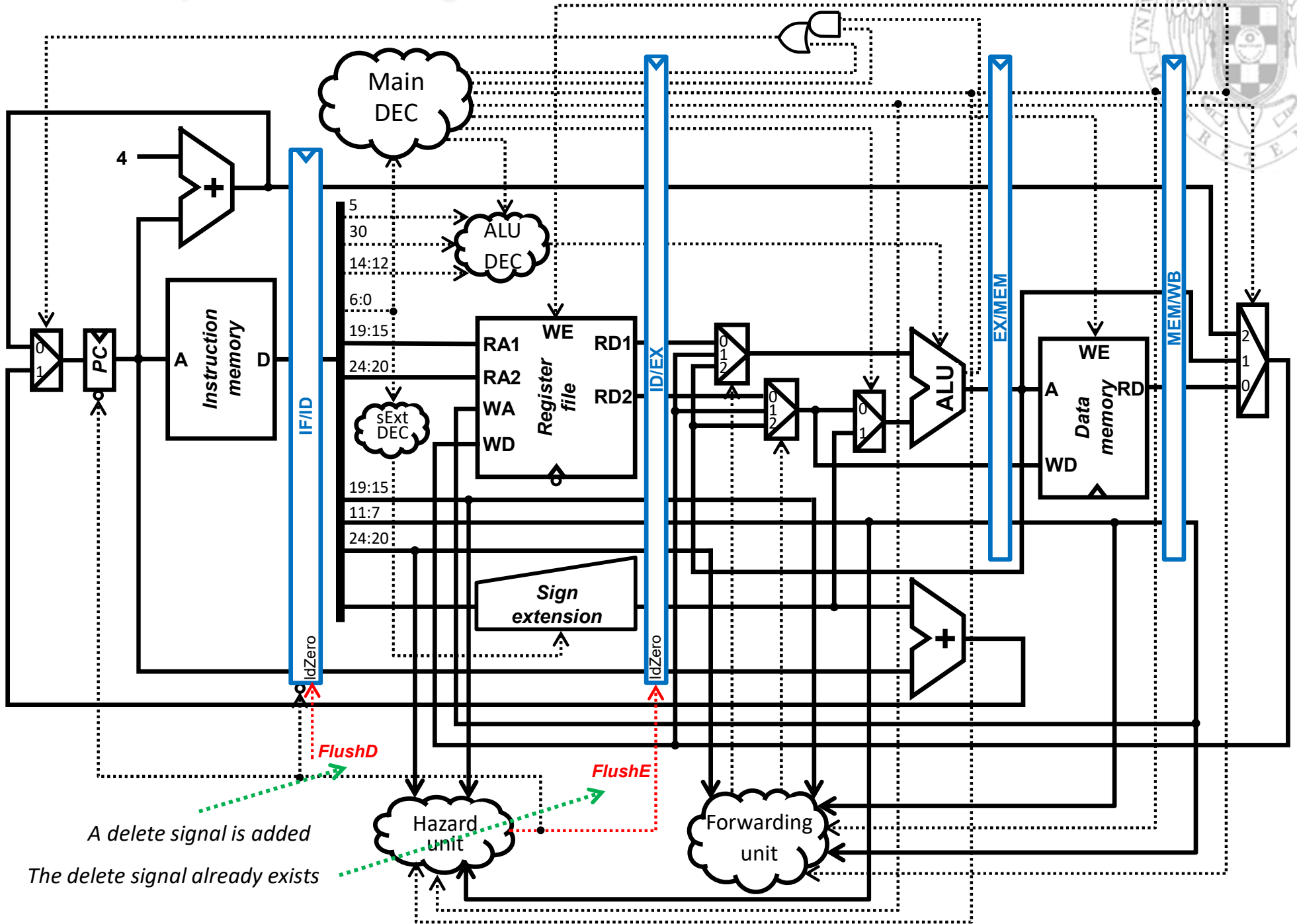

A delete signal is added
The delete signal already exists


Pipelined processor

+ branch prediction: status signals

 

27/10/23 version


module 7:
Pipelined processor design

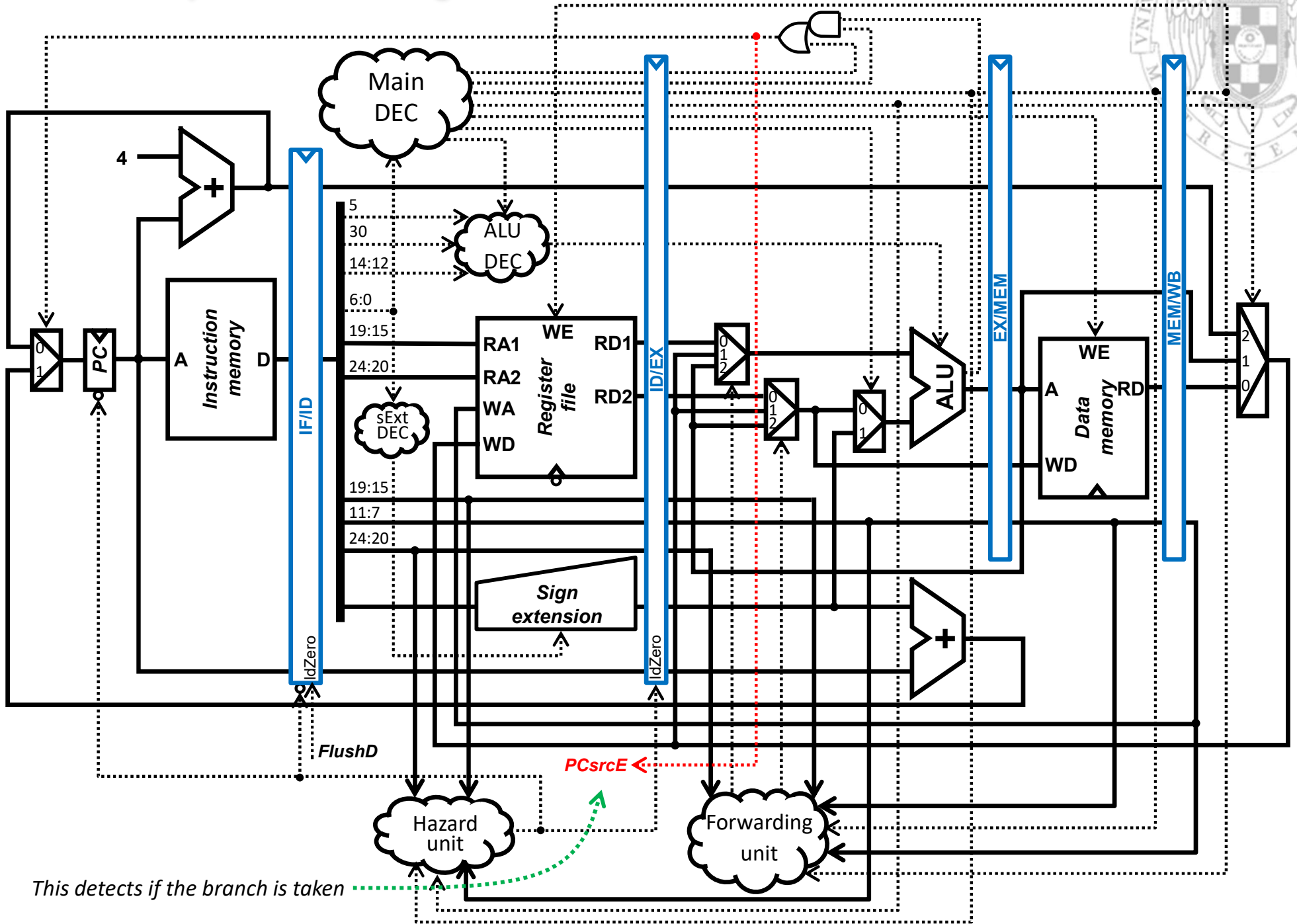

This detects if the branch is taken

Pipelined processor

With full hazard management

 


27/10/23 version

module 7:
Pipelined processor design

FC-2

130

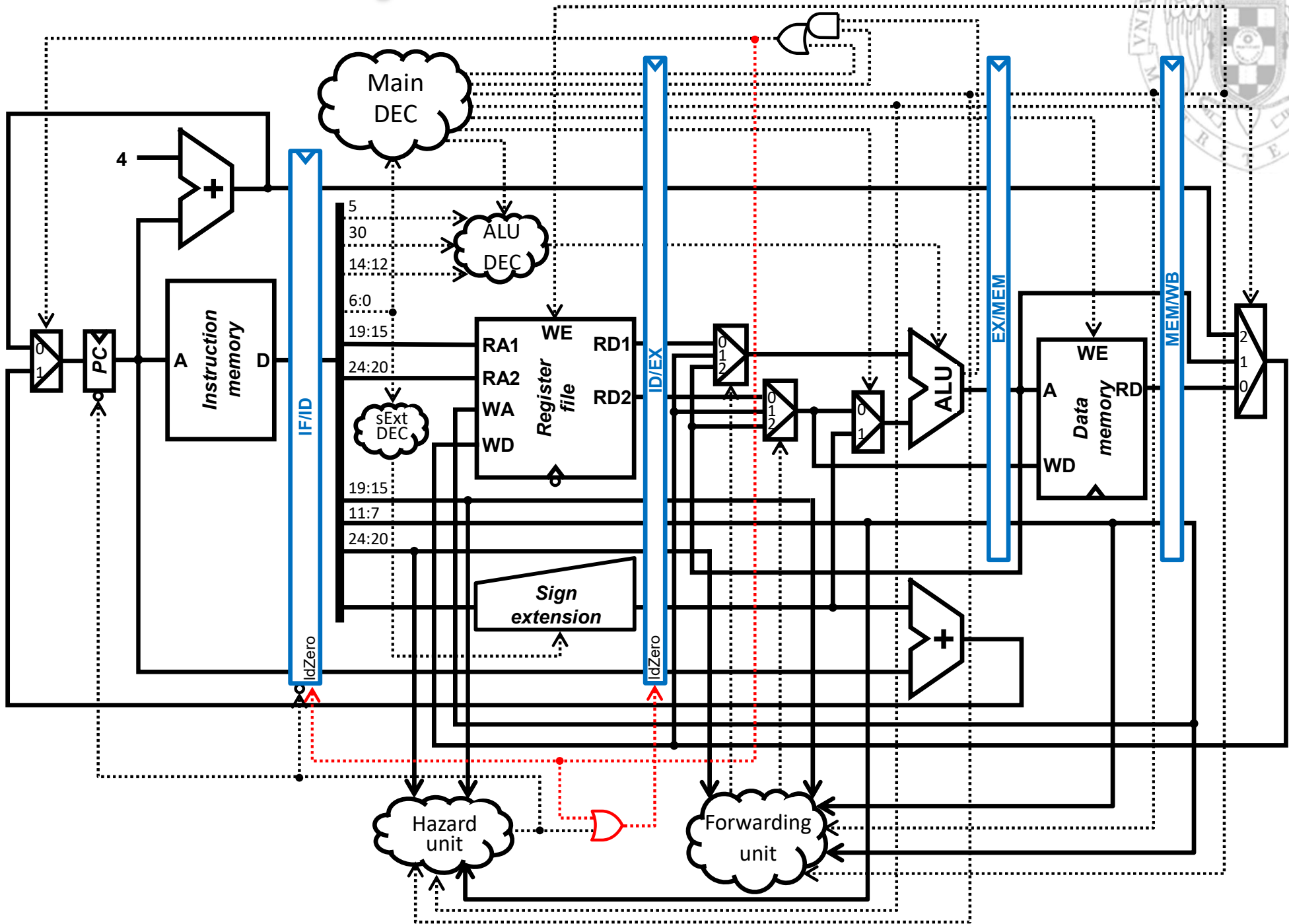



Pipelined processor

SW vs. HW hazard management

Hazard type	Involved instructions	Penalty (cycles)		Implemented HW solution
		SW	HW	
Structural	<i>(this does not exist)</i>	-	-	-
Data	add/i-like → others	1, 2 or 3	0	<i>forwarding</i>
	lw → add/i-like	1, 2 or 3	1	<i>stall + forwarding (avoidable by code reordering)</i>
	lw → lw	1, 2 or 3	1	<i>stall + forwarding (avoidable by code reordering)</i>
	lw → sw	1, 2 or 3	1	<i>stall + forwarding (avoidable by optimized forwarding)</i>
Control	beq	2	0 or 2	<i>branch prediction</i>
	jal	2	2	<i>branch prediction</i>



Pipelined processor


Cost and cycle time (CMOS 90 nm)

$$area = 77,018 \mu m^2$$

$$t_{clk} = 10.5 \text{ ns}$$

$$f_{clk} = \frac{1}{t_{clk}} = \frac{1}{10.5 \cdot 10^{-6} \text{ s}} = 95 \text{ MHz}$$

stage	critical path
IF	8,890 ps
ID	$\frac{1}{2}t_{clk} + 723 \text{ ps}$
EX	10,541 ps
MEM	8,667 ps
WB	1,122 ps
max.	10,541 ps

 

- Ideal pipelined CPI: without hazard penalty (CPI = 1).

$$CPI = 1$$

$$t_{exec} = 10^8 \cdot 1 \cdot 10.5 \text{ ns} = 1.05 \text{ s}$$

$$MIPS = 10^8 / (10^6 \cdot 1.05 \text{ s}) = 95.2 \text{ Minst/s}$$



Pipelined processor

Performance metrics

- Given a program that executes 10^8 instructions (100 million) so that:
 - 25% of the instructions are **lw**
 - 40% are followed by an instruction that needs the loaded value: 1-cycle stall.
 - 10% of the instructions are **sw**
 - 11% of the instructions are **beq**
 - 50% are taken branches: wrong prediction and 2 instructions are flushed.
 - 2% of the instructions are **jal**
 - 52% of the instructions are **arithmetic-logic**
- Actual pipelined CPI: with hazard penalty ($CPI > 1$).
 - **lw**: 1/2 cycles, **beq**: 1/3 cycles, **jal**: 3 cycles, **other**: 1 cycle

$$\begin{aligned}
 \mathbf{CPI} &= 0.25 \cdot (0.6 \cdot 1 + 0.4 \cdot 2) && \leftarrow \text{lw instructions} \\
 &+ 0.10 \cdot 1 && \leftarrow \text{sw instructions} \\
 &+ 0.11 \cdot (0.5 \cdot 1 + 0.5 \cdot 3) && \leftarrow \text{beq instructions} \\
 &+ 0.02 \cdot 3 && \leftarrow \text{jal instructions} \\
 &+ 0.52 \cdot 1 = \mathbf{1.25} && \leftarrow \text{Arithmetic-logic instructions}
 \end{aligned}$$

$$t_{exec} = 10^8 \cdot 1.25 \cdot 10.5 \text{ ns} = \mathbf{1.31 \text{ s}}$$

$$\mathbf{MIPS} = 10^8 / (10^6 \cdot 1.43 \text{ s}) = \mathbf{76.2 \text{ Minst/s}}$$




Comparison

Reduced RISC-V: single-cycle vs. multicycle vs. pipelined

- The **pipelined processor** is more expensive, but it has better performance

Processor	t_{clk} (ns)	CPI	Cost (μm^2)	t_{exec} (s)	↑ cost	Speedup
Single-cycle	27.6	1	59,181	2.76	1	1
Multicycle	9.8	4.14	65,626	4.06	1.12	0.68
Pipelined	10.5	1.25	77,018	1.31	1.30	2.11

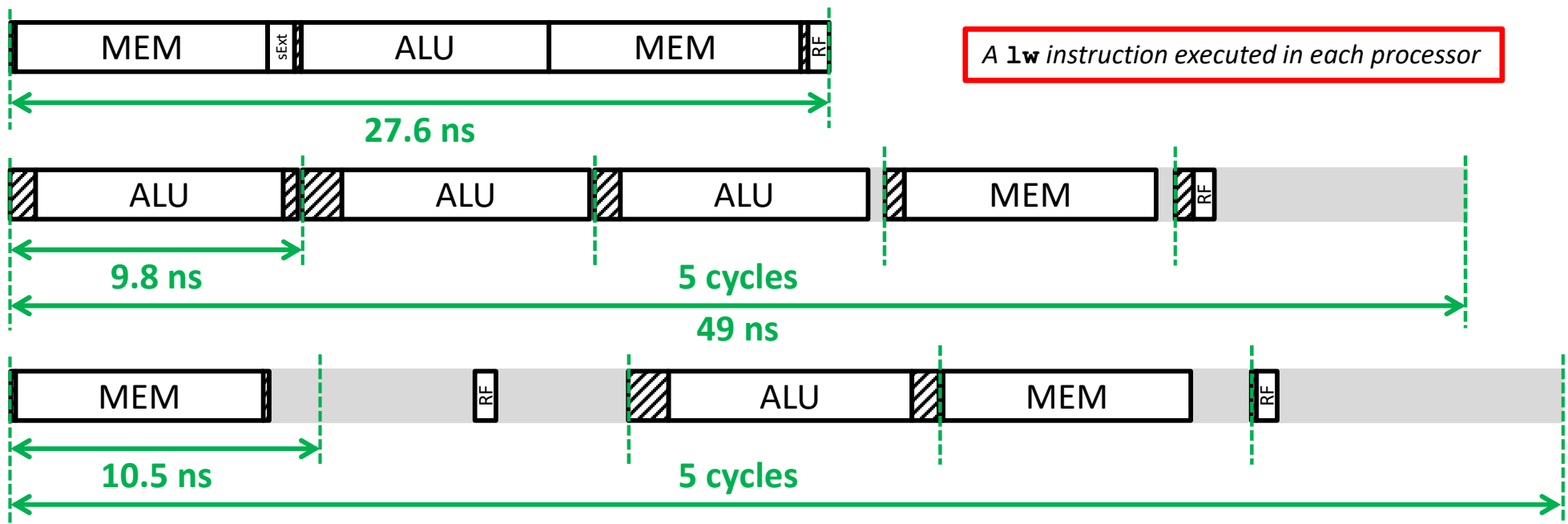



Advanced microarchitectures

Superscalar processors


27/10/23 version

module 7:
Pipelined processor design

FC-2

135

 - A **superscalar processor** contains **several copies** of the data path:
 - It executes in **parallel** several instructions of the **same program/thread**.
 - A **superscalar processor with 2 ways**:
 - Has 2 ALUs, and the RF and the memory have duplicated ports.
 - Fetches 2 instructions per cycle (ideal CPI = $\frac{1}{2}$).




- The data/control hazard probability increases:
 - To reduce it, **it executes instructions in an order different** from the one in which they are written in the program (out of order), making sure the result is correct



Advanced microarchitectures

Multicore processors

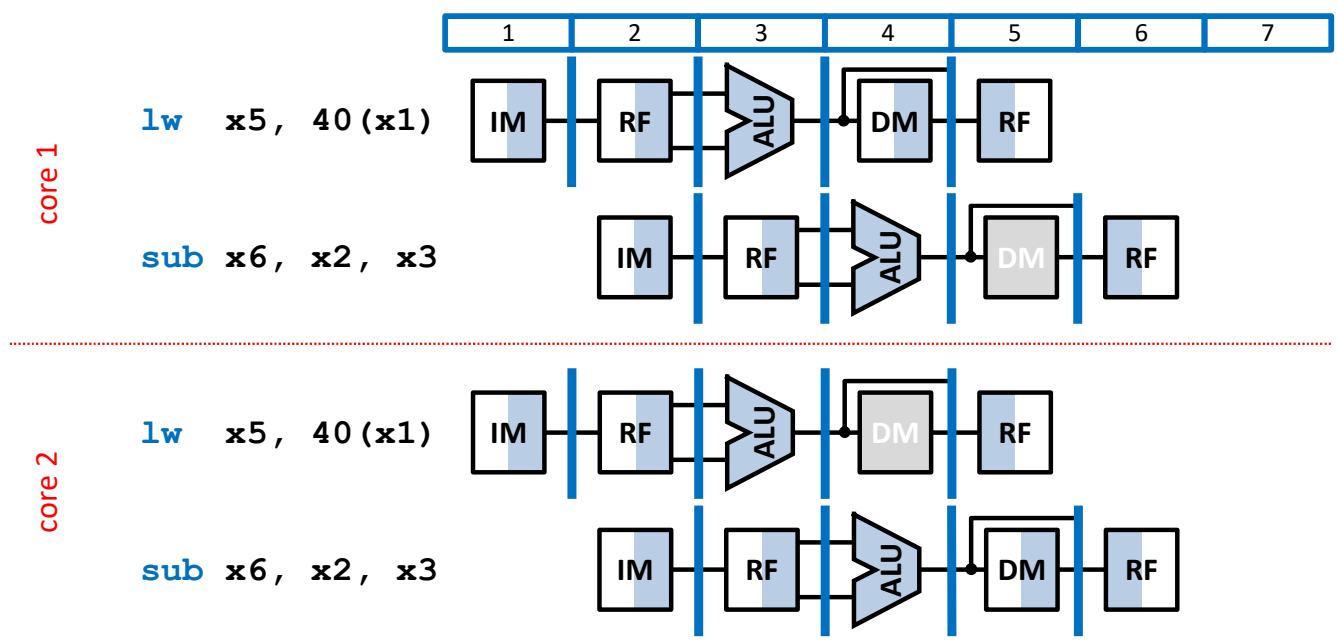- A **multicore processor** contains several copies of the full processor:
 - It executes in parallel several instructions of different programs/threads.
 - A **dual core processor**:
 - Has 2 full pipelined processors that share the memory.
 - Fetches 2 instructions per cycle (ideal CPI = 1/2).



- Each **core** may also be a **superscalar**:
 - A dual core superscalar with 2 ways, fetches 4 instructions per cycle (ideal CPI = 1/4).

Advanced microarchitectures

Intel processors




Microprocessor	Year	f_{clk} (MHz)	# Stages	# Ways	Out of order	# cores
486	1989	25	5	1	No	1
Pentium	1993	66	5	2	No	1
Pentium Pro	1997	200	10	3	Yes	1
Pentium 4 Willamette	2001	2000	22	3	Yes	1
Pentium 4 Prescott	2004	3600	31	3	Yes	1
Core	2006	3600	14	4	Yes	2
Core i7 Nehalem	2008	3600	14	4	Yes	2-4
Core Westmere	2010	3730	14	4	Yes	6
Core i7 Ivy Bridge	2012	3400	14	4	Yes	6
Core Broadwell	2014	3700	14	4	Yes	10
Core i9 Skylake	2016	3100	14	4	Yes	14
Ice Lake	2018	4200	14	4	Yes	16

source: A.A. Patterson & J.L. Hennessy, Computer Organization and Design, RISC-V Edition (2nd. edition). (2021)

- Cost calculation.
- Cycle time calculation.

Technology

 



Cost and cycle time calculation

90 nm CMOS






27/10/23 version




module 7:
Pipelined processor design

FC-2




139

   

area: 3,052 μm^2
delay: 8,360 ps

   

area: 202 μm^2
delay: 460 ps

   

area: 51,405 μm^2
read delay: 723 ps
write setup: 705 ps
(due to the DEC address)




Cost and cycle time calculation


CMOS 90 nm



 
Idealized behavior: delay comparable to the one of the ALU
(so that it can be read in one clock cycle)




area: -
access time: 8,500 ps

 

area: -
access time: 8,500 ps

 

 area: $32 \times 11.05 + 32 \times 32.26 = 1386 \mu\text{m}^2$
CLK→Q delay: 167 ps
setup: $1 \times 223 = 223 \text{ ps}$ (due to the load MUX)



area: $56 \mu\text{m}^2$
delay: 490 ps



area: $65 \mu\text{m}^2$
delay: 451 ps



area: $21 \mu\text{m}^2$
delay: 451 ps



area: $15 \mu\text{m}^2$
delay: 351 ps




Cost and cycle time calculation


CMOS 90 nm




27/10/23 version

 

 
area: $96 \times 11.05 + 96 \times 32.26 = 4,158 \mu\text{m}^2$
CLK→Q delay: 167 ps
setup: $1 \times 223 = 223 \text{ ps}$ (due to the load MUX)



 area: $185 \times 32.26 = 5,968 \mu\text{m}^2$
CLK→Q delay: $1 \times 167 = 167 \text{ ps}$
setup: 0 ps



 area: $105 \times 24.88 = 2,612 \mu\text{m}^2$
CLK→Q delay: 167 ps
setup: 0 ps




area: $104 \times 24.88 = 2,588 \mu\text{m}^2$
CLK→Q delay: 167 ps
setup: 0 ps



Hazard unit
area: 195 μm^2
delay: 881 ps




area: 7 μm^2
delay: 171 ps

 

Forwarding unit
area: 418 μm^2
delay: 744 ps

Cycle time calculation

IF stage: critical path

 


27/10/23 version

module 7:
Pipelined processor design

FC-2


143

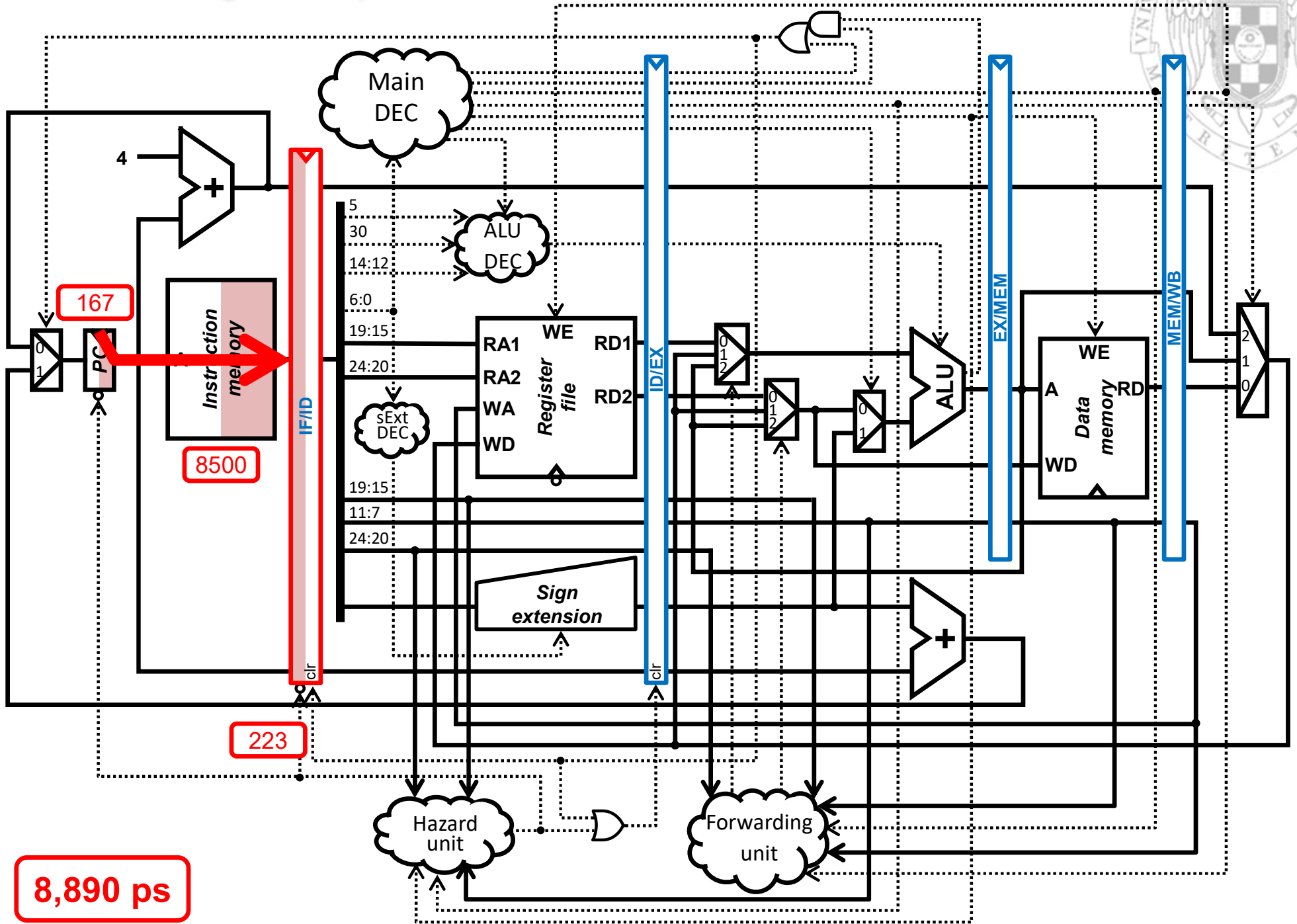

8,890 ps

Cycle time calculation

ID stage: critical path

 


27/10/23 version

module 7:
Pipelined processor design

FC-2


144

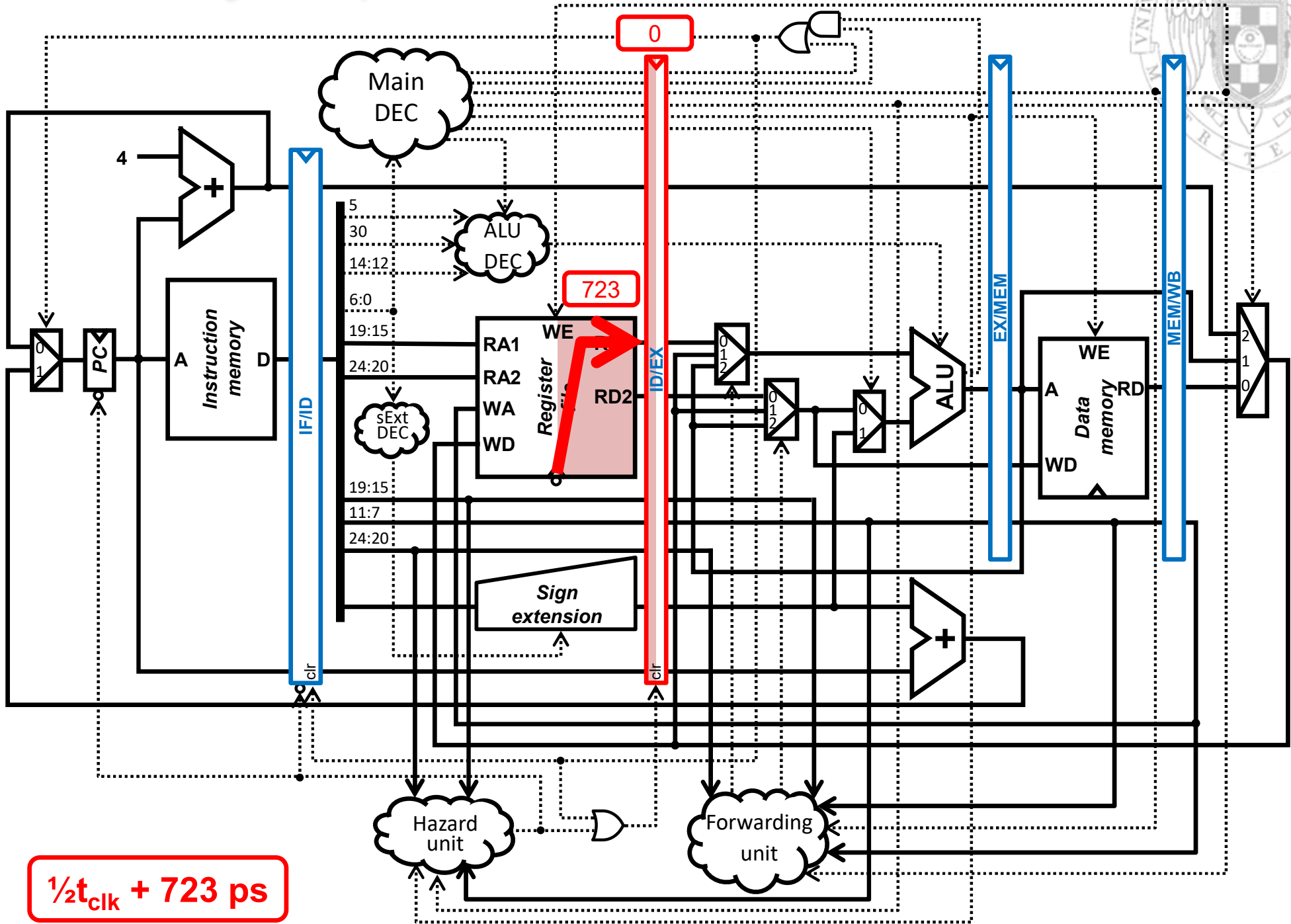


$\frac{1}{2}t_{clk} + 723 \text{ ps}$

Cycle time calculation

EX stage: critical path

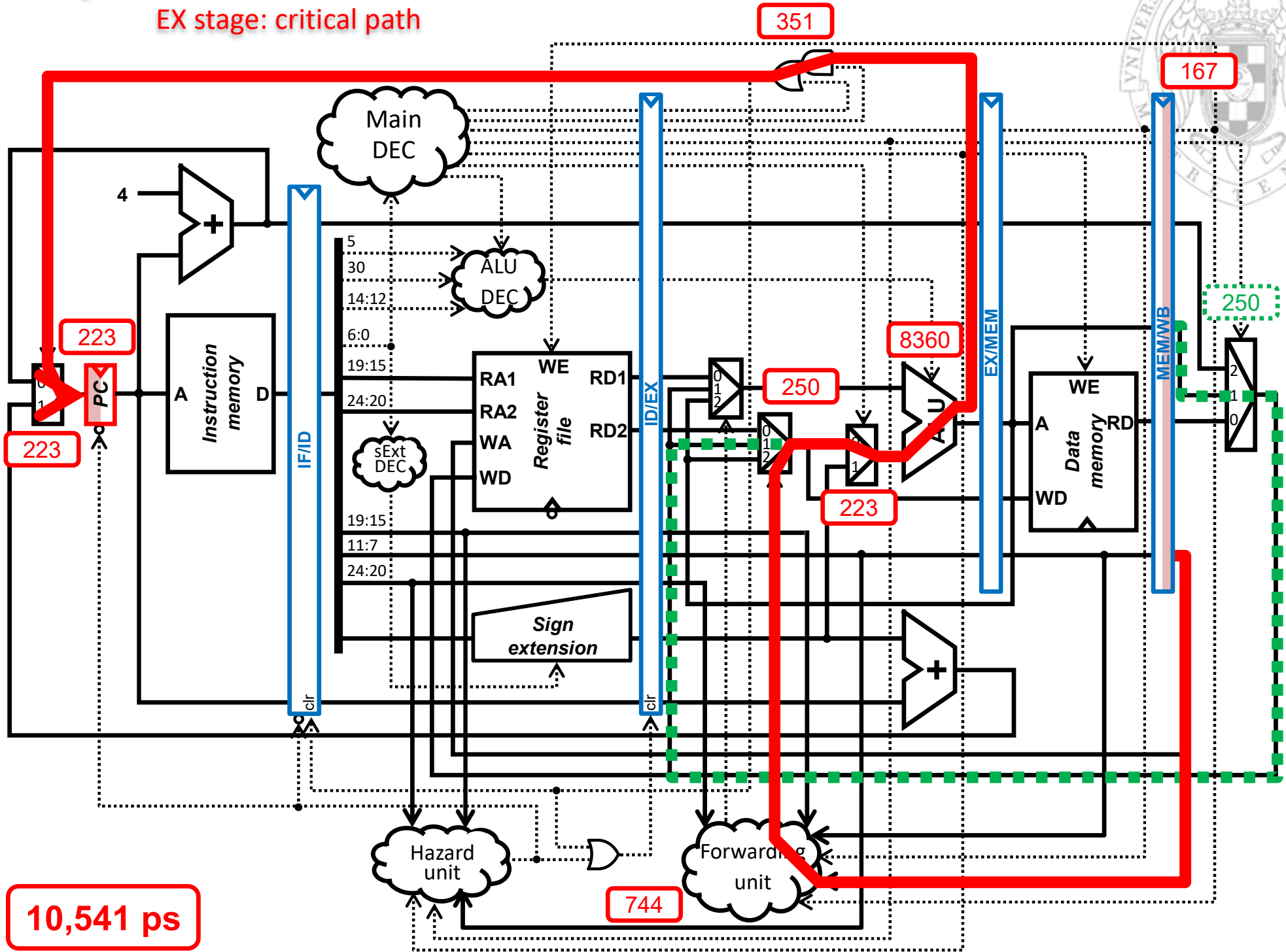


10,541 ps

 

Cycle time calculation

MEM stage: critical path

 


27/10/23 version

module 7:
Pipelined processor design

FC-2


146

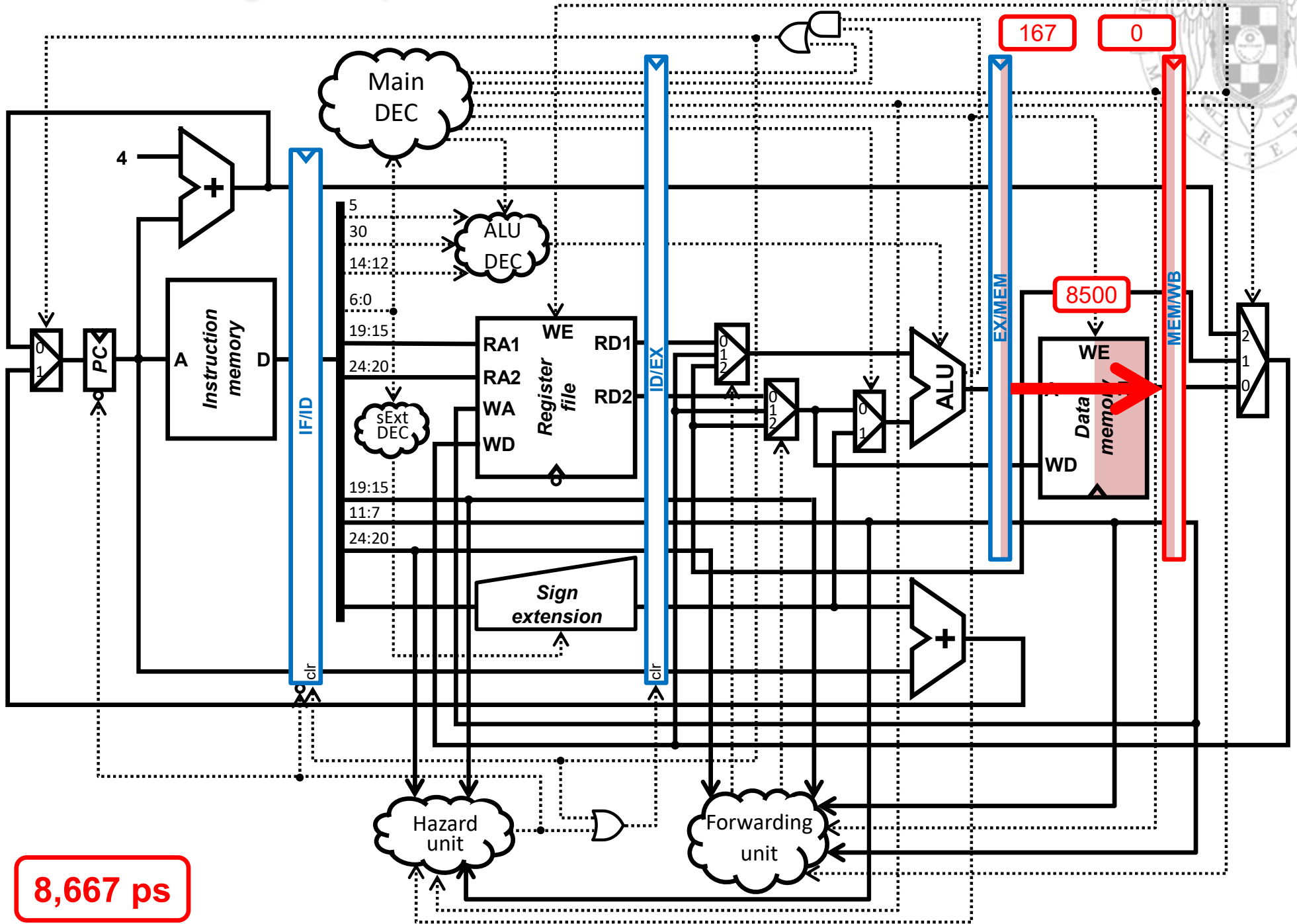

8,667 ps

Cycle time calculation

WB stage: critical path

 


27/10/23 version

module 7:
Pipelined processor design

FC-2

147

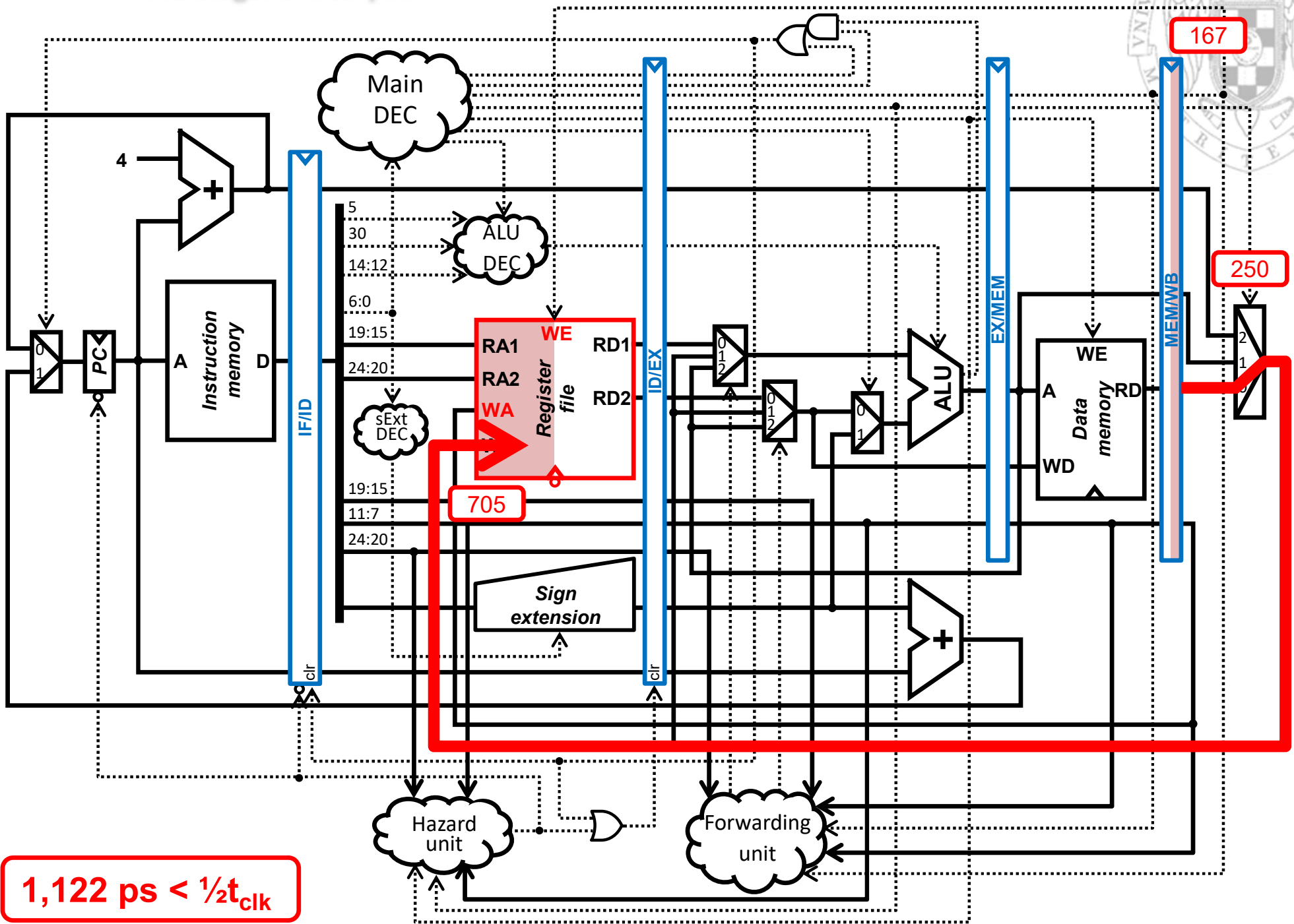

$1,122 \text{ ps} < \frac{1}{2}t_{\text{clk}}$

About *Creative Commons*



■ CC license (*Creative Commons*)

- This license enables reusers to distribute, remix, adapt, and build upon the material in any medium or format for noncommercial purposes only, and only so long as attribution is given to the creator. If you remix, adapt, or build upon the material, you must license the modified material under identical terms:



Attribution:

Credit must be given to the creator.



Non commercial:

Only noncommercial uses of the work are permitted.



Share alike:

Adaptations must be shared under the same terms.

More information: <https://creativecommons.org/licenses/by-nc-sa/4.0/>